

1a.

$x \backslash yz$	00	01	11	10
0	1			1
1			1	1

$$F = xy + x'z'$$

1b

$A \backslash BC$	00	01	11	10
0	1		1	1
1	1			1

$$F = C' + A'B$$

2a

$wx \backslash yz$	00	01	11	10
00		1	1	1
01		1	1	
11		1	1	
10		1	1	1

$$F = x'y + z$$

2b

$wx \backslash yz$	00	01	11	10
00			1	1
01		1	1	
11		1	1	1
10			1	1

$$F = xz + wy + x'y$$

3a

$x \backslash yz$	00	01	11	10
0	1	1	X	1
1	1	1	X	X

$$F = 1 = \Sigma(0,1,2,3,4,5,6,7)$$

3b

$AB \backslash CD$	00	01	11	10
00		1	1	
01	X	1	1	X
11	X	X	1	
10		1		

$$F = A'D + BD + C'D = \Sigma(1,3,5,7,9,13,15)$$

4a $F = xy'z + x'y'z + xyz$


x	y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

$= z(x+y')$


4d $F = xy'z + x'y'z + xyz$

x	y	Z	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	0	0
1	1	1	1

4b

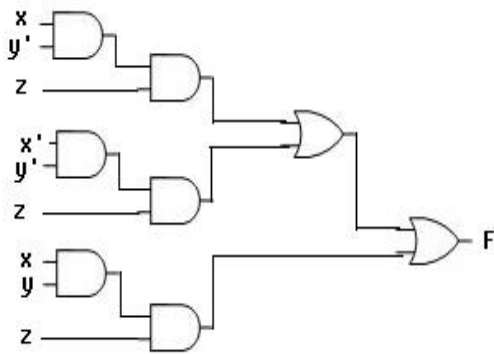

4e

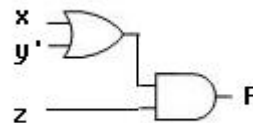


4c

$F = xy'z + x'y'z + xyz$

$= xz(y+y') + y'z(x+x')$

$= xz + y'z$

4f

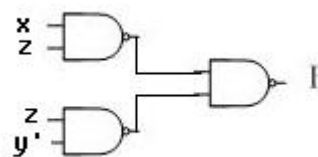


5

CD \ AB	00	01	11	10
00	1	1	0	X
01	0	0	0	0
11	0	0	X	X
10	X	1	1	X

$$F' = B + A'C$$

$$F = (B + A'C)' = B'(A + C')$$

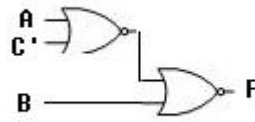


$$((A + C')' + B)' = (A + C')B'$$

6

Refer to your notes. We covered the even parity bit

generator. So odd parity bit generator is just the complement (this you should show

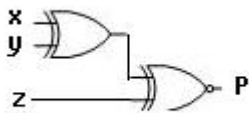with a table and then boolean algebra): $P = (x \oplus y \oplus z)'$



$$C = (x \oplus y \oplus z \oplus P)'$$

