



## EECE256 Quiz 2 - section 101

1. Simplify the following Boolean function with the associated don't care conditions using a Karnaugh map: (4 marks)

$$F(A,B,C,D) = \sum(3,7,11,13,14,15); \quad d = \sum(6, 12)$$


ABCD	F
0000	0
0001	0
0010	0
0011	1
0100	0
0101	0
0110	1
0111	1
1000	0
1001	0
1010	0
1011	0
1100	X
1101	1
1110	1
1111	1

		CD			
		00	01	11	10
AB	00	0	0	1	0
	01	0	0	1	X
	11	X	1	1	1
	10	0	0	1	0

$$F = AB + CD$$

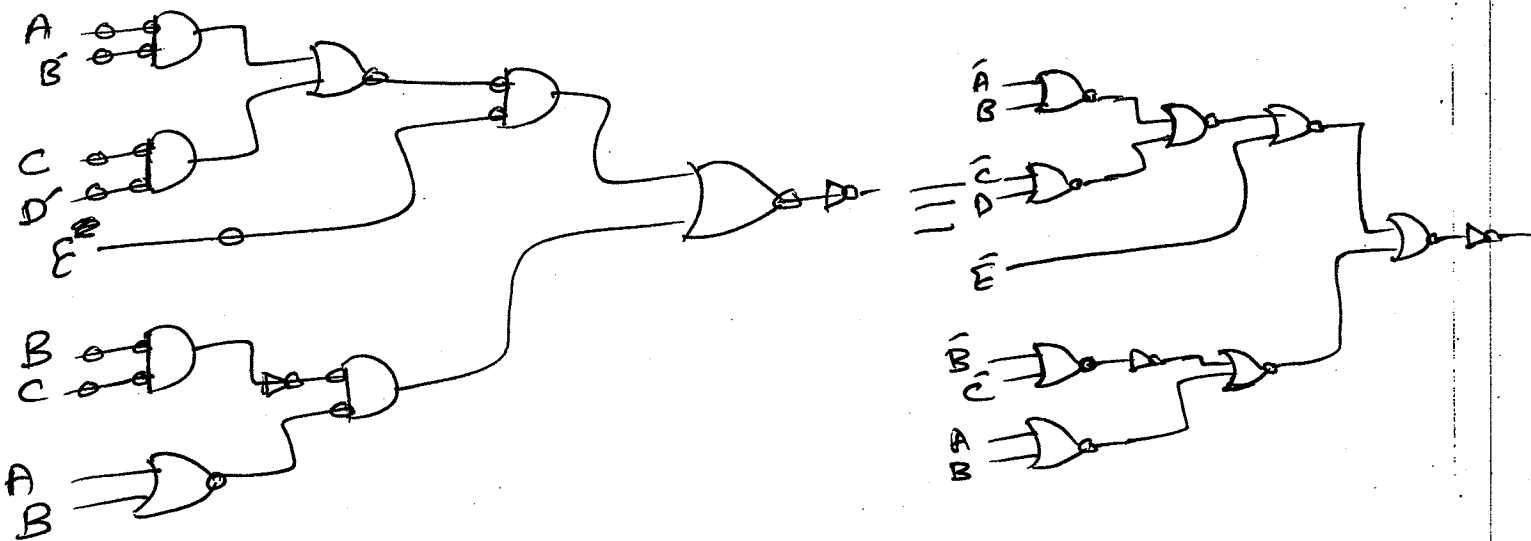2. Draw the multi-level NOR circuit for the following expression (4 marks):

$$F(A,B,C,D,E) = (AB' + CD'E) + BC(A+B)$$





3. A minority circuit is one whose output is equal to 1 if the input variables have less 1's than 0's. Show the following:

a) the truth table for a 3 input version of this circuit (4 marks):


X	Y	Z	Min
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

b) A simplified Boolean equation of this circuit (2 marks)

	yz		
x	00	01	11
0	1	1	0
1	1	0	0

$$Min = y'z' + x'y' + x'z'$$

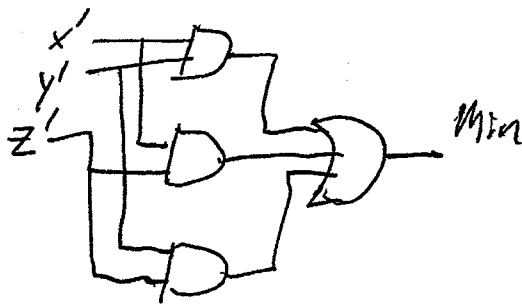c) A logic diagram of this circuit (2 marks)





# a place of mind

4. A 3 input combinational circuit is defined by the following three Boolean functions:

$$F1 = (y' + x)z$$

$$F2 = y'z' + xy' + yz'$$

$$F3 = (x' + y)z$$

Design the circuit with a decoder and external gates. Show your design. (4 marks)

$$F1 = y'z + xz = x'y'z + x'y'z + xy'z + xy'z + xyz$$

*(m1, m5, m5, m7)*

$$F2 = xy'z' + x'y'z' + xy'z + xy'z' + xyz' + x'y'z'$$

*(m4, m0, m5, m4, m6, m2)*

$$F3 = x'z + yz = x'y'z + x'y'z + x'yz + x'yz + xyz + xyz$$

*(m1, m3, m3, m7)*

x	y	z	F1	F2	F3
0	0	0	0	1	0
0	0	1	1	0	1
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	0	1	0
1	0	1	1	1	0
1	1	0	0	1	0
1	1	1	1	0	1

