




EECE256 Quiz 2 – section 102

1. Simplify the following Boolean function with the associated don't care conditions using a Karnaugh map: (4 marks)

$$F(A,B,C,D) = \sum(0,1, 2, 3, 7, 8); \quad d(A,B,C,D) = \sum(6, 10, 12)$$


A	B	C	D	F
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	1
0	1	0	1	x
0	1	1	0	x
0	1	1	1	1
1	0	0	0	1
1	0	0	1	x
1	0	1	0	x
1	0	1	1	1
1	1	0	0	x
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

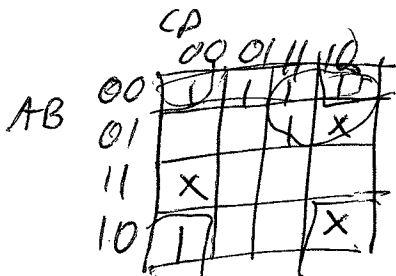

$$F = A'B' + B'D' + A'C$$

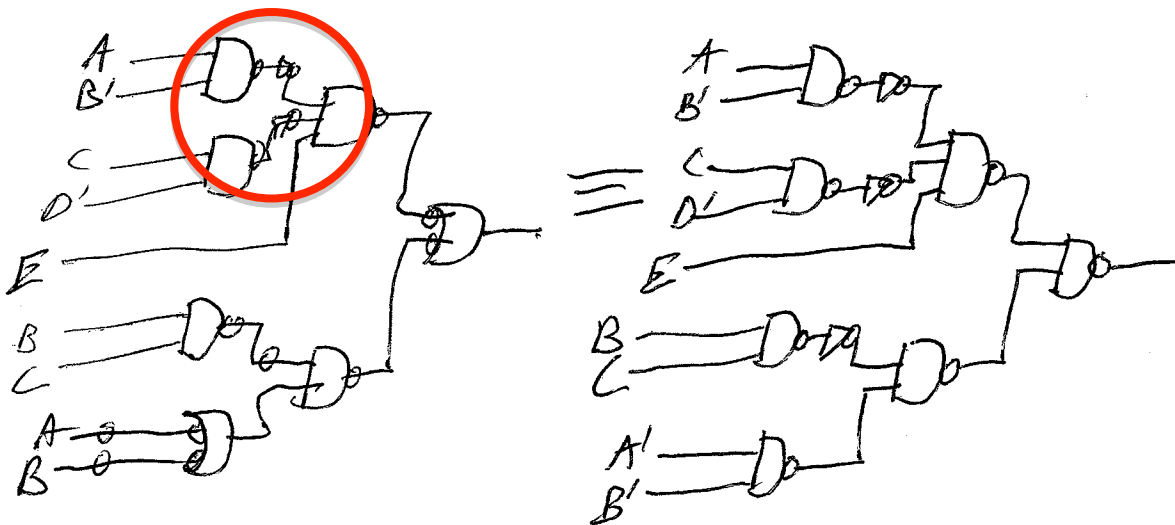2. Draw the multi-level NAND circuit for the following expression (4 marks):

$$F(A,B,C,D,E) = (AB' + CD')E + BC(A+B)$$





a place of mind

3. A GTE3 circuit is one whose output is equal to 1 if the binary value of the input variables is **greater than or equal to 3**. Show the following:

a) the truth table for a 3 input version of this circuit: (4 marks)

X	Y	Z	GTE3
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

b) A simplified Boolean equation of this circuit (2 marks)

		YZ					
		00	01	11	10		
X	0	0	0	1	1	0	
	1	1	1	1	1	1	

$GTE3 = YZ + X$

c) A logic diagram of this circuit (2 marks)





4. A 3 input combinational circuit is defined by the following three Boolean functions:

$$F1 = (y + x')z$$

$$F2 = yz' + x'y' + y'z'$$

$$F3 = (x + y')z$$

Design the circuit with a decoder and external gates. Show your design. (4 marks)

$$F1 = yz + x'z$$

$$F2 = yz' + x'y' + y'z'$$

$$F3 = xz + y'z$$

x	y	z	F1	F2	F3
0	0	0	0	1	0
0	0	1	1	1	1
0	1	0	0	1	0
0	1	1	1	0	0
1	0	0	0	0	0
1	0	1	1	1	1
1	1	0	1	0	0
1	1	1	1	0	1

