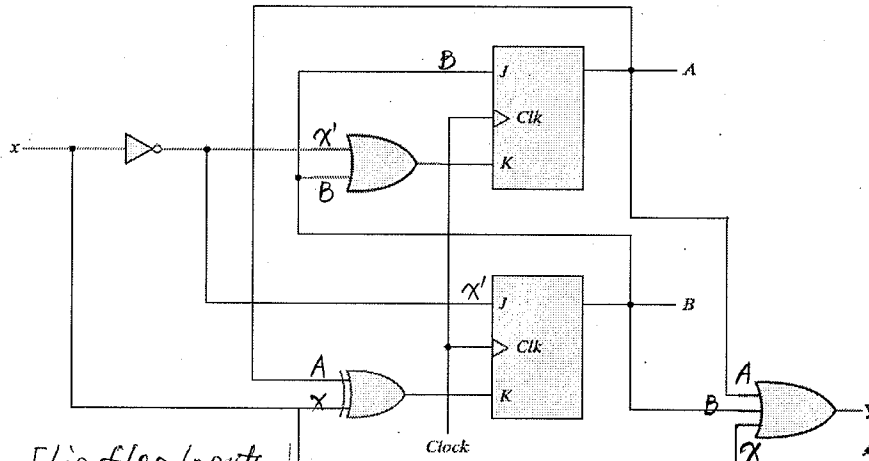




EECE256 Quiz 3 – section 101

(flip-flop input equations)

1. Derive the state table, including excitation equations (4 marks), and state diagram (3 marks) for the following circuit. Is the circuit a Mealy circuit or a Moore? (1 mark)





$J_A = B$
 $K_A = B + x'$
 $J_B = x'$
 $K_B = A \oplus x$

Flip-Flop Characteristic Table

J	K	$Q(t+1)$
0	0	$Q(t)$ No change
0	1	0 Reset
1	0	1 Set
1	1	$Q'(t)$ Complement

Present state Input			Flip-flop Inputs				Next State		Output
A	B	x	J_A	K_A	J_B	K_B	A	B	Y
0	0	0	0	1	1	0	0	1	0
0	0	1	0	0	0	1	0	0	1
0	1	0	1	1	1	0	1	1	1
0	1	1	1	1	0	1	1	0	1
1	0	0	0	1	1	1	0	1	1
1	0	1	0	0	0	0	1	0	1
1	1	0	1	1	1	1	0	0	1
1	1	1	1	1	0	0	0	1	1

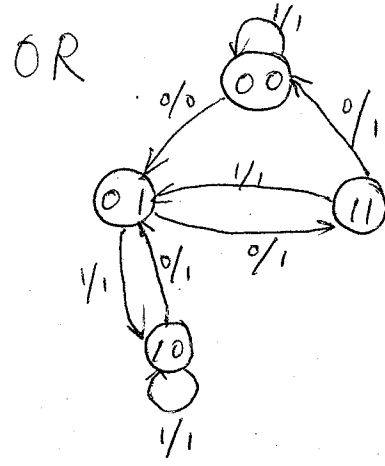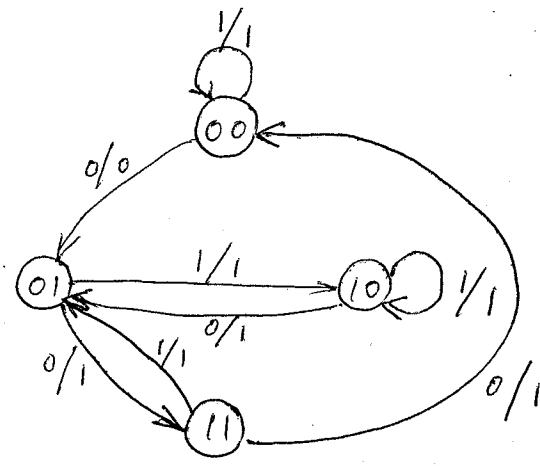


Mealy circuit.

(Since output y is a function of both the present state and the input)






a place of mind

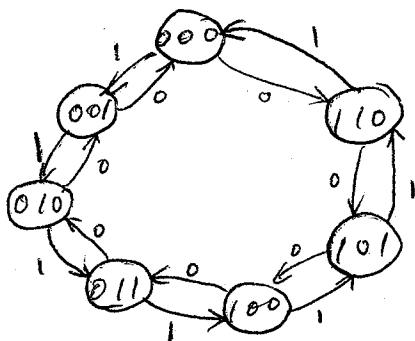2. Design an up-down binary counter that counts from 0-6 using T flip-flops. Show your state diagram (3 marks), state table (4 marks), and karnaugh maps (3 marks).



Q ₂ (t)	Q ₁ (t)	Q ₀ (t)	T
0	0	0	0
0	1	0	1
1	0	0	1
1	1	0	0

Present state			Input X	Next state			Flip-Flop Inputs		
A ₂	A ₁	A ₀		A ₂	A ₁	A ₀	T _{A₂}	T _{A₁}	T _{A₀}
0	0	0	0	1	1	0	1	1	0
0	0	0	1	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0	1
0	0	1	1	0	1	0	0	1	1
0	1	0	0	0	0	1	0	1	1
0	1	0	1	0	1	1	0	0	1
0	1	1	0	0	1	0	0	0	1
0	1	1	1	1	1	0	1	1	1
1	0	0	0	0	1	1	1	1	1
1	0	0	1	1	0	1	0	0	1
1	0	1	0	1	0	0	0	0	1
1	0	1	1	1	1	0	0	0	1
1	1	0	0	1	0	1	0	1	1
1	1	0	1	0	0	0	1	1	0
1	1	1	0	X	X	X	X	X	X
1	1	1	1	X	X	X	X	X	X

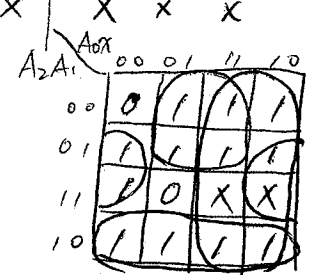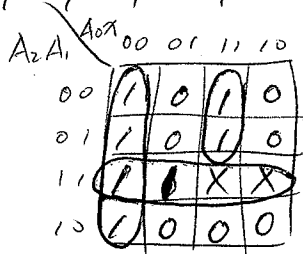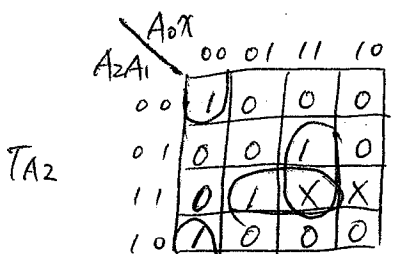

$$T_{A_2} = A_1' A_0' X + A_2 A_1' X + A_1 A_0 X$$


$$T_{A_1} = A_0' X' + A_2 A_1 + A_2' A_0 X$$

$$T_{A_0} = A_2 A_1' + A_0 + A_1 X' + A_2' X$$



a place of mind

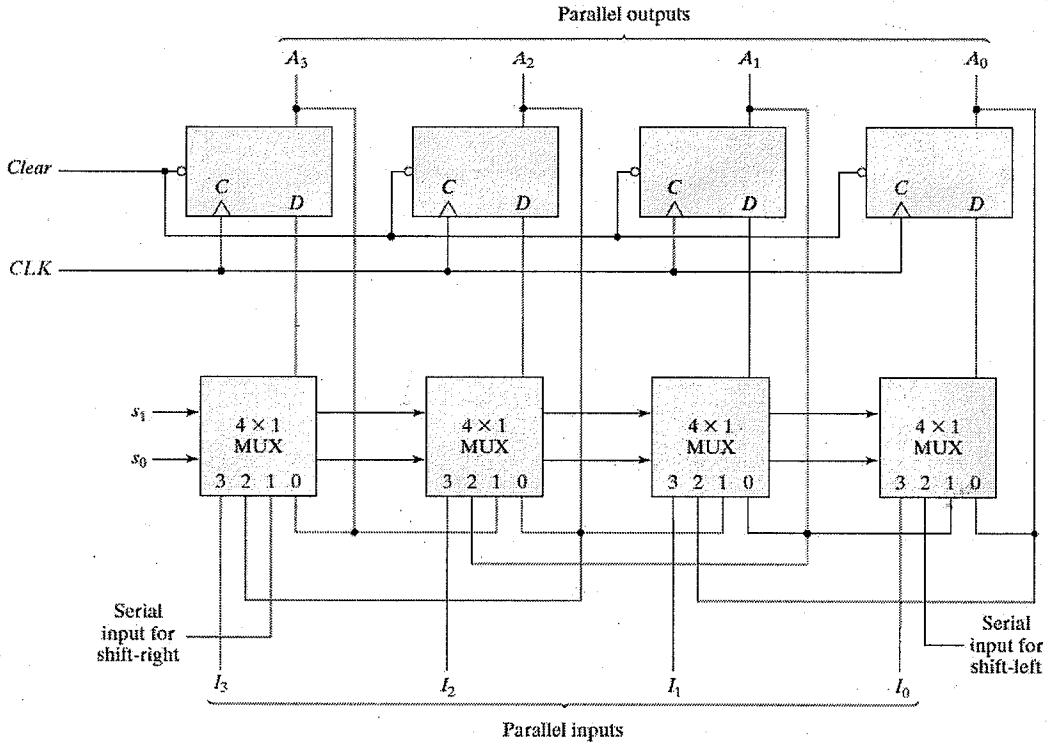3. Specify the next value in the register shown below based on the following sequence of inputs. The 'next' value becomes the 'current' value on the following line. Assume a starting 'current' value of 0001 (already specified in the chart). MSB is the serial input for shift right, while LSB is the input for shift left. (4 marks)



S	Clear	I	MSB	LSB	Current	Next
01	1	0101	1	1	0001	1000
11	0	0101	1	0	1000	0000
11	1	1010	0	1	0000	1010
10	1	0100	1	0	1010	0100
10	1	1010	0	1	0100	1001
01	1	0001	0	0	1001	0100

What are the five operations of this universal shift register? (2 marks)

Clear (Mode control) S

- 1 01 shift ~~right~~ right
- 1 10 shift left
- 1 11 parallel load
- 1 00 No change
- 0 xx clear the register to all 0's




a place of mind

Electrical and Computer Engineering

Nov 5, 2010

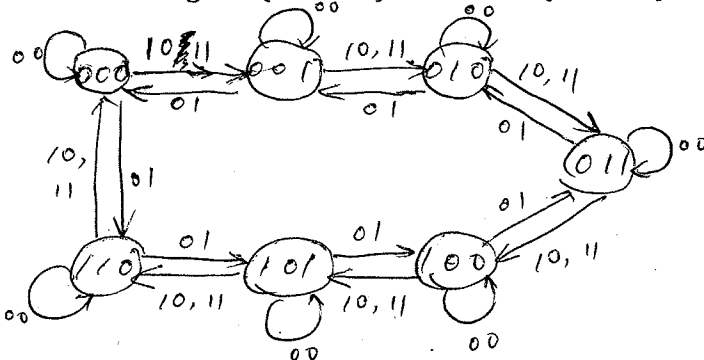2. Design an up-down binary counter that counts from 0-6 using T flip-flops. Show your state diagram (3 marks), state table (4 marks), and karnaugh maps (3 marks).




$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Input Up/down $X_1 X_0$	Present state $A_2 A_1 A_0$	Next state $A_2 A_1 A_0$	Flip-flop Inputs		
			T_{A_2}	T_{A_1}	T_{A_0}
0 0	0 0 0	0 0 0	0	0	0
0 0	0 0 1	0 0 1	0	0	0
0 0	0 1 0	0 1 0	0	0	0
0 0	0 1 1	0 1 1	0	0	0
0 0	1 0 0	1 0 0	0	0	0
0 0	1 0 1	1 0 1	0	0	0
0 0	1 1 0	1 1 0	0	0	0
0 0	1 1 1	X X X	X	X	X
0 1	0 0 0	1 1 0	1	1	0
0 1	0 0 1	0 0 0	0	0	1
0 1	0 1 0	0 0 1	0	1	1
0 1	0 1 1	0 1 0	0	0	1
0 1	1 0 0	0 1 1	1	1	1
0 1	1 0 1	1 0 0	0	0	1
0 1	1 1 0	1 0 1	0	1	1
0 1	1 1 1	X X X	X	X	X
1 0	0 0 0	0 0 1	0	0	1
1 0	0 0 1	0 1 0	0	1	1
1 0	0 1 0	0 1 1	0	0	1
1 0	0 1 1	1 0 0	1	1	1
1 0	1 0 0	1 0 1	0	0	1
1 0	1 0 1	1 1 0	0	1	1
1 0	1 1 0	0 0 0	1	1	0
1 0	1 1 1	X X X	X	X	X
1 1	0 0 0	0 0 1	0	0	1
1 1	0 0 1	0 1 0	0	1	1
1 1	0 1 0	0 1 1	0	0	1
1 1	0 1 1	1 0 0	1	1	1
1 1	1 0 0	1 0 1	0	0	1
1 1	1 0 1	1 1 0	0	1	1
1 1	1 1 0	0 0 0	1	1	0
1 1	1 1 1	X X X	X	X	X

$A_1 A_0$


$X_0 A_2$	00	01	11	10
00	0	0	0	0
01	0	0	X	0
11	1	0	X	0
10	1	0	0	0

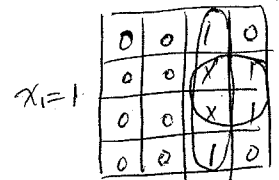

$$T_{A_2} = X_1' X_0 A_1' A_0' + X_1 A_1 A_0 + X_1 A_2 A_1$$

$A_1 A_0$


$X_0 A_2$	00	01	11	10
00	0	0	0	0
01	0	0	X	0
11	1	0	X	1
10	1	0	0	1

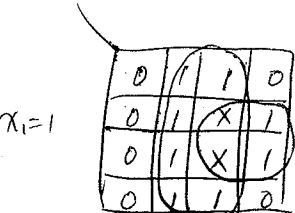

$$T_{A_1} = X_1' X_0 A_0' + X_1 A_0 + X_1 A_2 A_1$$

$A_1 A_0$

$X_0 A_2$	00	01	11	10
00	0	0	0	0
01	0	0	X	0
11	1	1	X	1
10	0	1	1	1

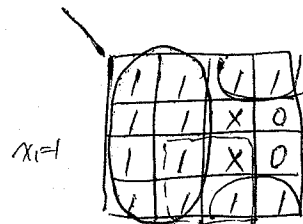

$$T_{A_0} = X_1' X_0 A_2 + X_1' X_0 A_1 + X_0 A_0 + X_1 A_1' + X_1 A_2' A_1$$