

Reminders : - buy DE1 for homework

- homework appointments Thurs/Fri (12hrs

- quiz Fri

advance
booking
req'd)

Computing

A computer system contains 3 essential components

1 - CPU

2 - input/output

3 - memory

The datapath circuit is an example of a very basic computer

CPU - ALU, mux

I/O - switches, constants (0 and 1), hex display

Memory - register file

We are using RTN to "program" the computer


low-level : $R3 \leftarrow 1$

high-level : $R3 \leftarrow R3 + 1 \Rightarrow \left. \begin{matrix} A \leftarrow 1 \\ B \leftarrow R3 \\ R3 \leftarrow A + B \end{matrix} \right\} \mu\text{-ops}$

Each $\mu\text{-op}$ is a machine instruction.

You input instructions by setting switches

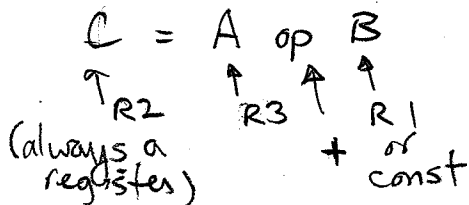Most typical CPU instructions use 3 operands:



written as: $R2 \leftarrow R3 + R1$

or "add R2, R3, R1"


Examples:

③ $R2 \leftarrow R2 + R2$

④ $R3 \leftarrow 2 + 1$

⑤ $R3 \leftarrow 7 * 9$

assembly
language

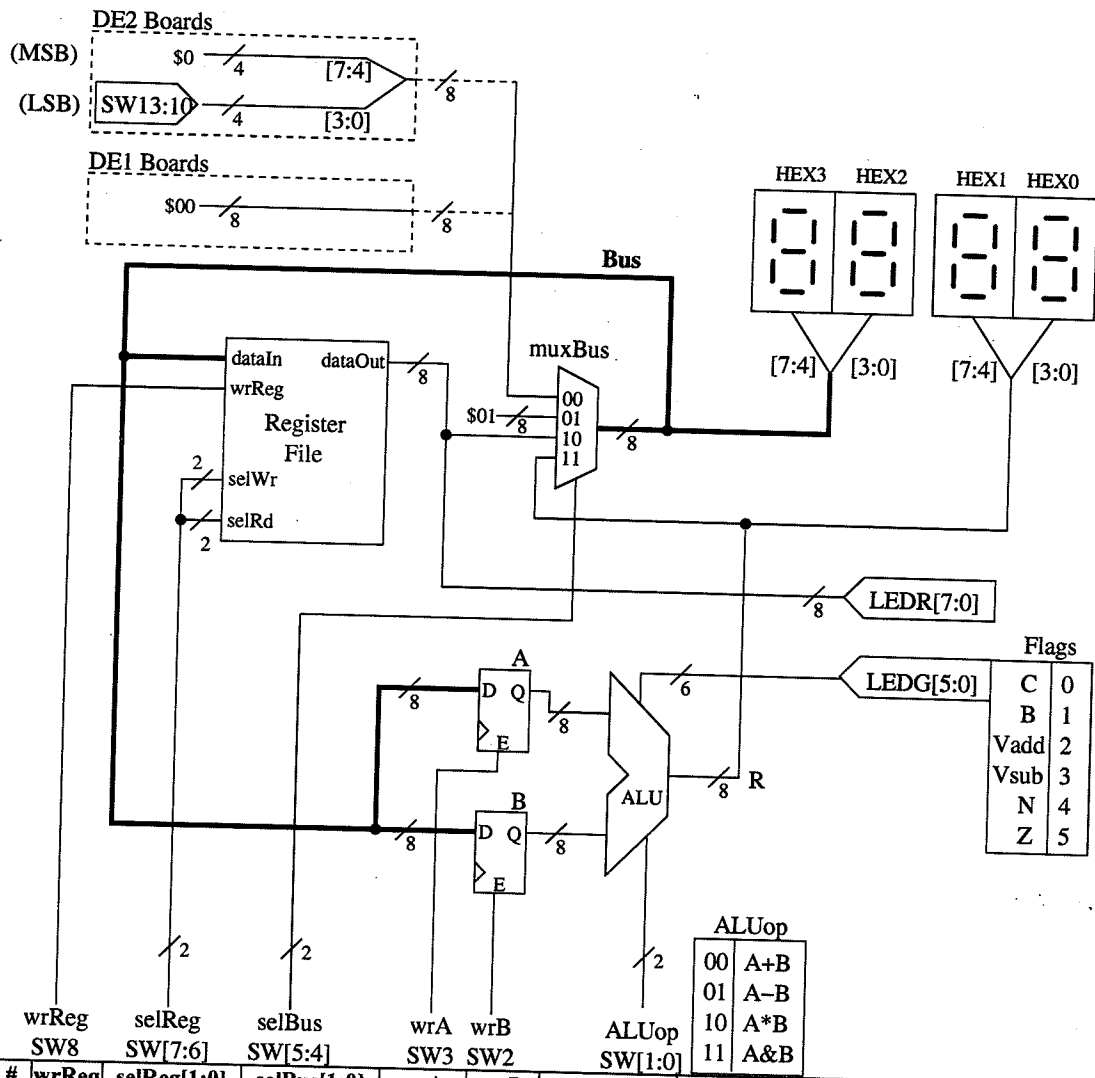

ALUop

00	A+B
01	A-B
10	A*B
11	A&B

Flags

C	0
B	1
Vadd	2
Vsub	3
N	4
Z	5

Cycle #	wrReg SW8	selReg SW[7:6]	selBus SW[5:4]	wrA SW3	wrB SW2	ALUop SW[1:0]	Micro-operation	Overall Operation
1.	0	10	10	1	1	XX	A ← R2 ; B ← R2	R2 ← R2 + R2
2.	1	10	11	0	0	00	R2 ← A + B	
3.								
4.	0	XX	01	1	1	XX	A ← 1 ; B ← 1	R3 ← 2 + 1
5.	0	XX	11	1	0	00	A ← A + B (1+1)	
6.	1	11	11	0	0	00	R3 ← A + B (2+1)	
7.								
8.								R3 ← 7 * 9
9.								
10.								<div style="border: 1px solid black; padding: 5px; display: inline-block;"> do NOT modify R0, R1, R2 try to not modify R3 until the very end </div> Use A and B to hold temps
11.								
12.								
13.								
14.								
15.								
16.								
17.								
18.								
19.								
20.								