

THE UNIVERSITY OF BRITISH COLUMBIA  
Department of Electrical and Computer Engineering  
EECE356 Quiz 2 – October 7, 2011

Time: 20min.

**This examination consists of 2 pages. Please check that you have a complete copy. You may use both sides of each sheet if needed.**

Surname \_\_\_\_\_ First \_\_\_\_\_

Student Number \_\_\_\_\_

Page #	MAX	GRADE
1	100	
TOTAL	100	

IMPORTANT NOTE: The announcement “stop writing” will be made at the end of the examination. Anyone writing after this announcement will receive a score of 0. No exceptions, no excuses.

*All writings must be on this booklet. The blank sides on the reverse of each page may also be used.*

*Each candidate should be prepared to produce, upon request, his/her Library/AMS card.*

*Read and observe the following rules:*

*Candidates are not permitted to ask questions of the invigilators, except in cases of supposed errors or ambiguities in examination-questions.*

**Caution** - *Candidates guilty of any of the following, or similar, dishonest practices shall be immediately dismissed from the examination and shall be liable to disciplinary action:*

- *Making use of any books, papers or memoranda, calculators, audio or visual cassette players or other memory aid devices, other than as authorized by the examiners.*
- *Speaking or communicating with other candidates.*
- *Purposely exposing written papers to the view of other candidates.*

*The plea of accident or forgetfulness shall not be received.*

**NOTE: NO CALCULATORS, NO CELLPHONES, NO OTHER ELECTRONIC AIDS, NO NOTES, NO FORMULA SHEET and NO BOOKS ARE PERMITTED.**

READ THIS


100p

1. The transfer function for the circuit shown below is given by:

$$\frac{V_o(s)}{V_i(s)} = A_0 \frac{s}{s+20} \frac{s}{s+200}$$

Here  $A_0$  is a constant value.

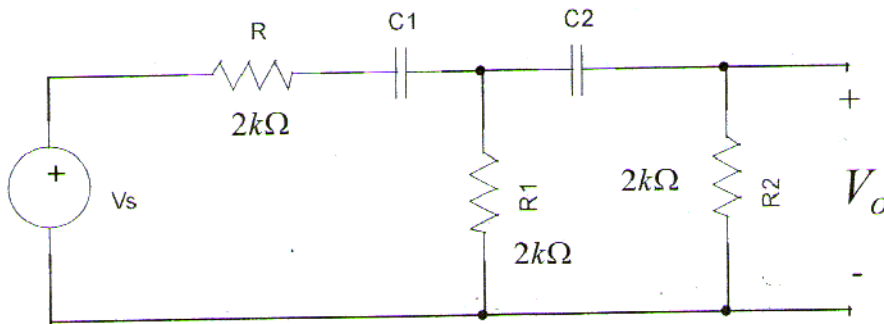
- Determine the value of  $A_0$
- Use the method of open-circuit/short-circuit time constants to estimate the values of  $C_1$  and  $C_2$ , assuming  $C_1 > C_2$



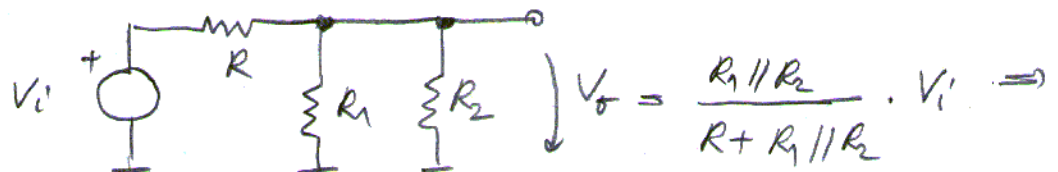a)  $A_0$  can be calculated from the value of the transfer function when  $\omega \rightarrow \infty$


$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)} \xrightarrow{\omega \rightarrow \infty} A_0$$

For  $\omega \rightarrow \infty$ , the circuit becomes:




$$\Rightarrow \left. \frac{V_o}{V_i} \right|_{\omega \rightarrow \infty} = \frac{1 \text{ k}\Omega}{2 \text{ k}\Omega + 1 \text{ k}\Omega} = \frac{1}{3} = 0.33 \Rightarrow \boxed{A_0 = 0.33} \quad (20p)$$

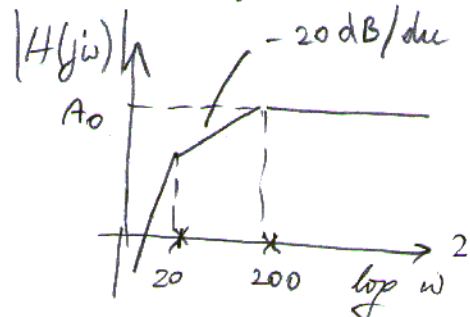b.) The circuit is a high-pass filter, with 2 zeros and 2 poles. The poles are 1 decade apart, so we can apply the method of SC time constants to approximate  $\omega < 3 \text{ dB}$  (the highest pole)



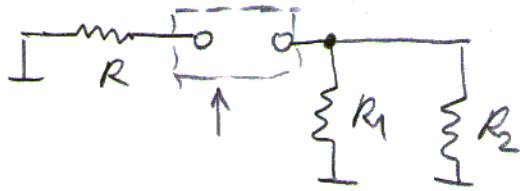
- Determine the SC time constant for  $C_1$



$$R_{1sc} = R + R_1 \parallel R_2 = 2k\Omega + 1k\Omega = 3k\Omega$$

$$\tau_{1sc} = R_{1sc} C_1 = 3 \cdot 10^3 C_1$$

- The SC time constant for  $C_2$

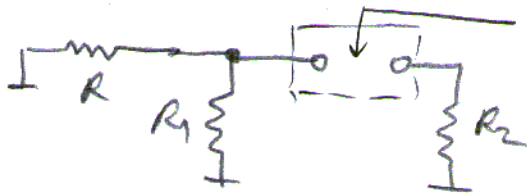

$$R_{2sc} = R_2 + R \parallel R_1 = 2k\Omega + 1k\Omega = 3k\Omega$$

$$\tau_{2sc} = R_{2sc} C_2 = 3 \cdot 10^3 C_2$$

$$\omega_{L3dB} = 200 = \frac{1}{\tau_{1sc}} + \frac{1}{\tau_{2sc}} = \frac{1}{3 \cdot 10^3 C_1} + \frac{1}{3 \cdot 10^3 C_2}$$

$$C_1 > C_2 \Rightarrow \omega_{L3dB} \approx \frac{1}{\tau_{2sc}} = \frac{1}{3 \cdot 10^3 C_2} \Rightarrow C_2 \approx \frac{1}{3 \cdot 10^3 \cdot 200}$$


$$C_2 \approx \frac{10^{-5}}{6} F = 1.67 \mu F \quad (+50p)$$

To determine  $C_2$ , we separate in the transfer function the part given by  $C_2$ :

$$H(s) = \frac{V_o(s)}{V_i(s)} = A_0 \left\{ \frac{s}{s+20} \right\} \frac{s}{s+200}$$

$\leftarrow$  LF → HF

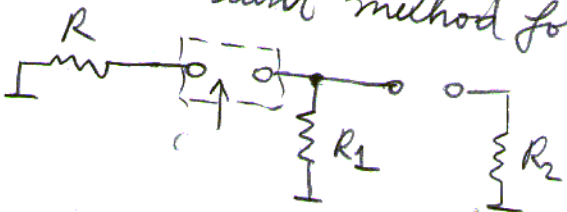As  $C_2$  is now a HF component relative to the pole at  $\omega = 20$ , it will appear as open-circuit when we apply again the SC time constant method for  $C_1$



$$R'_{1sc} = R_1 + R = 4k\Omega$$

$$\tau'_{1sc} = R'_{1sc} C_1 = 4 \cdot 10^3 C_1 \Rightarrow$$

$$\Rightarrow 20 \approx \frac{1}{\tau'_{1sc}} = \frac{1}{4 \cdot 10^3 C_1} \Rightarrow C_1 = \frac{1}{8 \cdot 10^4} = \frac{100}{8} \mu F$$

$$C_1 = 12.5 \mu F \quad (+30p)$$

Marking scheme:

- computation of  $A_0 = 0.33 \rightarrow +20p$
- apply SC time  $\tau$  method to get  $C_2 = 1.67 \mu F \rightarrow +50p$
- apply SC (with  $C_2$  open circuited) to get  $C_1 = 12.5 \mu F \rightarrow +30p$

---

100p