
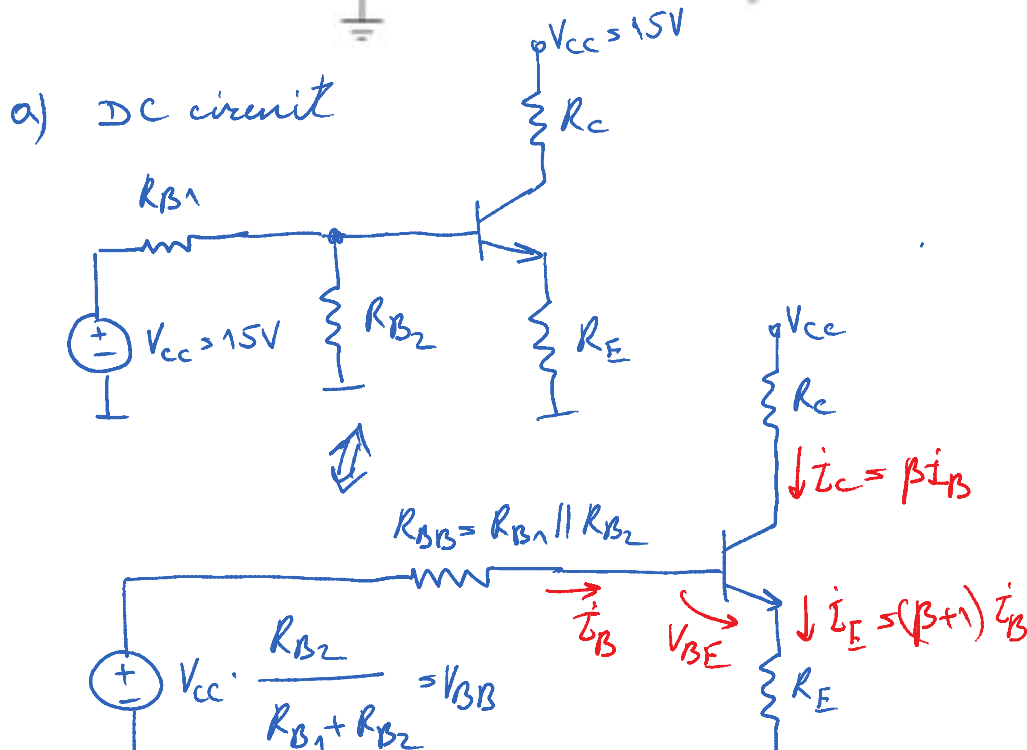


Quiz 3

November-20-11
9:09 PM

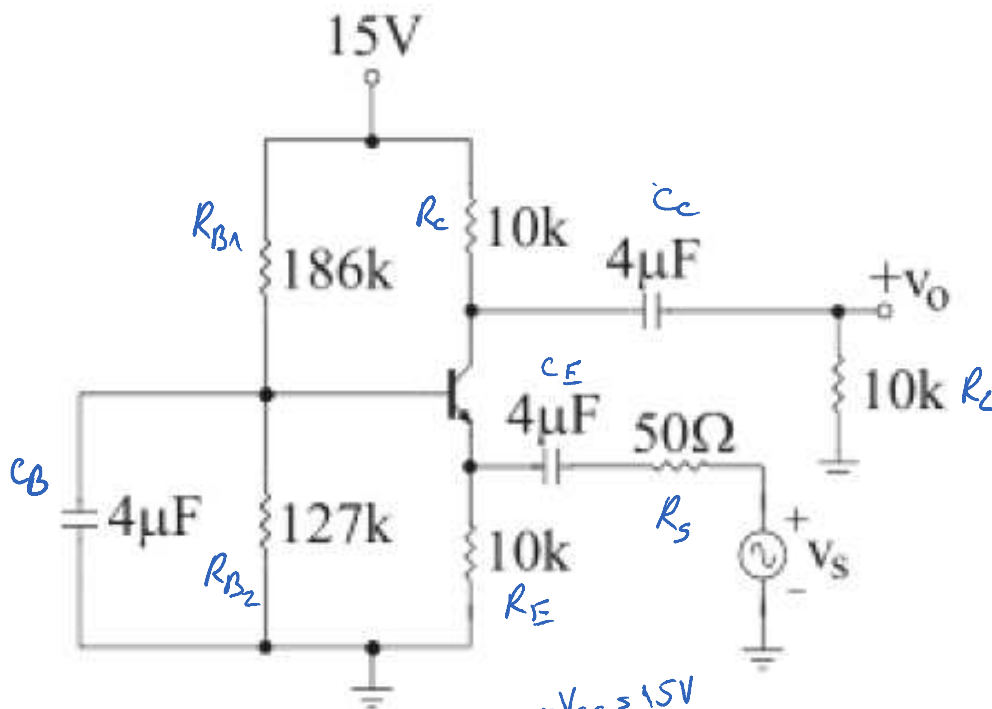1. For the circuit shown in the figure, the transistor has $\beta = 100$.
 - a. Find $I_B, I_C, V_C, V_B, g_m, r_\pi$
 - b. Draw the low frequency circuit, the midband circuit and the high frequency circuit
 - c. Find the midband gain (AM) and the corner frequencies $\omega_{3dB\text{L}}, \omega_{3dB\text{H}}$
- The hybrid-model has the following parameters: $C_\pi = 5\text{pF}, C_\mu = 1\text{pF}, r_o = \infty$



$$V_{CC} \cdot \frac{R_{B2}}{R_{B1} + R_{B2}} = V_{BB} \quad \left\{ R_E \right.$$

$$R_{BB} = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = \frac{186 \cdot 127}{186 + 127} \text{ k}\Omega = 75.5 \text{ k}\Omega$$

$$V_{BB} = V_{CC} \cdot \frac{R_{B2}}{R_{B1} + R_{B2}} = 15V \cdot \frac{127}{127 + 186} = 6V$$

$$V_{BB} = R_{BB} \dot{I}_B + V_{BE} + R_E \dot{I}_E$$

$$V_{BB} = R_{BB} \dot{I}_B + V_{BE} + R_E (\beta + 1) \dot{I}_B$$

Assume BJT operates in the active region (to be checked at the end) $\Rightarrow V_{BE} = V_{BE, on} \approx 0.7V$

$$\dot{I}_B = \frac{V_{BB} - V_{BE}}{R_{BB} + (\beta + 1) R_E} = \frac{6V - 0.7V}{75.5 \text{ k}\Omega + 101 \cdot 10 \text{ k}\Omega}$$

$$\boxed{\dot{I}_B = 4.9 \mu\text{A}} \Rightarrow \dot{I}_C = \beta \dot{I}_B = 490 \mu\text{A}$$

$$\dot{I}_E = (\beta + 1) \dot{I}_B = 495 \mu\text{A}$$

$$V_B = V_{BB} - R_{BB} \dot{I}_B = 6V - 75.5 \cdot 10^3 \cdot 4.9 \cdot 10^{-6} V$$

$$V_B = 5.63 V$$

$$V_C = V_{CC} - R_C \dot{I}_C = 15V - 10^4 \cdot 490 \cdot 10^{-6} V = 10.1 V$$


($V_{CB} > 0 \Rightarrow$ this confirms the operation in active mode)
 $V_{BE} > 0$

- Small signal parameters: $r_{\pi} = \frac{V_T}{\dot{I}_B} = \frac{26 \text{ mV}}{4.9 \mu\text{A}} = 5.3 \text{ k}\Omega$


$$g_m = \frac{\dot{I}_C}{V_T} = \frac{490 \mu\text{A}}{26 \text{ mV}} = 18.8 \text{ mA/V}$$

(b) The midband circuit:




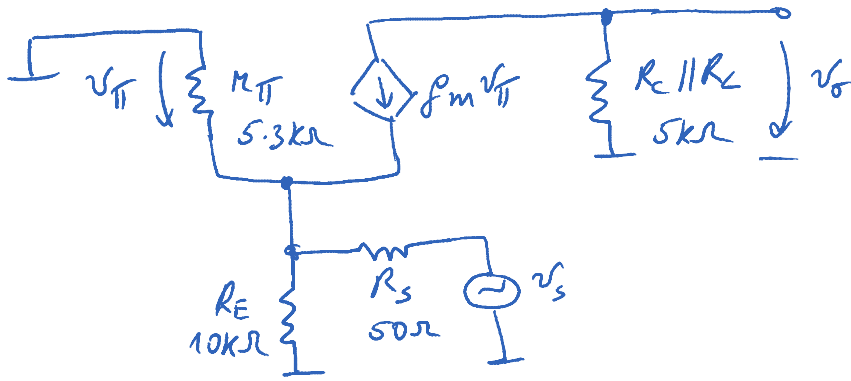


The HF circuit:

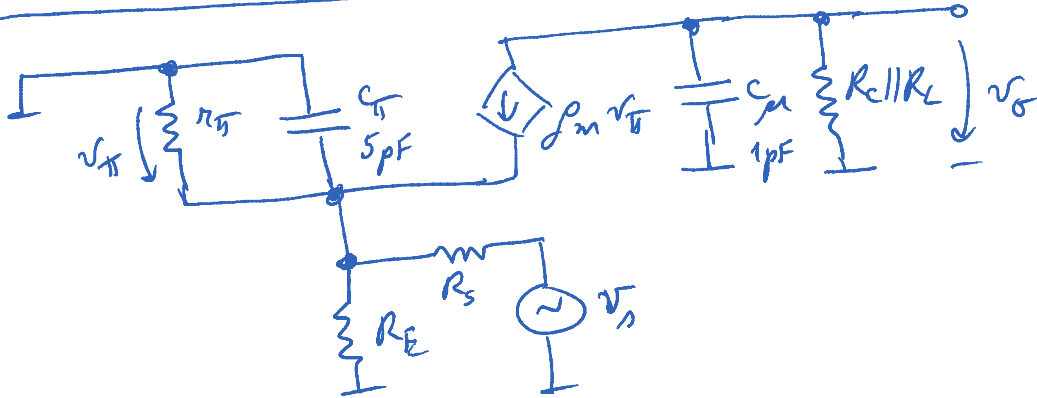

The LF circuit:

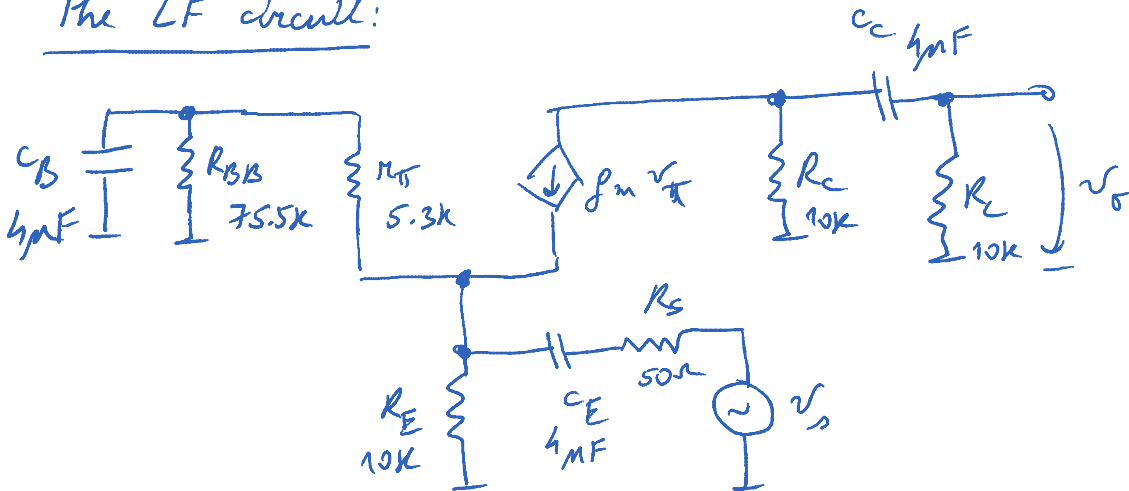

(c) The midband gain:

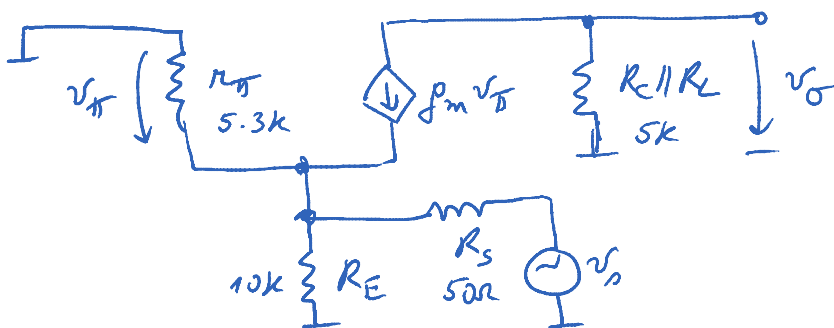

$$-v_{\pi} = \frac{R_E \parallel \frac{r_{\pi}}{\beta+1}}{R_s + R_E \parallel \frac{r_{\pi}}{\beta+1}} v_s$$


$$v_o = -\beta_m v_{\pi} (R_c \parallel R_L) = \frac{\beta_m (R_c \parallel R_L) \left(R_E \parallel \frac{r_{\pi}}{\beta+1} \right)}{R_s + R_E \parallel \frac{r_{\pi}}{\beta+1}} v_s \Rightarrow$$

$$\Rightarrow A_m = \frac{v_o}{v_s} = \frac{\beta_m \cdot (R_c \parallel R_L) R_E \parallel \frac{r_{\pi}}{\beta+1}}{R_s + R_E \parallel \frac{r_{\pi}}{\beta+1}}$$

$$R_E \parallel \frac{r_{\pi}}{\beta+1} = \frac{10 \cdot \frac{5.3}{101}}{10 + \frac{5.3}{101}} \text{ k}\Omega = 52.2 \Omega$$

$$A_m = \frac{18.8 \cdot 10^{-3} \cdot 5 \cdot 10^3 \cdot 52.2}{50 + 52.2} = 48$$

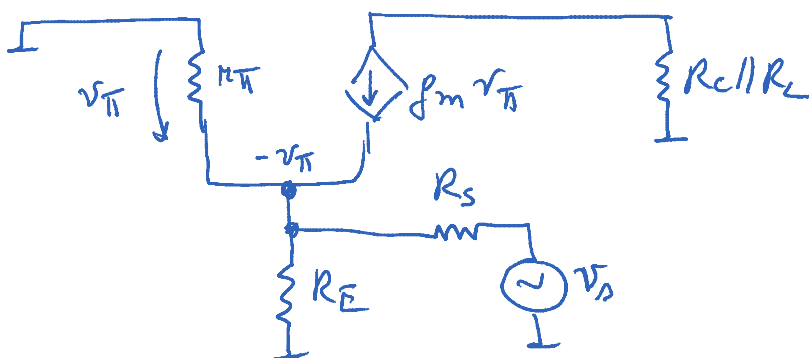Note: we could have used superposition (with dependent sources) to determine v_{π} :



$$-v_{\pi} = \frac{R_E \parallel r_{\pi}}{R_s + R_E \parallel r_{\pi}} v_s + \beta_m v_{\pi} (r_{\pi} \parallel R_E \parallel R_s) \Leftrightarrow$$

$$\Leftrightarrow -v_{\pi} \left(1 + \beta_m R_s \parallel R_E \parallel r_{\pi} \right) = \frac{R_E \parallel r_{\pi}}{R_s + R_E \parallel r_{\pi}} v_s \Rightarrow$$


$$\Rightarrow v_{\pi} = - \frac{R_E \parallel r_{\pi}}{1 + \beta_m R_s \parallel R_E \parallel r_{\pi}} \cdot \frac{1}{R_s + R_E \parallel r_{\pi}} v_s$$

$$\Rightarrow v_{\pi} = \frac{R_E \parallel r_{\pi}}{R_S + R_E \parallel r_{\pi}} \cdot \frac{1}{1 + \beta_m (r_{\pi} \parallel R_E \parallel R_S)} v_s$$

$$\begin{aligned} - \frac{v_{\pi}}{v_s} &= \frac{\left(\frac{1}{R_E} + \frac{1}{r_{\pi}}\right)^{-1}}{R_S + \frac{1}{\frac{1}{R_E} + \frac{1}{r_{\pi}}}} \cdot \frac{1}{1 + \beta_m \frac{1}{\frac{1}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S}}} \\ &= \frac{1}{1 + R_S \left(\frac{1}{R_E} + \frac{1}{r_{\pi}}\right)} \cdot \frac{\frac{1}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S}}{\beta_m + \frac{1}{r_{\pi}} + \frac{1}{R_E} + \frac{1}{R_S}} \\ &= \frac{\frac{1}{R_S}}{\frac{1}{R_S} + \frac{1}{R_E} + \frac{1}{r_{\pi}}} \cdot \frac{\frac{1}{R_S} + \frac{1}{R_E} + \frac{1}{r_{\pi}}}{\left(\frac{\beta+1}{r_{\pi}} + \frac{1}{R_E}\right) + \frac{1}{R_S}} = \frac{1}{1 + R_S \cdot (R_E \parallel \frac{r_{\pi}}{\beta+1})^{-1}} \end{aligned}$$

$$- \frac{v_{\pi}}{v_s} = \frac{R_E \parallel \frac{r_{\pi}}{\beta+1}}{R_S + R_E \parallel \frac{r_{\pi}}{\beta+1}} \quad \leftarrow \text{the same expression as before}$$


For ω_H - we take the HF circuit:

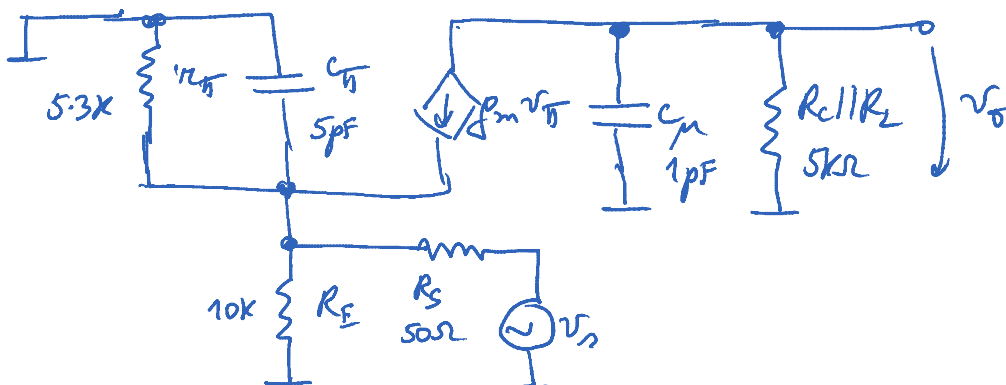

The method of OC:
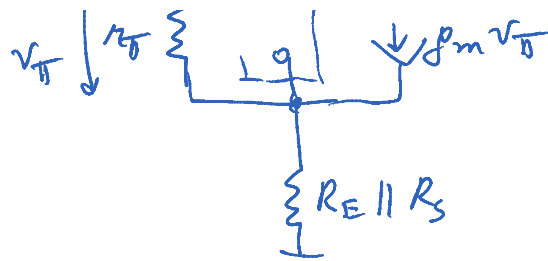
$$\text{For } C_{\mu}: \quad \tau_{M, OC} = C_{\mu} \cdot (R_E \parallel R_L) = 10^{-12} \cdot 5 \cdot 10^3 = 5 \text{ ns}$$






$$R_{\pi, oc} = R_E \parallel R_S \parallel \frac{r_{\pi}}{\beta + 1} \approx 50\Omega \parallel 53\Omega \approx 25.2\Omega$$

$$\tau_{\pi, oc} = \left(R_E \parallel R_S \parallel \frac{r_{\pi}}{\beta + 1} \right) C_{\pi} = 25 \cdot 5 \cdot 10^{-12} = 125 \text{ ps}$$

$$\omega_H = \frac{1}{\tau_{\pi, oc} + \tau_{\mu, oc}} = \frac{1}{5 \cdot 10^{-9} + 0.125 \cdot 10^{-9}} \text{ rad/s}$$

$$\omega_H = 195 \text{ rad/s} \Rightarrow f_H = \frac{\omega_H}{2\pi} = 31 \text{ MHz}$$

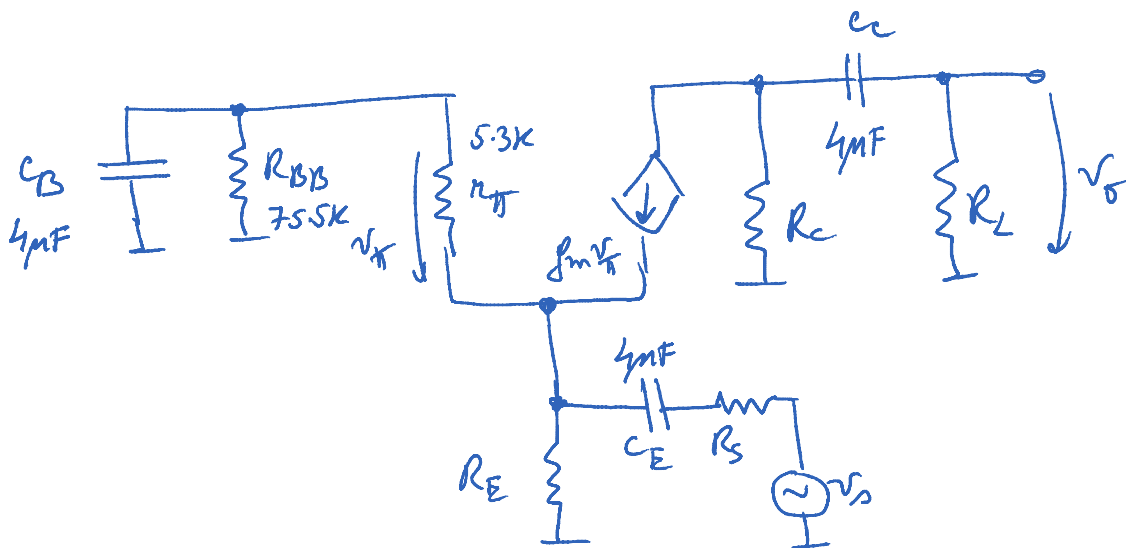
For $\omega_{3dB} = \omega_L \rightarrow$ the LF circuit:




The method of SC:

$$C_C: \tau_{C, sc} = C_C \cdot (R_C + R_L) = 4 \cdot 10^{-6} \cdot 10 \cdot 10^3 = 40 \text{ ms}$$

For C_B :

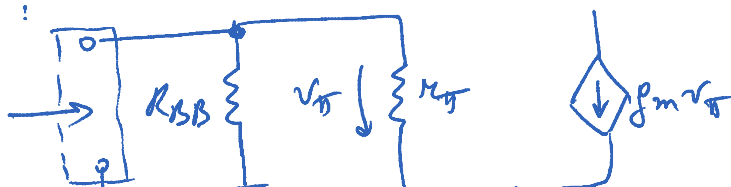

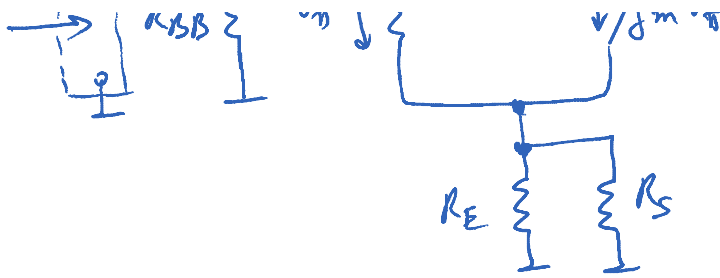


$$R_{B,ac} = R_{BB} \parallel (r_{\pi} + (\beta + 1) R_E \parallel R_S)$$

$$\approx 75.5 \text{ k}\Omega \parallel (5.3 \text{ k}\Omega + 101 \cdot 50 \Omega) \approx 9.1 \text{ k}\Omega$$

$$\tau_{B,ac} = 9.1 \cdot 10^3 \cdot 4 \cdot 10^{-6} \text{ s} \approx 36.4 \text{ ns}$$

For CE:

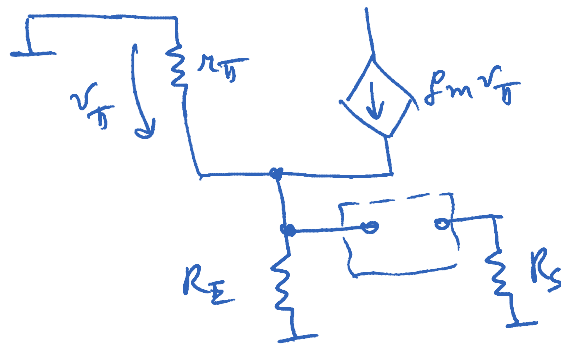

$$R_{E,ac} = \left(R_E \parallel \frac{r_{\pi}}{\beta + 1} \right) + R_S \approx 52.2 \Omega + 50 \Omega \approx 102.2 \Omega$$

$$\tau_{E,ac} = 102.2 \cdot 4 \cdot 10^{-6} \text{ s} \approx 408.8 \cdot 10^{-6} \text{ s}$$

$$\omega_L = \frac{1}{\tau_{E,ac}} + \frac{1}{\tau_{B,ac}} + \frac{1}{\tau_{C,ac}} \approx \frac{1}{408 \cdot 10^{-6}} + \frac{1}{36 \cdot 10^{-3}} + \frac{1}{40 \cdot 10^{-3}}$$

$$\omega_L \approx \frac{1}{\tau_{E,ac}} \approx 2446 \text{ rad/s} \Rightarrow f_L = 389 \text{ Hz}$$