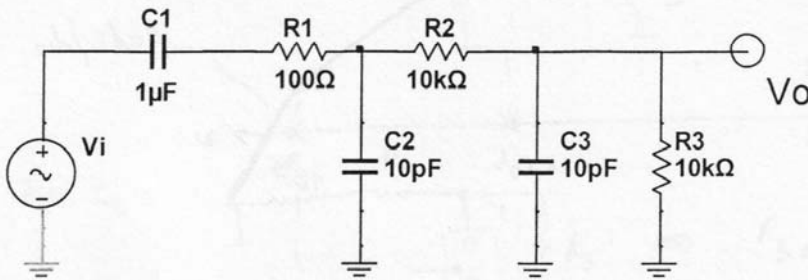


1. [ 50 marks] Compute the transfer function of the following circuit, using the open circuit and short circuit time constant method. State explicitly the values of  $\omega_{L3dB}$  and  $\omega_{H3dB}$ . Draw the amplitude and phase Bode plots of the transfer function,

$$H(s) = \frac{V_o(s)}{V_i(s)}$$




From circuit topology:  $C_1$  imposes a zero at  $\omega = 0$ , while  $C_2, C_3$  will short-circuit the signal path as  $\omega \rightarrow \infty \Rightarrow C_1$  will be a component relevant for LF transfer function, while  $C_2, C_3$  will count for the HF part

$$H(s) = H_{LF}(s) \cdot H_M \cdot H_{HF}(s)$$


$\uparrow$   $C_1$   $\uparrow$   $C_2, C_3$

This is further confirmed by their values:  $C_1 = 1 \mu F \gg C_2 = C_3 = 10 pF$

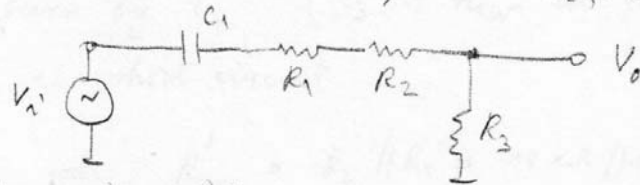The LF circuit reduces to:  
( $C_2, C_3$  are open circuited)



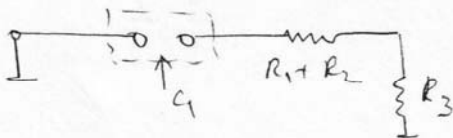We apply the short circuit time constant method to determine  $\omega_{LH}$




$$R_{1SC} = R_1 + R_2 + R_3 = 20.1 k\Omega$$

$$\tau_{1SC} = R_{1SC} \cdot C_1 = 20.1 \cdot 10^3 \cdot 10^{-6} = 20.1 \cdot 10^{-3}$$

$$\omega_{LH} = \frac{1}{\tau_{1SC}} = \frac{1}{20.1 \cdot 10^{-3}} \text{ rad/s} \approx \frac{1000}{20.1} \approx 50 \text{ rad/s}$$


$$H_{LF} = \frac{s}{s + \omega_{LH}} = \frac{s}{s + 50}$$

The circuit in midband:

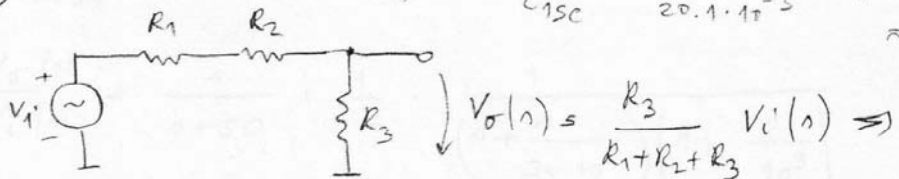


$$\Rightarrow H_M(s) = \frac{R_3}{R_1 + R_2 + R_3} = \frac{10 k\Omega}{20.1 k\Omega} \approx 0.5$$

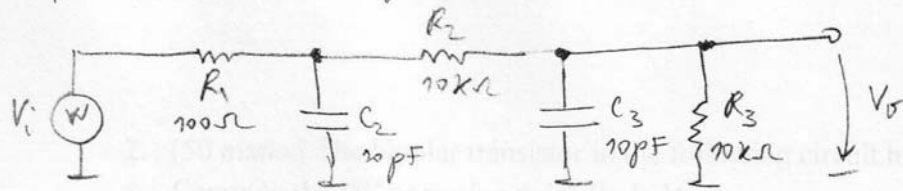► For the HF part, the circuit reduces to:



We apply the open circuit time constant method

# For  $C_2$ :

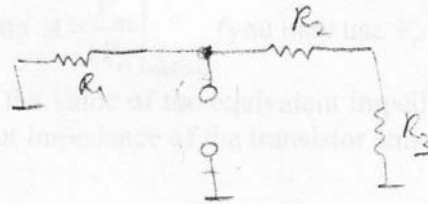


$$\Rightarrow R_{2oc} = (R_2 + R_3) \parallel R_1$$

$$= 20k\Omega \parallel 100\Omega \approx 100\Omega$$

$$\tau_{2oc} = R_{2oc} \cdot C_2 = 100 \cdot 10 \cdot 10^{-12} s$$

$$\tau_{2oc} = 10^{-9} s = 1 ns$$

# For  $C_3$ :

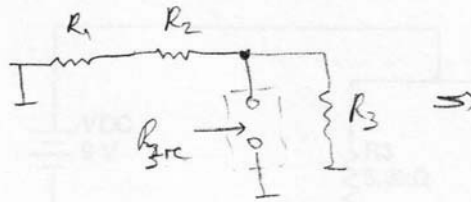

$$\Rightarrow R_{3oc} = R_3 \parallel (R_1 + R_2) = 10k\Omega \parallel 10.1k\Omega$$

$$R_{3oc} \approx 5k\Omega$$

↓

$$\tau_{3oc} = R_{3oc} \cdot C_3 = 5 \cdot 10^3 \cdot 10 \cdot 10^{-12} s$$


$$\tau_{3oc} = 50 \cdot 10^{-9} s = 50 ns$$

$$\omega_H = \frac{1}{\tau_{2oc} + \tau_{3oc}} = \frac{1}{10^{-9} + 50 \cdot 10^{-9} s^{-1}} = \frac{10^9}{51} \text{ rad/s} \approx \frac{1000}{51} \cdot 10^6 \text{ rad/s}$$

$$\omega_H \approx 20 \cdot 10^6 \text{ rad/s}$$

$\tau_{2oc} \ll \tau_{3oc} \Rightarrow C_3$  is the responsible for the dominant pole  $\omega_H, 3dB$

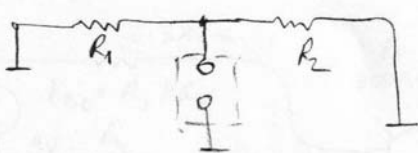It remains to compute the pole given by  $C_2$  ( $C_2$  is now in the lower frequency region, and it will be treated as short circuit)



$$\Rightarrow R'_{2oc} = R_2 \parallel R_1 = 10k\Omega \parallel 100\Omega \approx 100\Omega$$

↓

$$\tau'_{2oc} = R'_{2oc} C_2 = 10^{-9} s$$

↓


$$\omega_2 = \frac{1}{\tau'_{2oc}} = 10^9 \text{ rad/s}$$

The final transfer function is:


$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{s}{s+50} \cdot \frac{1}{2} \cdot \frac{1}{\left(1 + \frac{s}{20 \cdot 10^6}\right) \left(1 + \frac{s}{10^9}\right)}$$

► The Bode plot of

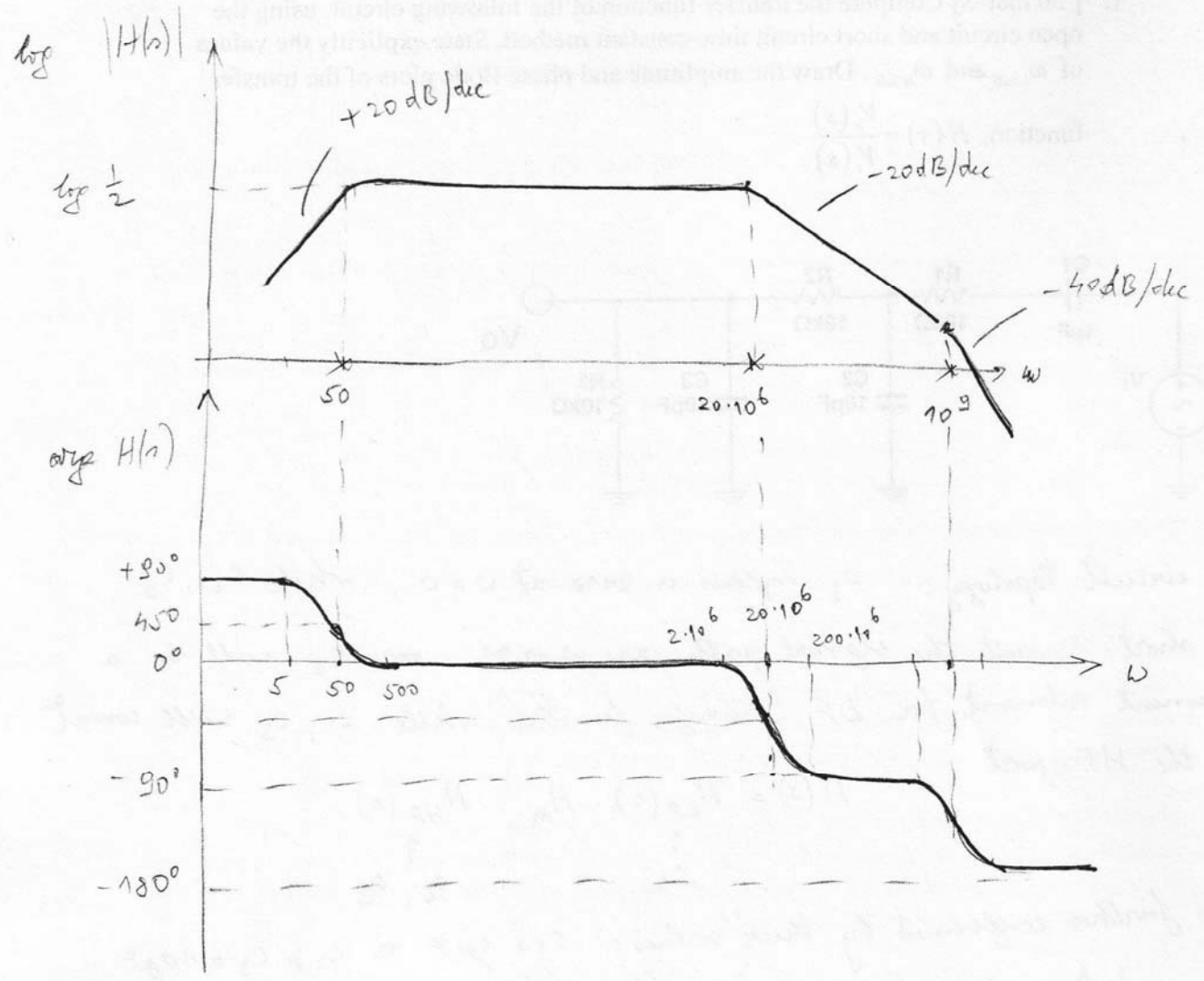
$$H(s) = \frac{s}{s+50} \cdot \frac{1}{2} \cdot \frac{1}{\left(1 + \frac{s}{20 \cdot 10^6}\right) \left(1 + \frac{s}{10^9}\right)}$$



2. [50 marks] The bipolar transistor in the following circuit has  $\beta = 100$ .
- Compute the DC operating point ( $I_B, I_C, V_{CE}$ )
  - Redraw the schematic for the small signal analysis. Compute the midband gain value  $A = \left. \frac{V_{out}}{V_{in}} \right|_{\text{midband}}$  (you may use  $V_T \approx 25mV$ )
  - What is the value of the equivalent impedance seen by the voltage source  $V_{in}$  (the input impedance of the transistor amplifier stage) in the midband?

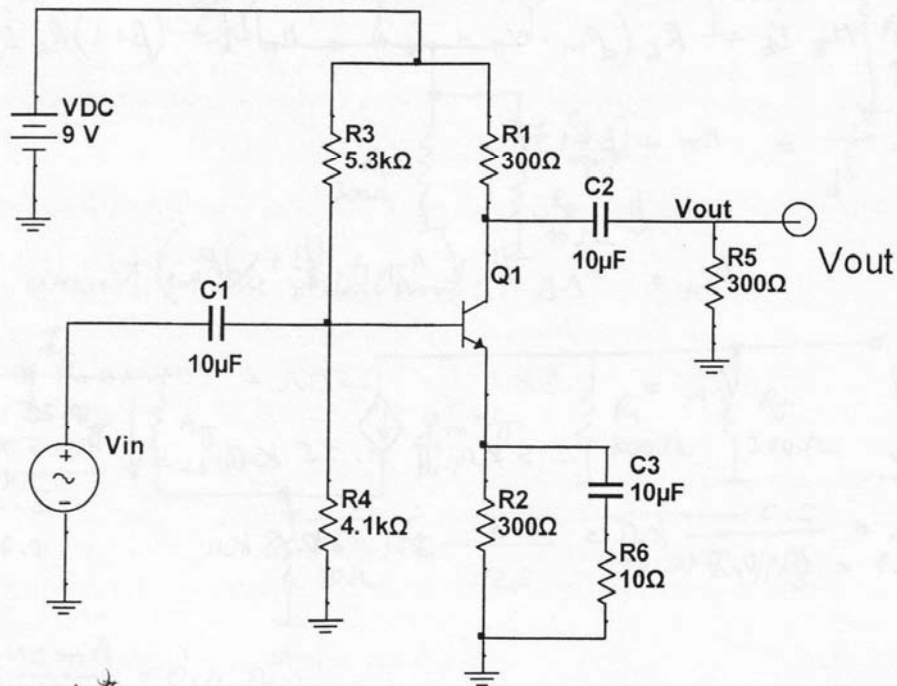

a) For the DC operating point

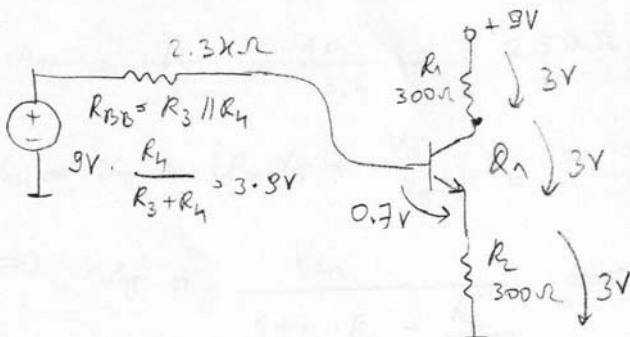

$$V_{BB} = 9V \cdot \frac{R_1}{R_3 + R_1} = 9V \cdot \frac{4.1}{4.1 + 5.3} = 9V \cdot \frac{4.1}{9.4}$$

$$\begin{array}{r} 36.9 \quad | \quad 94 \\ 282 \quad | \quad 3.9 \\ \hline = 870 \\ 846 \\ \hline 24 \end{array}$$

$$V_{BB} \approx 3.9V$$

$$R_3 || R_1 = \frac{4.1 \cdot 5.3}{9.4} = \frac{21.7 \text{ k}\Omega}{9.4} \approx 2.3 \text{ k}\Omega$$

$$\begin{array}{r} 4.1 \\ 5.3 \\ \hline 123 \\ 205 \\ \hline 21.73 \end{array}$$

$$\begin{array}{r} 217 \quad | \quad 94 \\ 188 \quad | \quad 2.3 \\ \hline = 290 \end{array}$$

We assume that  $Q_1$  is in the active operating region  $\Rightarrow V_{BE} \approx 0.7V$

$$V_{BB} = R_{BB} I_B + V_{BE} + R_2 I_E = V_{BE} + \left( \frac{R_{BB}}{\beta + 1} + R_2 \right) I_E \Rightarrow$$

$$\Rightarrow I_E = \frac{V_{BB} - V_{BE}}{\frac{R_{BB}}{\beta + 1} + R_2} = \frac{3.9V - 0.7V}{\frac{2.3 \text{ k}\Omega}{101} + 300\Omega} \approx \frac{3.2V}{320\Omega} = 10 \text{ mA}$$

$$I_c = \alpha I_E \approx I_E = 10 \text{ mA}$$


$$I_B = \frac{I_c}{\beta} = \frac{10 \text{ mA}}{100} = 100 \mu\text{A}$$

$$V_c = V_{CC} - R_1 I_c = 9 \text{ V} - 300 \cdot 10 \cdot 10^{-3} \text{ V} = 6 \text{ V}$$


↓

$$V_{CE} = V_{CC} - R_1 I_c - R_2 I_E = 3 \text{ V}$$

(b) Small signal analysis circuit:

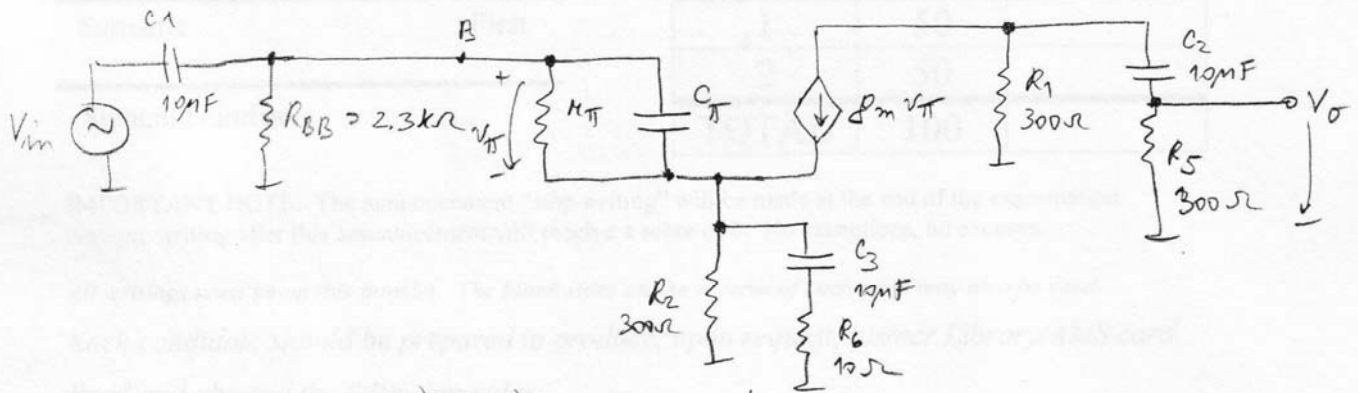

The small signal circuit in the midband:

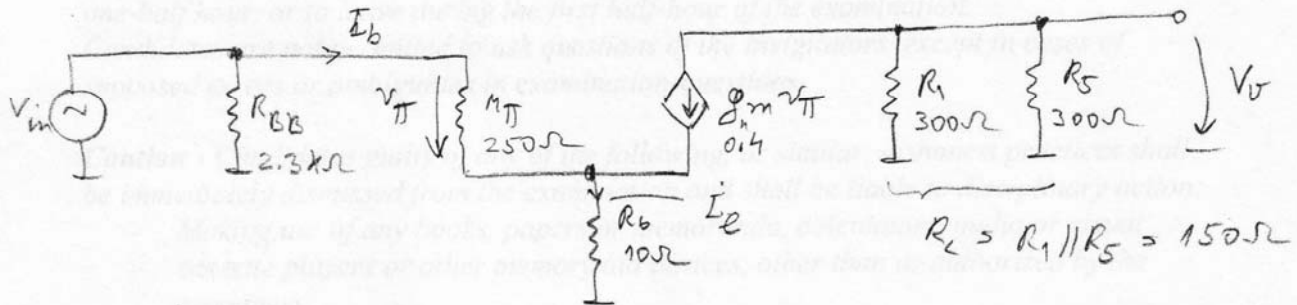

$$\beta_m = \frac{I_c}{V_T} \approx \frac{10 \text{ mA}}{25 \text{ mV}} = 0.4 \text{ S}^{-1}$$

$$r_{\pi} = \frac{\beta}{\beta_m} = \frac{100}{0.4} \Omega = 250 \Omega$$

$$V_{in} = v_{\pi} + \left( \beta_m v_{\pi} + \frac{v_{\pi}}{r_{\pi}} \right) R_6 = v_{\pi} \left( 1 + \beta_m R_6 + \frac{R_6}{r_{\pi}} \right) \Rightarrow$$

$$\Rightarrow v_{\pi} = \frac{V_{in}}{1 + \beta_m R_6 + \frac{R_6}{r_{\pi}}}$$


$$V_o = -\beta_m v_{\pi} R_L$$

$$V_o = -\frac{\beta_m}{1 + \beta_m R_6 + \frac{R_6}{r_{\pi}}} \cdot R_L \cdot V_{in}$$

$$A_{\text{midband}} = \left. \frac{V_o}{V_{in}} \right|_{\text{midband}} = -\frac{\beta_m R_L}{1 + \beta_m R_6 + \frac{R_6}{r_{\pi}}} = -\frac{0.4 \times 150}{1 + 0.4 \times 10 + \frac{10}{250}} =$$

$$= -\frac{60}{1 + 4 + 0.04} \approx -\frac{60}{5} = -12$$

c) The equivalent input impedance:

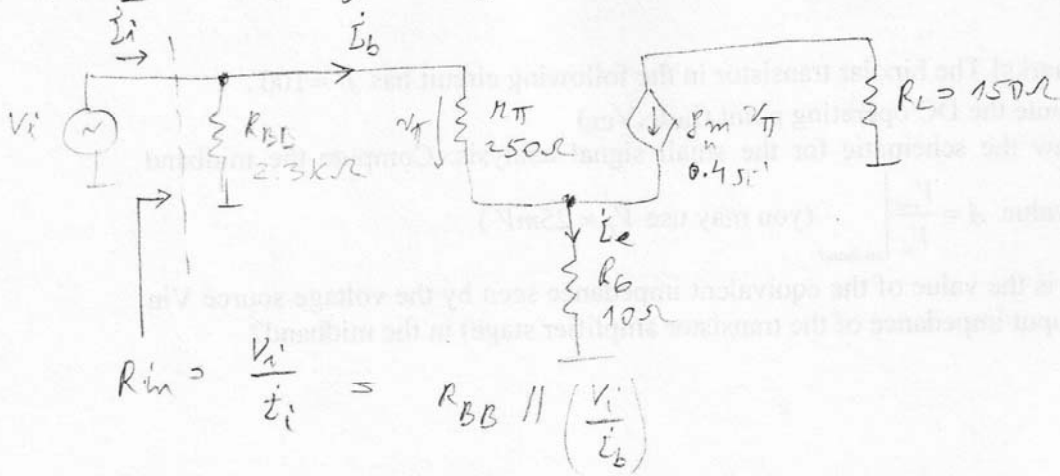

$$V_i = r_{\pi} I_b + R_e (\beta I_b + I_b) = r_{\pi} I_b + (\beta + 1) R_e I_b \Rightarrow$$

$$\Rightarrow \frac{V_i}{I_b} = r_{\pi} + (\beta + 1) R_e$$

$$R_{in} = R_{BB} \parallel (r_{\pi} + (\beta + 1) R_e)$$

$$R_{in} = 2.3 \text{ k}\Omega \parallel (250 \Omega + 101 \cdot 100 \Omega)$$

$$= 2.3 \text{ k}\Omega \parallel 1.25 \text{ k}\Omega = \frac{1.25 \times 2.3}{3.55} \text{ k}\Omega$$

$$R_{in} = \frac{2.3}{4 \cdot 0.71} \text{ k}\Omega = \frac{2.3}{2.84} \text{ k}\Omega \approx 0.8 \text{ k}\Omega$$