ELEC 343, Assignment 6: Solution:

Do Study Problem: SP6.2-2 and SP6.2-3; SP6.8-4. and do the Example 6C (this will help you for the Lab-5!) and Example 6D.

Textbook Chapter Problem(s): 15 and 21.

SP6.2-2. (a) The frequency of the rotor currents is

$$\frac{1}{2\pi} \left(\omega_{\rm e} - \omega_{\rm r} \right) = \frac{1}{2\pi} \left[(2\pi)(60) - (0.9)(2\pi)(60) \right] = 6 \text{ Hz}$$

- (b) From the rotor both appear to be traveling at $\omega_e \omega_r$. Thus, $\omega_e \omega_r = \omega_e 0.9 \,\omega_e = (0.1)(2\pi)(60) = 37.7 \text{ rad/s}$, ccw.
- (c) From the stator both appear to be traveling at $\omega_{\rm e}$, ccw; or 377 rad/s, ccw.

SP6.2-3. (a)
$$\frac{1}{2\pi}(\omega_e - \omega_r) = (1 - 1.1)60 = 6$$
 Hz.

We need not recognize a negative frequency here. Answer same regardless of the number of poles.

- (b) For two poles, $\omega_{\rm e}-\omega_{\rm r}=-0.1\,\omega_{\rm e}=37.7\,{\rm rad/s},$ cw. For six poles, $(\frac{2}{\rm P})37.7=\frac{37.7}{3}\,{\rm rad/s}$ cw.
- (c) $(\frac{2}{P})\omega_e = \frac{377}{3} \text{ rad/s, ccw.}$

SP6.8-4. (a)
$$Z = r_s + j \omega_e (L_{ls} + L_{ms}) = 20 + j (377)(0.025 + 0.3) = 20 + j 122.5$$

 $\tilde{I}_{as} = \frac{\tilde{V}_{as}}{Z} = \frac{115 / 0^{\circ}}{20 + j 122.5} = \frac{115 / 0^{\circ}}{124.1 / 80.75} = 0.927 / -80.75^{\circ} A$

(b)
$$Z = (r_s + r_r') + j \omega_e (L_{ls} + L_{lr}') = (20 + 20) + j (377)(0.025 + 0.025) = 40 + j 18.85$$

 $\tilde{I}_{as} = \frac{\tilde{V}_{as}}{Z} = \frac{115 / 0^{\circ}}{40 + j 18.85} = \frac{115 / 0^{\circ}}{44.3 / 25.2} = 2.6 / -25.2^{\circ} A$

15. From Example 6B with $\omega_e = 377 \text{ rad/s}$,

$$\begin{array}{lll} r_s &= 0.531 \; \Omega & & r_r^{'} &= 0.374 \; \Omega \\ X_{ss} = X_{ls} + X_{ms} & & X_{rr}^{'} = X_{lr}^{'} + X_{ms} \\ &= 2.29 + 26.2 = 28.49 \; \Omega & & = 2.29 + 26.2 = 28.49 \; \Omega \end{array}$$

Now, from (6.8-28) and (6.8-29),

$$s_m = r_r' G$$

$$G = \pm \left[\frac{r_{s}^{2} + X_{ss}^{2}}{(X_{ms}^{2} - X_{ss} X_{rr}^{'})^{2} + r_{s}^{2} X_{rr}^{'2}} \right]^{\frac{1}{2}}$$

(a)
$$s_m = 0.374 \left\{ \frac{(0.531)^2 + (4)(28.49)^2}{(4)[(26.2)^2 - (28.49)^2]^2 + (0.531)^2 (4)(28.49)^2} \right\}^{\frac{1}{2}}$$

 $= 0.0845$
 $\omega_r = (1 - 0.0845)(377)(2) = 690.3 \text{ rad/s}$
 $\omega_{rm} = \frac{2}{P} \omega_r = (\frac{2}{4})(690.3) = 345.2 \text{ rad/s}$

(b)
$$s_{m} = 0.374 \left\{ \frac{(0.531)^{2} + (28.49)^{2}}{[(26.2)^{2} - (28.49)^{2}]^{2} + (0.531)^{2} (28.49)^{2}} \right\}^{\frac{1}{2}}$$
$$= 0.0845$$
$$\omega_{rm} = (\frac{2}{4})(1 - 0.0845)(377) = 172.6 \text{ rad/s}$$

(c)
$$s_m = 0.374 \left\{ \frac{(0.531)^2 + (\frac{1}{4})(28.49)^2}{(\frac{1}{4})[(26.2)^2 - (28.49)^2]^2 + (0.531)^2 (\frac{1}{4})(28.49)^2} \right\}^{\frac{1}{2}}$$

$$= 0.0845$$

$$\omega_{rm} = (\frac{2}{4})(1 - 0.0845)(\frac{1}{2})(377) = 86.3 \text{ rad/s}$$

(d)
$$s_m = 0.374 \left\{ \frac{(0.531)^2 + (\frac{1}{100})(28.49)^2}{(\frac{1}{100})[(26.2)^2 - (28.49)^2]^2 + (0.531)^2(\frac{1}{100})(28.49)^2} \right\}^{\frac{1}{2}}$$

 $= 0.0859$
 $\omega_{rm} = (\frac{2}{4})(1 - 0.0859)(\frac{1}{10})(377) = 17.2 \text{ rad/s}$

21. (a)
$$\tilde{I}_{as} = \frac{\tilde{V}_{as}}{Z}$$

Neglecting the current flowing in X_M

Z =
$$(r_s + r'_r) + j(X_{ls} + X'_{lr})$$

= $(0.3 + 0.15) + j(377)(1.5 + 0.7) \times 10^{-3}$
= $0.45 + j0.829 = 0.944 / 61.5^{\circ} \Omega$

$$\tilde{I}_{as} = \frac{110 / 0^{\circ}}{0.944 / 61.5^{\circ}} = 116.6 / -61.5^{\circ} A$$

From (6.8-26),

$$T_{e} = \frac{(\frac{3}{2})(2)(\frac{P}{2})\frac{X_{M}^{2}}{\omega_{e}} r_{r}^{'} s |\tilde{V}_{as}|^{2}}{\left[r_{s}r_{r}^{'} + s(X_{M}^{2} - X_{ss}X_{rr}^{'})\right]^{2} + (r_{r}^{'}X_{ss} + s r_{s}X_{rr}^{'})^{2}}$$

For a 60 Hz supply,

$$X_{\rm M} = \omega_{\rm e}(\frac{3}{2})L_{\rm ms}$$

= $(377)(\frac{3}{2})(35 \times 10^{-3}) = 19.79 \ \Omega$

$$\begin{split} X_{ss} &= \omega_e \, (L_{ls} + \frac{3}{2} \, L_{ms}) = (377)[1.5 + (\frac{3}{2})(35)] \times 10^{-3} \\ &= 20.36 \, \, \Omega \end{split}$$

$$X'_{rr} = \omega_e (L'_{lr} + \frac{3}{2} L_{ms}) = (377)[0.7 + (\frac{3}{2})(35)] \times 10^{-3}$$

= 20.06 Ω

With s = 1,

$$T_{e} = \frac{(3)(\frac{4}{2})\frac{(19.79)^{2}}{377}(0.15)(110)^{2}}{[(0.3)(0.15) + (19.79)^{2} - (20.36)(20.06)]^{2} + [(0.15)(20.36) + (0.3)(20.06)]^{2}}$$

$$= 31.9 \text{ N·m}$$

(b)
$$\tilde{I}_{as} = \frac{\ddot{V}_{as}}{Z}$$

$$Z = r_s + j X_{ss} = 0.3 + j 20.36$$

= $20.36 / 89.2^{\circ}$

$$\tilde{I}_{as} = \frac{110/0^{\circ}}{20.36/89.2^{\circ}} = 5.40/-89.2^{\circ} A$$

Additional Problem:

Consider a 25hp, 3-phase, Y-connected, 220V line-to-line, 60Hz Induction Motor NEMA* Type B. The motor operates at full nominal load and the following is known: input electrical power $P_{e,in} = 20.8 \mathrm{kW}$; output mechanical power $P_{m,out} = 25 \mathrm{HP}$; stator phase current $I_{as} = 64 \mathrm{A(rms\ value)}$; motor shaft speed $n = 830 \mathrm{rpm}$. Establish and/or calculate the following:

- a) Number of magnetic poles f_r
- b) Actual electrical frequency of the rotor currents f_r (assuming stator frequency $f_s = f_e$ is 60Hz)
- c) Input power factor pf as seen by the source
- d) Mechanical (load) torque T_m
- e) Motor efficiency $\eta[\%]$ under the given load

Number of poles P

$$N_{syn} = \frac{120}{p} \cdot 5e^{-\frac{1205e}{N_{syn}}} = \frac{1206e}{n}$$
 $P = \frac{120 \cdot 60}{830} = \frac{120 \cdot 60}{830} = \frac{1206e}{830} = \frac{1206e}{8300} = \frac{1206e$