


Lecture 10

Static MOS Gate and Flip-Flop Circuits (HJS Chapter 5)

Res Saleh
Dept. of ECE
University of British Columbia
res@ece.ubc.ca


Combinational MOS Logic

- Now that we understand the logic abstraction and the properties of valid logic gates, we can consider the issues of design basic building blocks of digital systems
- Typical combinational gate is a multiple input – single output system
- Performs Boolean operations on multiple input variables, drives one or more gates
- Design parameters and considerations:
 - Propagation delay
 - Static and dynamic power
 - Area
 - Noise margins (VTC)

 

Pull-up and Pull-down Networks

 **Basic Structure
Of all CMOS logic gates**




- PMOS pull-up and NMOS pull-down networks are duals of each other
- Configuration of pull-up and pull-down networks create a current connection from the output to *either* V_{DD} or Gnd , based on the inputs
- PMOS devices have lower drive capability and thus require wider devices to achieve the same on-resistance as its pull-down counterpart

RAS

EECE481 Lecture 10

3

Static CMOS Logic Gates

 

- These are the most common type of static gates
- Can implement any Boolean expression with these two gates
- Why is static CMOS so popular?
 - It's very robust! ("nearly idiot-proof")
 - it will eventually produce the right answer
 - Power, shrinking V_{DD} , more circuit noise, process variations, etc. limit use of other design styles

RAS

EECE481 Lecture 10

4

More Properties of Static CMOS Logic

- Fully complementary
- Low static power dissipation!
- Outputs swing full rail – V_{dd} (V_{OH}) to Gnd (V_{OL})
- Works fine at low V_{dd} voltages
 - But lower V_{dd} = less current = slower speed
- Combinational operation
 - Feed it some inputs, wait some delay, result comes out
 - No clocks required for normal operation
- Moderately good performance
 - Drive strength is proportional to transistor size
 - Large loads require large W
- Dual logic networks for N- and P-Channel devices


RAS

EECE481 Lecture 10

5

“Beta Ratio” for Static Gates

- The ratio between the NMOS and PMOS device is called the beta ratio
- We need to size CMOS static gates to deliver a target speed. But how?
- Start by sizing the inverter to deliver the target speed, then map size to gate
- Suppose:
 - R_{eqp} (PMOS) $\approx 2.5 R_{eqn}$ (NMOS) under identical conditions
(actually $R_{eqp} = 30k\Omega$ and $R_{eqn} = 12.5k\Omega$)
- Then ratio between PMOS:NMOS should be 2.5:1
- Beta ratio sets:
 - Switching point of the gate output drive
 - Input capacitance
 - L-to-H vs. H-to-L transition times
 - Usually find a 2:1 ratio in CMOS inverter

 

Is 2:1 the right ratio?

For equal rise and fall times. 2.5:1

How about for minimum delay? 1.7:1


RAS

EECE481 Lecture 10

6


NAND and NOR Sizing

First Design Inverter

 


(a) Inverter

Then Map Results to Gates

 

(b) NAND

 



(c) NOR

- Drive strength determined by device widths - W (assume L is minimum size)
- For the moment, consider only C_L (we are ignoring the device self-capacitance)
- Pick the right sizes for the basic inverter and then assign values to gates
- What does that mean for parallel and series combinations?
 - For parallel transistors, direct mapping from inverter
 - For series transistors, need to compute equivalent sizes

Equivalent Sizes

 Consider a three-input NAND gate (NMOS portion only):





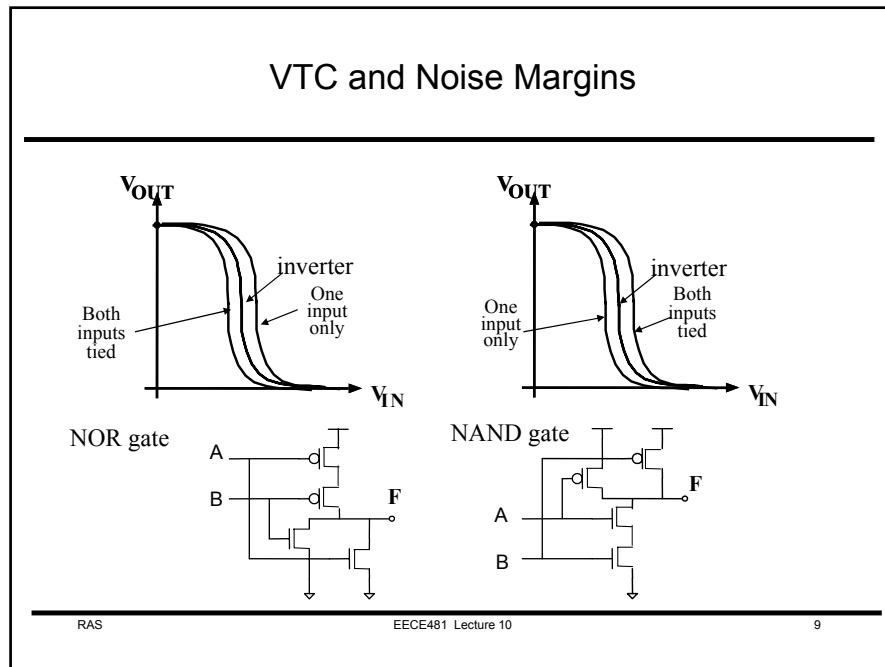

Complex Logic Circuits

- The ability to easily build complex logic gates is one of the most attractive features of MOS logic circuits
- Design principle of the pull-down network:
 - OR operations are performed by parallel connected drivers
 - AND operations are performed by series connected drivers
 - Inversion is provided by the nature of MOS circuit operation
- Don't get too carried away... Use this knowledge wisely
 - Remember that complex functions don't have to be implemented with a single gate
 - Can break up very complicated Boolean expressions into a cascade of gate stages
 - Limit series stacks to 3~4
- We will use De Morgan's Law to build the dual networks

Review of DeMorgan's Law

  

- De Morgan's theorem:
The complement of any logic function is found by complementing all input variables and replacing all AND operations with OR and all OR operations with AND
- Use De Morgan's law to find the complement of a function for the pull-down network (if needed)
- Use Duality to find the pull-up network


RAS

EECE481 Lecture 10

11

Complex CMOS Gate Design Example

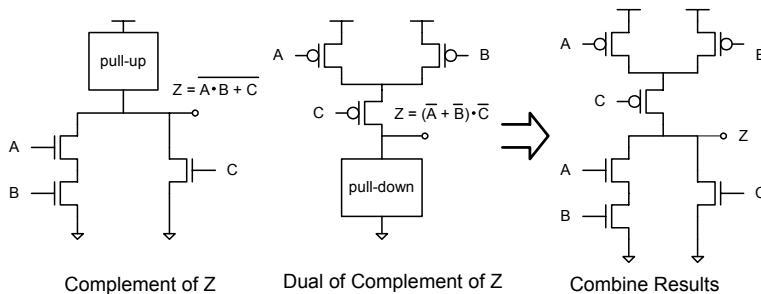- Implement an AND-OR-INVERT (AOI) function
 $Z = \overline{A \cdot B + C}$
- Get the expression into forms that enable easy implementation of pull-up and pull-down networks
 $\overline{Z} = (A \cdot B + C)$ $Z = (\overline{A + B}) \cdot \overline{C}$




RAS

EECE481 Lecture 10

12

XOR and XNOR Gates

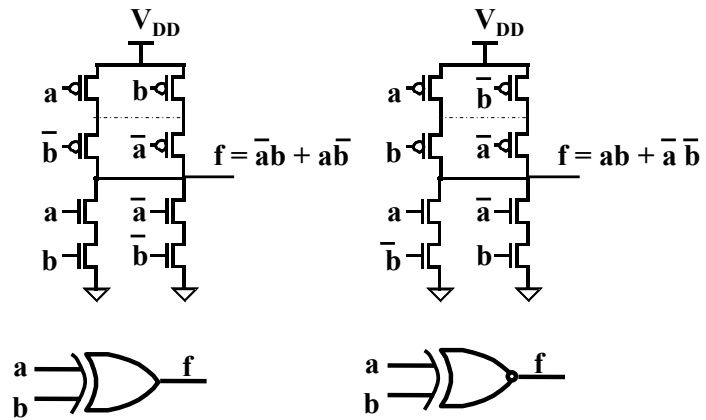


RAS

EECE481 Lecture 10

13

CMOS Multiplexer

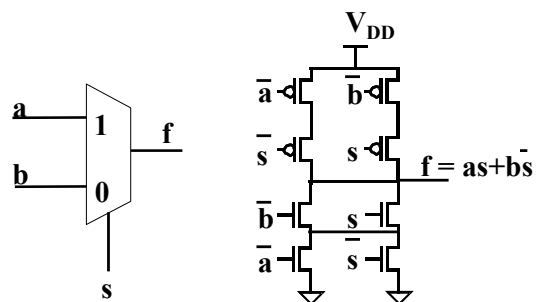

RAS

EECE481 Lecture 10

14

The Bad News


- Slows down dramatically for large fanins due to long series stack of transistors
 - fanin = number of inputs
 - PMOS series stacks worse than nMOS series stacks
- Large number of transistors
 - $2n$ devices for n -input NAND
 - At least 2 devices per input
- Bigger layout
 - $n+$ to $p+$ spacing rule and well spacing rule
 - Large device sizes required to counteract series stack
- Limit the fanin to 3 or 4...or delay and area will be too large

RAS

EECE481 Lecture 10

15

Eight-Input AND gate

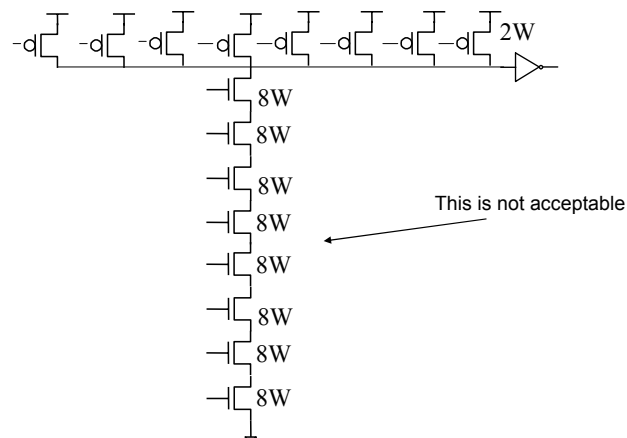


RAS


EECE481 Lecture 10

16

Multi-level Logic Implementations

 

NAND2-INV-NAND2-INV

 

NAND2-NOR2-NAND2-INV


- There are many more options to try
- Which is the best? We need a quick way of answering this question

RAS

EECE481 Lecture 10

17

Pseudo-NMOS Logic – NOR gate

 

A	B	Z
0	0	1
0	1	0
1	0	0
1	1	0



- Design issues:
 - Sizing Ratio
 - Ratio pull-up to pull-down (V_{OL} & V_{OH})
 - Propagation delay
 - Subthreshold current can degrade V_{OH} slightly
 - V_{OL} decreases as more devices turning on

RAS

EECE481 Lecture 10

18

Pseudo-nMOS Logic – NAND Gate

  

A	B	Z
0	0	1
0	1	1
1	0	1
1	1	0



- Issues
 - Sizing Ratio
 - Need to make pull-down devices wider
 - Parasitic cap goes up with bigger devices
 - Lower devices in stack slower compared to upper ones because they see more capacitance

RAS

EECE481 Lecture 10

19

AND8 Option - Use Pseudo-NMOS

  

RAS

EECE481 Lecture 10

20

Properties of Static Pseudo-NMOS Gates

- DC power
 - always conducting current when output is low
- V_{OL} and V_{OH} depend on sizing ratio and input states
- Poor low-to-high transition
- Large fanin NAND gates tend to get big due to ratioing
- As transistor count increases, power consumption is too high
 - Cannot use this approach for all gates on the chip
- But what are its advantages?
 - Good for wide NOR structures
 - Memory decoder
 - Smaller number of transistors (area) / logic function

RAS


EECE481 Lecture 10

21


Flip-Flops and Latches

Flip-flops and latches are important logic elements used for storage

 We typically build finite state machines from combinational logic (next state logic) and latches or flip-flops (storage elements) to store the state information.



 We then control latches and flip-flops with a clock to create synchronous logic circuits. The clock ensures that we can tell the difference between previous, current and future states of the logic circuit



RAS

EECE481 Lecture 10

22

Latch vs. Flip-flop

Latch (level-sensitive, transparent)
 When the clock is high it passes **In** value to **Out**
 When the clock is low, it holds value that **In** had when the clock fell

Flip-Flop (edge-triggered, non transparent)
 On the *rising* edge of clock (pos-edge trig), it transfers the value of **In** to **Out**
 It holds the value at all other times.

RAS
EECE481 Lecture 10
23

FF Clocking Overhead


FF have setup and hold times that must be satisfied:

If **Din** arrives before setup time and is stable after the hold time, FF will work; if **Din** arrives after hold time, it will fail; in between, it may or may not work; FF delays the slowest signal by the setup + clk-q delay in the worst case

RAS
EECE481 Lecture 10
24

Latch Clocking Overhead

 
Latches also have setup and hold times that must be satisfied:



But latch has small setup and hold times; however, it delays the late arriving signals by T_{d-q} and this is more important than the setup and hold times.


SR Latch with NOR Gates

 - Simplest FF is a cross-coupled pair of NOR gates
- When $S=1$, $Q=1$
- When $R=1$, $Q=0$
- By setting both $S=0$ and $R=0$, the previous state is held
- Illegal state occurs when $R=1$ and $S=1$ (actually, the final state is determined by which signal goes low last)



SR Latch with NAND Gates

 - Similar to NOR latch except that the signals are *active low*
- Illegal state is now $S=0$ and $R=0$
- Hold state is $S=1$ and $R=1$




RAS

EECE481 Lecture 10

27

JK Flip-flop

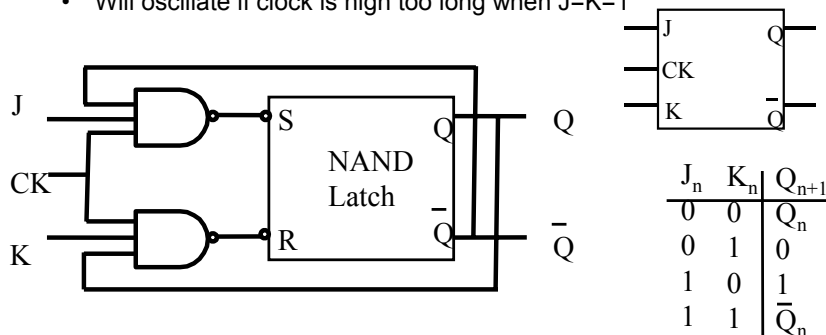- To avoid illegal state, use JK flip-flop
- In NAND implementation, $J=K=1$ flips the state of the output
- Clock is used to enable the output
- Will oscillate if clock is high too long when $J=K=1$




RAS

EECE481 Lecture 10

28

Master-Slave JK Flip-flop

 - Cascade of two JK Flip-flops
- Master activated by CK, Slave activated by \overline{CK}
- Master latches new data, slave launches old data



RAS



EECE481 Lecture 10

29

Clocked D Flip-flop

- Very useful FF
- Widely used in IC design for temporary storage of data
- May be *edge-triggered* (Flip-flop) or *level-sensitive (transparent D-latch)*

D	Q_{n+1}
0	0
1	1

  

Can implement
As AOI function

RAS

EECE481 Lecture 10

30