

Chapter 3

Logic and Fault Simulation

About the Chapter


- ❑ Circuit simulation models
- ❑ Logic simulation techniques
- ❑ Fault simulation techniques

Logic and Fault Simulation

- ❑ Introduction
- ❑ Simulation models
- ❑ Logic simulation
- ❑ Fault simulation
- ❑ Concluding remarks

Logic Simulation

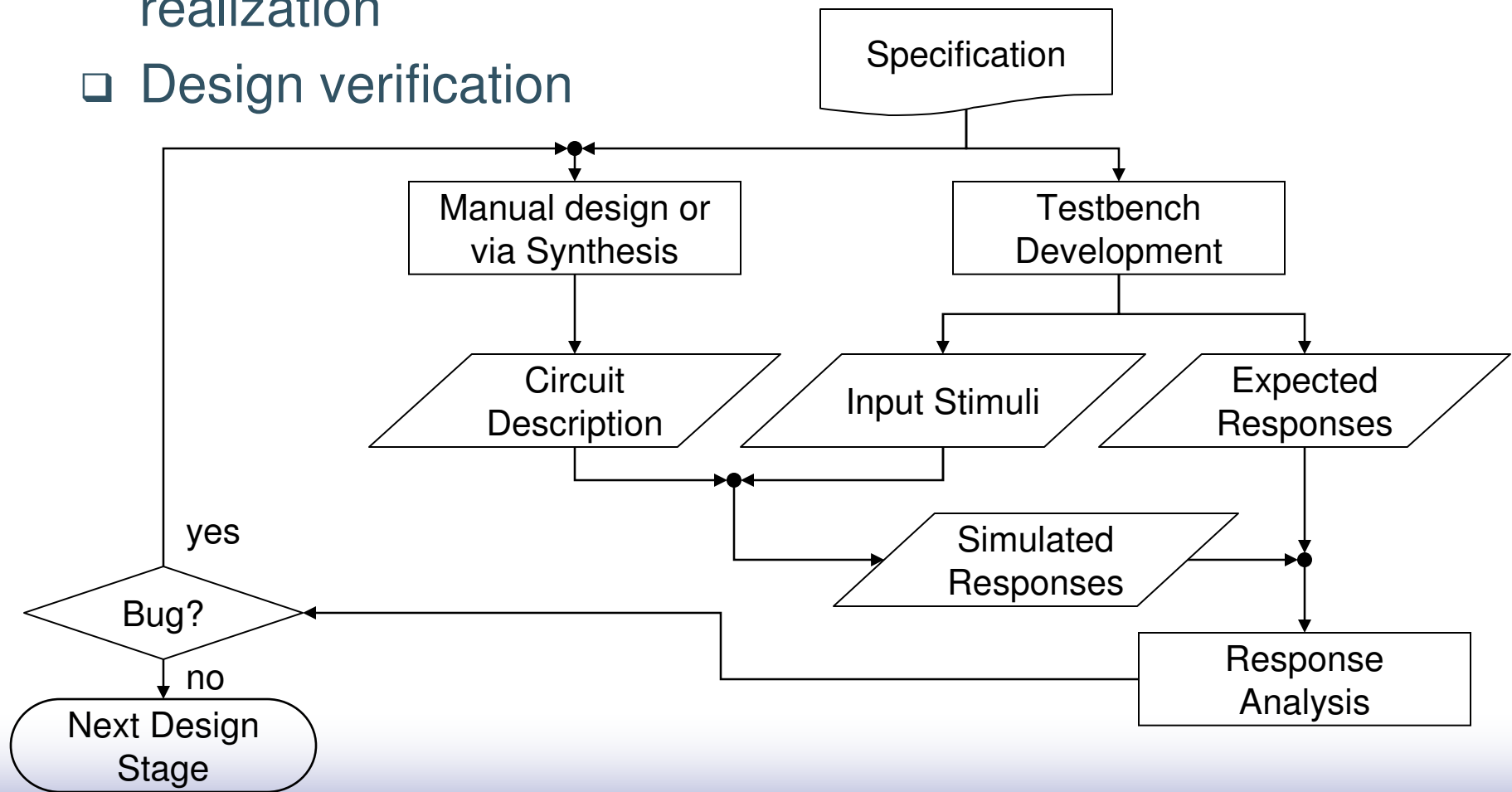- ❑ Predict the behavior of a design prior to its physical realization
- ❑ Design verification



Fault Simulation


- Predicts the behavior of faulty circuits
 - As a consequence of inevitable fabrication process imperfections
- An important tool for test and diagnosis
 - Estimate fault coverage
 - Fault simulator
 - Test compaction
 - Fault diagnosis

Logic and Fault Simulation

- ❑ Introduction
- ❑ **Simulation models**
- ❑ Logic simulation
- ❑ Fault simulation
- ❑ Concluding remarks

Gate-Level Network

- The interconnections of logic gates

 

Sequential Circuits


- The outputs depend on both the current and past input values

x_i : primary input (PI)


z_i : primary output (PO)

y_i : pseudo primary input (PPI)

Y_i : pseudo primary output (PPO)

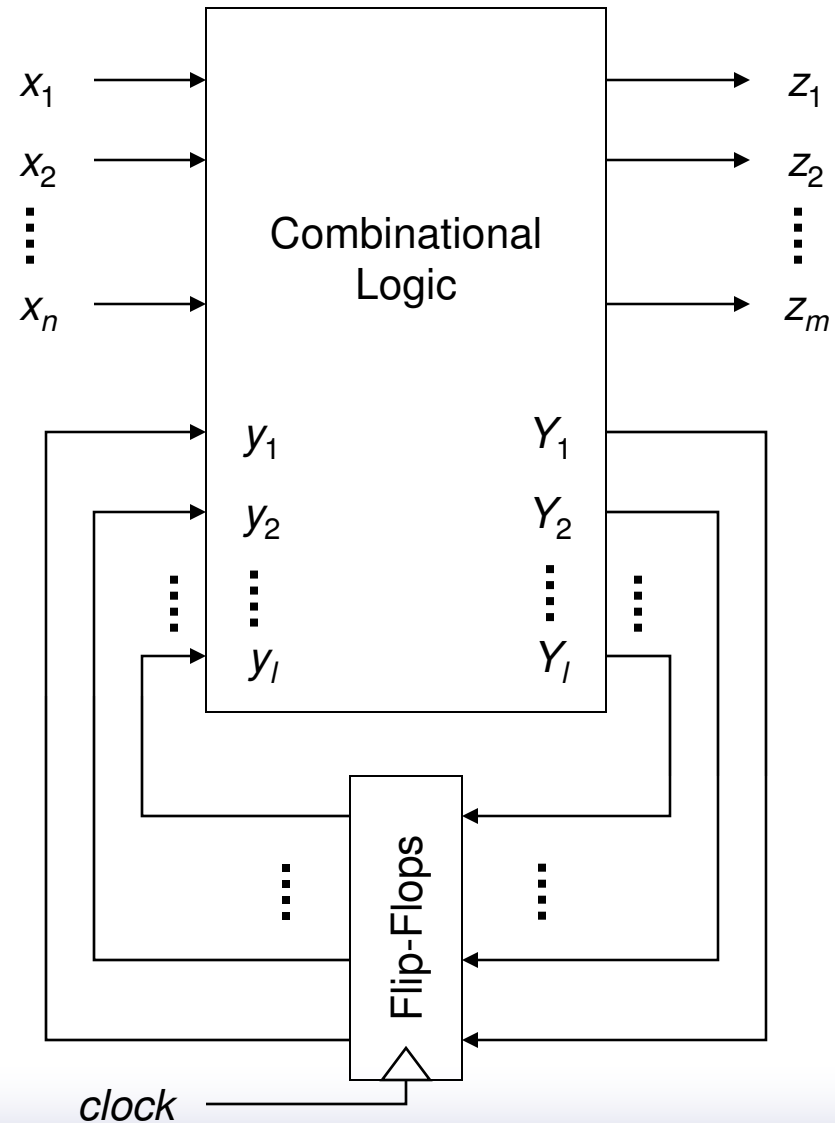

A Positive Edge-Triggered D-FF

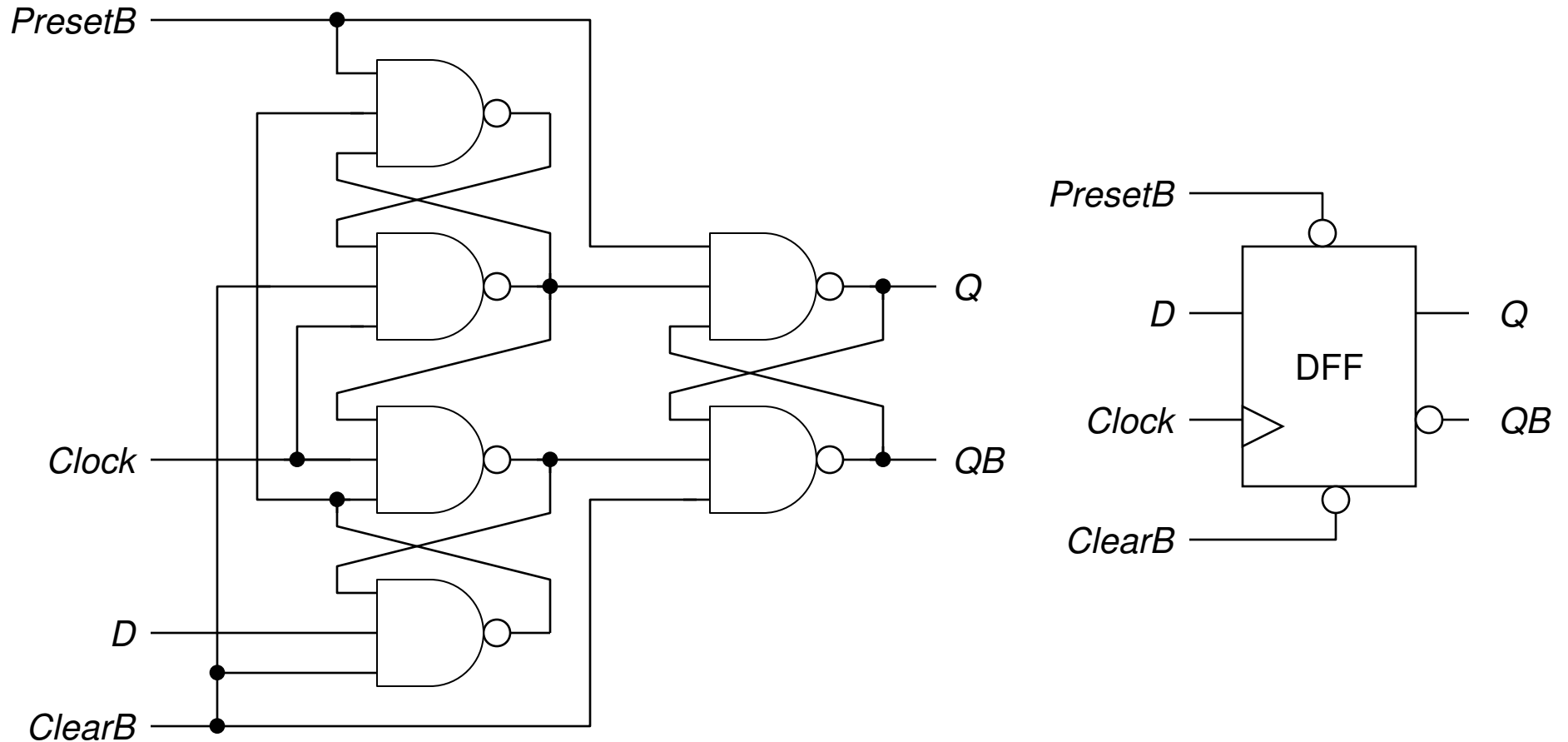

Logic Symbols

- ❑ The most commonly used are 0, 1, u and Z
- ❑ 1 and 0
 - *true* and *false* of the two-value Boolean algebra
- ❑ u
 - Unknown logic state (maybe 1 or 0)
- ❑ Z
 - High-impedance state
 - Not connected to V_{dd} or ground

Ternary Logic

- Three logic symbols: 0, 1, and u


AND	0	1	u
0	0	0	0
1	0	1	u
u	0	u	u

OR	0	1	u
0	0	1	u
1	1	1	1
u	u	1	u

NOT	0	1	u
	1	0	u


Information Loss of Ternary Logic

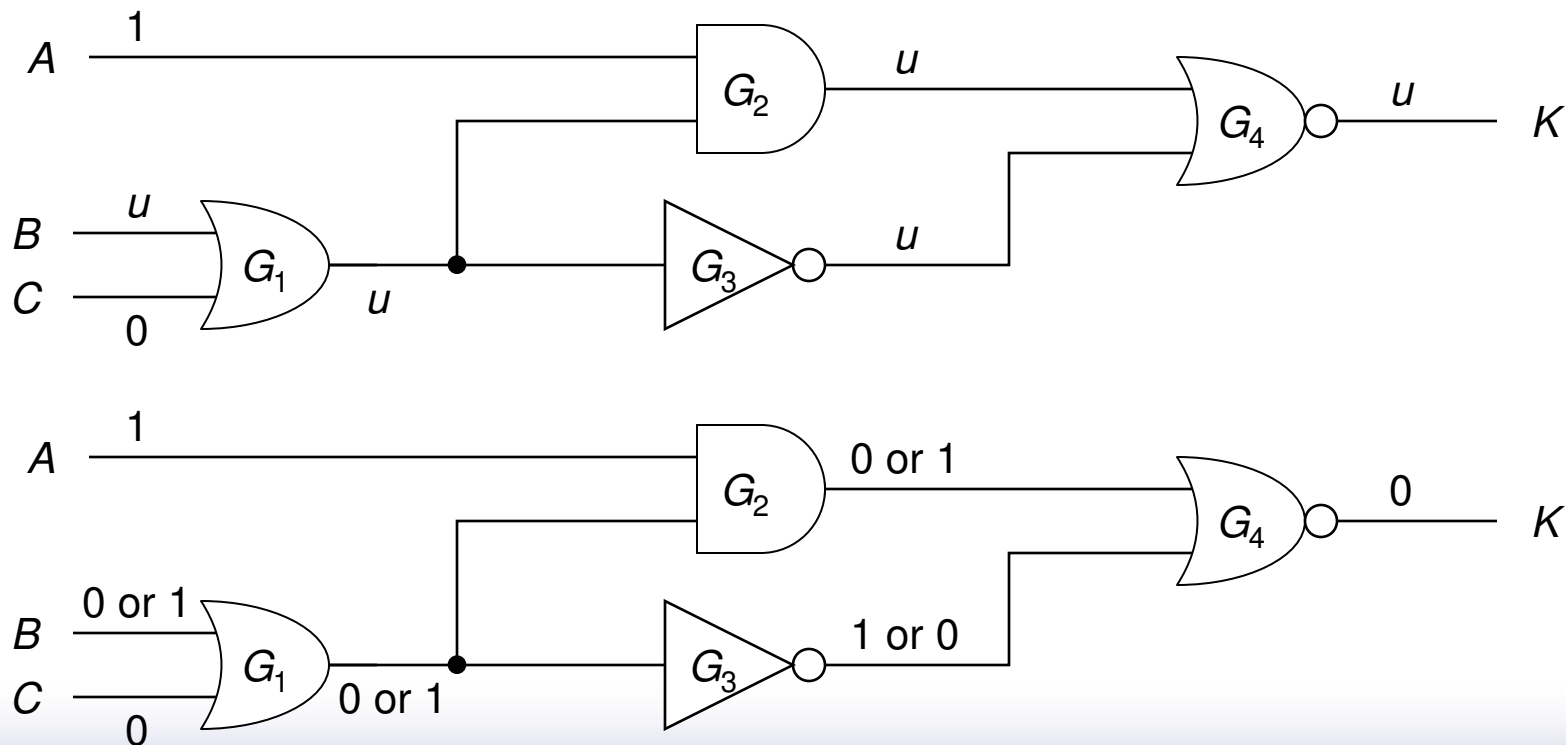- ❑ Simulation based on ternary logic is pessimistic
- ❑ A signal may be reported as unknown when its value can be uniquely determined as 0 or 1



High-Impedance State Z

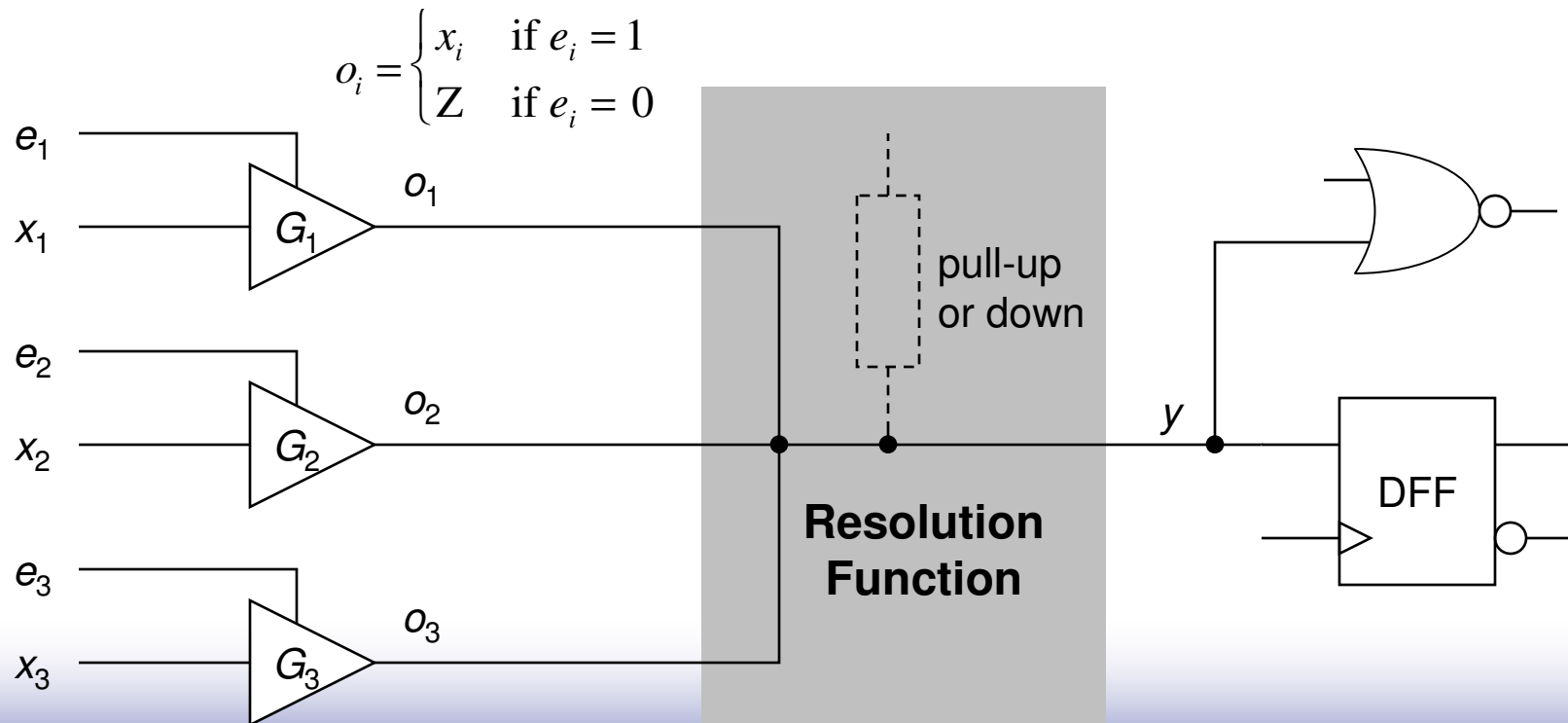- Tri-state gates permit several gates to time-share a common wire, called bus
- A signal is in high-impedance state if it is connected to neither V_{dd} nor ground



Resolving Bus Conflict

- ❑ Bus conflict occurs if at least two drivers drive the bus to opposite binary values
- ❑ To simulate tri-state bus behavior, one may insert a resolution function for each bus wire
 - May report only the occurrence of bus conflict
 - May utilize multi-valued logic to represent intermediate logic states (including logic signal values and strengths)

Logic Element Evaluation Methods

- Choice of evaluation technique depends on
 - Considered logic symbols
 - Types and models of logic elements
- Commonly used approaches
 - Truth table based
 - Input scanning
 - Input counting
 - Parallel gate evaluation

Truth Table Based Gate Evaluation

- ❑ The most straightforward and easy to implement
 - For binary logic, 2^n entries for n -input logic element
 - May use the input value as table index
 - Table size increases exponentially with the number of inputs
- ❑ Could be inefficient for multi-valued logic
 - A k -symbol logic system requires a table of 2^{mn} entries for an n -input logic element
 - $m = \lceil \log_2 k \rceil$
 - Table indexed by mn -bit words


Input Scanning

- The gate output can be determined by the types of inputs
 - If any of the inputs is the controlling value, the gate output is $c \oplus i$
 - Otherwise, if any of the inputs is u , the gate output is u
 - Otherwise, the gate output is $c' \oplus i$

Table 3.2: The c (controlling) and i (inversion) values of basic gates

	c	i
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1

Input Scanning - cont'd

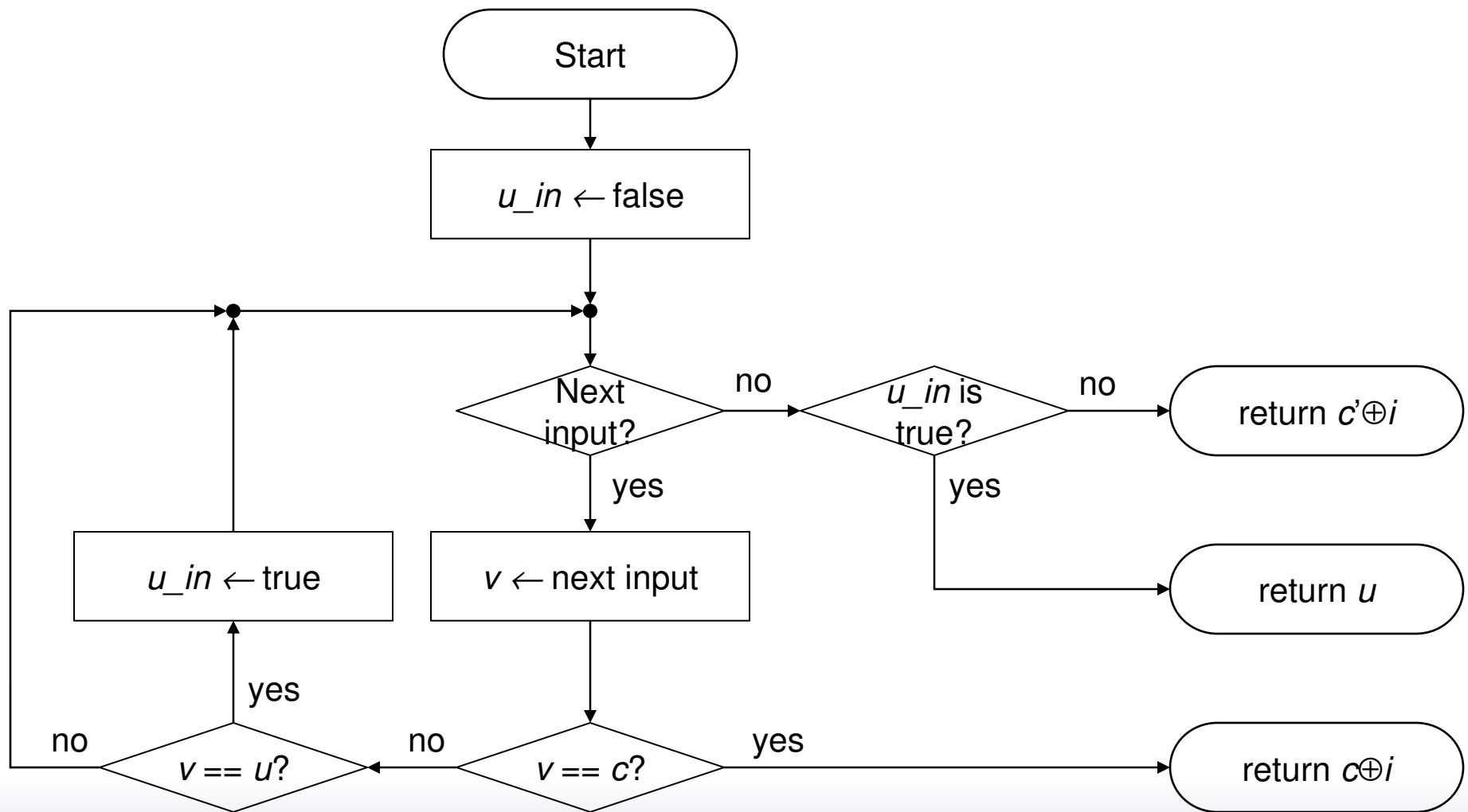


Input Counting

- Keep the counts of controlling and unknown inputs
 - *c_count*: the number of controlling inputs
 - *u_count*: the number of unknown inputs
- Update counts during logic simulation
 - Example:
One input of a NAND switches from 0 to *u*
 - *c_count* --
 - *u_count* ++
- Same rules as input scanning used to evaluate gate outputs

Parallel Gate Evaluation

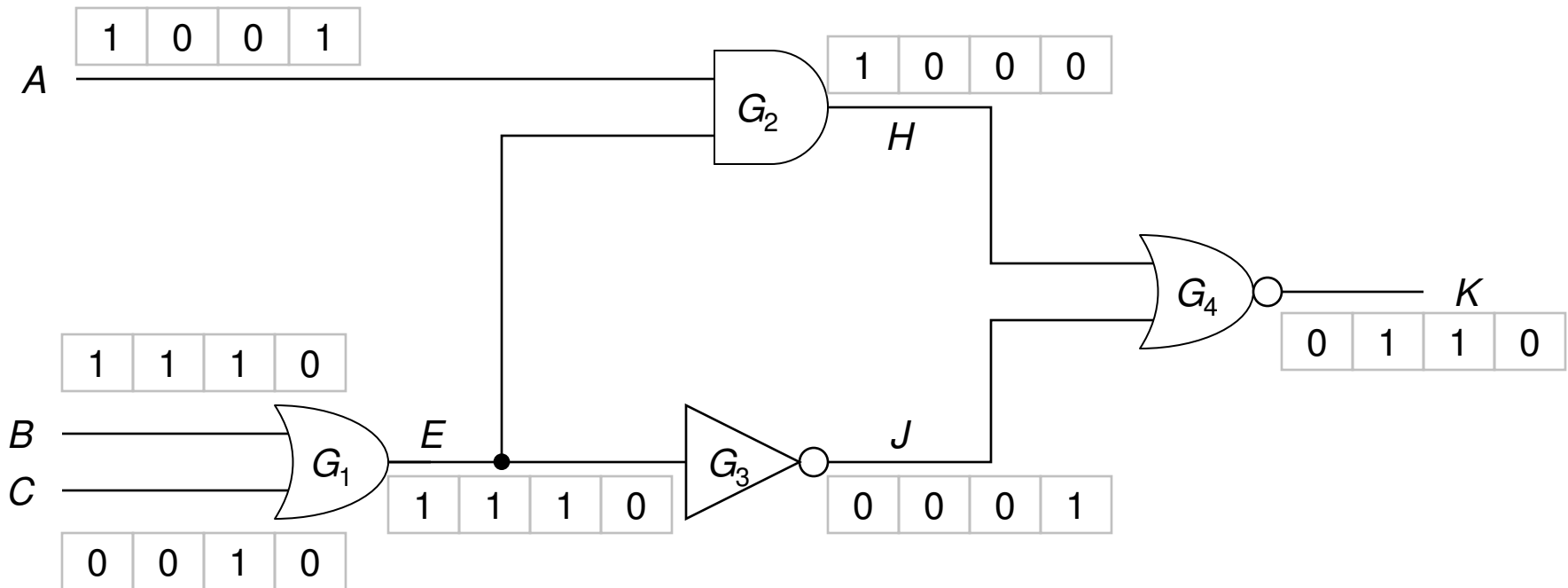- Exploit the inherent concurrency in the host computer
 - A 32-bit computer can perform 32 logic operations in parallel



Multi-Valued Parallel Gate Evaluation

□ Use ternary logic as example


- Assume
 - w -bit wide word
 - Symbol encoding: $v_0 = (00)$, $v_1 = (11)$, $v_u = (01)$
- Associate with each signal X two words, X_1 and X_2
 - X_1 stores the first bits and X_2 the second bits of the w copies of the same signal
- AND and OR operations are realized by applying the same bitwise operations to both words
 - $C = \text{OR}(A, B) \implies C_1 = \text{OR}(A_1, B_1)$ and $C_2 = \text{OR}(A_2, B_2)$
- Complement requires inversion
 - $C = \text{NOT}(A) \implies C_1 = \text{NOT}(A_2)$ and $C_2 = \text{NOT}(A_1)$

Timing Models


- ❑ Transport delay
- ❑ Inertial delay
- ❑ Wire delay
- ❑ Function element delay model

Transport Delay

 - The time duration it takes for the effect of gate input changes to appear at gate outputs




(a) Nominal delay
 $d_N = 2 \text{ ns}$

 

(b) Rise/fall delay
 $d_r = 2 \text{ ns}$
 $d_f = 1.5 \text{ ns}$




 (c) Min-max delay
 $d_{\min} = 1 \text{ ns}$
 $d_{\max} = 2 \text{ ns}$



Inertial Delay

 
- The minimum input pulse duration necessary for the output to switch states



(a) Pulse duration less than d_I




(b) Pulse duration longer than d_I

 

Wire Delay

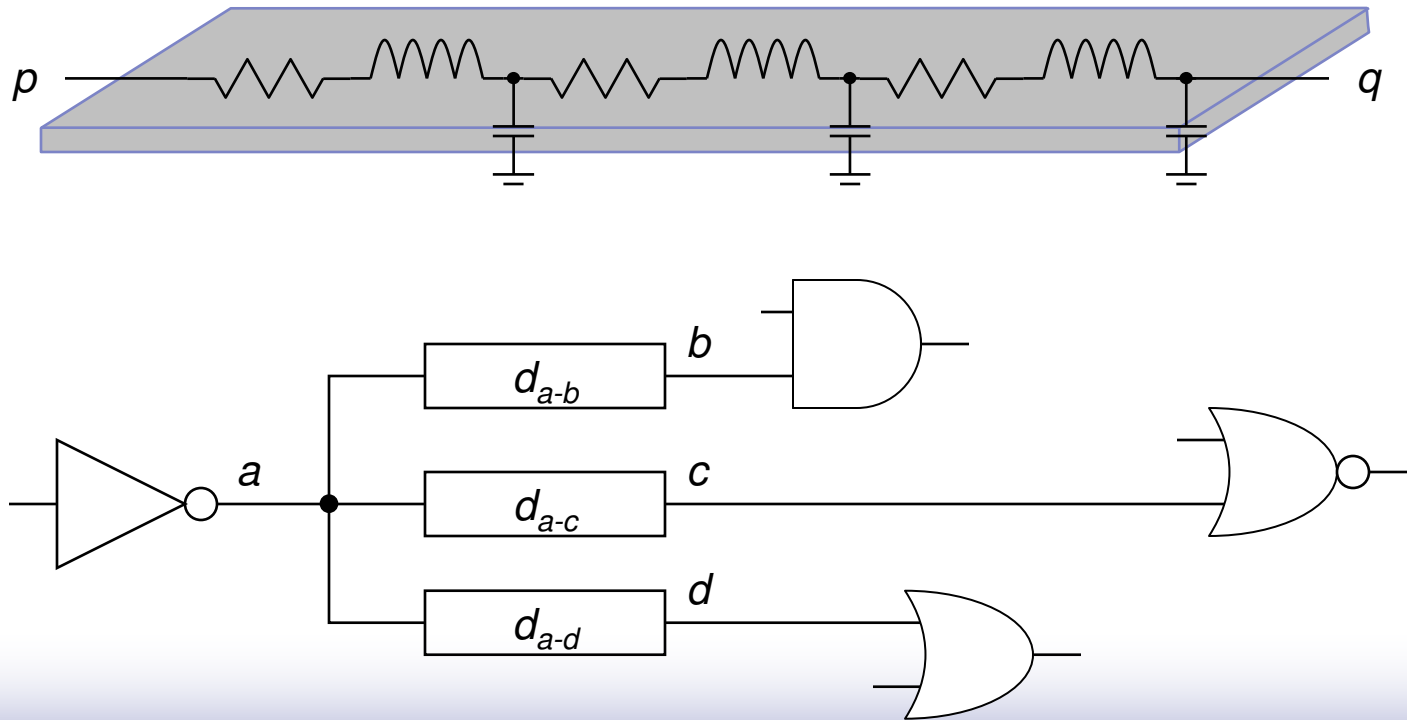- ❑ Wires are inherently resistive and capacitive
- ❑ It takes finite time for a signal to propagate along a wire



Functional Element Delay Model

- For more complicated functional elements like flip-flops

Table 3.3: The D flip-flop I/O delay model

Input condition				Present state q	Outputs		Delays (ns)		Comments
D	$Clock$	$Preset$	$Clear$		Q	QB	to Q	to QB	
X	X	\downarrow	0	0	\uparrow	\downarrow	1.6	1.8	Asynchronous preset
X	X	0	\downarrow	1	\downarrow	\uparrow	1.8	1.6	Asynchronous clear
1	\uparrow	0	0	0	\uparrow	\downarrow	2	3	$Q: 0 \rightarrow 1$
0	\uparrow	0	0	1	\downarrow	\uparrow	3	2	$Q: 1 \rightarrow 0$


X indicates don't care

Logic and Fault Simulation


- ❑ Introduction
- ❑ Simulation models
- ❑ **Logic simulation**
- ❑ Fault simulation
- ❑ Concluding remarks

Compiled Code Simulation

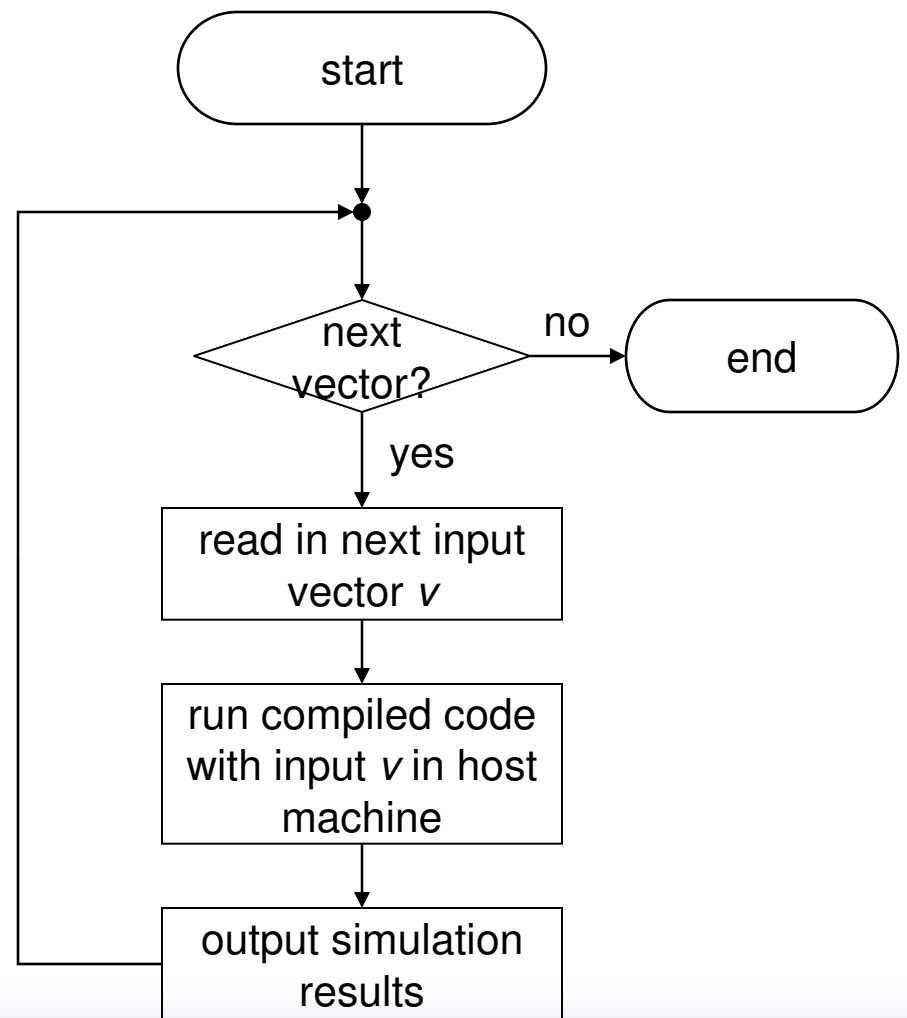- Translate the logic network into a series of machine instructions that model the gate functions and interconnections




Compiled Code Generation Flow

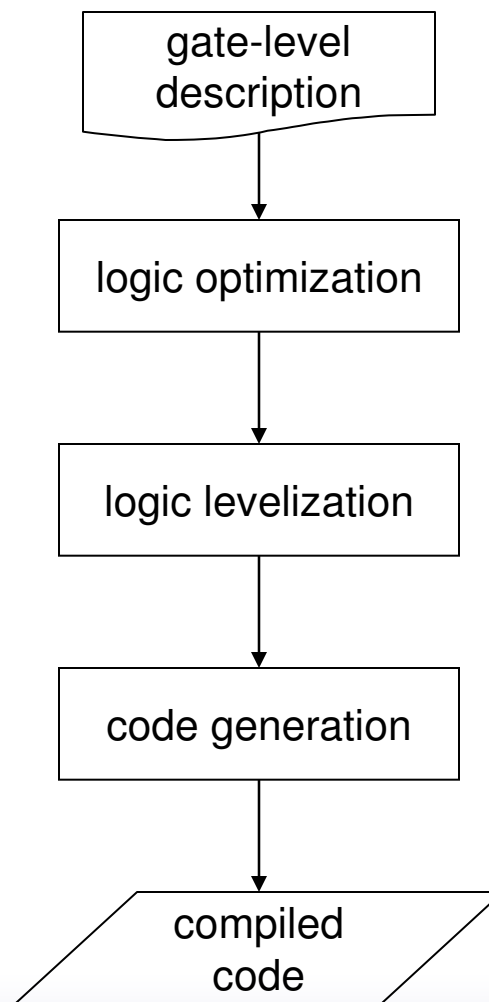


Logic Optimization

- Enhance the simulation efficiency

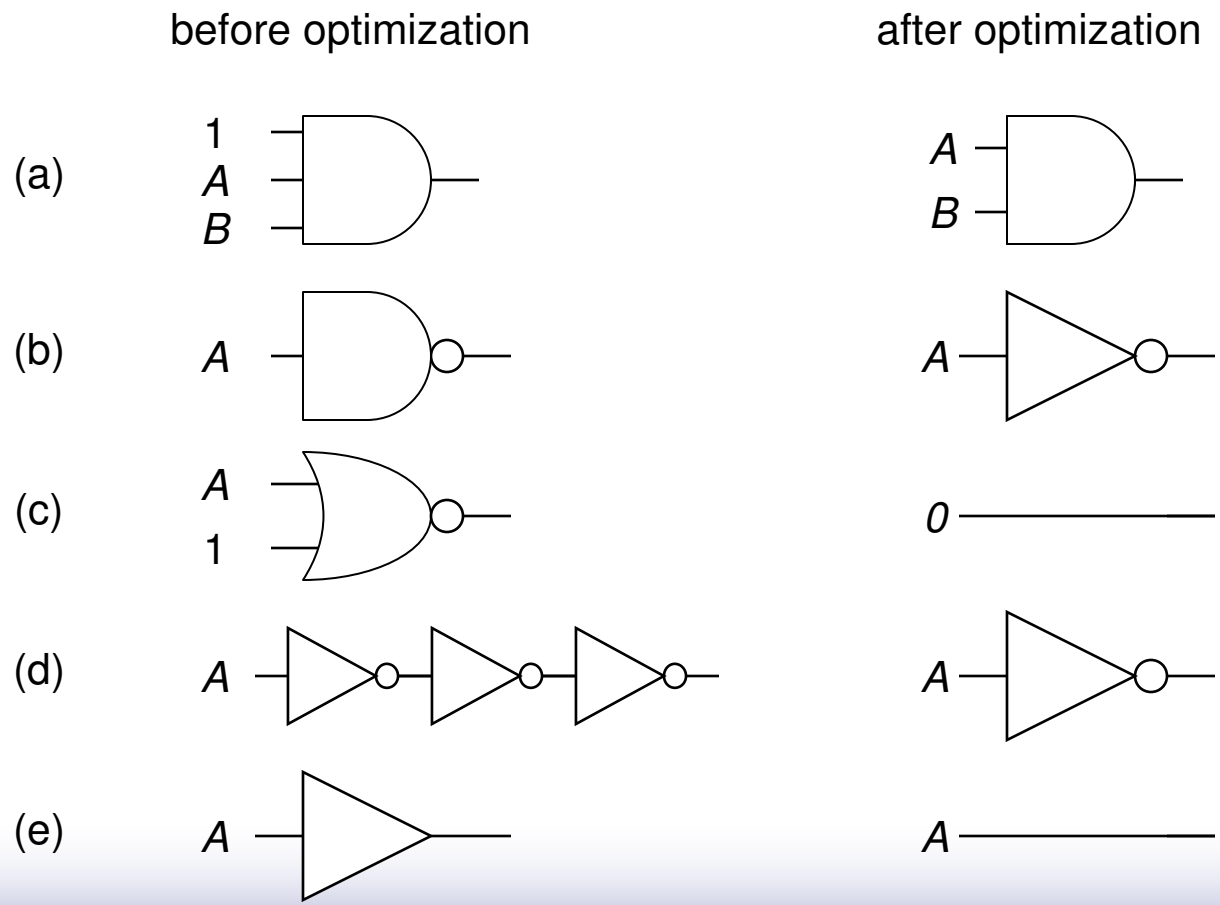

Logic Levelization

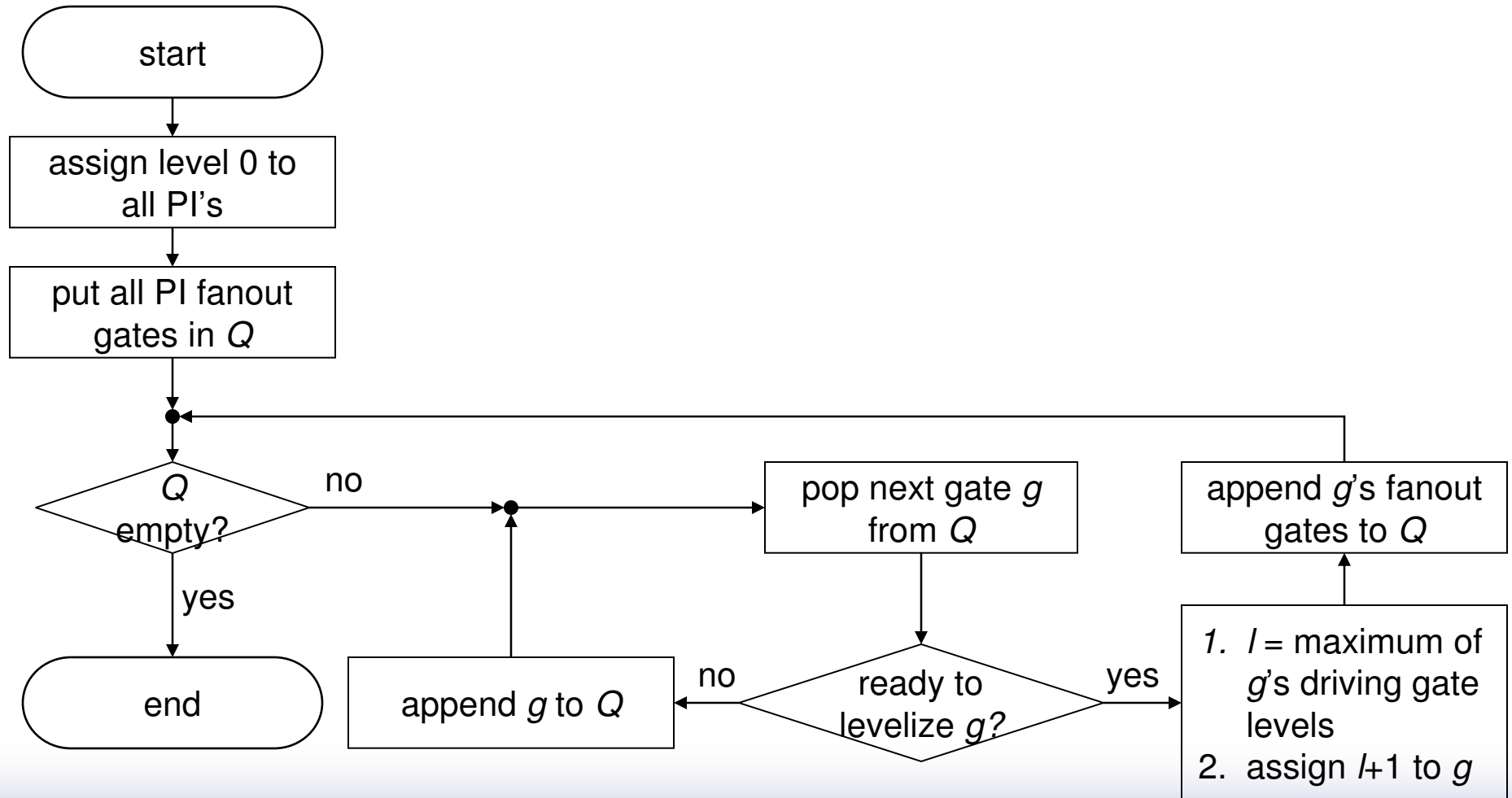- Determine the order of gate evaluations



Example

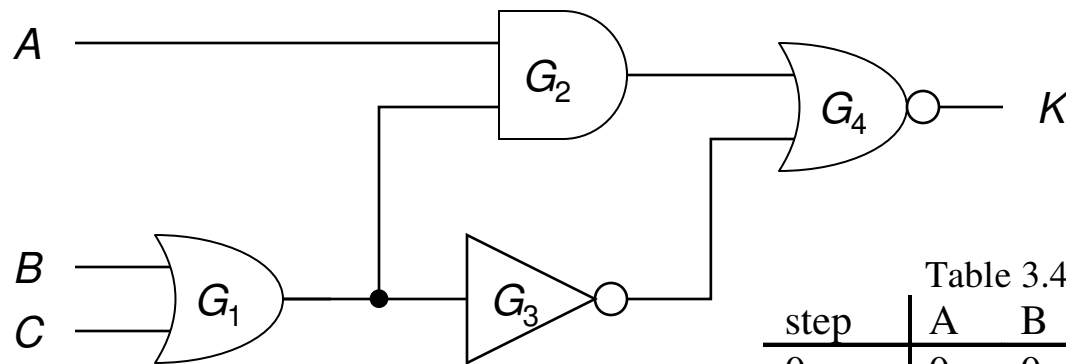


Table 3.4: The levelization process of circuit

step	A	B	C	G_1	G_2	G_3	G_4	Q
0	0	0	0					$\langle G_2, G_1 \rangle$
1	0	0	0					$\langle G_1, G_2 \rangle$
2	0	0	0	1				$\langle G_2, G_3 \rangle$
3	0	0	0	1	2			$\langle G_3, G_4 \rangle$
4	0	0	0	1	2	2		$\langle G_4 \rangle$
5	0	0	0	1	2	2	3	$\langle \rangle$

□ The following orders are produced

- $G_1 \Rightarrow G_2 \Rightarrow G_3 \Rightarrow G_4$
- $G_1 \Rightarrow G_3 \Rightarrow G_2 \Rightarrow G_4$

Code Generation

- ❑ High-level programming language source code
 - Easier to debug
 - Can be ported to any target machine that has the compiler
 - Limited in applications due to long compilation times
- ❑ Native machine code
 - Generate the target machine code directly
 - Higher simulation efficiency
 - Not as portable


Code Generation - cont'd

□ Interpreted code

- The target machine is a software emulator
- The codes are interpreted and executed one at a time
- Best portability and maintainability
- Reduced performance


Event-Driven Simulation

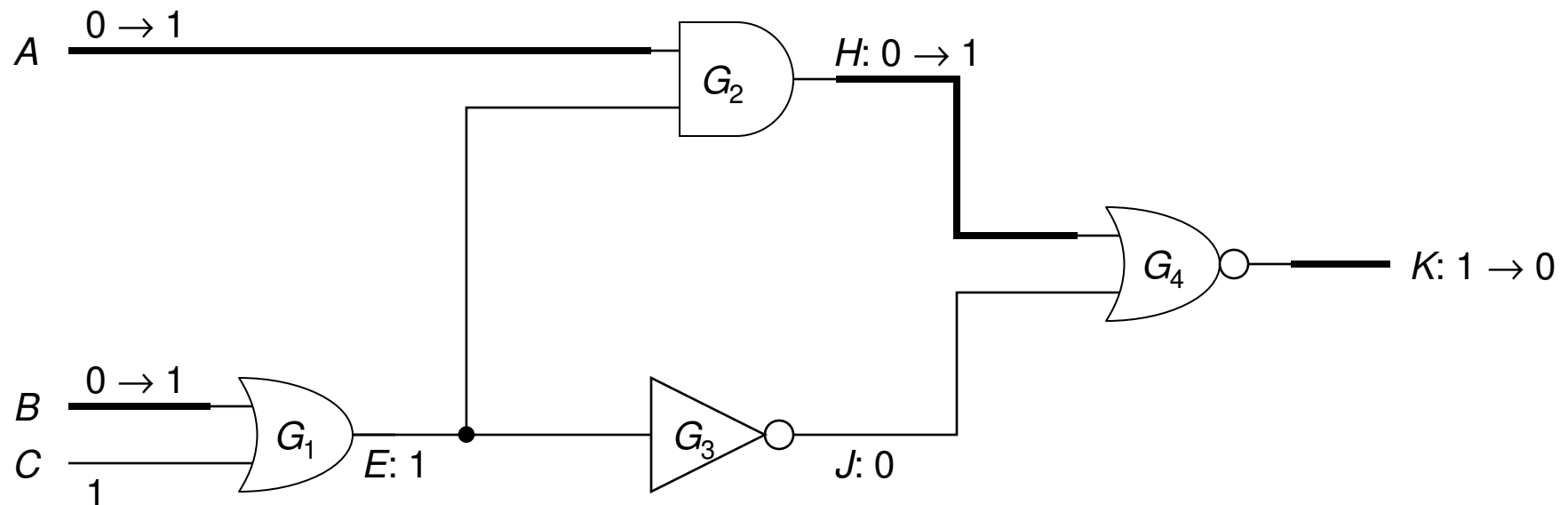- Event: the switching of a signal's value
- An event-driven simulator monitors the occurrences of events to determine which gates to evaluate




Zero-Delay Event-Driven Simulation

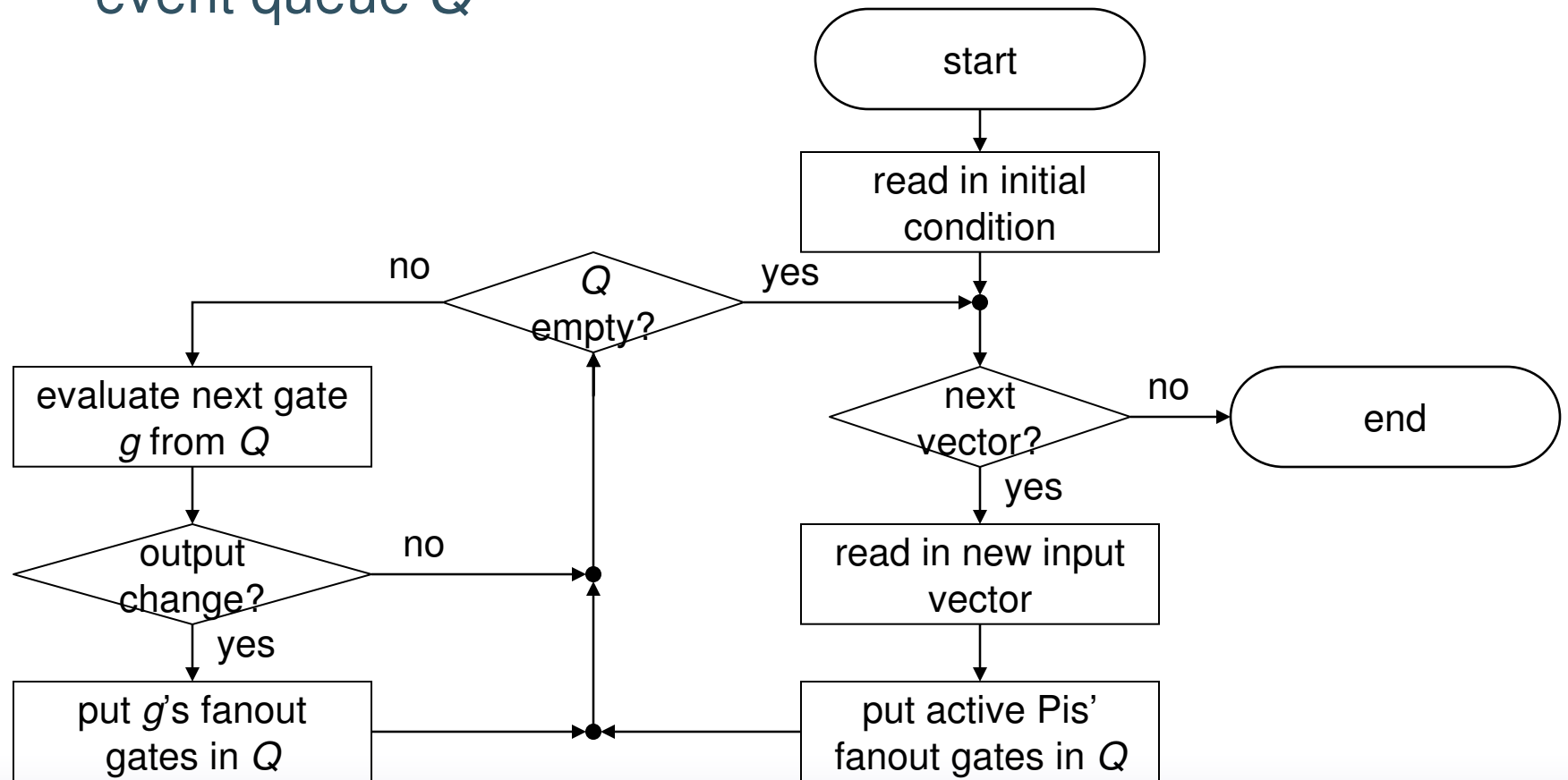- Gates with events at their inputs are places in the event queue Q




Nominal-Delay Event-Driven Simulation

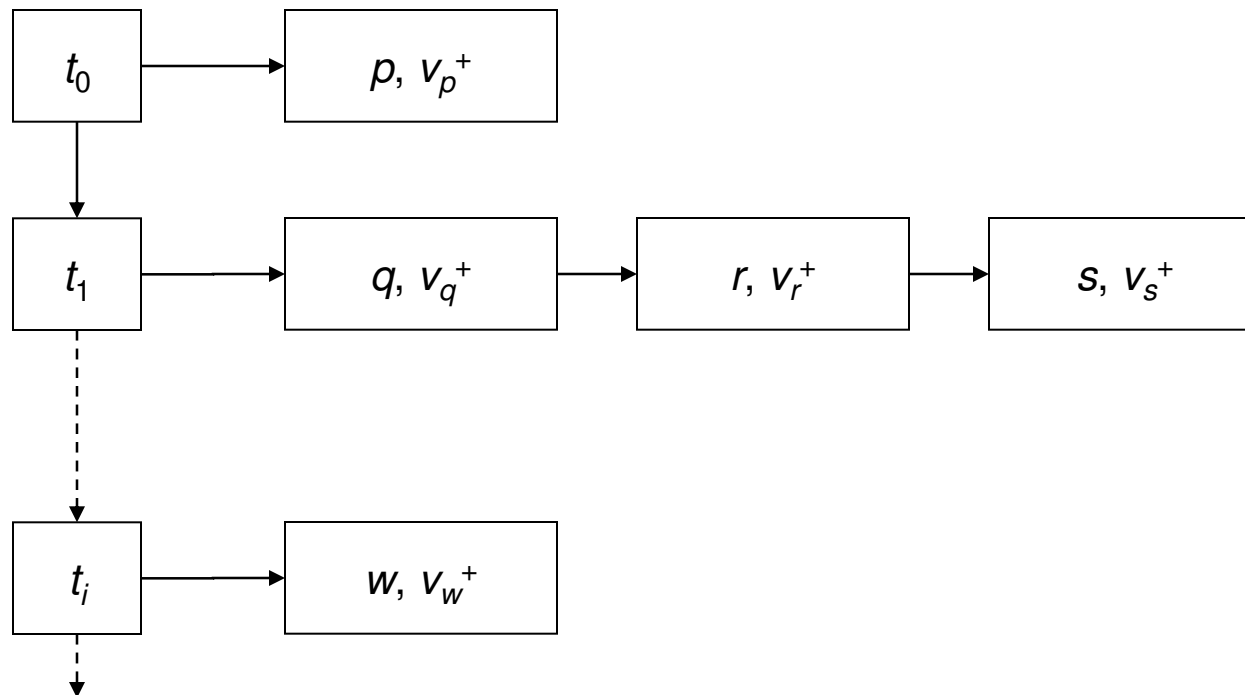- Need a smarter scheduler than the event queue
 - Not only which gates but also when to evaluate



Two-Pass Event-Driven Simulation

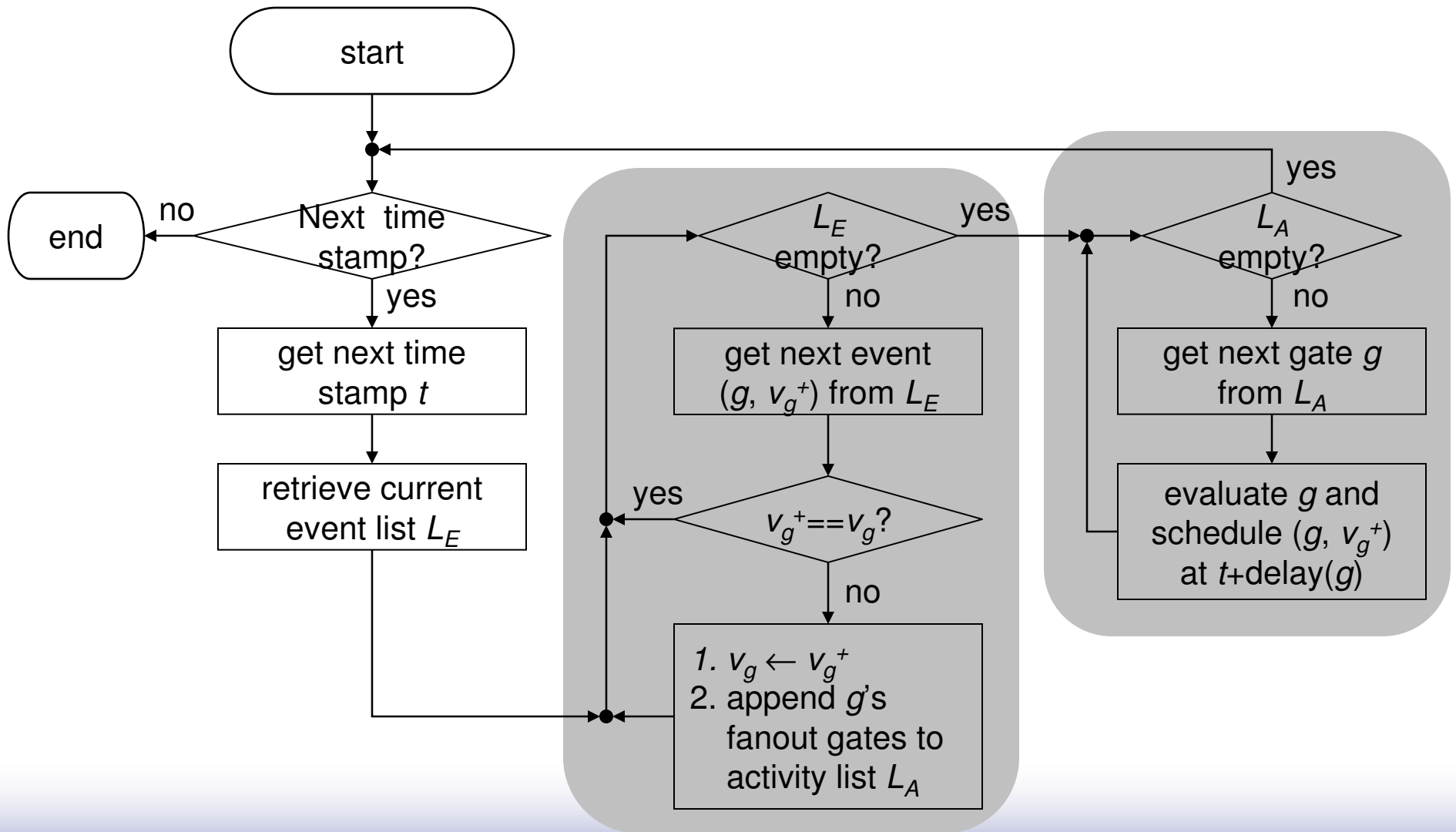

Example


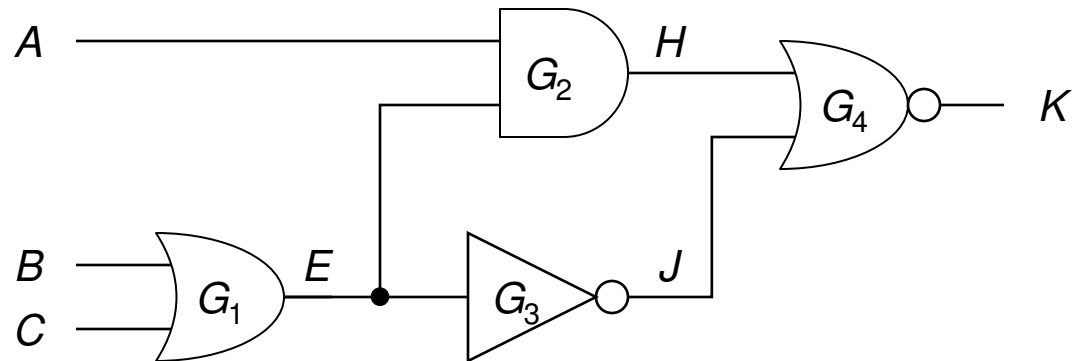


Table 3.5: Two-pass event-driven simulation

Time	L_E	L_A	Scheduled events
0	{(A,1)}	{G ₂ }	{(H,1,8)}
2	{(C,0)}	{G ₁ }	{(E,1,10)}
4	{(B,0)}	{G ₁ }	{(E,0,12)}
8	{(A,0),(H,1)}	{G ₂ ,G ₄ }	{(H,0,16),(K,0,14)}
10	{(E,1)}		
12	{(E,0)}	{G ₂ ,G ₃ }	{(H,0,20),(J,1,16)}
14	{(K,0)}		
16	{(H,0),(J,1)}	{G ₄ }	{(K,0,22)}
20	{(H,0)}		
22	{(K,0)}		

Example - cont'd

 

Compiled-Code vs. Event-Driven Simulation

□ Compiled-code



- Cycle-based simulation
- High switching activity circuits
- Parallel simulation
- Limited by compilation times

□ Event-driven

- Implementing gate delays and detecting hazards
- Low switching activity circuits
- More complicated memory management

Hazards

- Unwanted transient pulses or glitches

 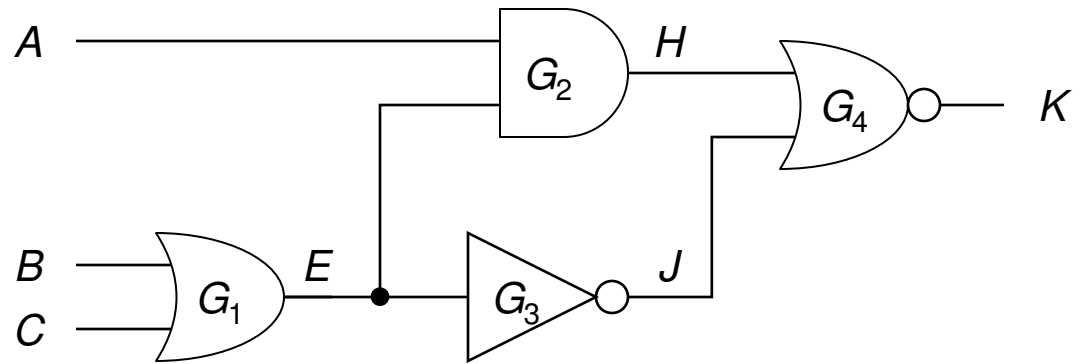


Types of Hazards


□ Static or dynamic

- A static hazard refers to the transient pulse on a signal line whose static value does not change
- A dynamic hazard refers to the transient pulse during a 0-to-1 or 1-to-0 transition


□ 1 or 0

 


Static 1-hazard

 

Static 0-hazard

 

Dynamic 1-hazard

 

Dynamic 0-hazard

Static Hazard Detection

- Let $V^1 = v_1^1 v_2^1 \cdots v_n^1$ and $V^2 = v_1^2 v_2^2 \cdots v_n^2$ be two consecutive input vectors
- Add a new vector $V^+ = v_1^+ v_2^+ \cdots v_n^+$ according to the following rule

$$v_i^+ = \begin{cases} v_i^1 & \text{if } v_i^1 = v_i^2 \\ u & \text{if } v_i^1 \neq v_i^2 \end{cases}$$

- Simulate the $V^1 V^+ V^2$ sequence using ternary logic
- Any signal that is $1u1$ or $0u0$ indicates the possibility of a static hazard.

Multi-Valued Logic for Hazard Detection

- ❑ 6-valued logic for static hazard detection
- ❑ 8-valued logic for dynamic hazard detection
- ❑ Worst case analysis

Table 3.6: Multi-valued logic for hazard detection

Symbol	Interpretation	6-valued logic	8-valued logic
0	Static 0	{000}	{0000}
1	Static 1	{111}	{1111}
R	Rise transition	{001,011}=0 μ 1	{0001,0011,0111}
F	Fall transition	{100,110}=1 μ 0	{1110,1100,1000}
0*	Static 0-hazard	{000,010}=0 μ 0	{0000,0100,0010,0110}
1*	Static 1-hazard	{111,101}=1 μ 1	{1111,1011,1101,1001}
R*	Dynamic 1-hazard		{0001,0011,0101,0111}
F*	Dynamic 0-hazard		{1000,1010,1100,1110}

Logic and Fault Simulation

- ❑ Introduction
- ❑ Simulation models
- ❑ Logic simulation
- ❑ **Fault simulation**
- ❑ Concluding remarks

Fault Simulation

- ❑ Introduction
- ❑ Serial Fault Simulation
- ❑ Parallel Fault Simulation
- ❑ Deductive Fault Simulation
- ❑ Concurrent Fault Simulation
- ❑ Differential Fault Simulation
- ❑ Fault Detection
- ❑ Comparison of Fault Simulation Techniques
- ❑ Alternative to Fault Simulation
- ❑ Conclusion

Introduction

□ What is fault simulation?

- Given
 - A circuit
 - A set of test patterns
 - A fault model
- Determine
 - Faulty outputs
 - Undetected faults
 - Fault coverage

Time Complexity

□ Proportional to


- n : Circuit size, number of logic gates
- p : Number of test patterns
- f : Number of modeled faults

□ Since f is roughly proportional to n , the overall time complexity is $O(pn^2)$


Serial Fault Simulation

- First, perform fault-free logic simulation on the original circuit
 - Good (fault-free) response
- For each fault, perform fault injection and logic simulation
 - *Faulty* circuit response

Algorithm Flow

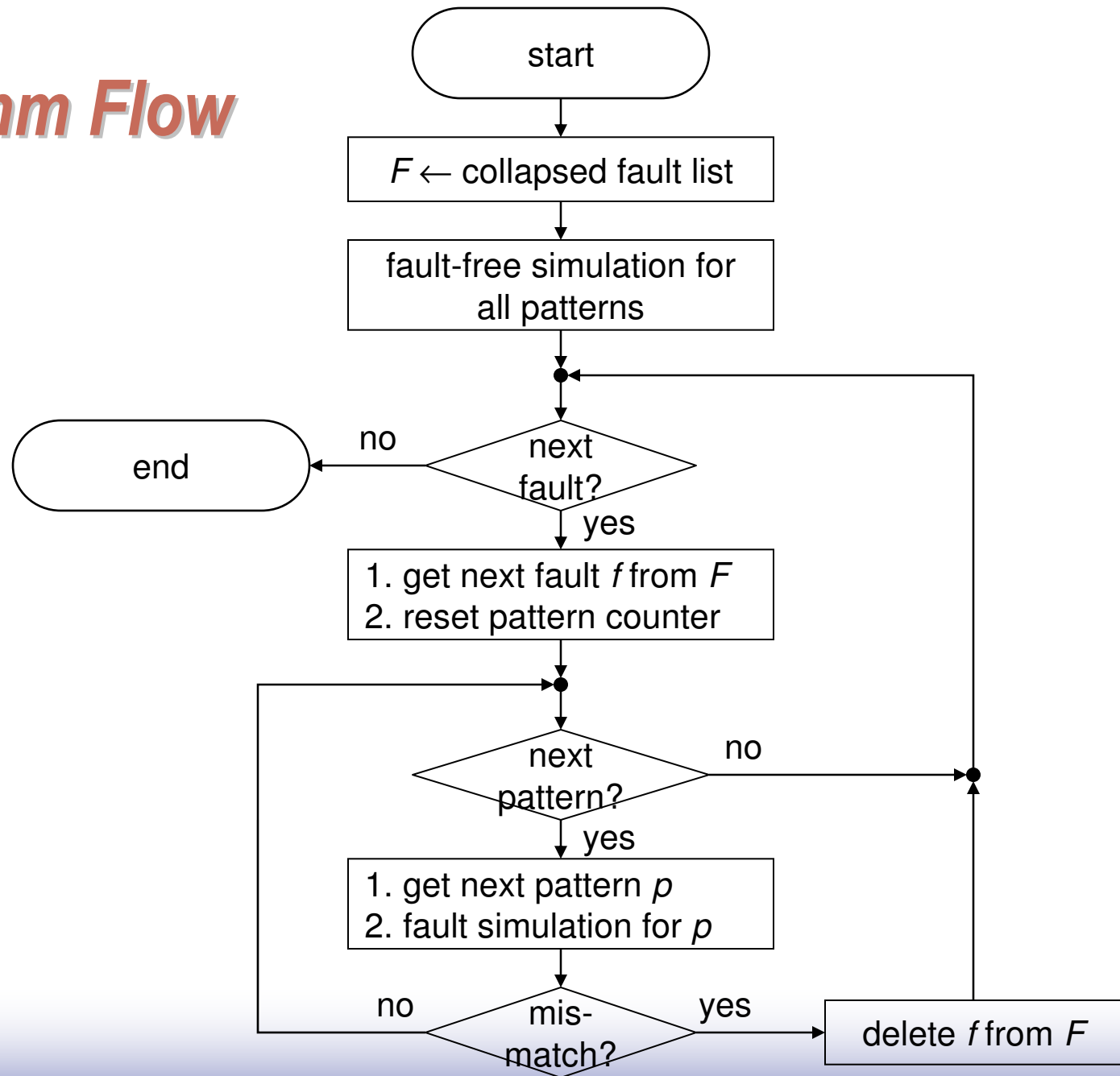

Example

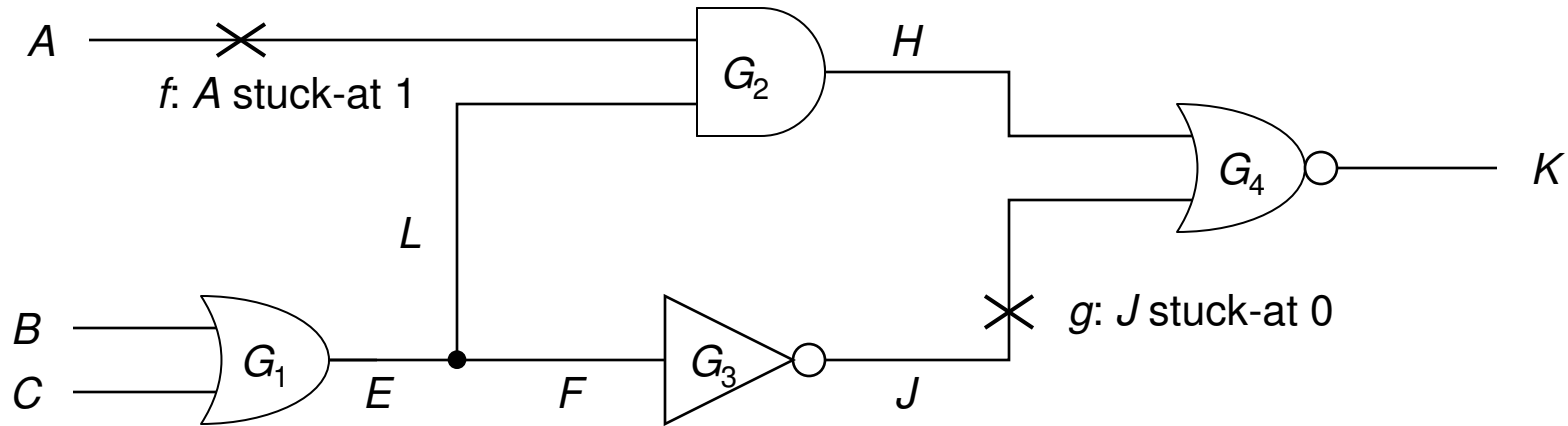

Pat. #	Input			Internal					Output		
	A	B	C	E	F	L	J	H	K_{good}	K_f	K_g
<i>P1</i>	0	1	0	1	1	1	0	0	1	0	1
<i>P2</i>	0	0	1	1	1	1	0	0	1	0	1
<i>P3</i>	1	0	0	0	0	0	1	0	0	0	1

Fault Dropping

- ❑ Halting simulation of the detected fault
- ❑ Example
 - Suppose we are to simulate P_1, P_2, P_3 in order
 - Fault f is detected by P_1
 - Do not simulate f for P_2, P_3
- ❑ For fault grading
 - Most faults are detected after relatively few test patterns have been applied
- ❑ For fault diagnosis
 - Avoided to obtain the entire fault simulation results

Pro and Con

□ Advantages

- Easy to implement
- Ability to handle a wide range of fault models
(stuck-at, delay, Br, ...)

□ Disadvantages

- Very slow

Parallel Fault Simulation

- ❑ Exploit the inherent parallelism of bitwise operations
- ❑ Parallel fault simulation [Seshu 1965]
 - Parallel in faults
- ❑ Parallel pattern fault simulation [Waicukauski 1986]
 - Parallel in patterns

Parallel Fault Simulation

□ Assumption


- Use binary logic: one bit is enough to store logic signal
- Use w -bit wide data word

□ Parallel simulation

- $w-1$ bit for faulty circuits
- 1 bit for fault-free circuit

□ Process faulty and fault-free circuit in parallel using bitwise logic operations

Fault Injection

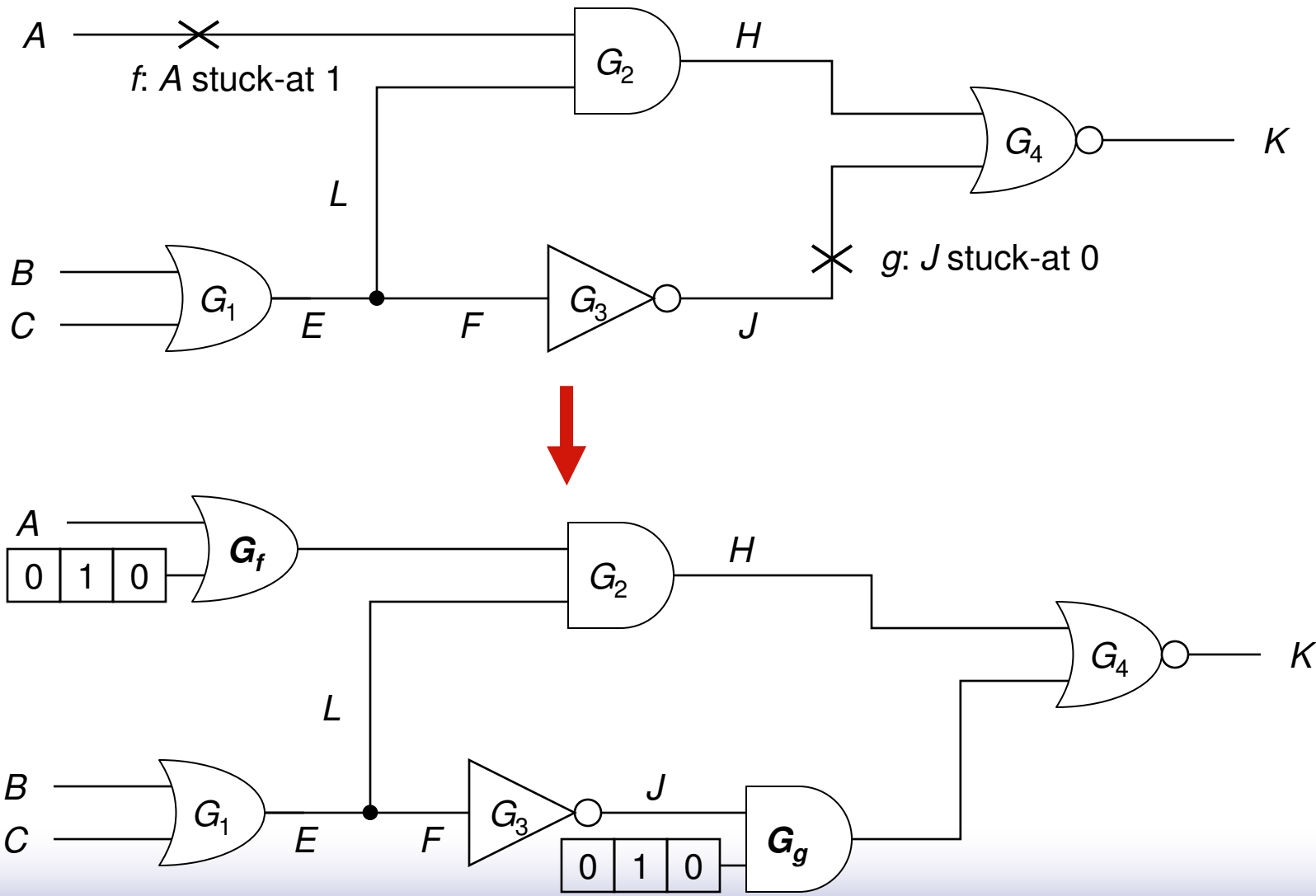

Example

Pat #	Input					Internal						Output
		<i>A</i>	<i>A_f</i>	<i>B</i>	<i>C</i>	<i>E</i>	<i>F</i>	<i>L</i>	<i>J</i>	<i>J_g</i>	<i>H</i>	<i>K</i>
<i>P₁</i>	FF	0	0	1	0	1	1	1	0	0	0	1
	f	0	1	1	0	1	1	1	0	0	1	0
	g	0	0	1	0	1	1	1	0	0	0	1
<i>P₂</i>	FF	0	0	0	1	1	1	1	0	0	0	1
	f	0	1	0	1	1	1	1	0	0	1	0
	g	0	0	0	1	1	1	1	0	0	0	1
<i>P₃</i>	FF	1	1	0	0	0	0	0	1	1	0	0
	f	1	1	0	0	0	0	0	1	1	0	0
	g	1	1	0	0	0	0	0	1	0	0	1

Pro and Con

□ Advantages

- A large number of faults are detected by each pattern when simulating the beginning of test sequence


□ Disadvantages

- Only applicable to the unit or zero delay models
- Faults cannot be dropped unless all $(w-1)$ faults are detected


Parallel Pattern Fault Simulation

- ❑ Parallel pattern single fault propagation (PPSFP)
- ❑ Parallel pattern
 - With a w -bit data width, w test patterns are packed into a word and simulated for the fault-free or faulty circuit
- ❑ Single fault
 - First, fault-free simulation
 - Next, for each fault, fault injection and faulty circuit simulation

Algorithm Flow

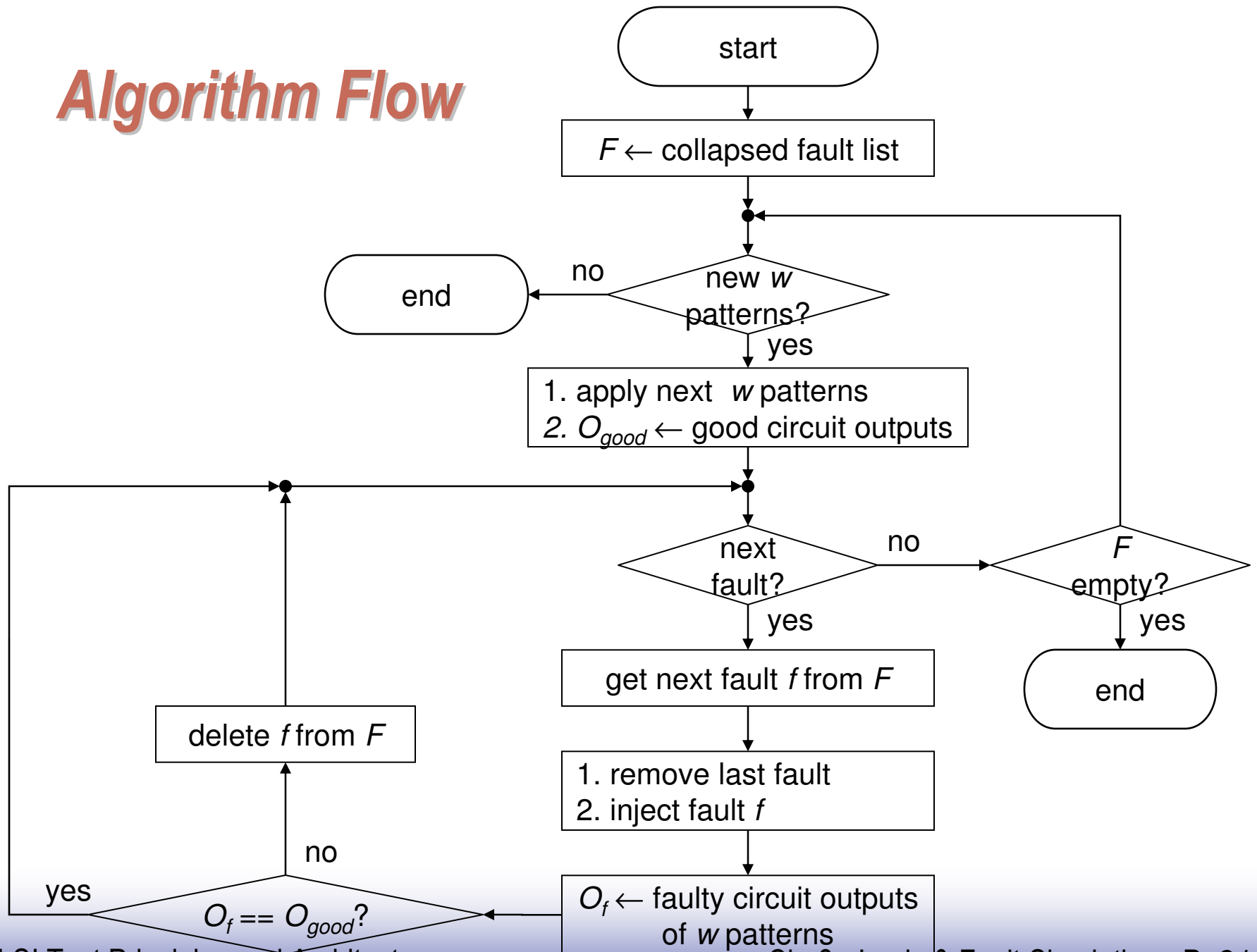

Example

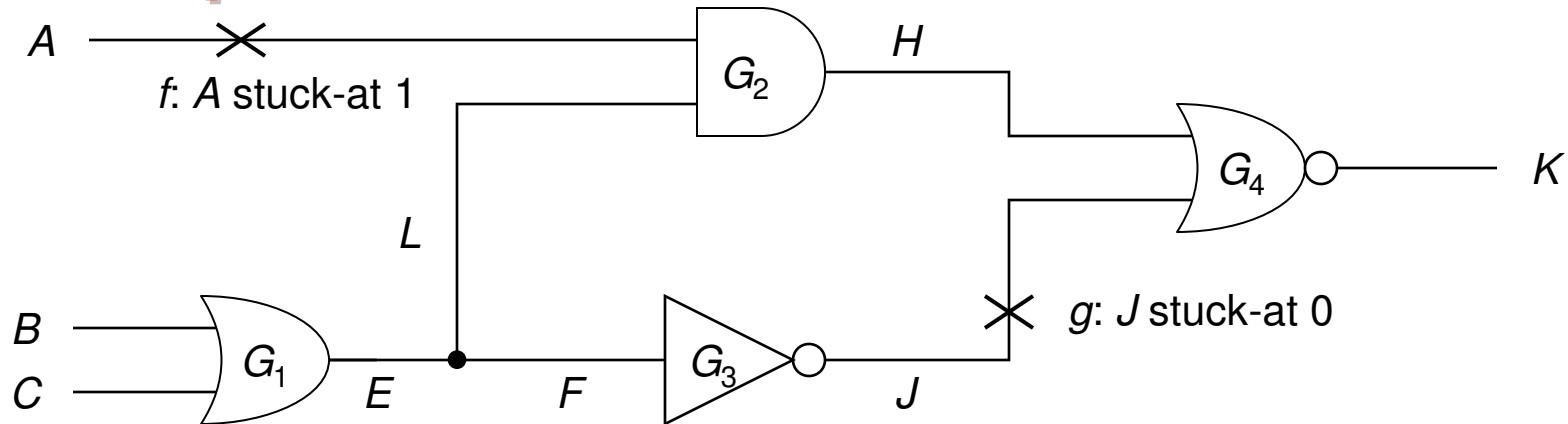

	Input				Internal					Output
		A	B	C	E	F	L	J	H	K
Fault Free	P_1	0	1	0	1	1	1	0	0	1
	P_2	0	0	1	1	1	1	0	0	1
	P_3	1	0	0	0	0	0	1	0	0
f	P_1	1	1	0	1	1	1	0	1	0
	P_2	1	0	1	1	1	1	0	1	0
	P_3	1	0	0	0	0	0	1	0	0
g	P_1	0	1	0	1	1	1	0	0	1
	P_2	0	0	1	1	1	1	0	0	1
	P_3	1	0	0	0	0	0	0	0	1

Pro and Con

❑ Advantages

- Fault is dropped as soon as detected
- Best for simulating test patterns that come later, where fault dropping rate per pattern is lower

❑ Disadvantages

- Not suitable for sequential circuits

Deductive Fault Simulation

- [Armstrong 1972]
- Based on logic reasoning rather than simulation
- Fault list attached with signal x denoted as L_x
 - Set of faults causing x to differ from its fault-free value
- Fault list propagation
 - Derive the fault list of a gate output from those of the gate inputs based on logic reasoning

Fault List Propagation Rules

c : controlling value

i : inversion value

I : set of gate inputs

z : gate output

S : inputs holding controlling value

	c	i
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1


- All gate inputs hold non-controlling value

$$L_z = \left(\bigcup_{j \in I} L_j \right) \cup \{z / (c \oplus i)\} \quad (3.1)$$

- At least one input holds controlling value

$$L_z = \left[\left(\bigcap_{j \in S} L_j \right) - \left(\bigcup_{j \in I-S} L_j \right) \right] \cup \{z / c \oplus i'\} \quad (3.2)$$


Algorithm Flow

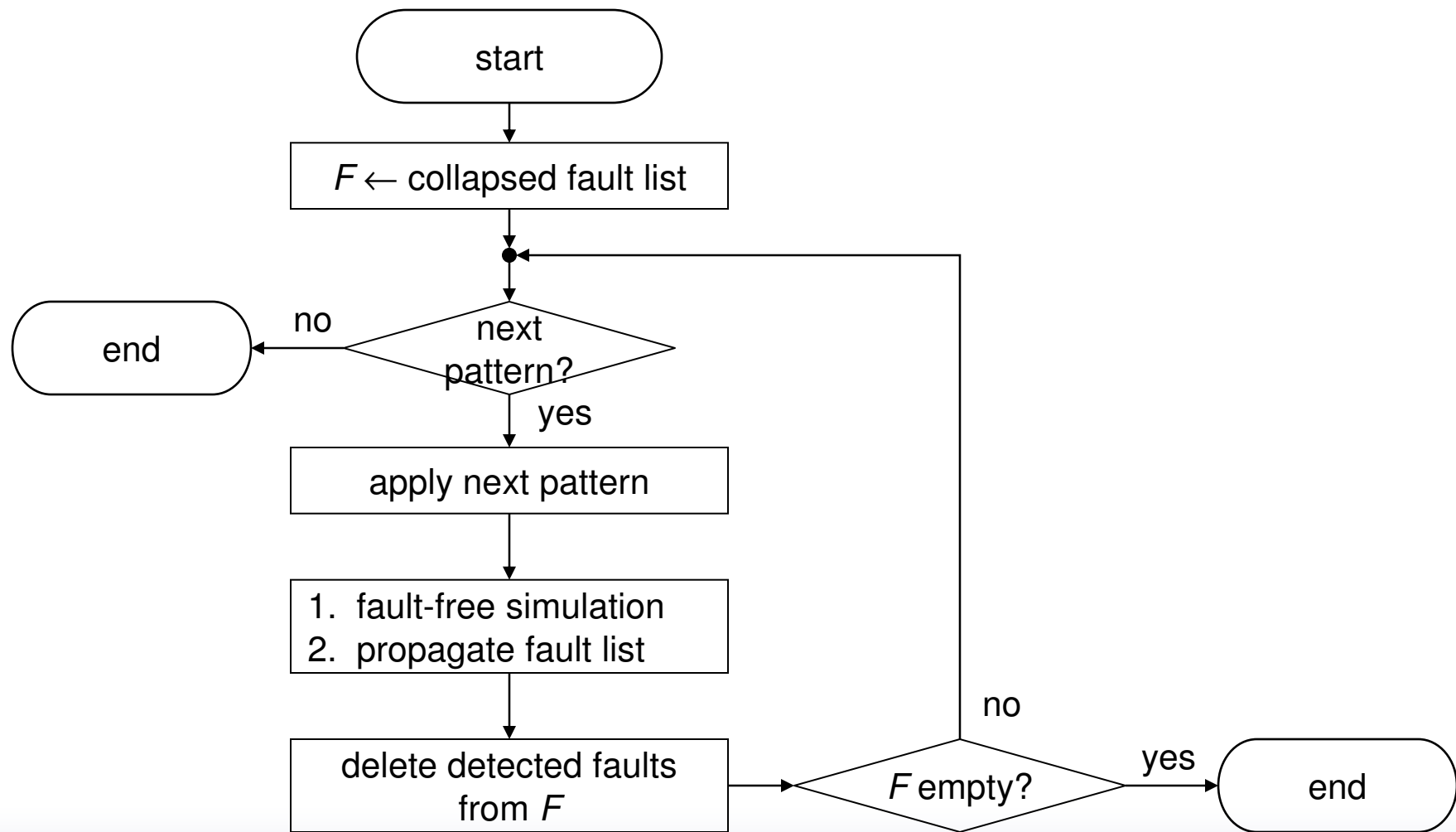

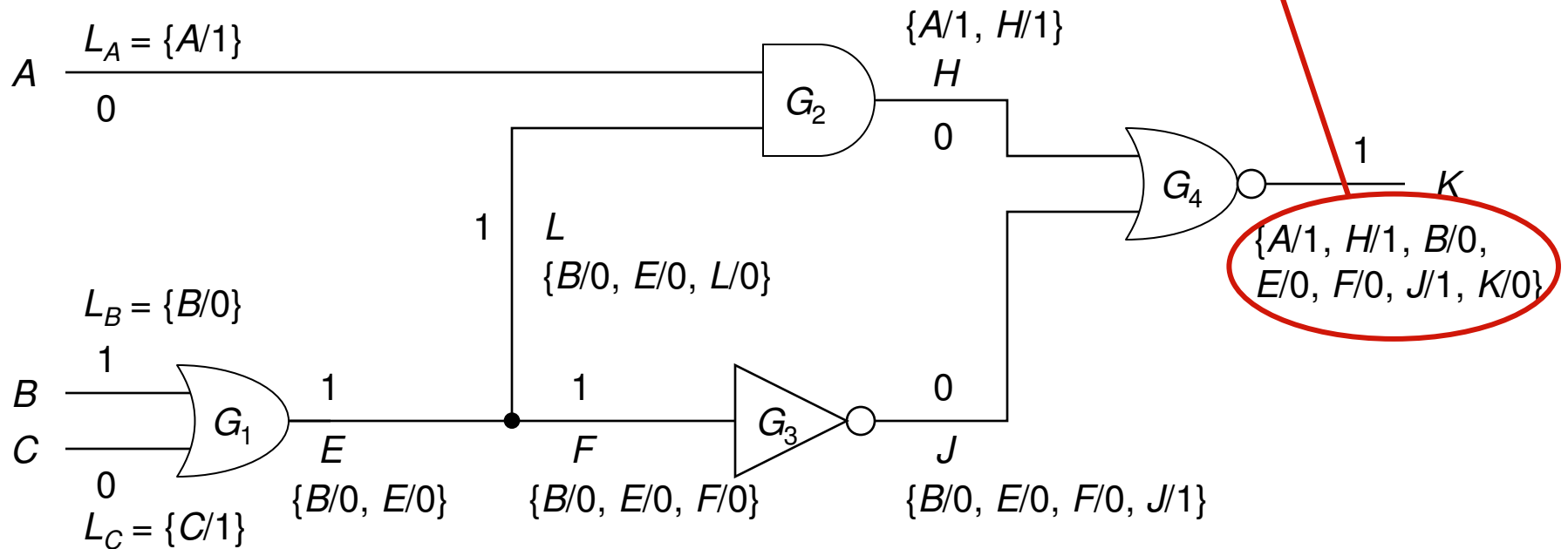Example


□ P_1

$$L_K = L_H \cup L_J \cup \{K/0\} \quad \text{by Eq. (3.1)}$$



Example (cont'd)


□ P_2

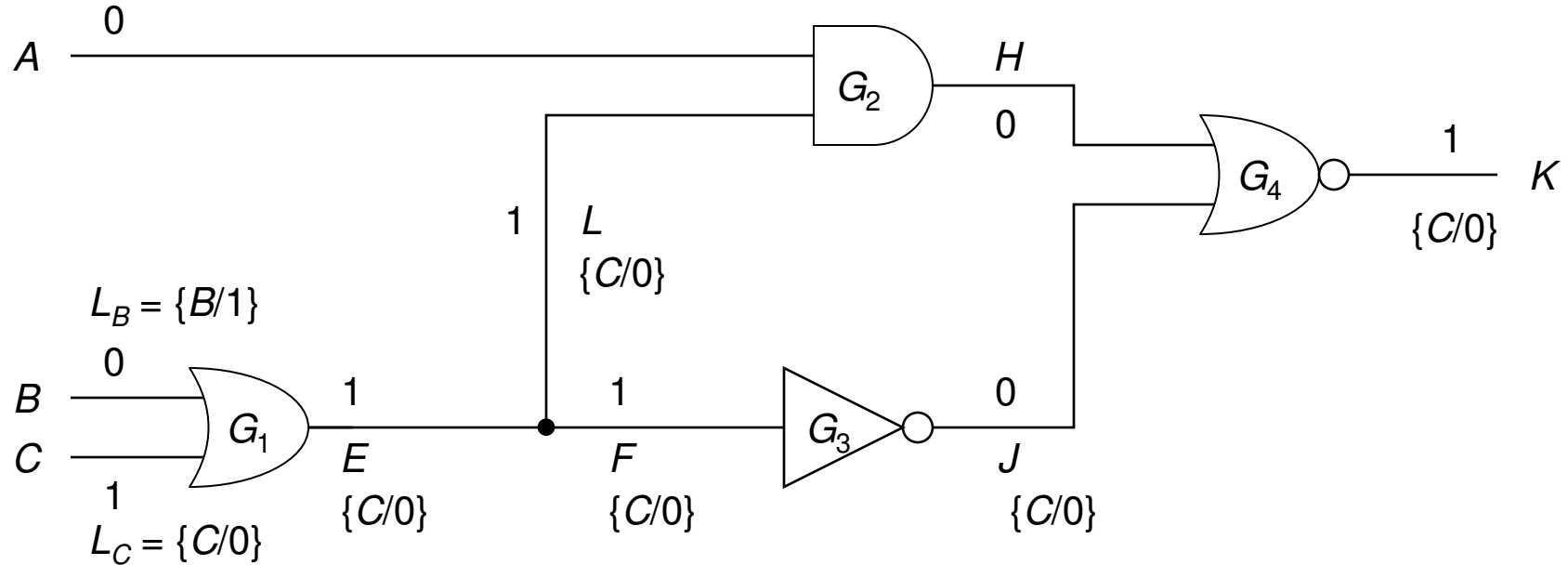

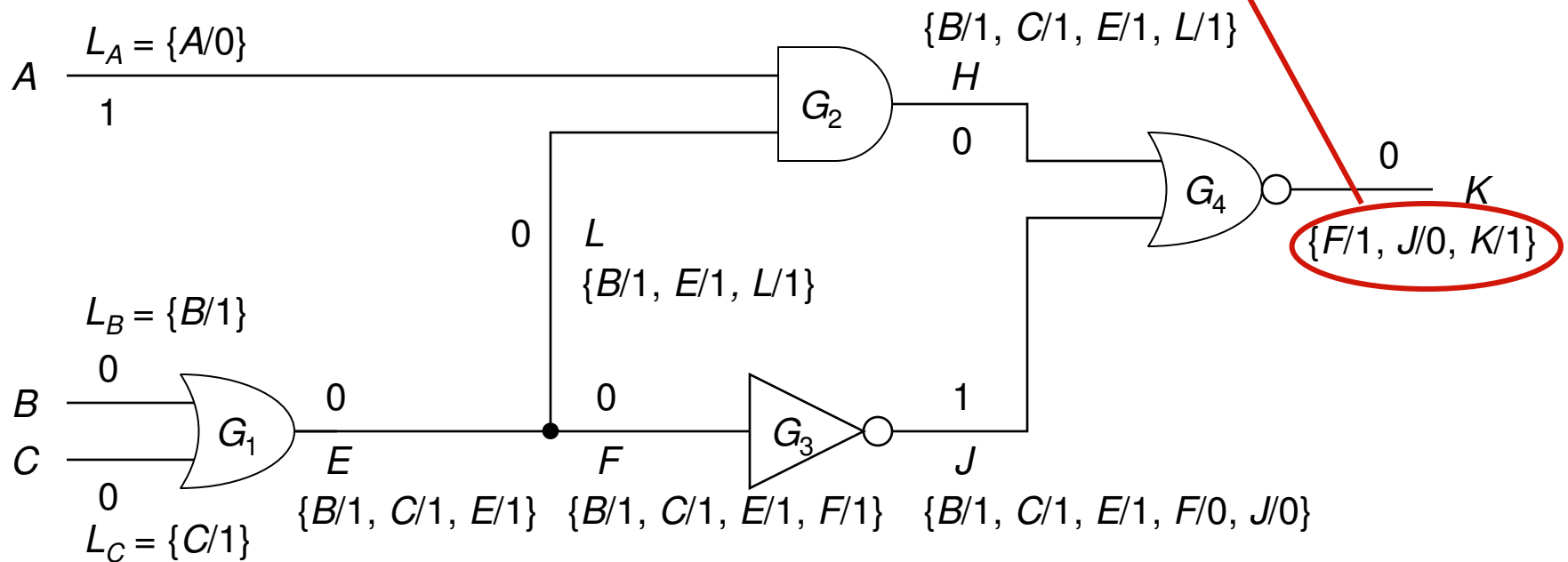Example (cont'd)

□ P_3

$$L_K = (L_J - L_H) \cup \{K/1\} \text{ by Eq. (3.2)}$$



Pro and Con

□ Advantages

- Very efficient
- Simulate all faults in one pass

□ Disadvantages

- Not easy to handle unknowns
- Only for zero-delay timing model
- Potential memory management problem


Concurrent Fault Simulation

- ❑ [Ulrich 1974]
- ❑ Simulate only differential parts of whole circuit
- ❑ Event-driven simulation with fault-free and faulty circuits simulated altogether
- ❑ Concurrent fault list for each gate
 - Consist of a set of bad gates
 - Fault index & associated gate I/O values
 - Initially only contains local faults
 - Fault propagate from previous stage

Good Event and Bad Event


- Good event
 - Events that happen in good circuit
 - Affect both good gates and bad gates
- Bad event
 - Events that occur in the faulty circuit of corresponding fault
 - Affect only bad gates
- Diverge
 - Addition of new bad gates
- Converge
 - Removal of bad gates whose I/O signals are the same as corresponding good gates

Algorithm Flow

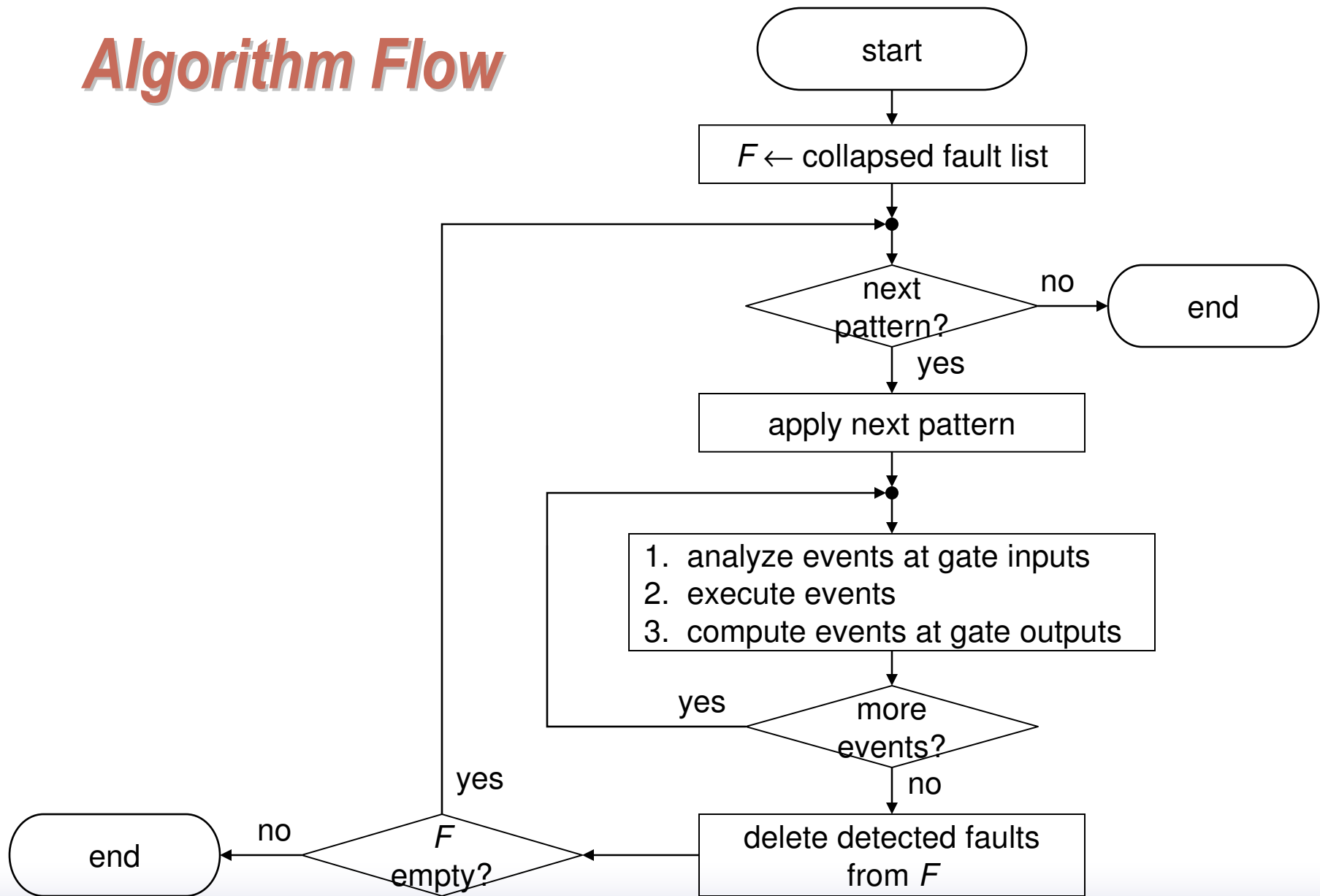


Example

□ P_1

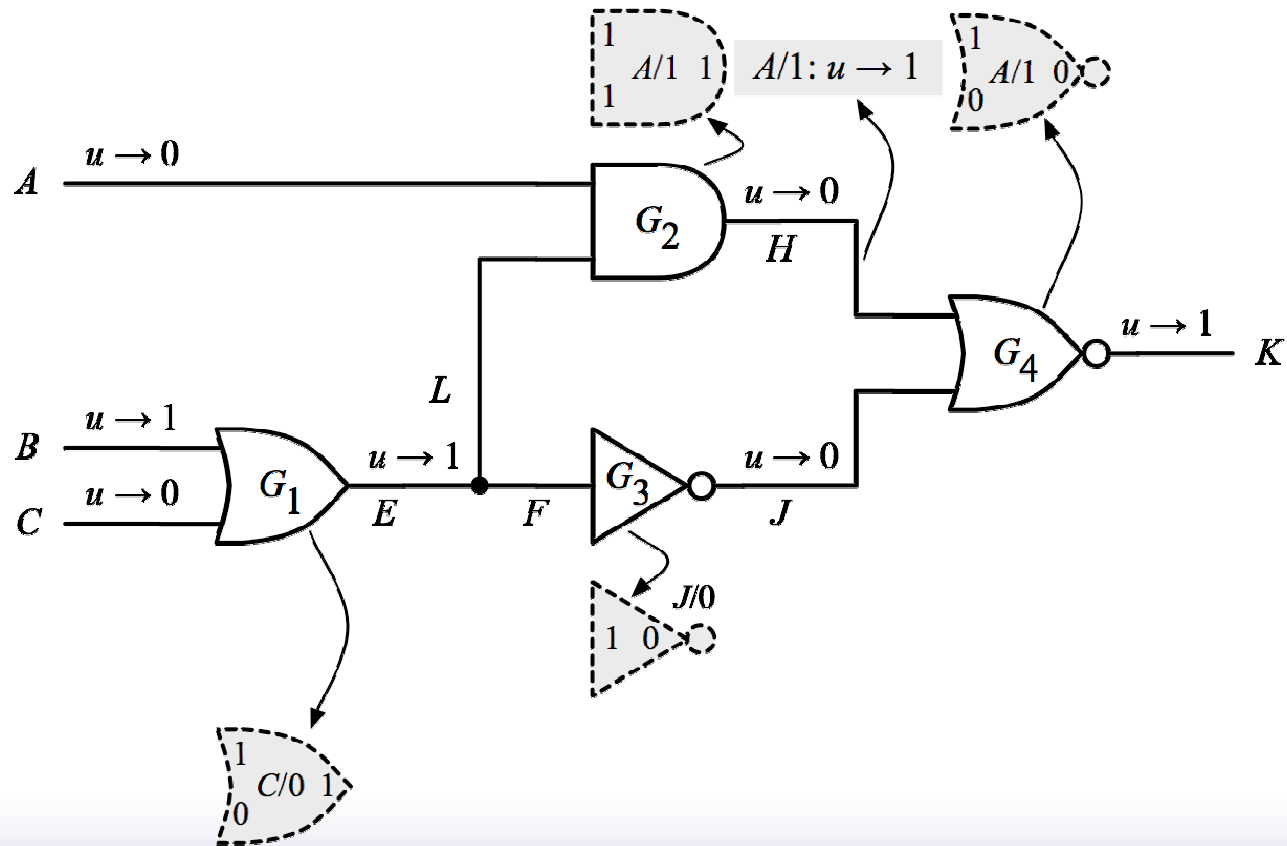


Example (cont'd)

□ P_2

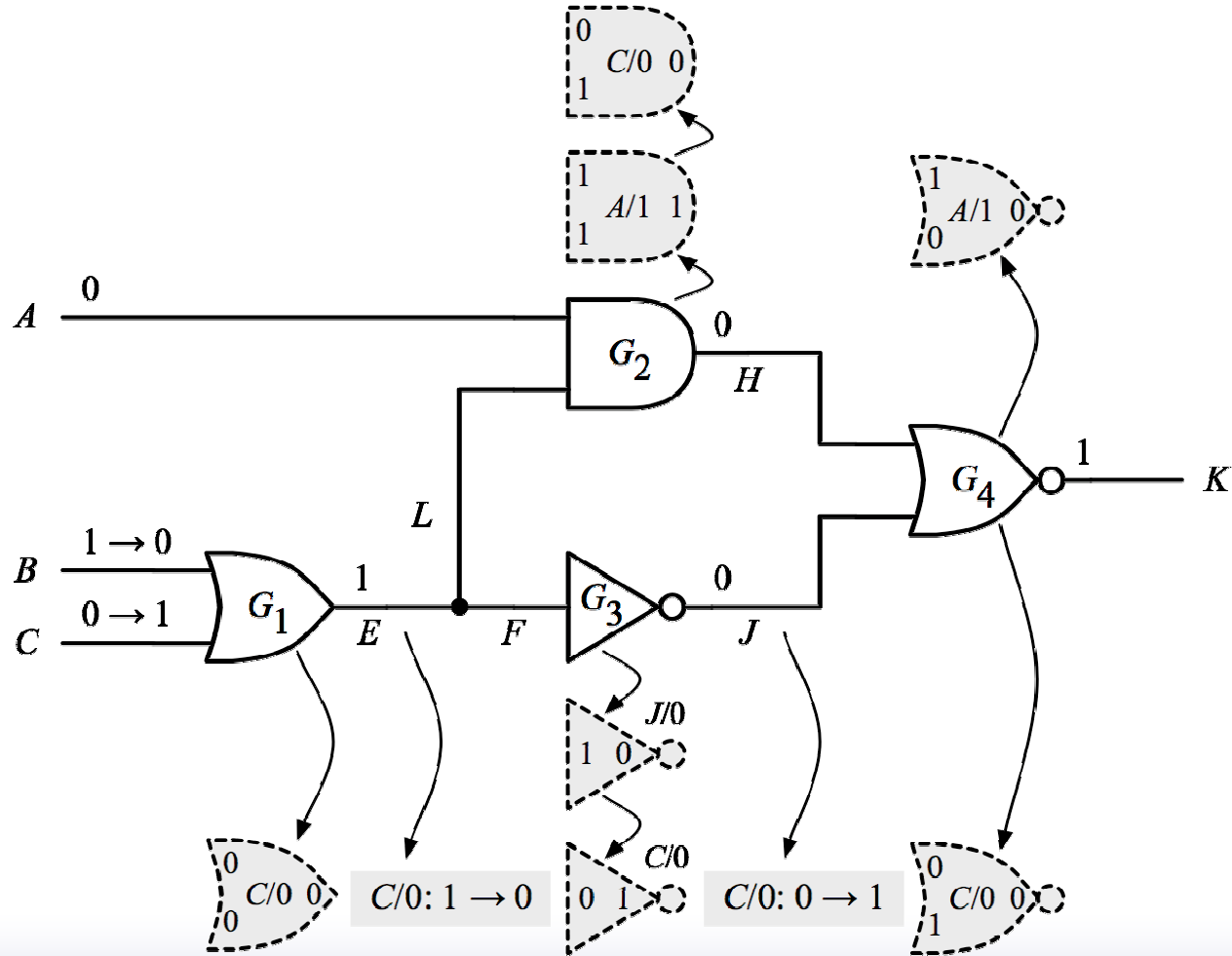

Example (cont'd)

□ P_3

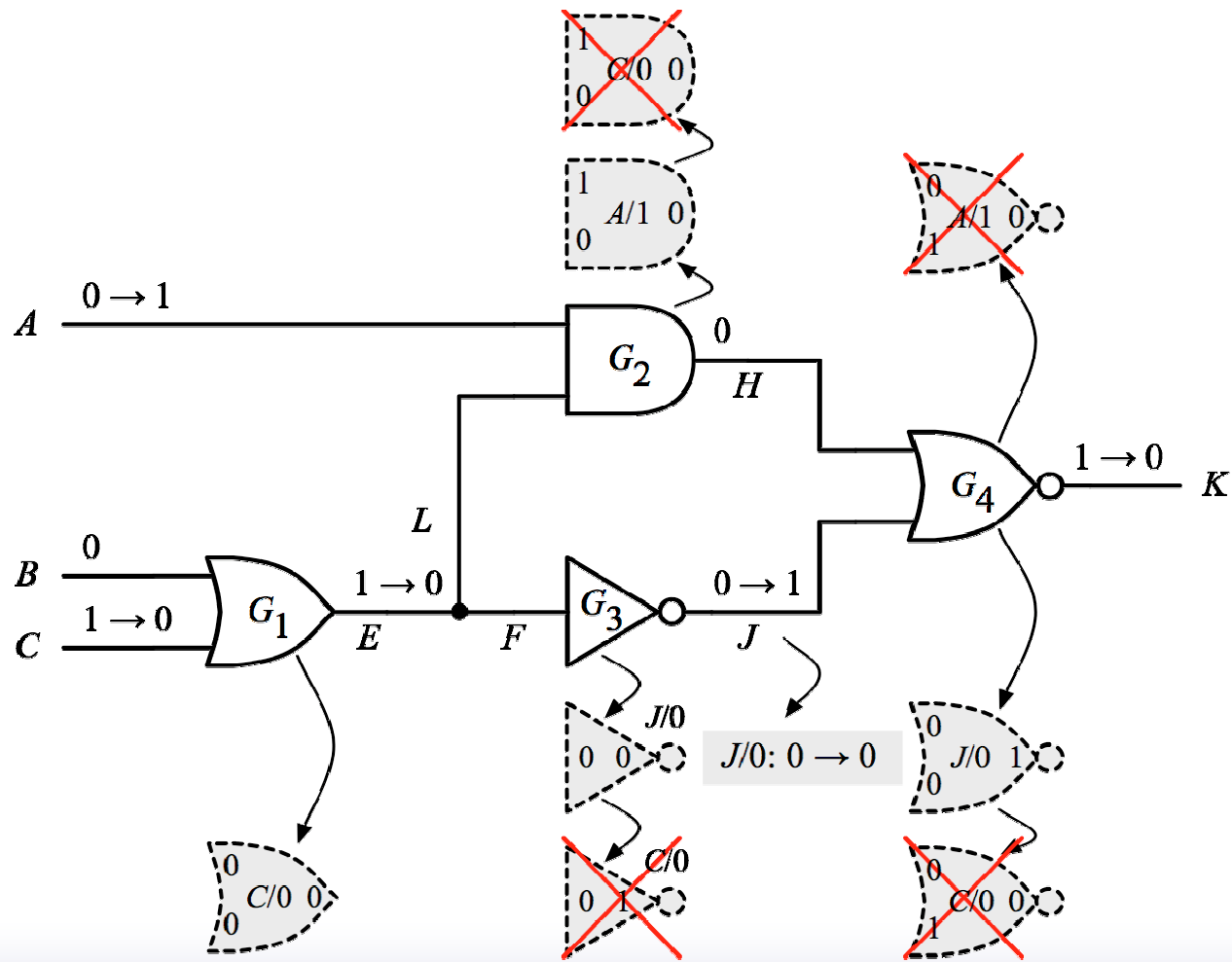

Pro and Con

□ Advantages

- Efficient

□ Disadvantages

- Potential memory problem
 - Size of the concurrent fault list changes at run time


Differential Fault Simulation

- [Cheng 1989]
- Combines the merits of two techniques
 - Concurrent fault simulation
 - PPSFP
- Idea
 - Simulate in turn every fault circuit
 - Track only difference between faulty circuit and last simulated one
 - Inject differences as events
 - Easily implemented by event-driven simulator

Simulation Sequence

	P_1	P_2	...	P_i	P_{i+1}	...	P_n
<i>Good</i>	G_1	G_2	...	G_i	G_{i+1}	...	G_n
f_1	$F_{1,1}$	$F_{1,2}$...	$F_{1,i}$	$F_{1,i+1}$...	$F_{1,n}$
f_2	$F_{2,1}$	$F_{2,2}$...	$F_{2,i}$	$F_{2,i+1}$...	$F_{2,n}$
.
f_k	$F_{k,1}$	$F_{k,2}$...	$F_{k,i}$	$F_{k,i+1}$...	$F_{k,n}$
f_{k+1}	$F_{k+1,1}$	$F_{k+1,2}$...	$F_{k+1,i}$	$F_{k+1,i+1}$...	$F_{k+1,n}$
.
f_m	$F_{m,1}$	$F_{m,2}$...	$F_{m,i}$	$F_{m,i+1}$...	$F_{m,n}$

Algorithm Flow

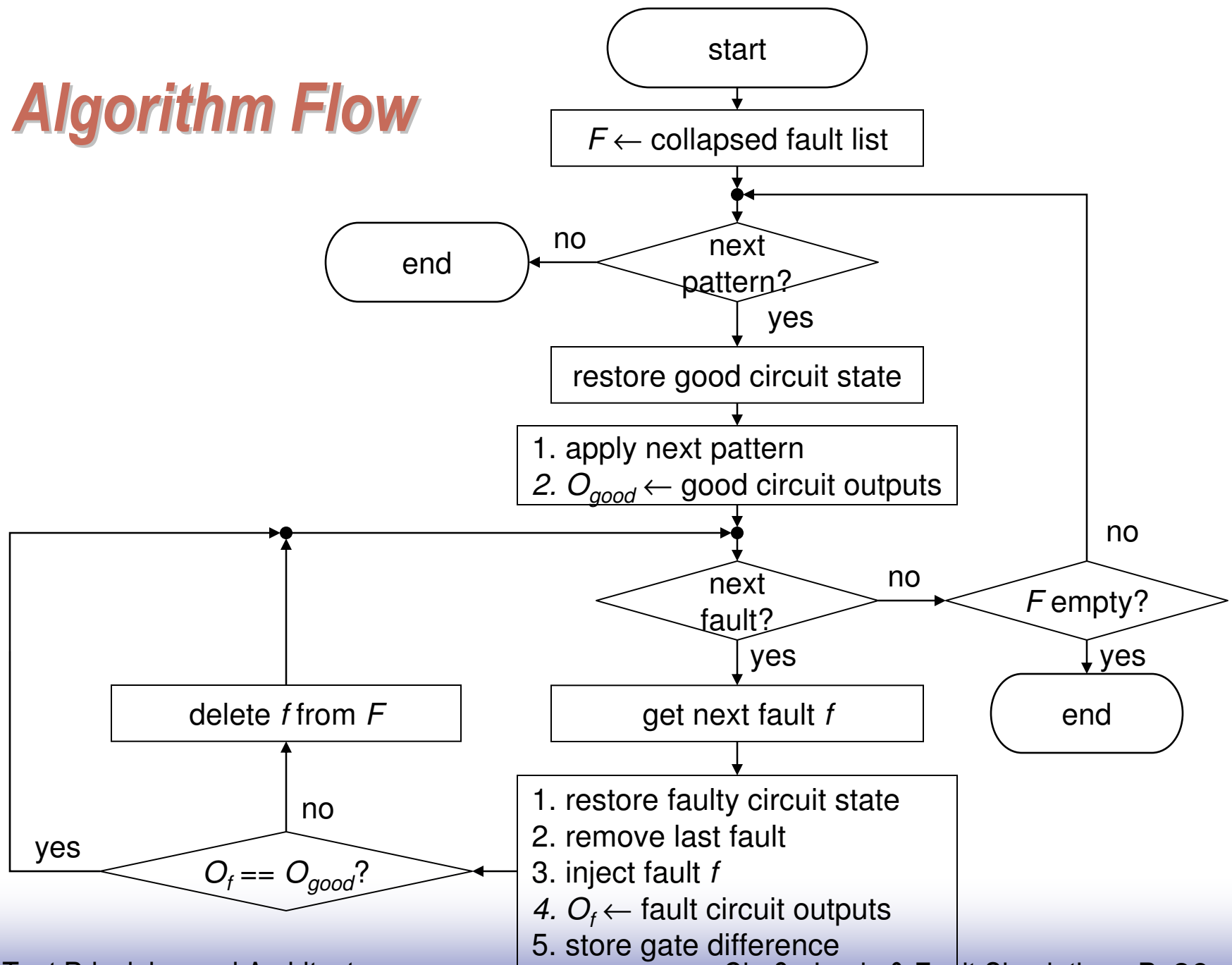

Pro and Con

❑ Advantages

- Suitable for sequential fault simulation

❑ Disadvantages

- Order of events caused by faulty sites is NOT the same as the order of the timing of their occurrence

Fault Detection

□ Hard detected fault

- Outputs of fault-free and faulty circuit are different
 - 1/0 or 0/1
 - No unknowns, no Z

□ Potentially detected fault

- Whether the fault is detected is unclear
- Example: stuck-at-0 on enable signal of tri-state buffer

Fault Detection (cont'd)

❑ Oscillation faults

- Cause circuit to oscillate
- Impossible to predict faulty circuit outputs

❑ Hyperactive faults

- Catastrophic fault effect
 - Fault simulation is time and memory consuming
- Example: stuck-at fault on clock
- Usually counted as detected
 - Save fault simulation time

Comparison of Fault Simulation Techniques (1)

□ Speed

- Serial fault simulation: slowest
- Parallel fault simulation: $O(n^3)$, n : num of gates
- Deductive fault simulation: $O(n^2)$
- Concurrent fault is faster than deductive fault simulation
- Differential fault simulation: even faster than concurrent fault simulation and PPSFP

□ Memory usage

- Serial fault simulation, parallel fault simulation: no problem
- Deductive fault simulation: dynamic allocate memory and hard to predict size
- Concurrent fault simulation: more severe than deductive fault simulation
- Differential fault simulation: less memory problem than concurrent fault simulation

Comparison of Fault Simulation Techniques (2)

- ❑ Multi-valued fault simulation to handle unknown (X) and/or high-impedance (Z)
 - Serial fault simulation, concurrent fault simulation, differential fault simulation: easy to handle
 - Parallel fault simulation: difficult
- ❑ Delay and functional modeling capability
 - Serial fault simulation: no problem
 - Parallel fault simulation, deductive fault simulation: not capable
 - Concurrent fault simulation: capable
 - Differential fault simulation: capable

Comparison of Fault Simulation Techniques (3)

□ Sequential circuit

- Serial fault simulation, parallel fault simulation, concurrent fault simulation, differential fault simulation: no problem
- PPSFP: difficult
- Deductive fault simulation: difficult due to many unknowns

Comparison of Fault Simulation Techniques (4)

- ❑ PPSFP and concurrent fault simulation are popular for combinational (full-scan) circuits
- ❑ Differential fault simulation and concurrent fault simulation is popular for sequential circuits
- ❑ Multiple-pass fault simulation
 - Prevent memory explosion problem
- ❑ Distributed fault simulation
 - Reduce fault simulation time

Alternative to Fault Simulation

- ❑ Toggle Coverage
- ❑ Fault Sampling
- ❑ Critical Path Tracing
- ❑ Statistical Fault Analysis

Toggle Coverage

- ❑ Popular for estimating fault grading
- ❑ Only one single fault-free simulation
- ❑ A net is toggled if
 - Relaxed def: its value has been set to zero and one during fault-free simulation
 - Stringent def: it has both a zero-to-one transition and a one-to-zero transition during fault-free simulation
- ❑ Toggle coverage

$$\frac{\text{number of toggled nets}}{\text{number of total nets in the circuit}}$$

Fault Sampling


- [Butler 1974]
- Simulate only a sampled group of faults
- Error depends on two factors
 - Sample size
 - The sample is biased or not

Critical Path Tracing

- ❑ [Abramovici 1984]
- ❑ Critical value
 - For net x , stuck-at v' can be detected by test pattern $t \leftrightarrow$ Net x has critical value v
- ❑ Critical path
 - Path consisting of nets with critical value
- ❑ Special attention required for fanout reconvergence


Example

□ P_1

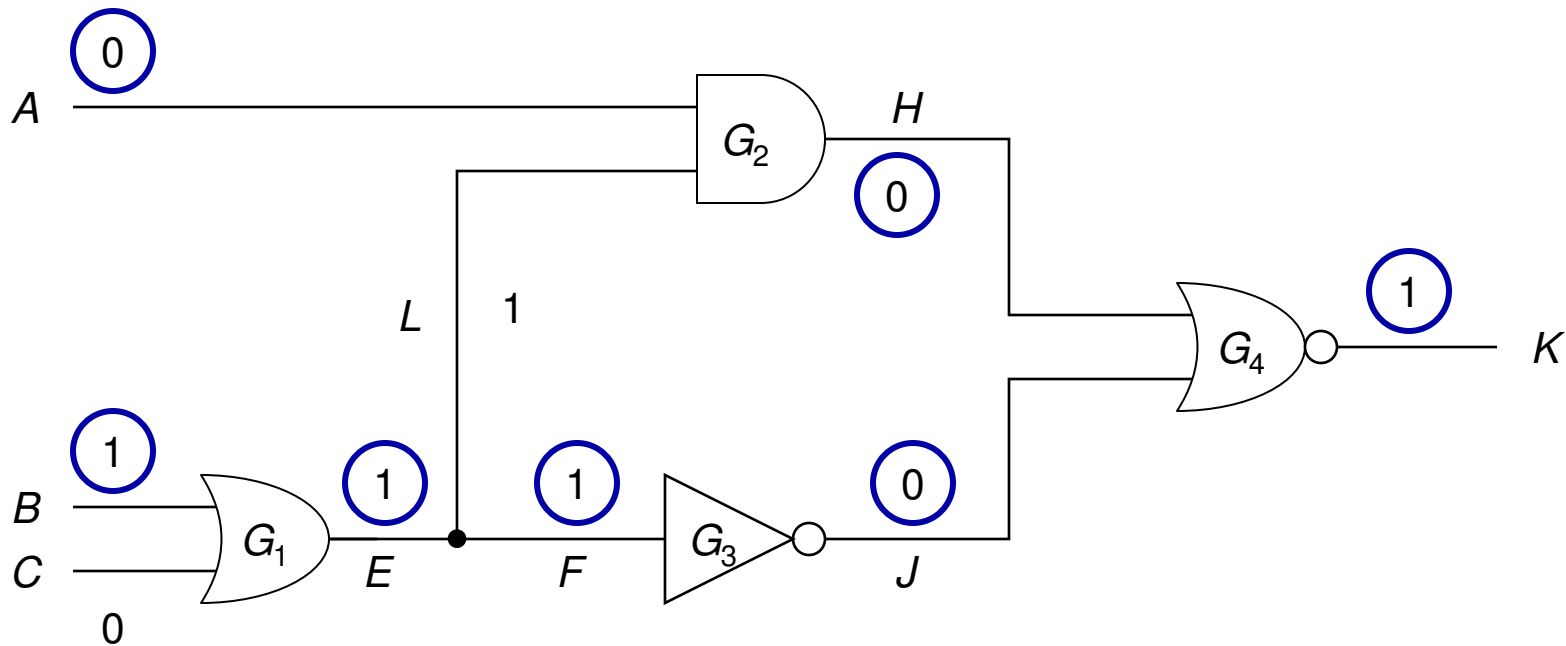

Example (cont'd)

□ P_3

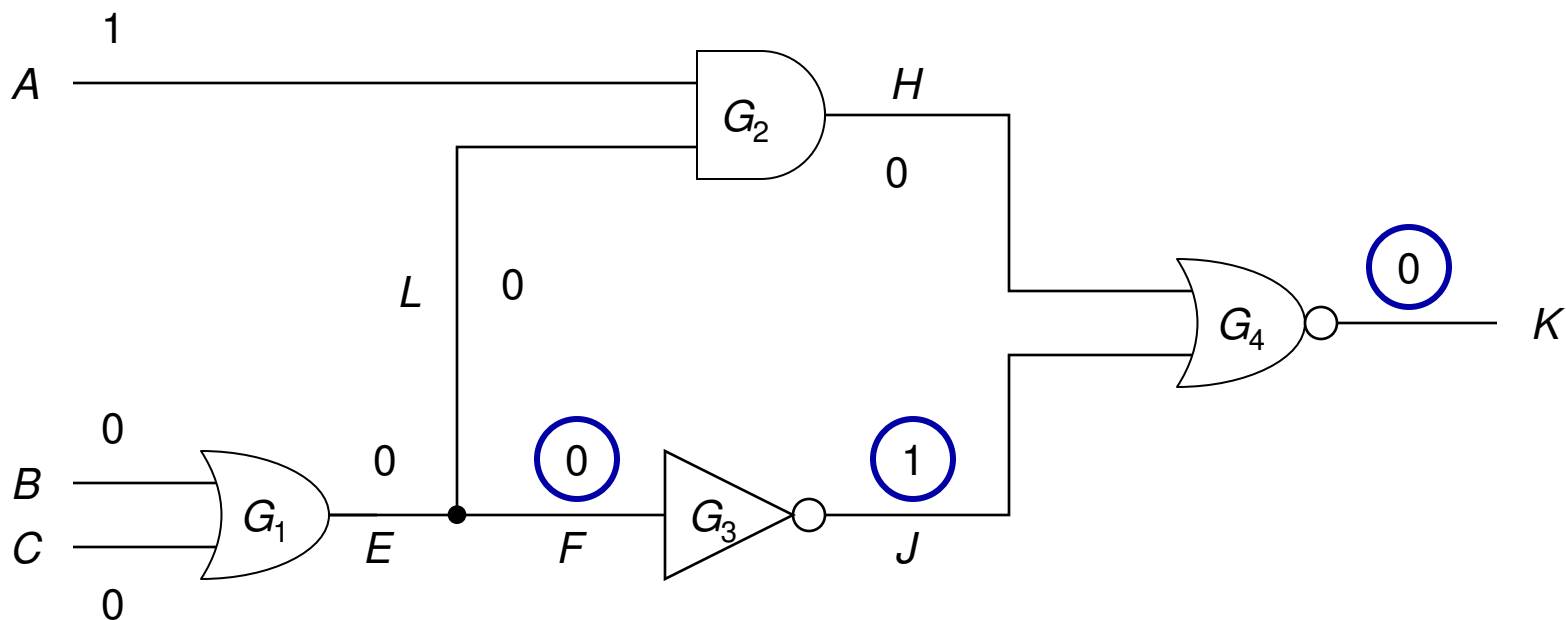

Statistical Fault Analysis (STAFAN)

- [Jain 1985]
- Use probability theory to estimate expected value of fault coverage
- Detectability of fault f (d_f)
 - 1-controllability, $C1(x)$
 - 0-controllability, $C0(x)$
 - Observability, $O(x)$
 - Sensitization probability, $S(x)$

Summary

- Fault simulation is very important for
 - ATPG
 - Diagnosis
 - Fault grading
- Popular techniques
 - Serial, Parallel, Deductive, Concurrent, Differential
- Requirements for fault simulation
 - Fast speed, efficient memory usage, modeling functional blocks, sequential circuits

Logic and Fault Simulation

- ❑ Introduction
- ❑ Simulation models
- ❑ Logic simulation
- ❑ Fault simulation
- ❑ **Concluding remarks**

Conclusions

- ❑ Logic and fault simulations, two fundamental subjects in testing, are presented
- ❑ Into the nanometer age, advanced techniques are required to address new issues
 - High performance
 - High capacity
 - New fault models