
Lecture 4

Power Distribution and Decap Design

Xiongfei Meng
Dept. of ECE
University of British Columbia
xmeng@ece.ubc.ca

Overview

Reading

HJS - Chapter 11 Power Grid and Clock Design

Introduction

Power distribution used to be an afterthought in the design process before the issues of deep submicron brought in new challenges. Today, designers must be concerned with IR drop, Ldi/dt and electromigration while constructing the power system. The design process involves the selection of the overall architecture, placement of Vdd and Vss pins, design of the trunks, and ultimately the width of the wires. The power system is usually done hierarchically to manage complexity, but in the end the overall design must satisfy the noise budgets specified for the chip.

Decoupling capacitor (decap) design in deep submicron presents its own challenges and also affects the power grid design. This lecture highlights some of the key considerations in designing decaps suitable for high-speed applications.

Purpose of Power Distribution

- Power distribution in the past was a fairly simple task
- Goal of power distribution system is to deliver the required current across the chip while maintaining the voltage levels necessary for proper operation of logic circuits
- Must route both power and ground to all gates
- Design Challenges:
 - How many power and ground pins should we allocate?
 - Which layers of metal should be used to route power/ground?
 - How wide should we make the wire to minimize voltage drops and reliability problems
 - How do we maintain V_{DD} and Gnd (i.e., V_{SS}) within noise budget?
 - How do we verify overall power distribution system?

RAS

Lecture 4

3

Importance of Power Distribution


- *Bad* power distribution: excessive voltage drop on the supply and/or excessive ground bounce due to IR drop and Ldi/dt effects.
- What problems can a bad power distribution cause?
 - Timing closure issues
 - Functional failure in extreme cases
- Power distribution has become a complex task in deep submicron
 - Thinner wires => increased wire resistance
 - More logic gates => higher current demand on chip
 - Higher operation frequency
- What if a power distribution problem that causes timing issues is identified at a late design stage (after placement & route)?

RAS

Lecture 4

4

Power Routing Examples

 


RAS

Lecture 4

5

Simple Routing Examples

 


RAS

Lecture 4


6

Interleaved Power/Ground Routing

 


Interleaved Vdd/Vss pairs (e.g., standard cells)


Power Grid Architecture

 

Other Popular Power Grid Architectures

 

Single layer: straps

 


Dual layers: grid

RAS

Lecture 4


9

 

RAS

10

Power Distribution Issues - IR Drop

 



- Narrow line widths increase metal line resistance
- As current flows through power grid, voltage drops occur
- Actual voltage supplied to transistors is less than V_{dd}
- Impacts speed and functionality
- Need to choose wire widths to handle current demands of each segment

RAS

Lecture 4

11

Block Interaction yields IR Drop

  


Plots courtesy of Simplex Solutions, Inc.

RAS

Lecture 4

12

Power Grid Issues – Static IR Drop

 

- Block placement and global power routing determines IR drop on the chip
- Possible solutions
 - Rearrange blocks
 - More Vdd pins
 - Connect bottom portion of grid to top portion


Plot courtesy of Simplex Solutions, Inc.

RAS

Lecture 4

13

Power Grid Issues – Static IR Drop

 

- If we connect bottom portion of grid to top portion, the IR drop is reduced significantly
- However, this is only one part of the problem
- We must also examine electromigration


Plot courtesy of Simplex Solutions, Inc.

RAS

Lecture 4

14

Power Grid Issues - Electromigration

 


- As current flows down narrow wires, metal begins to migrate
- Metal lines break over time due to metal fatigue
- Based on average/peak current density
- $MTTF \rightarrow J_{avg} \rightarrow \text{wire width}$
- Need to widen wires enough to avoid this phenomenon

RAS


Lecture 4

15

Case Study – IR and EM Tradeoff

 

 Simply connecting wires to remove IR drop violations may create more EM violations.



RAS


Lecture

Ldi/dt Effects in the Power Supply

- In addition to IR drop, power system inductance is also an issue
- Inductance may be due to power pin, power bump or power grid
- Overall voltage drop is:

$$V_{\text{drop}} = IR + Ldi/dt$$

 - A practical model for the power system:




RAS

Lecture 4

17

Decoupling Capacitors in the Power Supply

 - Distribute decoupling capacitors (decaps) liberally throughout design
 - Capacitors store up charge
 - Can provide instantaneous source of current for switching




RAS

Lecture 4

18

On-chip Decoupling Caps

 
- On-chip decaps help to stabilize the power grid voltage
- First line of defense against noise which can extend beyond 10GHz
- Simple Example:



- Drop across inductors = $2 \times L \times di/dt = 2 \times 0.2\text{nH} \times 20\text{mA}/100\text{ps} = 80\text{mV}$ (problematic if supply is 1V)
- Actual power pad or bump may need to support thousands of inverters
- Use capacitors to supply instantaneous charge to inverters

Making a Decoupling Capacitor

 
- Decaps are basically NMOS transistors. Top plate is polysilicon, bottom-plate is inverted channel, insulator is gate oxide.
- Connect poly to V_{dd} and source/drain to V_{ss}




- Low-frequency capacitance is roughly $C_{ox} W L$.
- Since these are large capacitance to be used at high frequencies, more accurate representation is needed.

Decap High-Frequency Response

 - Channel resistance in series with C_{decap} (affects response time)



 - Finite transit time (affects capacitance value)




RAS

Lecture 4

21

How much Decoupling Cap?

 - For a rough calculation, consider the following example:



- $C_{\text{decap}} = C_{\text{switching}} [(1-\text{NB})/\text{NB}]$
- For noise budget (NB) of 10%, $C_{\text{decap}} = 9 C_{\text{switching}}$
- Actual required decap is about 2~10X of the total on-chip switching capacitances. High-performance custom chips usually require more decaps.


RAS

Lecture 4

22

How much Decoupling Cap?

 - To estimate required decap value, run SPICE on patch of chip area with power grid, part of logic block, and sprinkle of decaps



- Amount of decap depends on:
 - Acceptable ripple on Vdd-Vss (typically 10% noise budget)
 - Switching activity of logic circuits (usually need 10X switched cap)
 - Current provided by power grid (di/dt)
 - Required frequency response (high frequency operation)
 - How much parasitic decap exists (non-switching cap, gate, wire caps)


RAS

Lecture 4

23

Simulation with Decoupling Caps

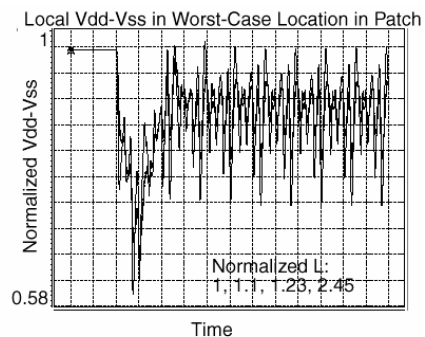- Plot center region of grid
- Local Vdd-Vss in worst-case location in patch (center)
- First dip can be dealt with by a low-frequency on-chip voltage regulator and low-frequency decaps
- Steady-state ripple is controlled by high-frequency decoupling caps
- Adjust location of decaps until the ripple is within noise budget




RAS

Lecture 4

24

Supply Noise is a Dynamic Phenomena

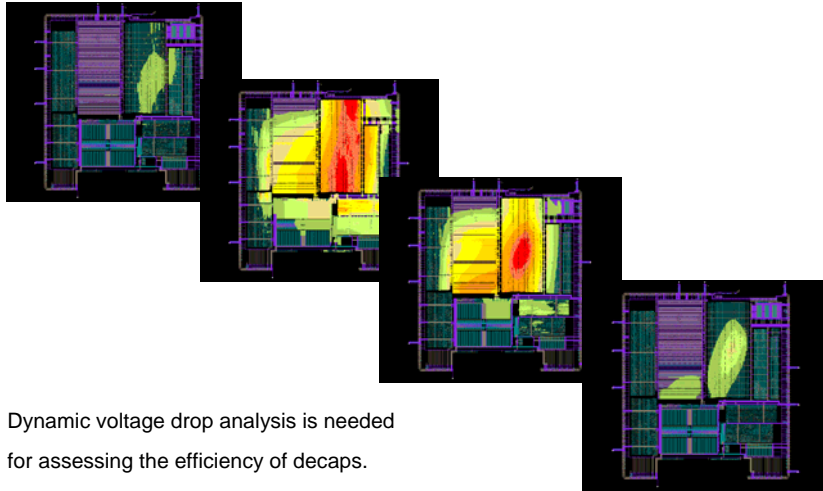

RAS

Lecture 4

25

Designing Power Distribution

- Floorplanner should be aware of $IR + Ldi/dt$ drop and EM problems and design accordingly
 - Requires knowledge of current distributions and voltage drop constraints of blocks being placed
- Provide adequate number of V_{DD} and Gnd pins
- Route power distribution system according to current demands of the blocks
- Widen wires based on expected current density in branches
- Distribute decoupling capacitors liberally throughout design
- Verify full chip with IR/EM tools

RAS

Lecture 4

26

Advanced Topics / Active Research Area

- Power gating
- Multiple voltage domains (voltage islands)
- On-chip voltage regulators
- Improving decap effectiveness
- Decap & logic codesign / IR drop aware floorplanning
- Optimal decap placement