

Digital Logic (256 Review)

Basic logic gates




a	f
0	1
1	0




a	b	c	f <sub>1</sub>	f <sub>2</sub>	f <sub>3</sub>
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	0	1	1
0	1	1	0	1	0
1	0	0	0	1	1
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	1	1	1



$$f_4 = bc + b\bar{c}$$

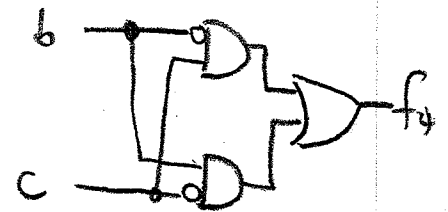


ASIDE

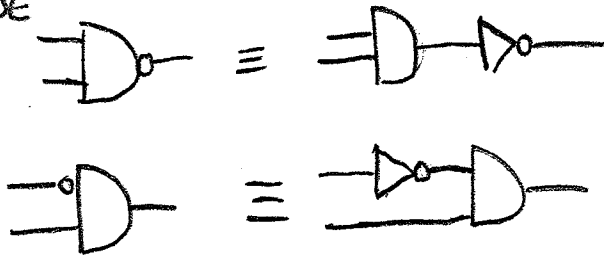

• can also build  $\Rightarrow$  using just 4x  $\Rightarrow$

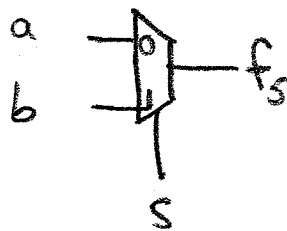In fact,  $\Rightarrow$  is a universal logic gate. You can build any digital system using just  $\Rightarrow$






s	a	b	fs
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

if  $s=1$   
 $f_s = b$   
 else  
 $f_s = a$


$$f_s = \bar{s}a + sb$$

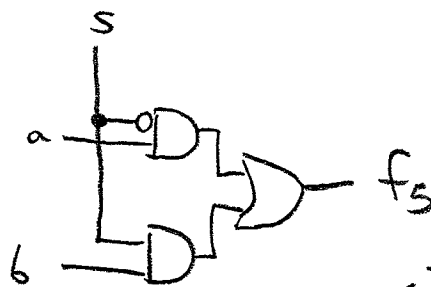

very similar to XOR!


Some Logic Rules: inputs + outputs are directional + have rules

① never connect 2 outputs together

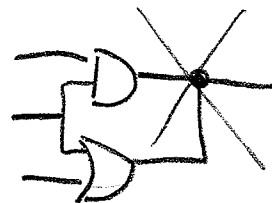


② make sure every input to a logic gate is connected  
 - to a 0 or 1 (constant)

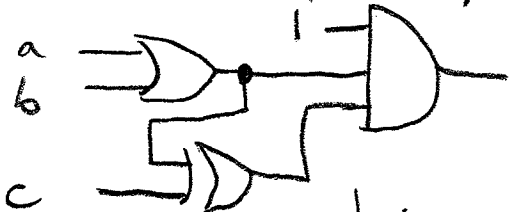- to the output of just 1 other gate
- to a "primary input" from outside world



note: an output can connect to multiple inputs

③ never form a logic loop

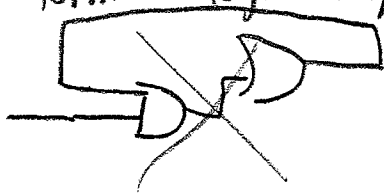


④ never use a mux backwards



# Digital Logic Review (contd)


## D flip flop - positive edge triggered

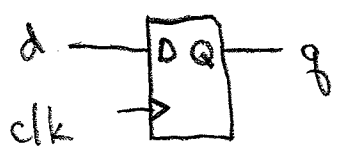


clk	d	q <sub>n+1</sub>
0	x	q <sub>n</sub>
1	x	q <sub>n</sub>
↑	0	0
↑	1	1
↓	x	q <sub>n</sub>

$q_{n+1} = \begin{cases} d & \text{on } \uparrow \text{clk} \\ q_n & \text{otherwise} \end{cases}$   
 } captures d


## DFF + enable input

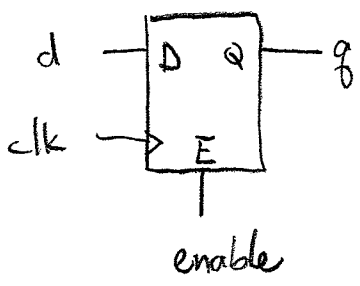

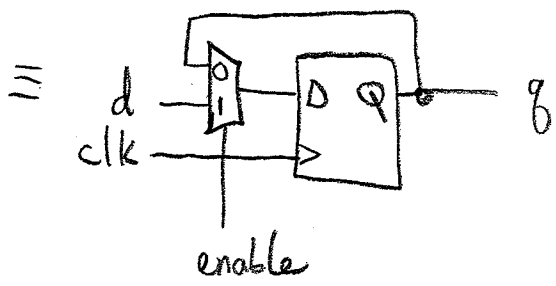$q_{n+1} = \begin{cases} d & \text{on } \uparrow \text{clk only if } E=1 \\ q_n & \text{otherwise} \end{cases}$


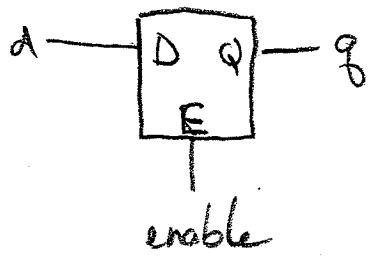
## Level-Sensitive Latch aka Flow-through Latch



if enable = 1  
 $q_{n+1} = d$   
 else  
 $q_{n+1} = q_n$   
 end if

repeats continuously  
 captures last d while enable = 1



# Binary Numbers

EECE259: Introduction to Microcomputers

Prof. Guy Lemieux

# Binary Numbers

- Humans
  - Powers of 10: 1, 10, 100, 1000, ...
  - Example:  $2113 = 2113_{10}$
- Computers
  - Powers of 2: 1, 2, 4, 8, ...
  - Example:  $2113 = 2048+64+1$   
 $= 1000\ 0100\ 0001_2$   
 $= \%1000\ 0100\ 0001$

# Binary Numbers

- Why?
  - Humans have 10 fingers
    - 0, 1, 2, 3, 4, 5, 6, 7, 8, 9
    - Fingers are called digits!
  - Computer switches have 2 states: on, off
    - 0, 1
    - Called **binary digits**, or “bits” for short

# Common Number Bases

- Base 2: binary 0,1  
 $\%0100$  or  $0b0100$  or  $0100_2$
- Base 10: decimal 0 to 9  
 $2113$  or  $2113_{10}$
- Base 8: octal 0 to 7  
 8 digits  
 $04101$  or  $@4101$  or  $4101_8$
- Base 16: hexadecimal 0 to 9, A to F  
 16 digits, also known as “hex”  
 $\$841$  or  $0x841$  or  $841_{16}$

# Computer Number Storage

- Computers use binary **exclusively**
  - Everything stored as sequence of 0s and 1s
    - 0110010110100001101101111000100110...
  - Grouped into...
 

• Nibble	4 bits	1 hex digit
• Byte	8 bits	2 hex digits
• <b>Halfword</b> / short / word	16 bits	4 hex digits
• <b>Word</b> / long	32 bits	8 hex digits
• <b>Long</b> / long long	64 bits	16 hex digits


# Number Format

- In any base, each digit has a **rank**
  - Example
    - $2113_{10} = 2*10^3 + 1*10^2 + 1*10^1 + 3*10^0$
- Notice the increasing exponents or **rank**s
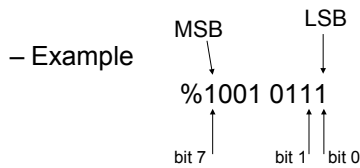
## Important Ranks

- Important Definitions

- MSB Most Significant Bit (leftmost digit)
  - Always “bit 7 of byte”, “bit 31 of word”
- LSB Least Significant Bit (rightmost digit)
  - Always “bit 0”



7

## Base Conversions

- Converting Binary to Decimal is easy
  - Just expand digits with ranks, and add

- Example

$$\begin{aligned}
 1001_2 \text{ or } \%1001 \text{ to decimal} \\
 \%1001 &= 1 \cdot 2^3 + 0 \cdot 2^2 + 0 \cdot 2^1 + 1 \cdot 2^0 \\
 &= 1 \cdot 8 + 0 \cdot 4 + 0 \cdot 2 + 1 \cdot 1 \\
 &= 8 + 0 + 0 + 1 \\
 &= 9 \\
 &= 9_{10}
 \end{aligned}$$

8

## Base Conversions

- Example

$$\begin{aligned}
 \%1001 \ 0111 \text{ to decimal} \\
 &= 1 \cdot 2^7 + 0 \cdot 2^6 + 0 \cdot 2^5 + 1 \cdot 2^4 + 0 \cdot 2^3 + 1 \cdot 2^2 + 1 \cdot 2^1 + 1 \cdot 2^0 \\
 &= 1 \cdot 128 + 0 \cdot 64 + 0 \cdot 32 + 1 \cdot 16 + 0 \cdot 8 + 1 \cdot 4 + 1 \cdot 2 + 1 \cdot 1 \\
 &= 128 + 16 + 4 + 2 + 1 \\
 &= 144 + 7 \\
 &= 151
 \end{aligned}$$

9

## Base Conversions

- Leading 0s don't change value

– Example

$$\begin{aligned}
 \%101 &= 4 + 0 \cdot 2 + 1 = 5 \\
 \%0101 &= 0 \cdot 8 + 4 + 0 \cdot 2 + 1 = 5
 \end{aligned}$$

- We often drop leading 0s in written form
  - Computers cannot!
  - Must store all 8 bits of byte, 32 bits of word

10

## Base Conversions

- Converting Decimal to Binary a bit harder
  - Expand value using powers of 2

- Example

$$\begin{aligned}
 53_{10} &= 32 + 16 + 4 + 1 \\
 &= 32 + 16 + 0 \cdot 8 + 4 + 0 \cdot 2 + 1 \\
 &= \%110101
 \end{aligned}$$

11

## Base Conversions

- Converting Decimal to Binary
  - Easier way: divide by 2 approach (produces LSB first)

• 53	odd?	Y = 1	
• 53/2 = 26	odd?	N = 0	
• 26/2 = 13	odd?	Y = 1	
• 13/2 = 6	odd?	N = 0	
• 6/2 = 3	odd?	Y = 1	
• 3/2 = 1	odd?	Y = 1	
• 1/2 = 0	<b>stop</b>		

How do you modify this to convert decimal → hexadecimal ?

12

## Memorize These!

<b>0</b>	<b>1</b>	<b>8</b>	<b>256</b>	<b>16</b>	<b>65,536</b>
<b>1</b>	<b>2</b>	9	512		
<b>2</b>	<b>4</b>	<b>10</b>	<b>1024</b>	20	1,048,576 Mega
<b>3</b>	<b>8</b>				
<b>4</b>	<b>16</b>	11	2048		
<b>5</b>	<b>32</b>	<b>12</b>	<b>4096</b>	24	16,771,216 "16 Meg"
<b>6</b>	<b>64</b>				
<b>7</b>	<b>128</b>	13	8192		
		<b>14</b>	<b>16384</b>	30	1,073,741,824 <sub>13</sub> Giga