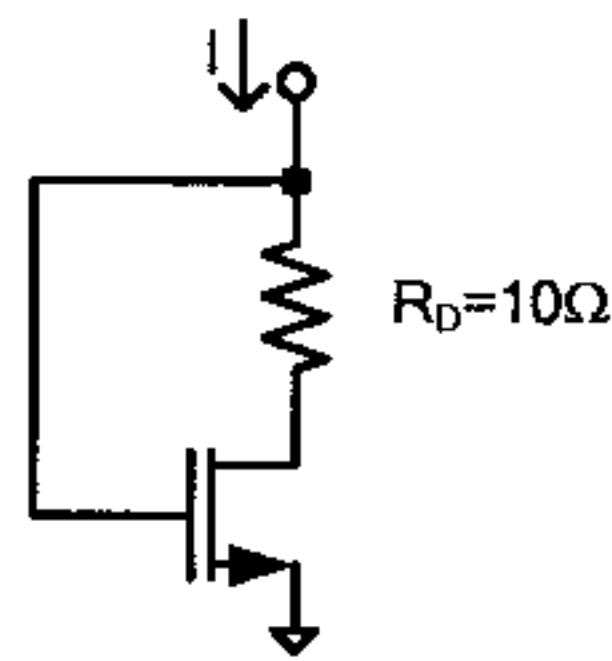


Solutions, Final exam 2010

1. Find the maximum bias current I for which the transistor in the following circuit operates in the saturation region. [10 marks]

Assume $\lambda = \gamma = 0$, $V_{TH} = 0.5 \text{ V}$, $\mu_n C_{ox} = 1 \text{ mA/V}^2$, $(W/L)_{NMOS} = 10$, $R_D = 10 \Omega$.



Sat. condition : $V_{GD} \leq V_{th}$

$$\left. \begin{array}{l} V_{GD} \leq V_{th} \\ V_{GD} = R_D I \end{array} \right\} \rightarrow R_D \cdot I \leq V_{th} \rightarrow I \leq \frac{0.5 \text{ V}}{10 \Omega} = 50 \text{ mA}$$

Write your answer in this box

$$I = \underline{50} \text{ mA}$$

2. The magnitude frequency response of a unity-gain closed-loop amplifier shows a peaking of 93% in the vicinity of the gain crossover frequency. What is the phase margin? [10 marks]

$$\text{closed loop transfer function} = \frac{\frac{1}{\beta}}{1 + \text{loop gain}}$$

$$\text{low freq. gain is } 1 \Rightarrow \beta = 1$$

$$PM = 180 + \angle \beta H$$

$$\Rightarrow \left| \frac{1}{1 + 1 \angle (180 - PM)} \right| = 1.93$$

$$\left| \frac{1}{1 + \cos(180 - PM) + j \sin(180 - PM)} \right| = 1.93 \rightarrow \left| \frac{1}{1 - \cos PM + j \sin PM} \right| = 1.93$$

$$\rightarrow \frac{1}{\sqrt{(1 - \cos PM)^2 + \sin^2 PM}} = 1.93 \rightarrow \frac{1}{1 + \cos^2 PM - 2 \cos PM + \sin^2 PM} = (1.93)^2$$


$$\rightarrow \frac{1}{1 + (\cos^2 PM + \sin^2 PM) - 2 \cos PM} = (1.93)^2 \rightarrow 2 - 2 \cos PM = \left(\frac{1}{1.93} \right)^2$$

$$\rightarrow PM \approx 30^\circ$$

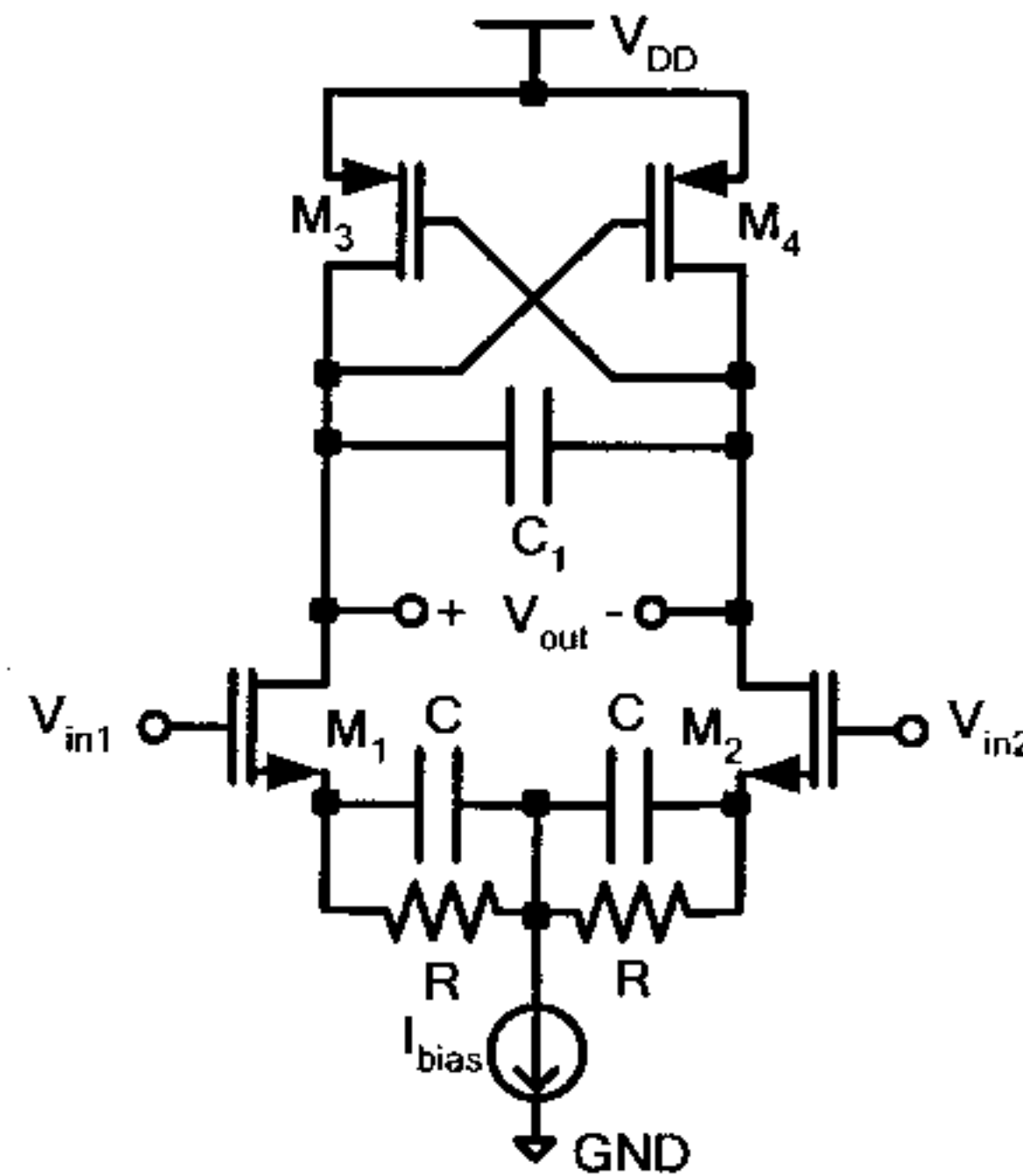3. Assuming that the following circuit is symmetrical and $\gamma = \lambda = 0$:

- Find the expression for the small-signal differential voltage gain ($\frac{V_{out}}{V_{in1} - V_{in2}}$) of the circuit at very low frequencies. [10 marks]
- What is the gain of the circuit at very high frequencies? [5 marks]
- Repeat part (ii) assuming $\lambda \neq 0$. [5 marks]


Note: In this question neglect all other capacitances that are not shown in the circuit.




$$r_o = \infty$$

i) at very low freq. caps are open.

Half circuit:

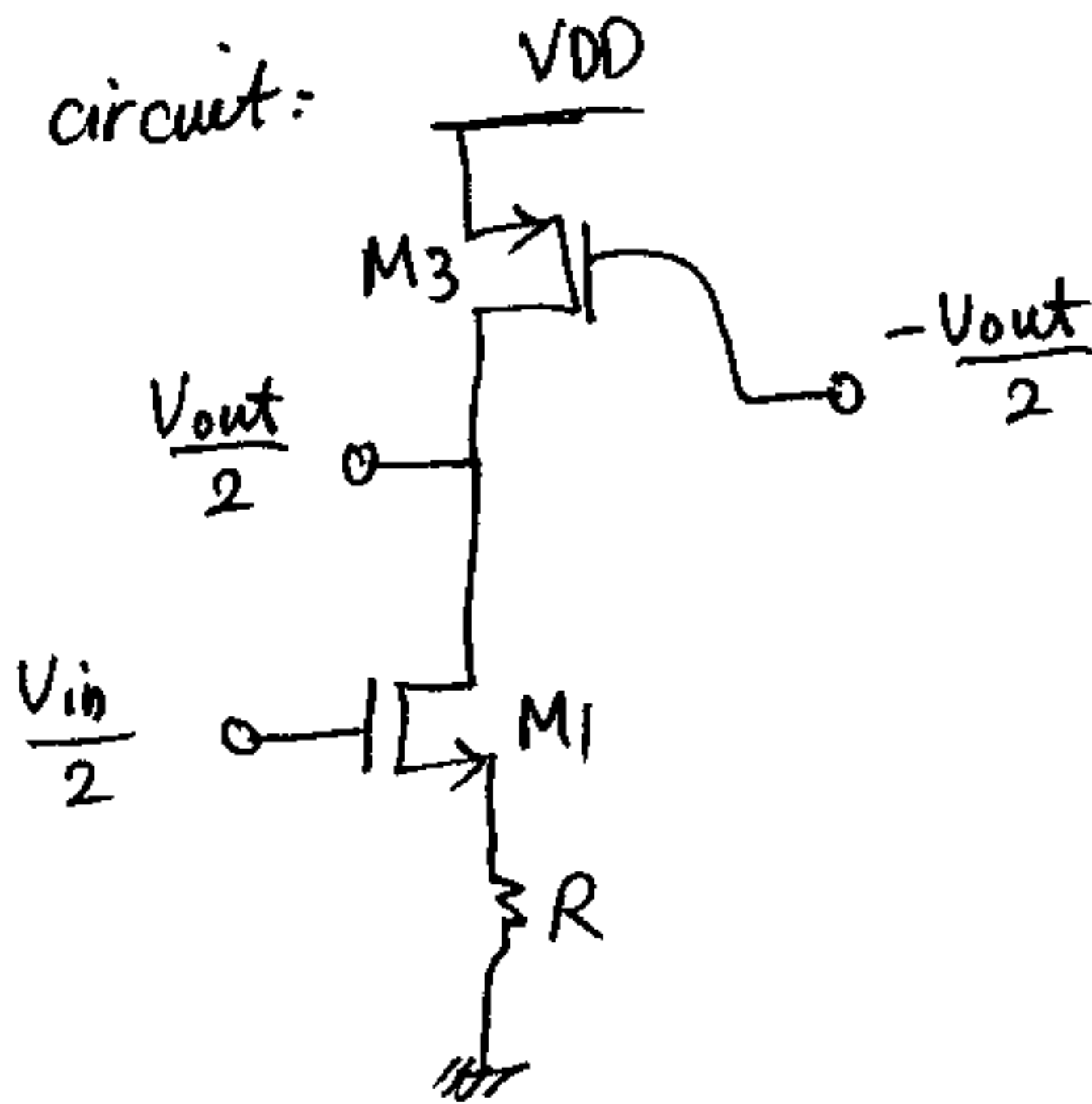

small signal model:

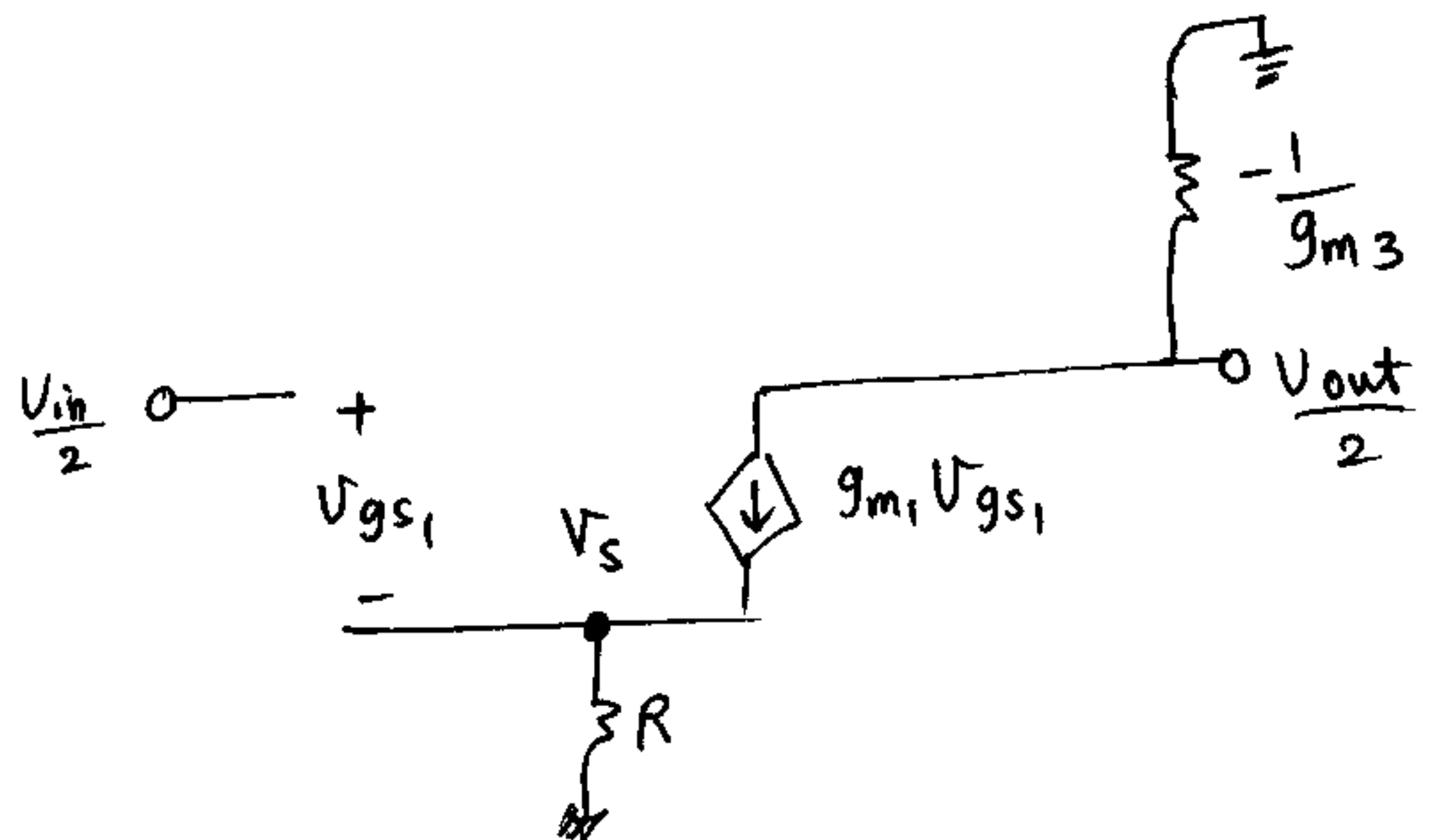


$$\frac{V_{out}}{2} = \left(\frac{-1}{g_{m3}} \right) (-g_{m1} V_{gs1}) = \frac{g_{m1}}{g_{m3}} V_{gs1} \quad \text{I}$$

$$\frac{V_{in}}{2} = V_s + V_{gs1} = (g_{m1} V_{gs1} \cdot R) + V_{gs1} = (1 + g_{m1} R) V_{gs1} \quad \text{II}$$

$$\text{I, II} \rightarrow \frac{\frac{V_{out}}{2}}{\frac{V_{in}}{2}} = \frac{\frac{g_{m1}}{g_{m3}} V_{gs1}}{(1 + g_{m1} R) V_{gs1}} \rightarrow A_{v \text{ Low Freq.}} = \frac{g_{m1}}{g_{m3} (1 + g_{m1} R)}$$

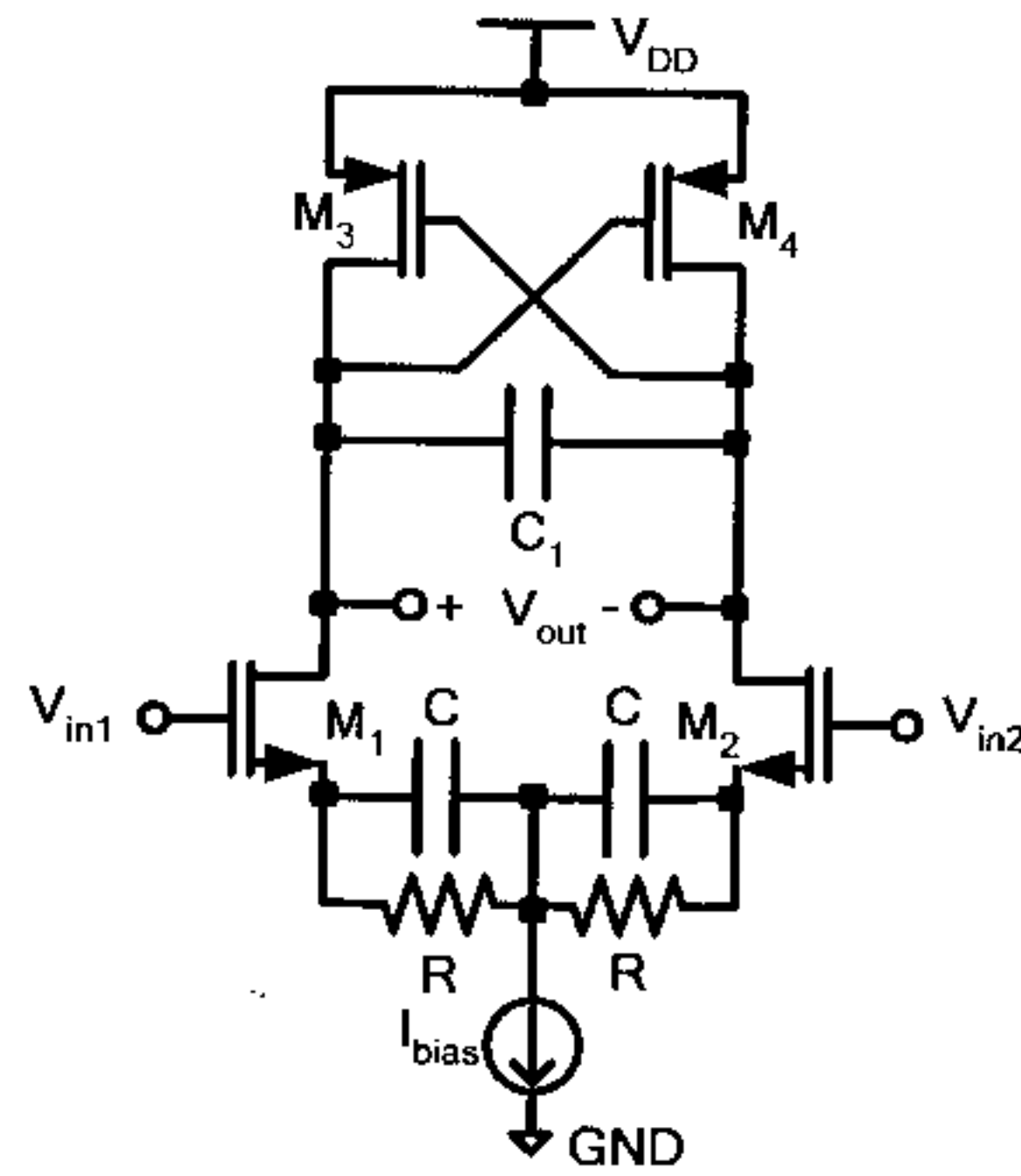For your convenience the circuit diagram is replicated here:



ii) C_1 is short at very high frequencies ,

$$A_{V_{high\ freq.}} = 0$$


iii) again the high freq. gain is zero.

4. Neglecting all other capacitances and assuming $\lambda = 0$, for the following circuit:

i) Calculate the input impedance. [8 marks]

ii) Calculate the output impedance. [8 marks]

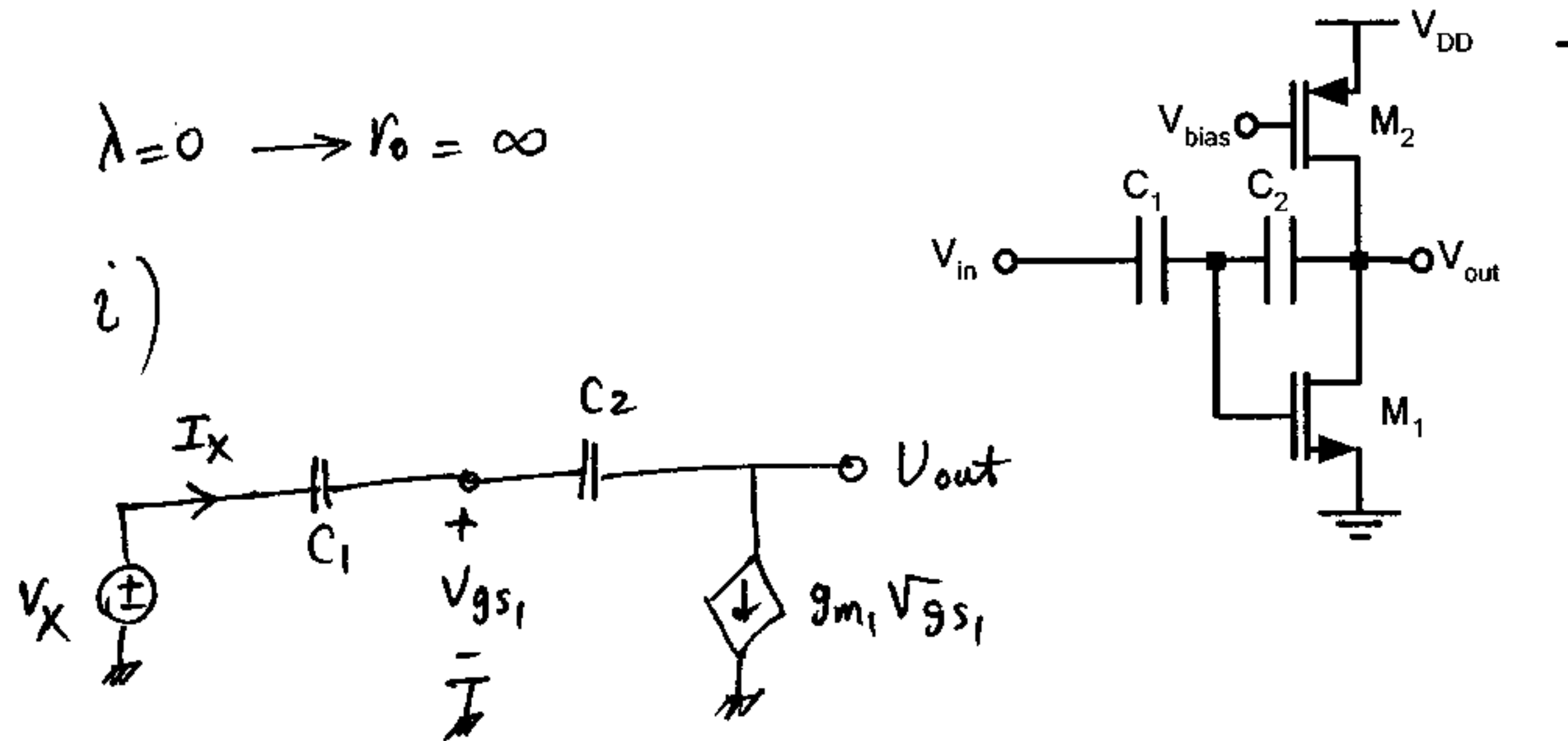
iii) How would the input impedance change if C_2 is replaced with a resistor. [4 marks]



$$I_x = g_{m1} V_{gs1} \rightarrow V_{gs1} = \frac{I_x}{g_{m1}}$$

$$I_x = C_1 s (V_x - V_{gs1}) = C_1 s \left(V_x - \frac{I_x}{g_{m1}} \right) \rightarrow I_x \left(1 + \frac{C_1 s}{g_{m1}} \right) = C_1 s V_x$$
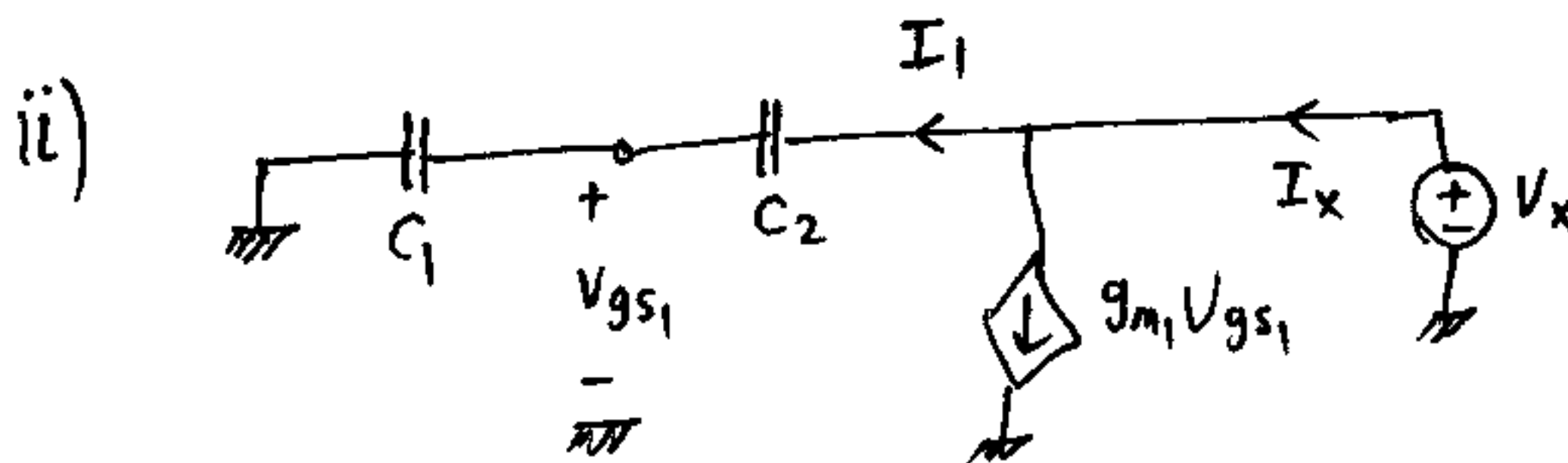
$$\rightarrow Z_{in} = \frac{V_x}{I_x} = \frac{1 + \frac{C_1 s}{g_{m1}}}{C_1 s} = \frac{1}{g_{m1}} + \frac{1}{C_1 s}$$



$$I_1 = I_x - g_{m1} V_{gs1}$$


$$\left. \begin{aligned} I_1 &= C_2 s (V_x - V_{gs1}) \\ I_1 &= C_1 s (V_{gs1} - 0) \end{aligned} \right\} \rightarrow C_1 s V_{gs1} = C_2 s (V_x - V_{gs1}) \rightarrow V_{gs1} (C_1 s + C_2 s) = C_2 s V_x$$

$$\rightarrow V_{gs1} = \frac{C_2 s}{C_1 s + C_2 s} V_x = \frac{C_2}{C_1 + C_2} V_x$$

$$I_x - g_{m1} V_{gs1} = C_1 s V_{gs1} \rightarrow I_x = (g_{m1} + C_1 s) V_{gs1} = (g_{m1} + C_1 s) \frac{C_2}{C_1 + C_2} V_x$$

$$\rightarrow Z_{out} = \frac{V_x}{I_x} = \frac{(C_1 + C_2)}{C_2 (g_{m1} + C_1 s)}$$

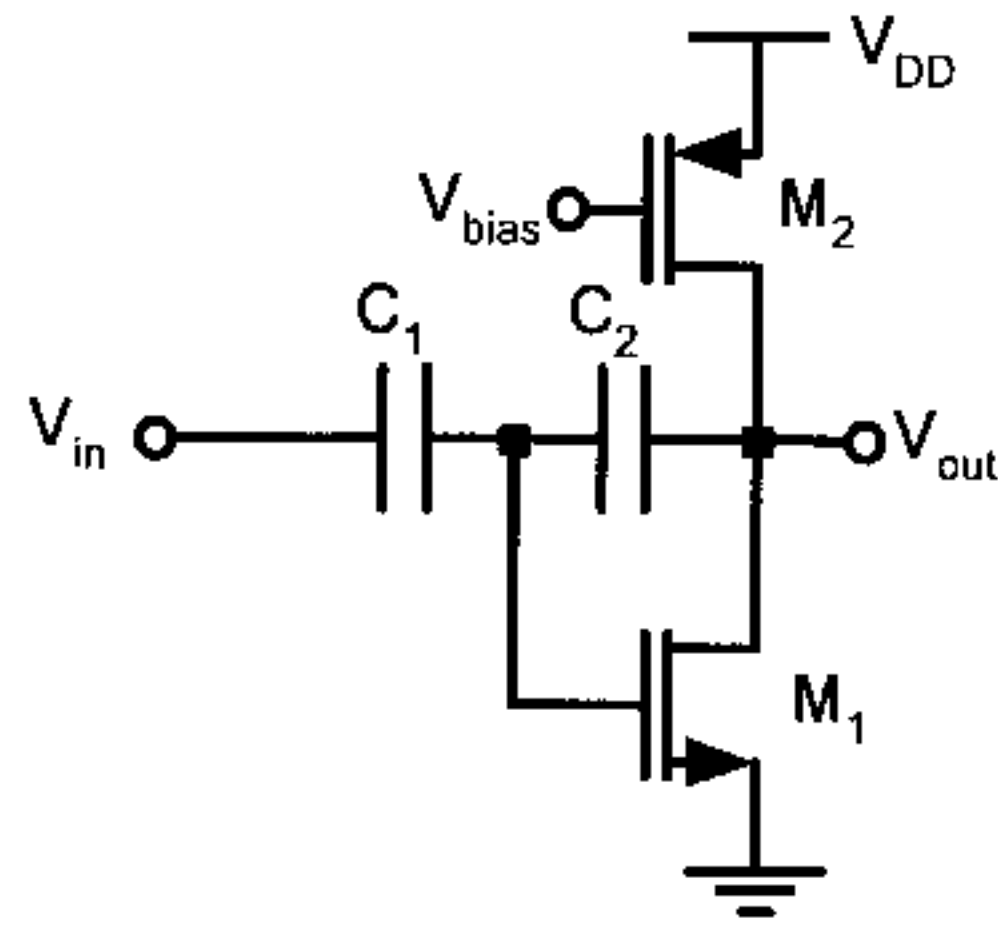For your convenience the circuit diagram is replicated here:



iii) Z_{in} will not change as it does not depend on the value of C_2 .

5. Design a two-stage op amp based on the topology shown below with the following design specifications:

- $V_{DD}=3\text{ V}$
- Total power consumption of 3 mW
- Output swing of 2.6 V
- Total gain of 1000
- $L = 0.4\mu\text{m}$ for all the device


Use the following assumptions for your design

- Allocate equal overdrive voltages to M_5 and M_6
- Assume the bias currents of the first stage and the second stage are equal.
- $V_{SG3}=V_{SG5}$

The technology parameters are:

$\lambda_{(NMOS)} = \lambda_{(PMOS)} = 0.1\text{ V}^{-1}$, $\gamma = 0$, $V_{DD} = 3\text{ V}$, $V_{TH(NMOS)} = |V_{TH(PMOS)}| = 0.5\text{ V}$, $\mu_n C_{ox} = 1\text{ mA/V}^2$, $\mu_p C_{ox} = 0.5\text{ mA/V}^2$.

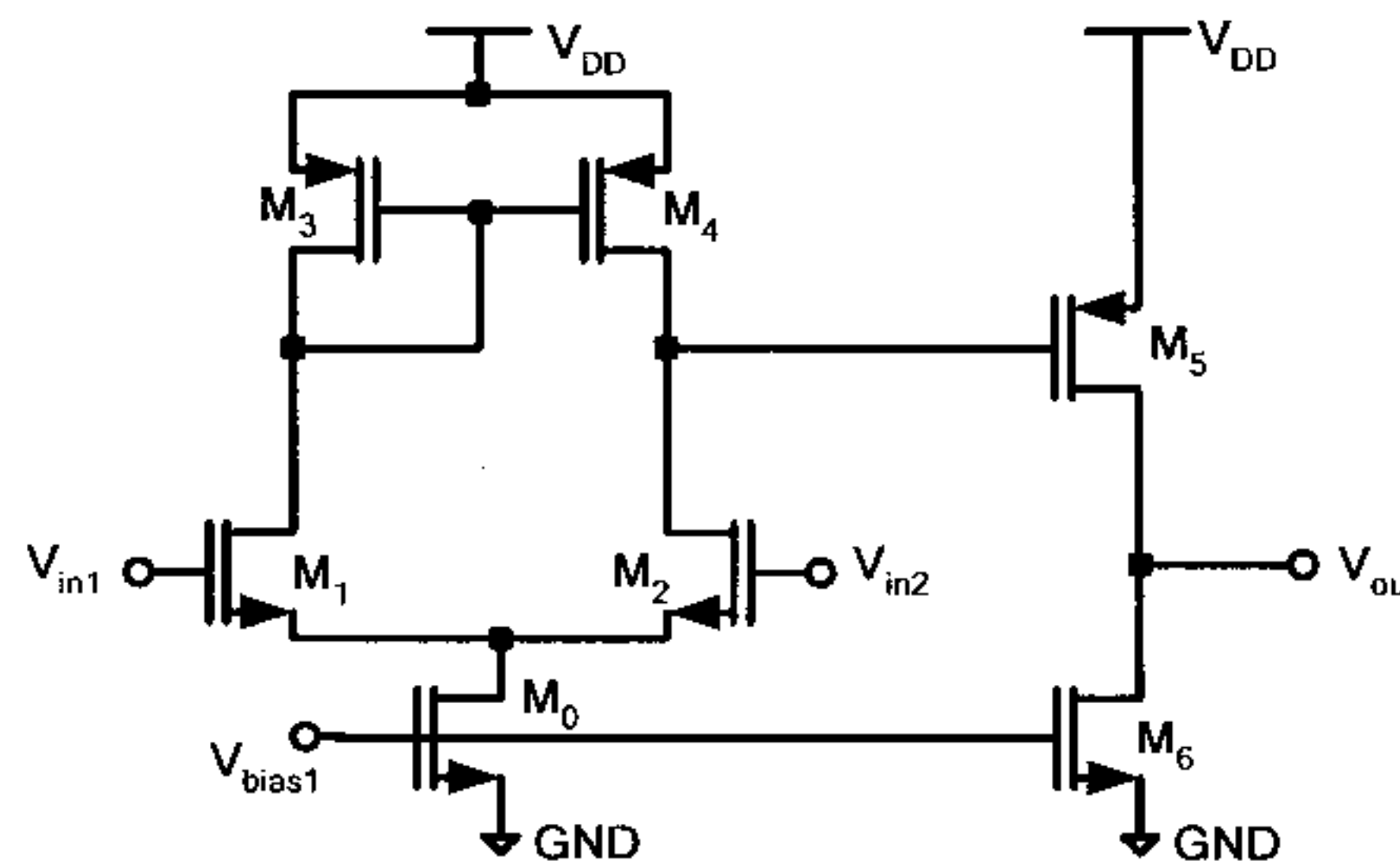Note: Use the parameter λ only for calculating the r_o of the transistors. **Do not** use λ in any other calculation including your bias currents.



Find V_{bias1} , and all the transistor widths (i.e., $W_0, W_1, W_2, W_3, W_4, W_5, W_6$). [20 marks]

$$V_{OD5} = V_{OD6}$$

$$\text{Output swing} = V_{DD} - |V_{OD5}| - V_{OD6} = 3 - 2|V_{OD5}| = 2.6\text{ V} \rightarrow |V_{OD5}| = V_{OD6} = 0.2\text{ V}$$


$$V_{SG3} = V_{SG5} \rightarrow |V_{OD3}| = |V_{OD5}| = 0.2\text{ V}$$

$$I_0 = I_5 \rightarrow I_0 = I_5 = \frac{1}{2} \times \frac{3\text{ mW}}{3\text{ V}} = 0.5\text{ mA}$$

$$I_5 = 0.5\text{ mA} = \frac{1}{2} \times 0.5 \frac{\text{mA}}{\text{V}^2} \times \left(\frac{W}{L}\right)_5 \times V_{OD5}^2 \rightarrow \left(\frac{W}{L}\right)_5 = 50 \left. \begin{array}{l} L = 0.4\mu\text{m} \end{array} \right\} \rightarrow W_5 = 20\mu\text{m}$$

For your convenience the circuit diagram and transistor parameters are replicated here:

$\lambda_{(NMOS)} = \lambda_{(PMOS)} = 0.1 \text{ V}^{-1}$, $\gamma = 0$, $V_{DD} = 3 \text{ V}$, $V_{TH(NMOS)} = |V_{TH(PMOS)}| = 0.5 \text{ V}$, $\mu_n C_{ox} = 1 \text{ mA/V}^2$, $\mu_p C_{ox} = 0.5 \text{ mA/V}^2$.

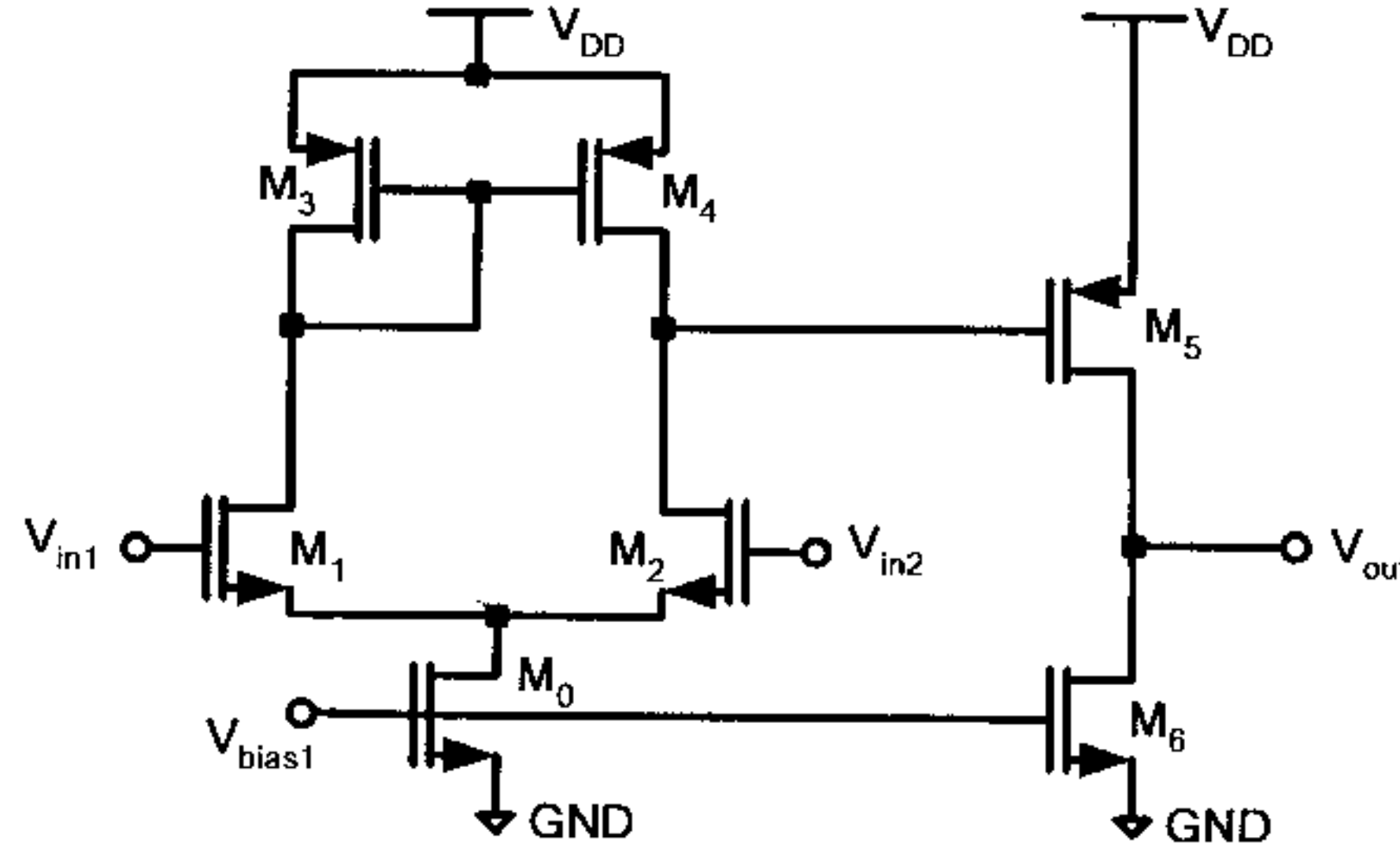

$$I_6 = 0.5 \text{ mA} = \frac{1}{2} \times 1 \times \frac{W_6}{0.4} \times V_{OD6}^2 = \frac{1}{2} \frac{W_6}{0.4} (0.2)^2 \rightarrow W_6 = 10 \mu\text{m}$$

$$I_3 = 0.25 \text{ mA} = \frac{1}{2} \times 0.5 \times \frac{W_3}{0.4} (0.2)^2 \rightarrow W_3 = W_4 = 10 \mu\text{m}$$

$$g_{m5} = \frac{2 I_{D5}}{|V_{OD5}|} = \frac{2 \times 0.5}{0.2} = 5 \frac{\text{mA}}{\text{V}}$$

$$r_{o2} = r_{o4} = \frac{1}{\lambda I_{D2}} = \frac{1}{0.1 (0.25 \text{ mA})} = 40 \text{ k}\Omega$$

$$r_{o5} = r_{o6} = \frac{1}{0.1 \times 0.5 \text{ mA}} = 20 \text{ k}\Omega$$

$$|A_V| = g_{m1} (r_{o2} \parallel r_{o4}) \cdot g_{m5} (r_{o5} \parallel r_{o6}) = 1000 \rightarrow g_{m1} \times 20 \text{ k}\Omega \times 5 \times 10 \text{ k}\Omega = 1000$$

$$\rightarrow g_{m1} = 1 \frac{\text{mA}}{\text{V}} = \sqrt{2 k_n I_{D1}} \rightarrow 1 = \sqrt{2 \times 1 \times \frac{W_1}{0.4} \times 0.25 \text{ mA}} \rightarrow W_1 = 0.8 \mu\text{m}$$

$$W_1 = W_2 = 0.8 \mu\text{m}$$

$$V_{OD0} = 0.2 \text{ V} \rightarrow V_{bias1} = V_{th} = 0.2 \rightarrow V_{bias1} = 0.2 + 0.5 = 0.7 \text{ V}$$

$$I_0 = 1 \text{ mA} = \frac{1}{2} \times 1 \times \frac{W_0}{0.4} \times (0.2)^2 \rightarrow W_0 = 20 \mu\text{m}$$