


1. In the following circuit, assuming that the transistor is operating in the saturation region:

a) Find the required V_{bias} for which the dc value of the V_{out} is 1.5 V. [10 marks]

b) Is the assumption that the transistor is in the saturation region correct? [4 marks]

 c) Find the small-signal gain V_{out}/V_{sig} . [6 marks]

Assume $\lambda = 0$, $\gamma = 1 \text{ V}^{1/2}$, $2\Phi_F = 0.64 \text{ V}$, $V_{TH0} = 0.5 \text{ V}$, $\mu_n C_{ox} = 1 \text{ mA/V}^2$, $(W/L)_{NMOS} = 48$, $R_D = 1 \text{ k}\Omega$, and $V_{DD} = 3.0 \text{ V}$.



No body effect

$$a) \quad I_D = \frac{V_{DD} - V_{out}}{R_D} = \frac{3 - 1.5}{1 \text{ k}} = 1.5 \text{ mA}$$

$$I_D = 1.5 \text{ mA} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{bias} - V_{th})^2 \rightarrow 1.5 = \frac{1}{2} \times 1 \times 48 (V_{bias} - 0.5)^2$$

$$\rightarrow V_{bias} = 0.75 \text{ V}$$

$$b) \quad V_{GD} = V_{bias} - V_{out} = 0.75 - 1.5 < V_{th} \rightarrow \text{The device is in sat.}$$

$$c) \quad A_v = -g_m \cdot R_D$$


$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{th}) = 1 \times 48 \times 0.25 = 12 \frac{\text{mA}}{\text{V}}$$

$$\Rightarrow A_v = -12 \times 1 = -12 \frac{\text{V}}{\text{V}}$$

2. In the following circuit assume that:

$$\lambda_{(NMOS)} = \lambda_{(PMOS)} = 0V^{-1}, \gamma = 0, V_{DD} = 3V, V_b = 2.3V, V_{TH(NMOS)} = |V_{TH(PMOS)}| = 0.5V, \mu_n C_{ox} = 1 \text{ mA/V}^2, \mu_p C_{ox} = 0.25 \text{ mA/V}^2.$$

 Furthermore, assume that $I_1 = I_{out}$ and all transistors have the same size ($\frac{W}{L} = 40$). Find the value of R that results in the minimal voltage headroom required at node V_{out} . [20 marks]



$$I_{out} = I_5 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right) (V_{SG5} - |V_{th}|)^2 = \frac{1}{2} \times 0.25 \times 40 (3 - 2.3 - 0.5)^2 = 0.2 \text{ mA}$$

$$I_1 = I_{out} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS1} - V_{th})^2 \rightarrow 0.2 \text{ mA} = \frac{1}{2} \times 1 \times 40 (V_{GS1} - 0.5)^2$$

$$\rightarrow V_{GS1} = V_{GS3} = V_{GS2} = V_{GS4} = 0.6V, \quad V_{out} = V_{GS2} = 0.6V$$

M_2 must be biased at the edge of saturation, therefore $V_{GD2} = V_{th} \rightarrow$

$$V_{out} - V_{D2} = 0.5 \rightarrow 0.6 - V_{D2} = 0.5 \rightarrow V_{D2} = 0.1V$$

$$\begin{cases} V_Y = V_{G4} = V_{D2} + V_{GS4} = 0.1 + 0.6 = 0.7V \\ V_X = V_{G3} = V_{D1} + V_{GS3} = V_{GS1} + V_{GS3} = 0.6 + 0.6 = 1.2V \end{cases}$$


$$R = \frac{V_X - V_Y}{I} = \frac{1.2 - 0.7}{0.2 \text{ mA}} = 2.5 \text{ k}\Omega$$

3. Assuming that all transistors are in saturation, $\left(\frac{W}{L}\right)_3 = \left(\frac{W}{L}\right)_4$, and $\lambda = \gamma = 0$:

i) Find an expression for I_{out} in terms of R , transistor parameters (e.g., μ and C_{ox}), and transistor sizes [10 marks].

ii) What would be the percentage change in I_{out} if V_{DD} is increased by 10%. [5 marks]

 iii) How would the expression for I_{out} derived in part (i) change if $\gamma \neq 0$ and why? [5 marks]



i) $I_1 = I_{out}$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_2 (V_{GS2} - V_{thn})^2 \rightarrow V_{GS2} = V_{thn} + \sqrt{\frac{2 I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}}$$

Similarly: $V_{GS1} = V_{thn} + \sqrt{\frac{2 I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}}$

$$V_{GS1} - V_{GS2} = R I_{out} \rightarrow \sqrt{\frac{2 I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} - \sqrt{\frac{2 I_{out}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} = R I_{out} \rightarrow$$

$$R \sqrt{I_{out}} = \sqrt{\frac{2}{\mu_n C_{ox}}} \left(\sqrt{\left(\frac{L}{W}\right)_1} - \sqrt{\left(\frac{L}{W}\right)_2} \right) \rightarrow I_{out} = \frac{2}{\mu_n C_{ox} R^2} \left[\sqrt{\frac{L_1}{W_1}} - \sqrt{\frac{L_2}{W_2}} \right]^2$$

ii) no change, I_{out} does not depend on V_{DD} .

iii) no change, there is no body effect ($V_{SB1} = V_{SB2} = 0$)


4. Design a symmetric differential amplifier based on the topology shown below with the following design specifications:

- $V_{DD}=3.0\text{ V}$
- Total power consumption of 3.0 mW
- Output DC level of 1.5 V
- Differential gain of 40 V/V
- $L=0.4\text{ }\mu\text{m}$ for all devices

Assume that the minimum required voltage at the drain of M_0 to keep it in saturation is 0.2 V .

The technology parameters are:

$\lambda_{(NMOS)}=0\text{ V}^{-1}$, $\lambda_{(PMOS)}=0\text{ V}^{-1}$, $\gamma=0$, $V_{DD}=3.0\text{ V}$, $V_{TH(NMOS)}=|V_{TH(PMOS)}|=0.5\text{ V}$, $\mu_n C_{ox}=1\text{ mA/V}^2$, $\mu_p C_{ox}=0.25\text{ mA/V}^2$.

 

a) Find V_{bias1} , and all the transistor widths (i.e., W_0, W_1, W_2, W_3 , and W_4). [14 marks]

b) Find the minimum and maximum allowable input common-mode (input DC) levels [6 marks].

a) M_0 is biased at the edge of the sat. region, therefore $V_{GD0} = V_{th}$
 $\rightarrow V_{bias1} - 0.2 = 0.5\text{ V} \rightarrow V_{bias1} = \boxed{0.7\text{ V}}$

$$I_{M0} = \frac{P}{V_{DD}} = \frac{3\text{ mW}}{3\text{ V}} = 1\text{ mA}$$

$$I_3 = \frac{I_{M0}}{2} = 0.5\text{ mA} = \frac{1}{2} \times 0.25 \times \frac{W_3}{0.4} (3 - 1.5 - 0.5)^2 \rightarrow W_3 = W_4 = \boxed{1.6\text{ }\mu\text{m}}$$

$$I_{M0} = \frac{1}{2} \mu_n C_{ox} \frac{W_0}{L} (V_{bias1} - V_{th})^2 \rightarrow 1\text{ mA} = \frac{1}{2} \times 1 \times \frac{W_0}{0.4} \times (0.7 - 0.5)^2 \rightarrow W_0 = \boxed{20\text{ }\mu\text{m}}$$


$$g_{m3} = \mu_p C_{ox} \left(\frac{W}{L}\right)_3 (V_{SG3} - |V_{th}|) = 0.25 \times \frac{1.6}{0.4} \times 1 = 1\text{ }\frac{\text{mA}}{\text{V}}$$

$$A_V = -\frac{g_{m1}}{g_{m3}} = -40 \rightarrow \frac{g_{m1}}{1} = 40 \rightarrow g_{m1} = 40\text{ }\frac{\text{mA}}{\text{V}}$$

$$g_{m1} = 40 = \sqrt{2 K_n I_{D1}} = \sqrt{2 \times 1 \times \frac{W_1}{0.4} \times 0.5} \rightarrow W_1 = \boxed{640\text{ }\mu\text{m}} = W_2$$

For your convenience the circuit diagram and transistor parameters are replicated here:

$\lambda_{(NMOS)}=0 \text{ V}^{-1}$, $\lambda_{(PMOS)}=0 \text{ V}^{-1}$, $\gamma=0$, $V_{DD}=3.0 \text{ V}$, $V_{TH(NMOS)}=|V_{TH(PMOS)}|=0.5 \text{ V}$, $\mu_n C_{ox}=1 \text{ mA/V}^2$, $\mu_p C_{ox}=0.25 \text{ mA/V}^2$.

 

$$I_{D1} = 0.5 \text{ mA} = \frac{1}{2} \times 1 \times \frac{640}{0.4} (V_{GS1} - 0.5)^2 \rightarrow V_{GS1} = 0.525 \text{ V}$$

$$V_{in \text{ CM min}} = V_{D0 \text{ min}} + V_{GS1} = 0.2 + 0.525 = 0.725 \text{ V}$$

$V_{in \text{ CM max}}$: M_1 must stay in saturation for the maximum input voltage.

$$V_{GD1} \leq V_{th} \rightarrow V_{in \text{ CM max}} - V_{out} \leq V_{th} \rightarrow$$

$$V_{in \text{ CM}} - 1.5 \leq 0.5 \rightarrow V_{in \text{ CM max}} = 2 \text{ V}$$