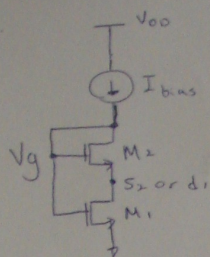


Year 2011

EECE 488 Assignment 1 Solution

Q1.



(a) M_2 is diode connected, so it's operating in the saturation region.

$$\Rightarrow V_{GS2} - V_{T2} > 0$$

Since S_2 is the same node as d_1

$$\Rightarrow V_{GD1} - V_{T2} > 0$$


Now, the bulk of M_1 is connected to ground, so $V_{S1B1} = 0$. The bulk of M_2 is connected to ground as well, so $V_{S2B2} > 0 \Rightarrow V_{T2} > V_{T1}$.

Therefore, $V_{GD1} > V_{T2} > V_{T1} \Rightarrow V_{GD1} - V_{T1} > 0$


$\Rightarrow V_{GS1} - V_{T1} > V_{DS1}$, so M_1 operates in the triode region. Note that $V_{GS1} - V_{DS1} = V_{GD1}$.

(b) No, it doesn't. M_1 is always in triode region as derived in (a).

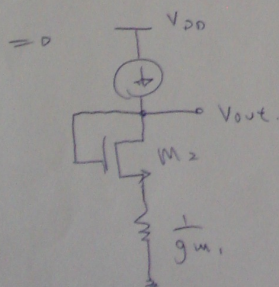(c) $V_{DS1} \approx 0 \Rightarrow M_1$ in deep triode region, and can be modeled as a linear resistor $\frac{1}{g_{m1}}$.



small sig

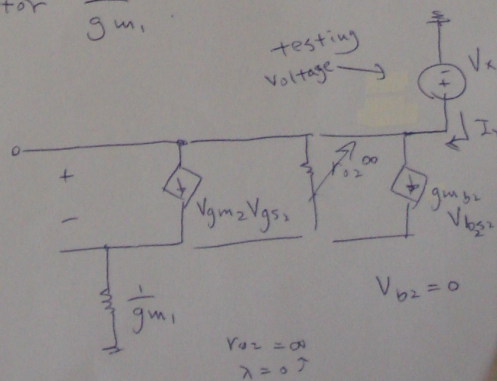

$$I_x = -g_{mb2} V_{s2} + g_{m2} (V_x - V_{s2})$$

$$I_x = V_{s2} g_{m1}$$

$$V_{s2} = \frac{I_x}{g_{m1}}$$

$$I_x = \frac{-g_{mb2}}{g_{m1}} I_x + g_{m2} V_x - \frac{g_{m2}}{g_{m1}} I_x$$


$$I_x + \frac{g_{mb2}}{g_{m1}} I_x + \frac{g_{m2}}{g_{m1}} I_x = g_{m2} V_x$$

$$I_x \left(1 + \frac{g_{mb2}}{g_{m1}} + \frac{g_{m2}}{g_{m1}} \right) = g_{m2} V_x$$

$$\frac{V_x}{I_x} = R_{out} = \frac{1 + \frac{g_{mb2}}{g_{m1}} + \frac{g_{m2}}{g_{m1}}}{g_{m2}}$$

$$= \frac{g_{m1} + g_{mb2} + g_{m2}}{g_{m1} g_{m2}}$$

Q 2.

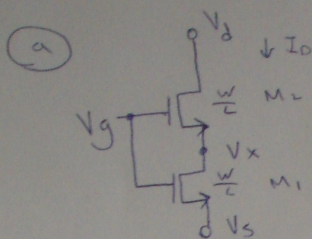

First, M_1 and M_2 both need to be on to have I_D flow through.

Let's first assume M_1 is in saturation,

$$\Rightarrow V_{gs} - V_t < V_{xs}$$

$$\Rightarrow V_g - V_t < V_x \quad \dots (*)$$

Since M_2 is on, $V_{gx} - V_t > 0$

$$\Rightarrow V_g - V_x - V_t > 0 \text{ which contradicts } (*)$$

so M_1 is not in saturation,

it has to be in triode.

So, M_1 has to be in triode, and M_2 can be in either triode or saturation.

Case #1, M_1 & M_2 both in triode.

$$I_{D1} = \mu_n C_{ox} \frac{W}{L} \left[(V_{gs} - V_t) V_{xs} - \frac{1}{2} V_{xs}^2 \right] = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[2(V_{gs} - V_t) V_{xs} - V_{xs}^2 \right]$$

$$I_{D2} = \mu_n C_{ox} \frac{W}{L} \left[(V_{gs} - V_{xs} - V_t)(V_{ds} - V_{xs}) - \frac{1}{2} (V_{ds} - V_{xs})^2 \right]$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} \left[2(V_{gs} - V_{xs} - V_t)(V_{ds} - V_{xs}) - (V_{ds} - V_{xs})^2 \right]$$

$$\text{Note that } V_{gs} - V_{xs} = V_{gx} \quad V_{ds} - V_{xs} = V_{dx}$$

I_{D1} has to be equal to I_{D2}

$$\Rightarrow 2(V_{gs} - V_t) V_{xs} - V_{xs}^2 = 2(V_{gs} - V_{xs} - V_t)(V_{ds} - V_{xs}) - (V_{ds} - V_{xs})^2$$

$$\Rightarrow 2 \left[2(V_{gs} - V_t) V_{xs} - V_{xs}^2 \right] = 2(V_{gs} - V_t) V_{ds} - V_{ds}^2$$

$$\Rightarrow I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \cdot \frac{1}{2} \right) \left[2(V_{gs} - V_t) V_{ds} - V_{ds}^2 \right]$$

$$\downarrow$$

$$\frac{W}{2L}$$

Case #2 M_1 triode M_2 Saturation

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} [2(V_{gs} - V_t)V_{xs} - V_{xs}^2]$$

$$I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t)^2$$

$$I_{D1} = I_{D2}$$


$$\Rightarrow 2(V_{gs} - V_t)V_{xs} - V_{xs}^2 = (V_{gs} - V_{xs} - V_t)^2$$

$$= (V_{gs} - V_t)^2 - 2V_{xs}(V_{gs} - V_t) + V_{xs}^2$$

$$\Rightarrow 2[2(V_{gs} - V_t)V_{xs} - V_{xs}^2] = \frac{1}{2}(V_{gs} - V_t)^2$$

$$\Rightarrow I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{2L} \right) (V_{gs} - V_t)^2$$

(b) Figure can be redrawn:

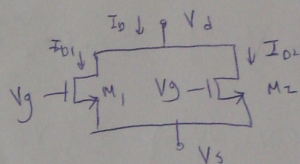

$$I_D = I_{D1} + I_{D2}$$

Since $V_{D1} = V_{D2}$, $V_{S1} = V_{S2}$, $V_{G1} = V_{G2}$, the transistors are always in the same operating region.

Case #1 M_1 , M_2 both in triode:

$$I_{D1} = I_{D2} = \mu_n C_{ox} \frac{W}{L} [(V_{gs} - V_t)V_{ds} - \frac{1}{2} V_{ds}^2]$$

$$I_D = I_{D1} + I_{D2} = \mu_n C_{ox} \left(\frac{2W}{L} \right) [(V_{gs} - V_t)V_{ds} - \frac{1}{2} V_{ds}^2]$$


Case #2 M_1 , M_2 both in Saturation

$$I_{D1} = I_{D2} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t)^2$$

$$I_D = I_{D1} + I_{D2} = \frac{1}{2} \mu_n C_{ox} \left(\frac{2W}{L} \right) (V_{gs} - V_t)^2$$

Q3. Assume all bulks are connected to source


Circuit 1. Small signal model.

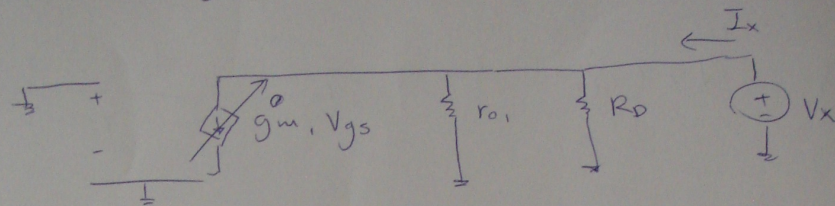

$$I_x = \frac{V_x}{r_{o1}} + \frac{V_x}{R_D}$$

$$\Rightarrow \frac{V_x}{I_x} = R_{out} = r_o \parallel R_D.$$

Circuit 2. small signal model

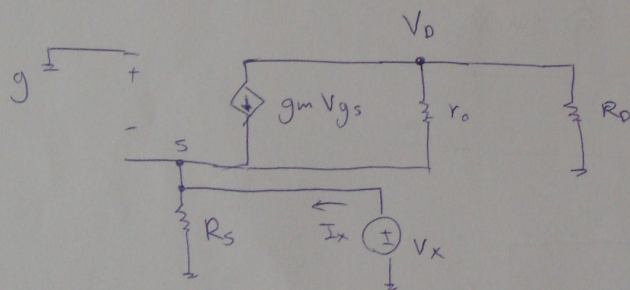

$$g_m V_{gs} = -g_m V_x \quad \text{because } V_g = 0 \quad V_s = V_x.$$

$$I_x = \frac{V_x}{R_s} + g_m V_x + \frac{V_x - V_D}{r_o} \dots (*)$$

$$\frac{V_D}{R_D} = \frac{V_x}{r_o} - \frac{V_D}{r_o} + g_m V_x$$

$$V_D \left(\frac{1}{R_D} + \frac{1}{r_o} \right) = V_x \left(\frac{1}{r_o} + g_m \right)$$


$$V_D = \frac{V_x \left(\frac{1}{r_o} + g_m \right)}{\frac{1}{R_D} + \frac{1}{r_o}} = \frac{V_x \left(\frac{1}{r_o} + g_m \right) R_D r_o}{r_o + R_D} \quad \text{plug in } (**)$$

$$I_x = \frac{V_x}{R_s} + g_m V_x + \frac{V_x}{r_o} - \frac{V_x \left(\frac{1}{r_o} + g_m \right) R_D}{r_o + R_D}$$

$$I_x = V_x \left(\frac{1}{R_s} + g_m + \frac{1}{r_o} - \frac{R_D \left(\frac{1}{r_o} + g_m \right)}{r_o + R_D} \right)$$

$$\frac{V_x}{I_x} = R_{out} = \frac{1}{\frac{1}{R_s} + g_m + \frac{1}{r_o} - \frac{R_D \left(\frac{1}{r_o} + g_m \right)}{r_o + R_D}}$$

circuit 3. small signal.

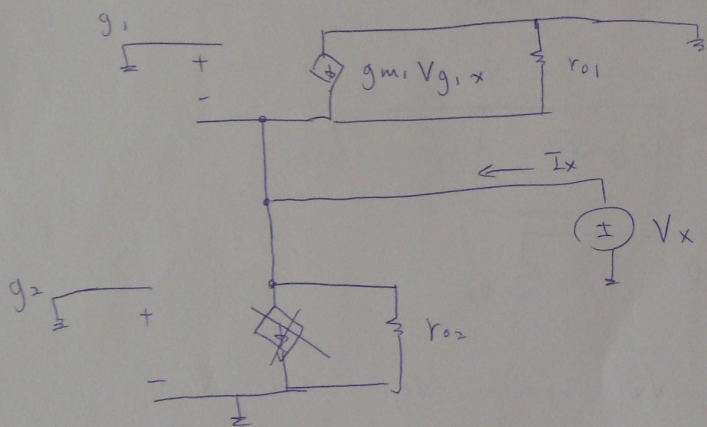

$$-\frac{V_x}{r_{o1}} - g_m V_x + I_x = \frac{V_x}{r_{o2}}$$

$$I_x = \frac{V_x}{r_{o2}} + \frac{V_x}{r_{o1}} + g_m V_x$$

$$I_x = V_x \left(\frac{1}{r_{o2}} + \frac{1}{r_{o1}} + g_m \right)$$

$$\begin{aligned} \frac{V_x}{I_x} = R_{out} &= \frac{1}{\frac{1}{r_{o1}} + \frac{1}{r_{o2}} + g_m} \\ &= r_{o1} \parallel r_{o2} \parallel \frac{1}{g_m} \end{aligned}$$