

Year 2011 ECE 488 Assignment 2 Solution.

Data point	V_{gs}	V_{ds}	V_{bs}	I_D	g_{m0}	V_{th}
1	1	1	0	312 μ	1.12 m	565 m
2	1	2	0	336 μ	1.16 m	556 m
3	2	2	0	1.76 m	1.56 m	558 m
4	2	2	-0.5	1.6 m		675 m
5	2	2	-1	1.45 m		769 m

(b) Note the data points are taken when transistor is in saturation region since $V_{ds} > V_{gs} - V_{th}$.

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

To find V_{th0} , we use data point 2 and 3

since they have 0V V_{bs} and constant V_{ds} .

$$V_{bs} = 0 \Rightarrow V_{th} = V_{th0}$$

$$\Rightarrow \frac{I_{D2}}{I_{D3}} = \frac{(V_{gs2} - V_{th0})^2}{(V_{gs3} - V_{th0})^2}$$

$$V_{th0} = \frac{V_{gs2} \sqrt{I_{D3}} - V_{gs3} \sqrt{I_{D2}}}{\sqrt{I_{D3}} - \sqrt{I_{D2}}}$$

$$= 0.224 \text{ V} \quad \text{or} \quad 1.39 \text{ V}$$

$\uparrow$ quite off
too
 $\uparrow$ too off

To find λ , we use constant V_{gs} , data point 1 and 2

$$\Rightarrow \frac{I_{D1}}{I_{D2}} = \frac{1 + \lambda V_{ds1}}{1 + \lambda V_{ds2}}$$

$$\lambda = \frac{I_{D2} - I_{D1}}{V_{ds2} I_{D1} - V_{ds1} I_{D2}} = 0.0833 V^{-1}$$

To find $\mu_n C_{ox}$, just use data point 1 and know V_{th0} and λ .

$$I_{D1} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})$$

$$\Rightarrow \mu_n C_{ox} = \frac{2 I_{D1} L}{W (V_{gs} - V_{th})^2 (1 + \lambda V_{ds})}$$

$$= 4.783 \times 10^{-5} A/V^2$$

For γ , we know

$$V_{th} = V_{th0} + \gamma (\sqrt{|2\phi_F + V_{sb}|} - \sqrt{|2\phi_F|})$$

We know V_{th} and V_{th0} from data points and previous calculation. We know V_{sb} . But we don't know ϕ_F and γ . So we need 2 equations for 2 unknowns.

Use data point 4 and 5.

$$\#4 \quad 675 \text{ mV} = 224 \text{ mV} + \gamma (\sqrt{|2\phi_F + 0.5|} - \sqrt{|2\phi_F|})$$

$$\#5 \quad 769 \text{ mV} = 224 \text{ mV} + \gamma (\sqrt{|2\phi_F + 1|} - \sqrt{|2\phi_F|})$$

or
No solution

if we use $V_{th0} = 559 \text{ mV}$ directly off data point 3, where $V_{bs} = 0 \text{ V}$. Then,

$$675 \text{ mV} = 559 \text{ mV} + \gamma \left(\sqrt{|2\phi_F + 0.5|} - \sqrt{|2\phi_F|} \right)$$

$$769 \text{ mV} = 559 \text{ mV} + \gamma \left(\sqrt{|2\phi_F + 1|} - \sqrt{|2\phi_F|} \right)$$

use matlab $\Rightarrow$

$$\gamma = 0.4492 \text{ V}^{-1}$$

$$2\phi_F = 0.6883 \text{ V}$$

Yes, the question is tricky.


Another way to do it is to plot I_D vs V_{gs} and estimate V_{th0} at $V_{bs} = 0$. That'll work, too.

(c). $g_m = \frac{2I_D}{V_{gs} - V_t}$ plug in from data points.

	data point	V_{gs}	V_{ds}	V_{bs}	g_{m0}	calculated g_m
error -23%	1	1	1	0	1.12m	0.809m
error -25%	2	1	2	0	1.16m	0.87m
error 28%	3	2	2	0	1.56m	2m

Year 2011 EECE 488 Assignment 2 Solution

Q2.

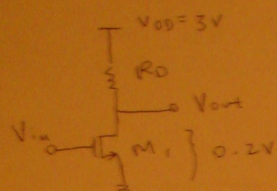

- (a) Assume M_1 has the minimum V_{ds} to keep it in Sat. so it's given $V_{ds} = 0.2V$ and $V_{ds} = V_{gs} - V_t$
 $V_t = 0.5V$. so $V_{gs} = 0.7V = V_g = 0.7V$

- (b) It's given $P = 3\mu W$. so current I_D flowing through the circuit is $1\mu A$. since $P = IV$ $L = 0.5\mu m$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t)^2$$

$$1\mu A = \frac{1}{2} \frac{1\mu A}{V^2} \frac{W}{0.5\mu m} (0.2)^2$$

$$W = 25\mu m$$

- (c) For common source amplifier configured in this question, gain $|A_v| = | -g_m R_D |$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t) = 10\mu S$$


$$15 = 10\mu S R_D \Rightarrow R_D = 1.5k\Omega$$

- (d) $V_{out, DC} = V_{DD} - I_D R_D = 1.5V$

- (e) as long as M_1 has $0.2V$ across then the circuit will operate correctly. so, it's from $0.2V$ to V_{DD} .

Q3.

(a)

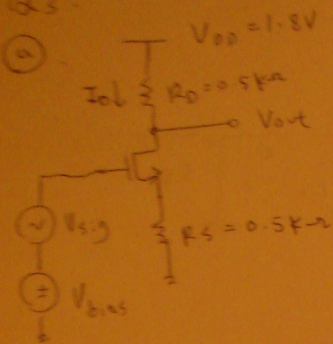

Find the drain current first to figure out dc node voltages.

We know $V_{out} = 1.44V$

$$I_D = \frac{V_{DD} - V_{out}}{R_D} = \frac{1.8V - 1.44V}{0.5k\Omega} = 0.72mA$$

$$V_D = V_{out} = 1.44V$$

$$V_S = R_S \cdot I_D = 0.36V$$

$$V_{DS} = 1.08V$$

For transistor to be in saturation, the drain current satisfy the following:

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2$$

$$0.72mA = \frac{1}{2} \frac{800\mu A}{V^2} 20 (V_{GS} - V_t)^2 \Rightarrow V_{GS} - V_t = 0.3V$$

Assume V_b is connected to ground,

$$V_t = V_{th0} + \gamma (\sqrt{V_{SB} + 2\phi_F} - \sqrt{2\phi_F})$$

$$= 0.4V + 1V^{1/2} (\sqrt{0.36 + 0.64} - \sqrt{0.64})$$

$$= 0.6V$$

$$V_{GS} - V_t = 0.3V$$


$$V_{GS} = 0.9V$$

$$V_g = 0.9V + V_S = 1.26V$$

(b)

Yes, because $V_{DS} = 1.08V > \frac{V_{GS} - V_t}{2} = 0.15V$

② Small signal Model

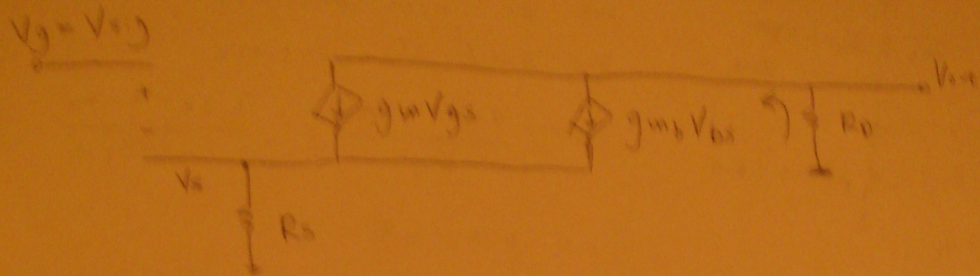

$$\frac{-V_{out}}{R_D} = g_m V_{gs} - g_{mb} V_{bs}$$

$$\frac{-V_{out}}{R_D} = \frac{V_s}{R_s}$$

$$V_s = -\frac{R_s}{R_D} V_{out}$$

$$\frac{-V_{out}}{R_D} = g_m \left(V_{sig} + \frac{R_s}{R_D} V_{out} \right) + g_{mb} \frac{R_s}{R_D} V_{out}$$

$$= g_m V_{sig} + \frac{g_m R_s}{R_D} V_{out} + g_{mb} \frac{R_s}{R_D} V_{out}$$

$$\Rightarrow -g_m V_{sig} = V_{out} \left(\frac{1}{R_D} + \frac{g_m R_s}{R_D} + g_{mb} \frac{R_s}{R_D} \right)$$


$$\frac{V_{out}}{V_{sig}} = \frac{-g_m}{\frac{1}{R_D} + g_m \frac{R_s}{R_D} + g_{mb} \frac{R_s}{R_D}}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_t) = 4.8 \text{ mS}$$


$$g_{mb} = \frac{Y}{2\sqrt{2}\phi_F + V_{sel}} g_m = 3.4 \text{ mS}$$

$$\Rightarrow \frac{V_{out}}{V_{sig}} = -0.52$$

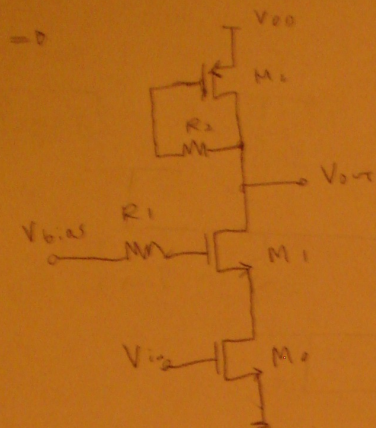Q4. Very low frequency, capacitors are like open circuit




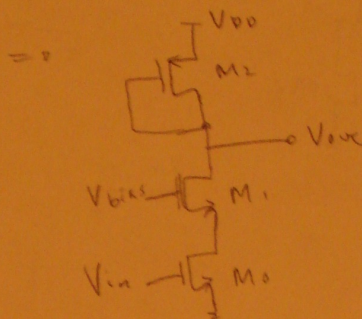No current flow into gate so R_2 and R_1 can be replaced by a wire.




M_2 is diode connected, so impedance looking up to M_2

is $\frac{1}{g_{m2}}$

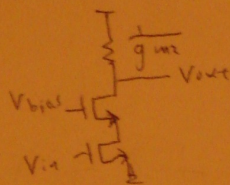

small signal,

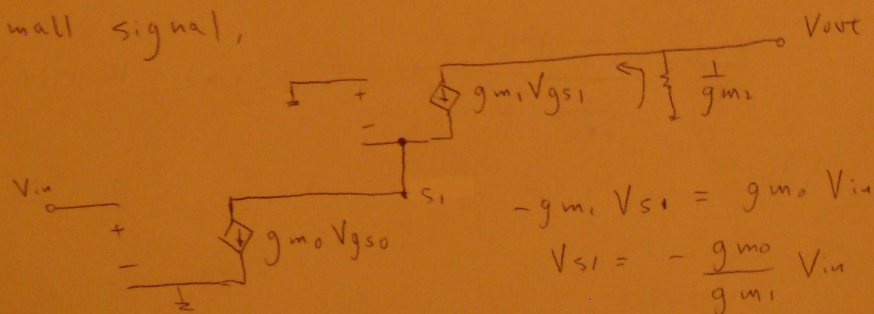

$$-g_{m1} V_{s1} = g_{m0} V_{in}$$

$$V_{s1} = -\frac{g_{m0}}{g_{m1}} V_{in}$$

$$-\frac{V_{out}}{\frac{1}{g_{m2}}} = g_{m0} V_{in}$$

$$-g_{m2} V_{out} = g_{m0} V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{-g_{m0}}{g_{m2}}$$

$$\frac{-V_{out}}{R_2} = \frac{V_{out}}{R_1} + g_{m1}(V_{out} - V_{s1})$$

$$g_m (V_{out} - V_{s1}) = g_m V_{in}$$