
 


EECE488 Analog CMOS Integrated Circuit Design
Assignment 4
Due: Thursday March 28, 2013 at 9:30am

 1. Assuming that the following circuit is symmetrical and $\gamma = \lambda = 0$:
- i) Find the expression for the small-signal differential voltage gain ($\frac{V_{out}}{V_{in1} - V_{in2}}$) of the circuit at very low frequencies.
 - ii) What is the gain of the circuit at very high frequencies?
 - iii) Repeat parts (i) and (ii) assuming $\lambda \neq 0$.
- Note:** In this question neglect all other capacitances that are not shown in the circuit.



2. In the following cascode circuit (typically referred to as self-biased cascode circuit) the resistor R is used to maintain a proper voltage to allow both M_1 and M_2 remain in saturation.



Assume both M_1 and M_2 have the same size W/L . Ignoring the channel length modulation and the body effect, show that for M_1 and M_2 to remain in the saturation region we should have:

$$\frac{2}{\mu_p C_{ox} \left(\frac{W}{L}\right) R^2} \leq I_{ref} \leq \frac{|V_{tp}|}{R}$$

3. Design a two-stage amplifier based on the topology shown below with the following design specifications:

- $V_{DD}=1.8V$
- Total power consumption of 1.8 mW
- Differential output swing of 2.8V
- Total gain of 1000
- $L=0.4\mu m$ for all the device


Use the following assumptions for your design

- The circuit is symmetric
- The bias currents of the first stage and second stage are equal (i.e., $I_0=I_5+I_6$).
- The magnitude of overdrive voltages of M_4 , M_6 , and M_8 are equal

The technology parameters are:

$\lambda_{(NMOS)}=\lambda_{(PMOS)}=0.1V^{-1}$, $\gamma = 0$, $V_{DD}=1.8V$, $V_{TH(NMOS)}=|V_{TH(PMOS)}|=0.4V$, $\mu_n C_{ox}=0.5 \text{ mA/V}^2$, $\mu_p C_{ox}=0.25 \text{ mA/V}^2$.

 Note: Use the parameter λ only for calculating the r_o of the transistors. **Do not** use λ in any other calculation including your bias currents.



Find V_{bias1} , V_{bias2} , and all the transistor widths (i.e., $W_0, W_1, W_2, W_3, W_4, W_5, W_6, W_7$, and W_8).

4. The unity-gain closed-loop buffer has a phase margin of 50° . What is the percentage of peaking in magnitude frequency response of the closed-loop system in the vicinity of the gain crossover frequency (i.e., the frequency at which the loop-gain is 1)?

Good luck