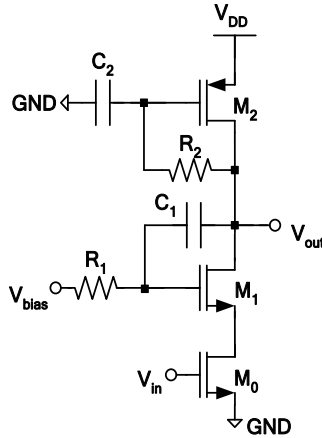


EECE488 Analog CMOS Integrated Circuit Design
Assignment 2
Due: Tuesday February 28th, 2013 at 9:30am

1. Calculate the gain of the following circuit (i.e., provide an expression of the gain in terms of circuit parameters):

- a) at very low frequencies
- b) at very high frequencies.

In this problem, neglect all other capacitances that are not shown in the circuit and assume $\gamma = 0$ for all three transistors, while $\lambda_0 = \lambda_1 = 0$ and $\lambda_2 \neq 0$.




2. Design a common-source amplifier with a diode-connected load based on the schematic shown below with the following design specifications:

- Transistor M1 is in saturation
- The minimum possible output voltage to keep M1 in saturation is 0.2V
- Total power consumption of the amplifier is 3mW
- Both transistors have $L=0.5\mu\text{m}$ and for transistor M2 we have $W_2=1\mu\text{m}$

The technology parameters are:

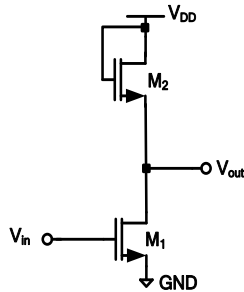
$$\lambda(\text{NMOS}) = 0, \gamma = 0, V_{DD}=3\text{V}, V_{TH}(\text{NMOS}) = 0.5\text{V}, \mu_n C_{ox}=1 \text{ mA/V}^2$$



Find the following values:

- a) DC level of the input, b) DC level of the output, c) width (W_1) of transistor M1, d) small-signal gain, and e) Maximum output signal swing for a symmetric output signal.

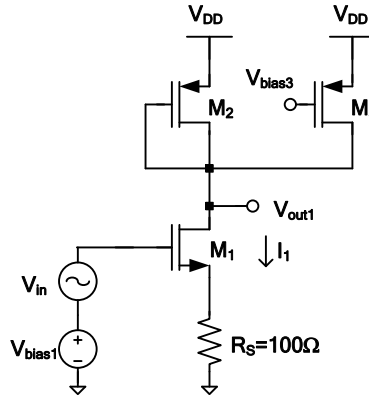3. In the following circuit assume that all transistors are operating in the saturation region. Also, assume that $\lambda = \gamma = 0$, $V_{DD}=1.8V$, $V_{bias3}=1.15V$, $V_{TH(NMOS)} = 0.4V$ and $V_{TH(PMOS)} = -0.4V$, $\mu_n C_{ox}=800 \mu A/V^2$, $(W/L)_1 = 40$, $\mu_p C_{ox}=400 \mu A/V^2$, $(W/L)_2 = 40$, $(W/L)_3 = 40$, and $R_S=100\Omega$.



- Find V_{bias1} such that the bias current of M_1 is $I_1=1mA$.
- Calculate the small-signal voltage gain $A_{V1}=V_{out1}/V_{in}$.
- Calculate the small-signal output impedance seen at the output node V_{out1} .

Good luck!