 


EECE488 Analog CMOS Integrated Circuit Design
Assignment 2
Due: Tuesday October 15th, 2013 at 8:00 am

1. Consider the following circuit:



The technology parameters are:

$\lambda_{(NMOS)} = \lambda_{(PMOS)} = 0 \text{ V}^{-1}$, $\gamma = 0$, $V_{DD} = 3.0 \text{ V}$, $V_{TH(NMOS)} = |V_{TH(PMOS)}| = 0.5 \text{ V}$, $\mu_n C_{ox} = 0.1 \text{ mA/V}^2$, $\mu_p C_{ox} = 0.05 \text{ mA/V}^2$, and $C_{ox} = 5 \text{ fF}/\mu\text{m}^2$.

Assuming the transistor sizes are: $L_1 = 0.5 \mu\text{m}$, $L_2 = 4 \mu\text{m}$, $W_1 = 5 \mu\text{m}$, and $W_2 = 20 \mu\text{m}$, and furthermore, $V_{bias} = 0.5 \text{ V}$:

- a) What is the region of operation of each transistor?
- b) If the input signal, V_{in} , is a step function with a small magnitude of 10 mV (i.e., V_{in} abruptly changes from 0 V to 10 mV at time $t = 0$), what is $V_{out}(t)$ for $t \geq 0$?


2. In the following circuit the DC current of M1 and M2 is 1 mA each and the current of M3 and M4 is 0.5 mA. Assume all transistors are in saturation and the aspect ratio of transistors is as follows:

$(W/L)_1 = 125$, $(W/L)_2 = 250$, $(W/L)_3 = 40$, and $(W/L)_4 = 80$.

- a) Find g_m of all transistors and r_o of PMOS transistors.
- b) Find the voltage gains V_{out1}/V_{in} and V_{out2}/V_{in}

The technology parameters are:

$\lambda_{(NMOS)} = 0 \text{ V}^{-1}$, $\lambda_{(PMOS)} = 0.05 \text{ V}^{-1}$, $V_{DD} = 3.0 \text{ V}$, $V_{TH(NMOS)} = |V_{TH(PMOS)}| = 0.5 \text{ V}$, $\mu_n C_{ox} = 0.1 \text{ mA/V}^2$, $\mu_p C_{ox} = 0.05 \text{ mA/V}^2$, and $\gamma = 0$.

 

3. In this question, we will estimate the transistor parameters. We will use HSPICE to find these parameters for an NMOS and a PMOS transistor in the 0.35- μm CMOS process used in our class. In all parts of this question, assume that the transistor has a width of $W=3.5 \mu\text{m}$ and length of $L=0.35 \mu\text{m}$ (unless otherwise specified) and $V_{DD} = 3.0 \text{ V}$ and use two V_{GS} (or V_{SG} in the case of PMOS) of 1 and 2 V. Please make sure to include your HSPICE code.

- a) Estimate λ for the NMOS and PMOS transistor ($L=0.35 \mu\text{m}$)
Hint: Draw I_D versus V_{DS} for the given values of V_{GS} and from the curve in saturation region estimate λ .
- b) Estimate $\mu_n C_{ox}$ and $\mu_p C_{ox}$. Are they equal? What is your intuitive conclusion on the speed of NMOS device versus PMOS?
- c) Increase the length to $L' = 3 \times 0.35 \mu\text{m}$ for both NMOS and PMOS and recalculate λ . What will happen to r_o ?
- d) For $L=0.35 \mu\text{m}$, use DC – sweep to change V_{BS} (body-source voltage) from 0 to V_{DD} and plot V_{th} versus V_{BS} for V_{GS} (or V_{SG} in the case of PMOS) of 1 and 2 V.
- e) Based on your estimated parameters in parts a and b and using the quadratic equation for the current of MOS transistor, calculate the current of the NMOS ($W=3.5 \mu\text{m}$ and $L=0.35 \mu\text{m}$) for $V_{GS} = 1.5 \text{ V}$ and $V_{DS} = V_{DD} = 3.0 \text{ V}$. Compare your calculated result with that of HSPICE simulation for the same NMOS transistor.