## EECE488 Analog CMOS Integrated Circuit Design Assignment 3 Due: Thursday March 8<sup>th</sup>, 2012 at 9:30am

1. Calculate the gain of the following circuit at very low and very high frequencies. Neglect all other capacitances that are not shown in the circuit and assume  $\lambda = \gamma = 0$ .



2. In the following cascode circuit (typically referred to as self-biased cascode circuit) the resistor R is used to maintain a proper voltage to allow both  $M_1$  and  $M_2$  remain in saturation.



Assume both  $M_1$  and  $M_2$  have the same size W/L. Ignoring the channel length modulation and the body effect, show that for  $M_1$  and  $M_2$  to remain in the saturation region we should have:

$$\frac{2}{\mu_{p}C_{ox}\left(\frac{W}{L}\right)R^{2}} \le I_{ref} \le \frac{\left|V_{tp}\right|}{R}$$

- 3. Assuming the following two circuits are symmetric and  $\gamma = 0$ : and  $\lambda \neq 0$ :
- a) Find the expressions for the small-signal differential voltage gain of each circuit.
- b) Assuming that the corresponding transistors of each of the circuits are identical and the two circuits have the same small-signal differential voltage gain, find the relationship between  $R_1$  and  $R_2$ .



4. Assuming all the transistors in the following symmetric circuits are in saturation,  $\lambda \neq 0$  (for the circuit on the right assume  $\lambda = 0$ ) and  $\gamma = 0$ , calculate the small-signal differential voltage gain of each circuit.

