
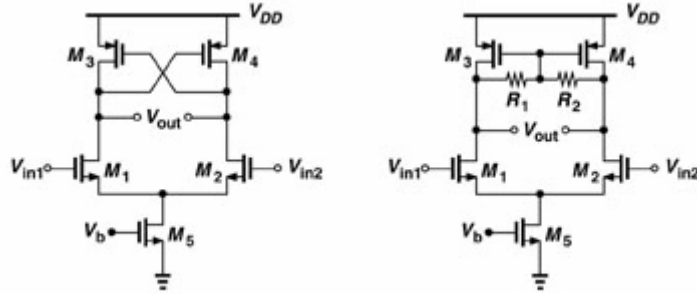



EECE488 Analog CMOS Integrated Circuit Design
Assignment 4
Due: Thursday March 18th, 2010 at 9:30am

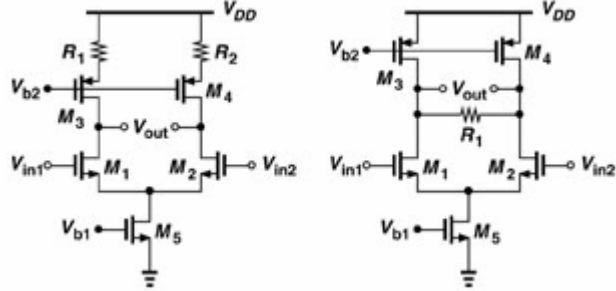1. Assuming all the transistors in the following symmetric circuits are in saturation, $\lambda \neq 0$ and $\gamma = 0$, calculate the small-signal differential voltage gain of each circuit.




2. In the following symmetric circuit, assume all transistors are operating in saturation region, $\lambda = 0$, and $\gamma = 0$.

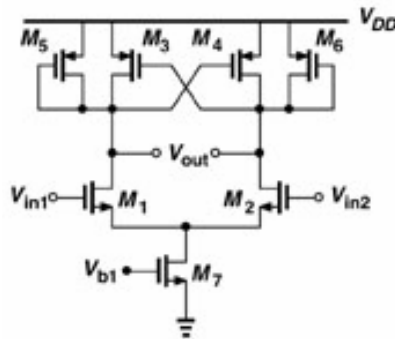- a) Find an expression for the small-signal differential voltage gain of the following circuit.
 b) What is the small-signal differential voltage gain if $(W/L)_3/(W/L)_5=0.5$?



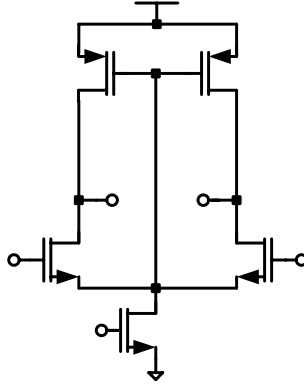3. In the following circuit all transistors have a W/L of $7\mu\text{m}/0.35\mu\text{m}$ and M_3 and M_4 are to operate in deep triode region with an on-resistance of $2\text{k}\Omega$. Assuming $I_5=40\mu\text{A}$ and $\lambda=\gamma=0$, $V_{\text{DD}}=3\text{V}$, $V_{\text{TH(NMOS)}}=0.5\text{V}$, $V_{\text{TH(PMOS)}}=-0.6\text{V}$, $\mu_n C_{\text{ox}}=200\mu\text{A}/\text{V}^2$, $\mu_p C_{\text{ox}}=100\mu\text{A}/\text{V}^2$.



- Calculate the dc level of the input (input common-mode level) that yields such an on-resistance for M_3 and M_4 .
- Calculate the required V_{bias} of the gate of M_5 .
- Calculate the small-signal differential gain, i.e., $(V_{\text{out1}}-V_{\text{out2}})/(V_{\text{in1}}-V_{\text{in2}})$, of the circuit when the input common-mode level is equal to value calculated in part a.

Good luck.