

EECE488: Analog CMOS Integrated Circuit Design

Set 5

Current Mirrors

Shahriar Mirabbasi

Department of Electrical and Computer Engineering

University of British Columbia


shahriar@ece.ubc.ca

SM

EECE488 Set 5 - Current Mirrors

1

Applications of Current Sources

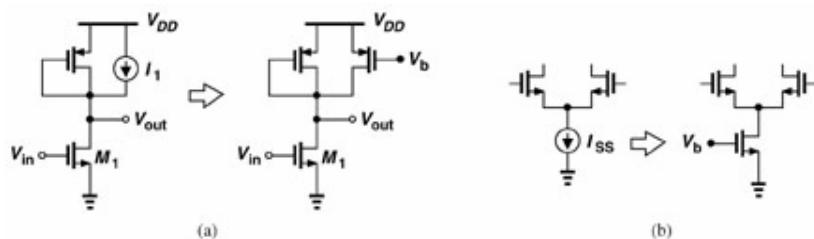


SM

EECE488 Set 5 - Current Mirrors

2

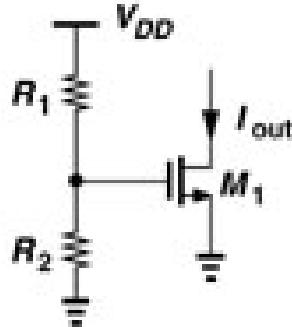Simple Resistive Biasing for Current Source



$$I_{OUT} \approx \frac{\mu_n C_{ox}}{2} \frac{W}{L} \left(\frac{R_2}{R_2 + R_1} V_{DD} - V_{TH} \right)^2$$

SM

EECE488 Set 5 - Current Mirrors

3

Problems

- Output current depends on:
 - Supply
 - Process
 - Temperature
- What if the bias voltage is independent of supply voltage?
- Is there a way of generating reliable currents?


SM

EECE488 Set 5 - Current Mirrors

4

Basic Idea

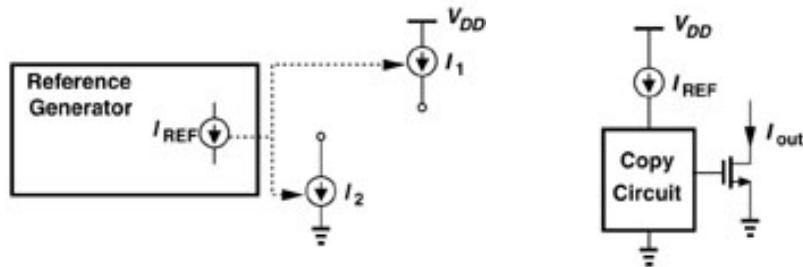Typically we assume that one precisely defined current source is available and other current sources copy their current from this precise source.




I_{out} is a function of gate-source voltage

SM

EECE488 Set 5 - Current Mirrors

5

Basic Idea

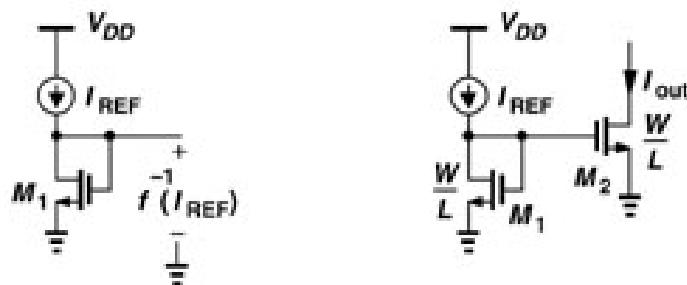

This structure is called current mirror

SM

EECE488 Set 5 - Current Mirrors

6

Question

- What happens if the two transistors in the basic current mirror have different sizes?


SM

EECE488 Set 5 - Current Mirrors

7

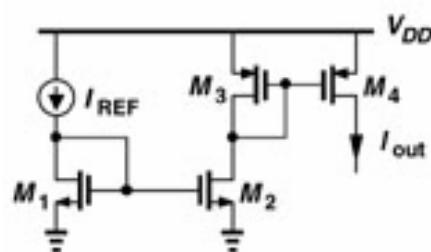Example

Assuming all the transistors are in saturation region, find I_{out} :




SM

EECE488 Set 5 - Current Mirrors

8

Current Mirrors: Amplifier Bias Example

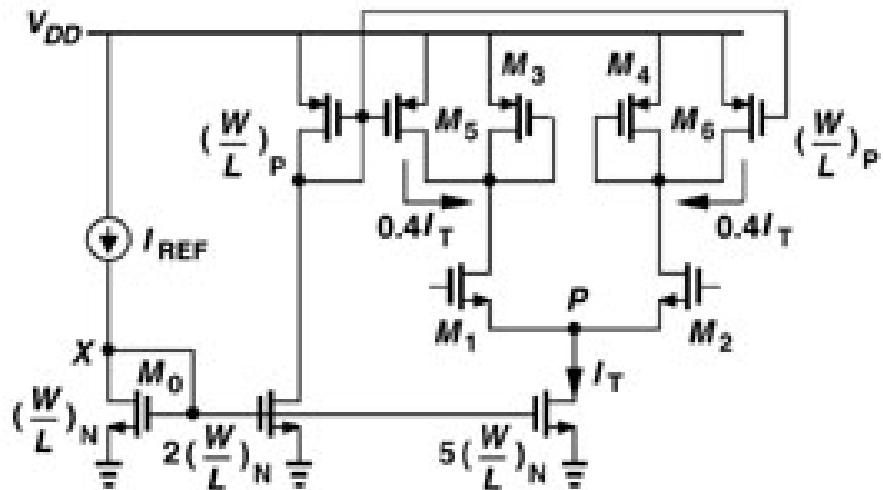

SM

EECE488 Set 5 - Current Mirrors

9

Board Notes


SM

EECE488 Set 5 - Current Mirrors

10

Current Mirrors: Signal Amplification Example

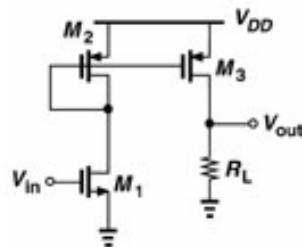- Find the small signal voltage gain of the following circuit.



SM

EECE488 Set 5 - Current Mirrors

11


Effect of Channel Length Modulation

SM

EECE488 Set 5 - Current Mirrors

12

Cascode Current Mirror

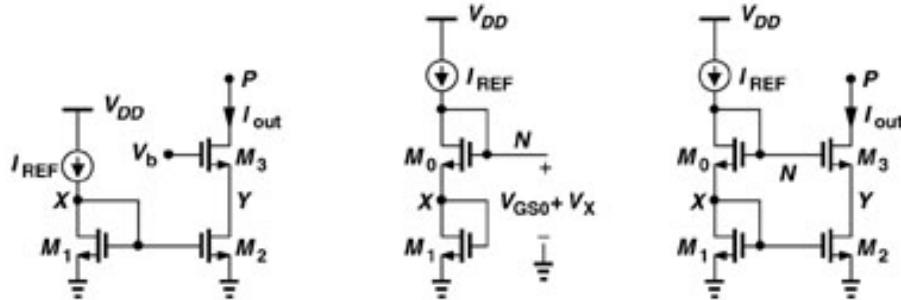

SM

EECE488 Set 5 - Current Mirrors

13


Board Notes

SM


EECE488 Set 5 - Current Mirrors

14


Cascode Current Mirror

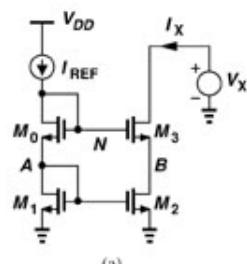

(a)

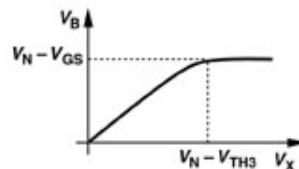

(b)

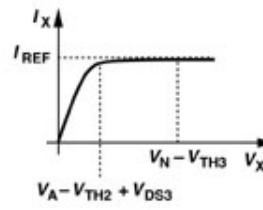


(c)

SM


EECE488 Set 5 - Current Mirrors

15

Cascode Current Mirror

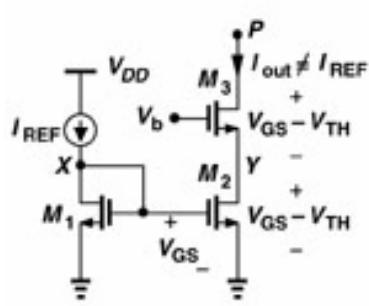

(a)

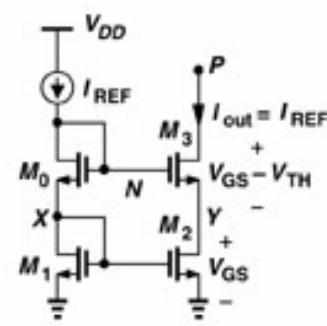


(b)

SM


EECE488 Set 5 - Current Mirrors

16

Cascode Current Mirror

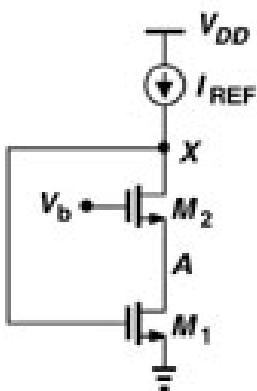


(a)

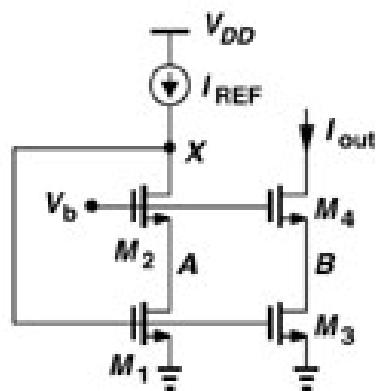

(b)

Board Notes

Cascode Current Mirror Biasing

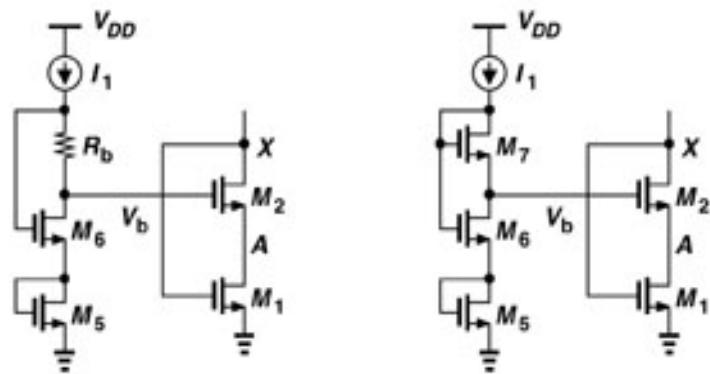


SM

EECE488 Set 5 - Current Mirrors

19

Cascode Current Mirror Biasing


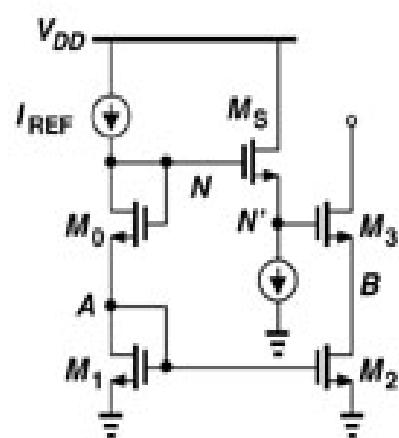


SM

EECE488 Set 5 - Current Mirrors

20

Current Mirror Biasing

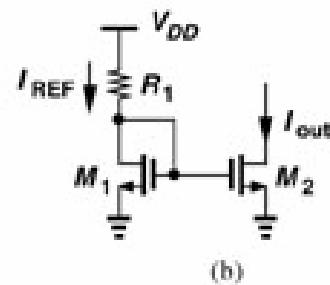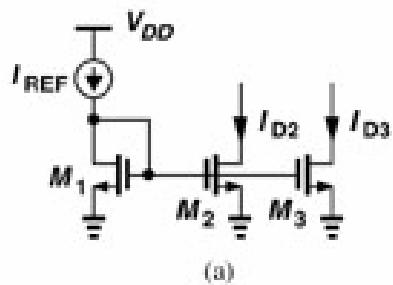


SM

EECE488 Set 5 - Current Mirrors

21

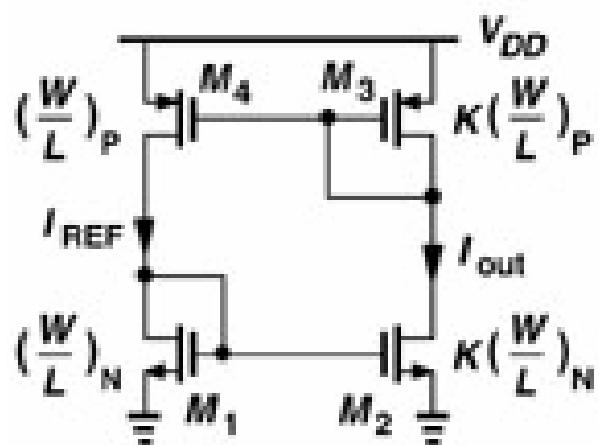Basic Circuit to Generate Supply Independent Current




SM

EECE488 Set 5 - Current Mirrors

22


Supply Independent Current

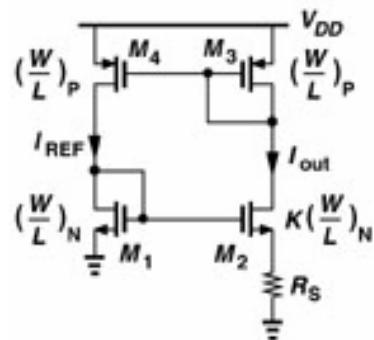

(a)

Board Notes

Supply Independent Current

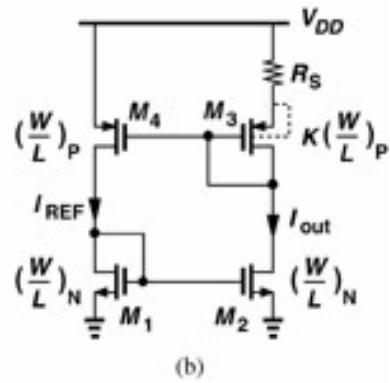


(b)

SM

EECE488 Set 5 - Current Mirrors

25

Start-up Problem

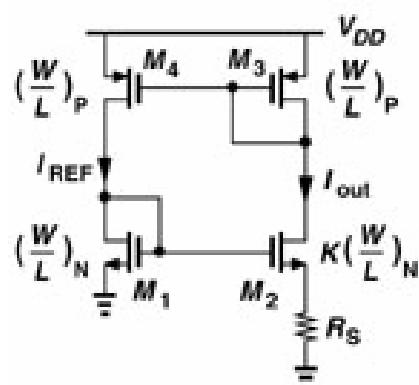


(a)

SM

EECE488 Set 5 - Current Mirrors

26

Start-up Problem

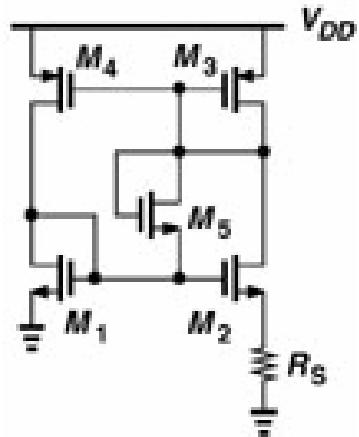

$$V_{TH1} + V_{TH5} + |V_{TH3}| < V_{DD} \quad \text{and} \quad V_{GS1} + V_{TH5} + |V_{GS3}| > V_{DD}$$

SM

EECE488 Set 5 - Current Mirrors

27


Board Notes

SM

EECE488 Set 5 - Current Mirrors

28

Active Current Mirrors

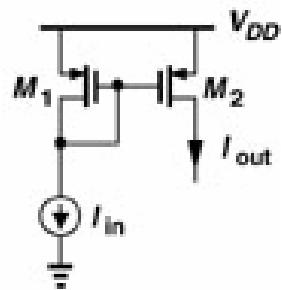


SM

EECE488 Set 5 - Current Mirrors

29

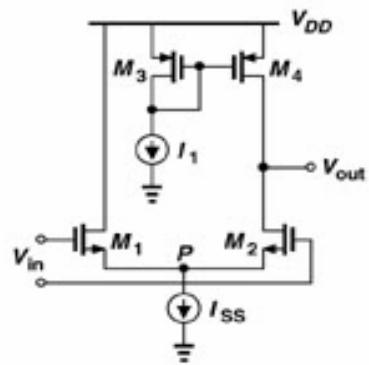Active Current Mirrors in Differential to Single-Ended Amplifiers





SM

EECE488 Set 5 - Current Mirrors

30

Differential to Single-Ended Amplifiers

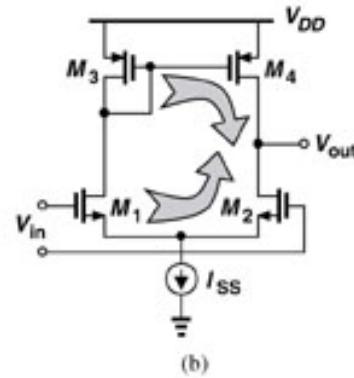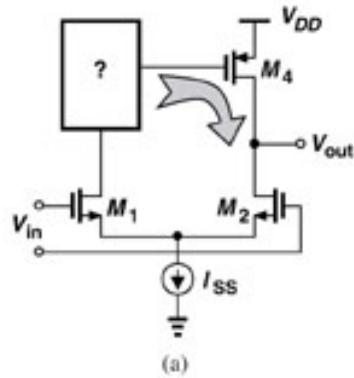


SM

EECE488 Set 5 - Current Mirrors

31

Calculation of G_m

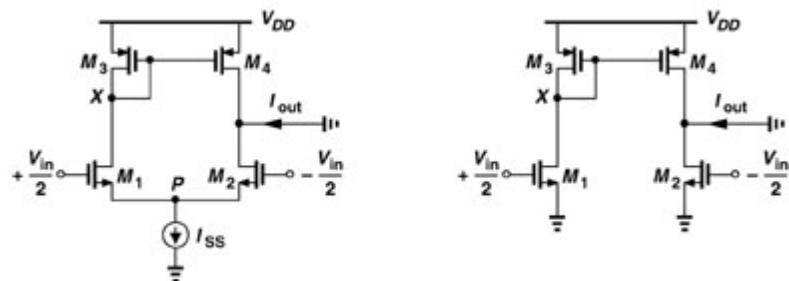

$$I_{D1} = I_{D3} = I_{D4} = g_{m1,2} V_{in} / 2 \quad I_{D2} = -g_{m1,2} V_{in} / 2$$


$$I_{out} = I_{D2} - I_{D4} = -g_{m1,2} V_{in}, \Rightarrow G_m = g_{m1,2}$$

SM

EECE488 Set 5 - Current Mirrors

32

Small-Signal Gain

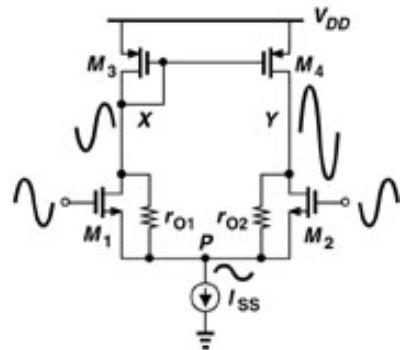


$$A_v \approx g_{m1,2}(r_{o2} \parallel r_{o4})$$

SM

EECE488 Set 5 - Current Mirrors

33

Common Mode Characteristics

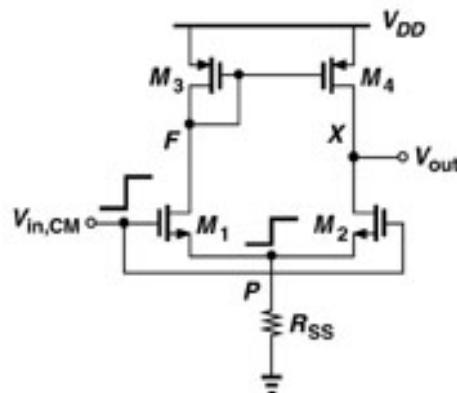


$$A_{CM} = \frac{\Delta V_{out}}{\Delta V_{in,CM}}$$

SM

EECE488 Set 5 - Current Mirrors

34

Common Mode

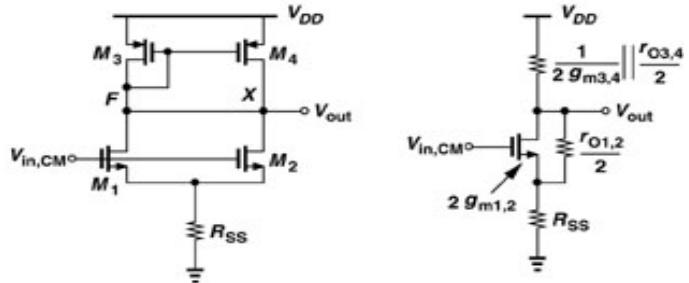

$$A_{CM} \approx \frac{-\frac{1}{2g_{m3,4}} \parallel \frac{r_{o3,4}}{2}}{\frac{1}{2g_{m1,2}} + R_{SS}} = \frac{-1}{1 + 2g_{m1,2}R_{SS}} \frac{g_{m1,2}}{g_{m3,4}}$$

SM

EECE488 Set 5 - Current Mirrors

35

Common Mode

$$CMRR = \left| \frac{A_{DM}}{A_{CM}} \right|$$

$$= g_{m1,2} (r_{o1,2} \parallel r_{o3,4}) \frac{g_{m3,4} (1 + 2g_{m1,2}R_{SS})}{g_{m1,2}}$$

$$= g_{m3,4} (r_{o1,2} \parallel r_{o3,4}) (1 + 2g_{m1,2}R_{SS})$$

SM

EECE488 Set 5 - Current Mirrors

36