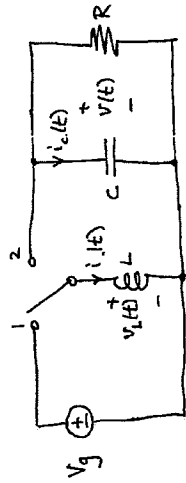


ECE 493 2008W1 ASSIGNMENT #1 SOLUTION


Solution to Problem 2.1

Analysis and Design of a buck-boost converter



a)

Inductor voltage waveform

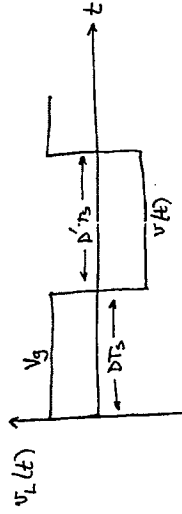

volt-second balance


$$\langle v_L(t) \rangle = D(V_g) + D'(-V_g) \approx DV_g + D'V = 0$$

small ripple approximation

solve for V:

$$V = -\frac{D}{D'} V_g$$

Capacitor current waveform

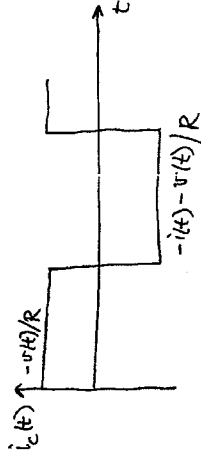

Capacitor charge balance:

$$\langle i_C(t) \rangle = D\left(-\frac{v(t)}{R}\right) + D'\left(-i(t) - \frac{v(t)}{R}\right)$$


$$\approx D\left(-\frac{V}{R}\right) + D'\left(-I - \frac{V}{R}\right) = 0$$

solve for I:

$$D'I = -\frac{V}{R} (D + D')$$

$$\Rightarrow I = -\frac{V}{D'R} = \frac{D}{(D')^2} \frac{V_g}{R}$$

b)

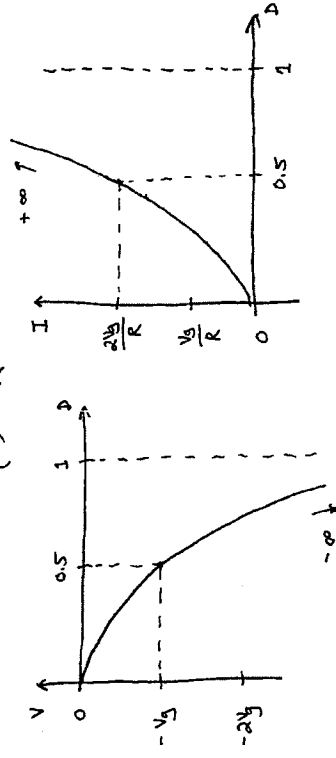

c) DC design

Given $V_g = 30V$
 $V = -20V$
 $R = 4\Omega$
 $f_s = 40kHz \Rightarrow T_s = \frac{1}{40kHz} = 25\mu sec$

i) Find D and I

we know that $\frac{V}{V_g} = -\frac{D}{1-D}$


so $V(1-D) = -DV_g$

$\Rightarrow V = D(V - V_g)$

$\Rightarrow D = \frac{V}{V - V_g} = \frac{-20}{-20-30} = 0.4$

$I = \frac{D}{(1-D)^2} \frac{V_g}{R} = \frac{0.4}{(0.6)^2} \frac{30V}{4\Omega} = 8.33A$

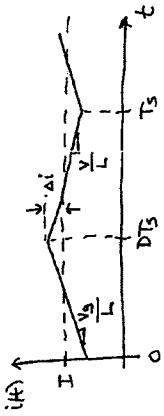(ii) Choose L such that Δi is 10% of $I = 0.833A$




$$2\Delta i = \frac{V_g}{L} DT_s \Rightarrow L = \frac{V_g DT_s}{2\Delta i}$$

$$= \frac{(30V)(0.4)(25\mu sec)}{2(0.833A)}$$

$$= 180\mu H$$

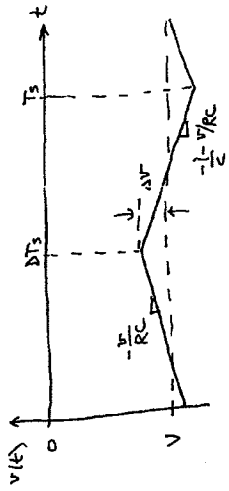(iii) Choose C such that $\Delta V = 0.1V$




$2\Delta V = \frac{V}{RC} DT_s \approx \frac{V}{RC} DT_s$

Solve for C:

$C = \frac{V DT_s}{2\Delta V R} = \frac{(-20V)(0.4)(25\mu s)}{2(0.1V)(4\Omega)} = 250\mu F$

Note: in practice, capacitor equivalent series resistance (ESR) would contribute to ΔV , and would require use of a larger capacitance to achieve $\Delta V = 0.1V$.

d)

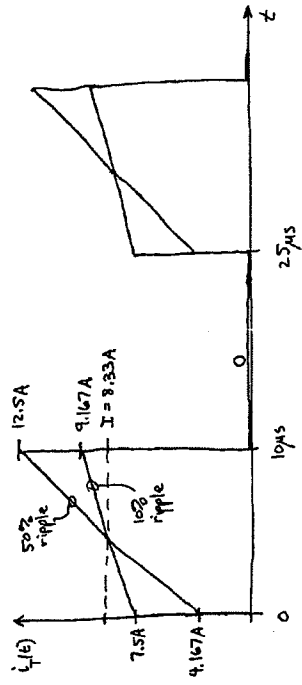


$i_T = i_L$ during $0 < t < DT_s$, and $i_T = 0$ during $DT_s < t < T_s$

Increasing Δi to 50% of I increases the peak transistor current from 9.167A to 12.5A.

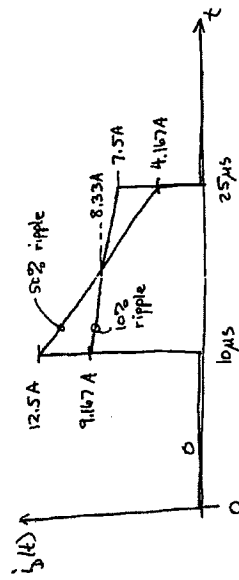e) Diode current $i_D(t)$

$$i_D(t) = \begin{cases} 0 & \text{during } 0 \leq t < DT_s \\ i_L(t) & \text{during } DT_s \leq t < T_s \end{cases}$$



Increasing Δi also increases the peak diode current.


End of Problem 2.1

Tutorial


Solution to Problem 2.2

A dc voltage regulator based on the SEPIC Converter analysis

Fig. 2.29

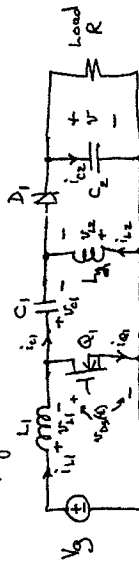

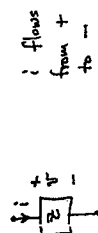Label voltage and current for each inductor and capacitor. Defined directions of current and voltage must be consistent:



A current

First subinterval: $0 \leq t \leq D \cdot T_s$

transistor is on, diode is off circuit becomes



A current

Note: be careful to be consistent in your defined polarities of voltage and current. The same polarities must be followed during all subintervals!


Inductor voltages and capacitor currents for this subinterval:

$$v_{L1}(t) = V_g, \quad v_{L2}(t) = v_{C1}(t), \quad i_{C1}(t) = -i_{L2}(t), \\ i_{C2}(t) = -v(t)/R$$

Second subinterval: $D \cdot T_s \leq t \leq T_s$

transistor is off, diode is on

Circuit becomes

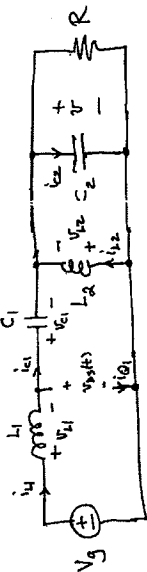

Inductor voltages and capacitor currents for this subinterval:

$$v_{L1}(t) = V_g - v_{C1}(t) - v(t)$$

$$v_{L2}(t) = -v(t)$$

$$i_{C1}(t) = i_{L1}(t)$$

$$i_{C2}(t) = i_{L1}(t) + i_{L2}(t) - v(t)/R$$

Again, note that v_{L1} , v_{L2} , i_{C1} , and i_{C2} are expressed in terms of quantities that have small ripple (i.e., $i_{L1}(t)$, $i_{L2}(t)$, $v_{C1}(t)$, $v(t)$, and V_g) and not as functions of quantities whose ripples are not small (such as $v_{L1}(t)$, $v_{L2}(t)$, $i_{C1}(t)$, $i_{C2}(t)$, and $i(t)$). Use of the small ripple approximation now leads to

$$v_{L1}(t) \approx V_g - V_{C1} - V$$

$$v_{L2}(t) \approx -V$$

$$i_{C1}(t) \approx I_{L1}$$

$$i_{C2}(t) \approx I_{L1} + I_{L2} - V/R$$

Note that each inductor voltage and capacitor current has been expressed in terms of quantities that have small ripple when L_1, L_2, C_1 and C_2 are sufficiently large. We can therefore make the small ripple approximation and write

$$\begin{aligned} v_{L1}(t) &\approx I_{L1} \\ v_{L2}(t) &\approx I_{L2} \\ v_{C1}(t) &\approx V \\ v_{C2}(t) &\approx V \end{aligned}$$


So we obtain

$$\begin{aligned} v_{L1}(t) &= V_g \\ v_{L2}(t) &\approx V_{C1} \\ i_{C1}(t) &\approx -I_{L2} \\ i_{C2}(t) &\approx -V/R \end{aligned}$$

We could have written the equations for subinterval 2 in other ways. For example, we could have expressed $i_{C1}(t)$ as





$$i_{C1}(t) = i_{L1}(t) - i_{Q1}(t)$$

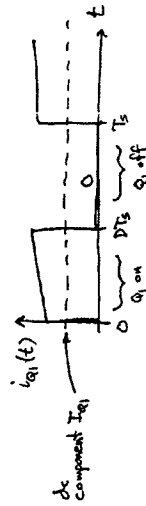While this equation is true, it is not as useful because the switching ripple in the transistor current $i_{Q1}(t)$ is not small:



So we cannot write $i_{Q1}(t) \approx I_{Q1}$ for subinterval 1

Waveforms:

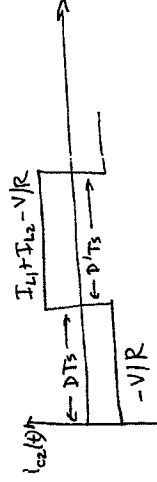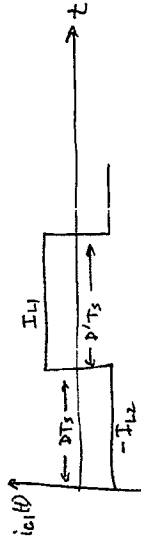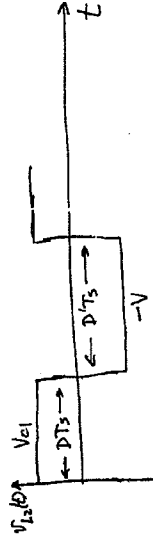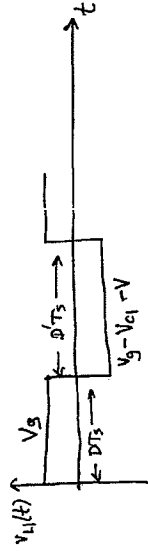

Volt-second balance

$$\Delta v_{L1} = D(V_g) + D'(V_g - V_{C1} - V) = 0$$

$$\Delta v_{L2} = D(V_{C1}) + D'(-V) = 0$$

with $D' = 1 - D$

charge balance

$$\Delta i_{L1} = D(I_{L1}) + D'(-I_{L2}) = 0$$

$$\Delta i_{L2} = D(I_{L1} + I_{L2} - V/R) + D'(-V/R) = 0$$

Four equations and four unknowns ($V, V_{C1}, I_{L1}, I_{L2}$).

Solution:

$$V_{C1} = V_g$$

$$V = \frac{D}{1-D} V_g$$

$$I_{L1} = \frac{D}{1-D} \frac{V}{R} = \left(\frac{D}{1-D}\right)^2 \frac{V_g}{R}$$

$$I_{L2} = \frac{V}{R} = \frac{D}{(1-D)} \frac{V_g}{R}$$

Part (b): Voltage regulator behavior

Controller automatically adjusts D , to maintain $V = 28$ volts.

Input voltage varies over the range $18 \leq V_g \leq 36$.

Load current $= 2A = \frac{V}{R}$, so $R = \frac{(28 \text{ volts})}{(2 \text{ amps})} = 14 \Omega$.

over what ranges do D and I_{L1} vary?

We know that $V = \frac{D}{1-D} V_g$. Solve for D :

$$V - DV = DV_g$$

$$V = D(V + V_g)$$

$$\Rightarrow D = \frac{V}{V + V_g}$$

and from above,

$$I_{L1} = \frac{D}{1-D} \frac{V}{R} = \frac{V^2}{V_g R}$$

$$\frac{V}{28} \quad \frac{V_g}{18} \quad \frac{D}{\frac{28}{18}} = 0.609$$


$$\frac{28}{36} \quad \frac{36}{64} \quad \frac{28}{64} = 0.438$$

$$\frac{I_{L1}}{\frac{28^2}{(18)(14)}} = 3.11 A$$

$$\frac{28^2}{(36)(14)} = 1.56 A$$

End of problem 2.2

Problem 2.9

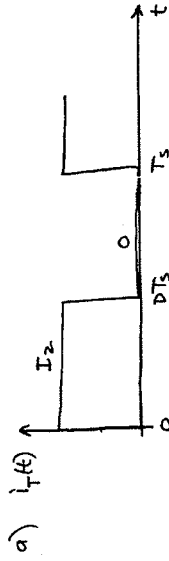

b)

$$V_{C1} = V_g$$

$$V = DV_{C1} = DV_g$$

$$I_2 = \frac{V}{R} = \frac{DV_g}{R}$$

$$I_1 = DI_2 = \frac{D^2 V_g}{R}$$

c)


Ripple on L_2

$$\Delta i_2 = \frac{V_g DT_s}{2L_2}$$

$$\Delta V = \frac{\Delta i_2 T_s}{8C_2} \quad (\text{see Eq. (2.60)})$$

$$= \frac{V_g D T_s^2}{16L_2 C_2}$$

Ripple on C_2

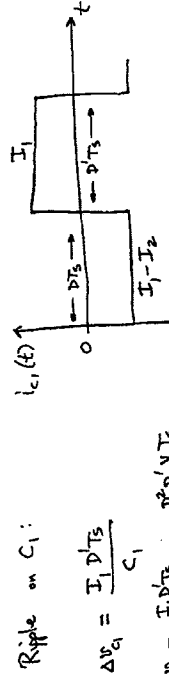


$$2\Delta v_{C1} = \frac{I_1 DT_s}{C_1}$$

$$\Rightarrow \Delta v_{C1} = \frac{I_1 DT_s}{2C_1} = \frac{D^2 V_g T_s}{2RC_1}$$

Ripple on L_1 :

Voltage waveform applied to L_1 is nonpulsating $\Rightarrow$ must use arguments as in Fig. 2.27
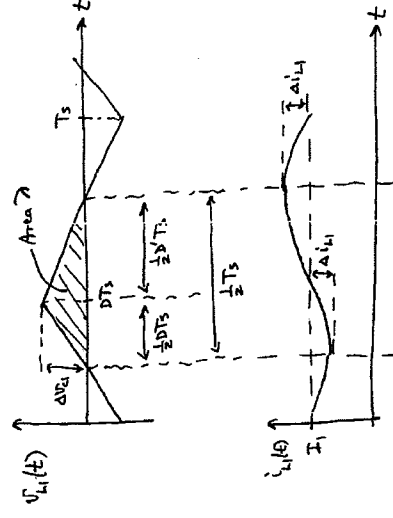
$$v_{L1}(t) = L_1 \frac{di_{L1}(t)}{dt} = V_g - v_{C1}(t)$$



Area $A = \frac{1}{2} \left(\frac{1}{2} T_s \right) (\Delta v_{L1}) = L_1 \cdot 2\Delta i_{L1}$

so $\Delta i_{L1} = \frac{T_s \Delta v_{C1}}{8L_1} = \frac{T_s}{8L_1} \frac{D^2 V_g T_s}{2RC_1}$

$$\Delta i_{L1} = \frac{D^2 V_g T_s^2}{16L_1 C_1 R}$$


d)

$$C_1 = \frac{D^2 V_g T_s}{2R(2\Delta i_{L1})} = \frac{(0.75)^2 (0.25) (10\mu s)}{2(6\Omega)(0.02)} = 5.86\mu F$$


$D = \frac{36}{48} = 0.75$

$$L_1 = \frac{D^2 V_g T_s^2}{16C_1 R \Delta i_{L1}} = \frac{(0.75)^2 (0.25) (49\mu s)^2}{16(5.86\mu F)(6\Omega)(20mA)} = 60\mu H$$


Solution to Problem 3.1

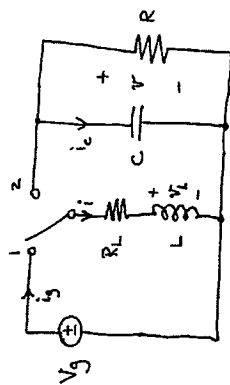
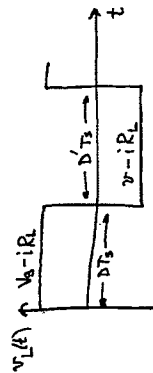
$$\begin{aligned} \langle v_L \rangle &= 0 = D(V_g - i_L R_L) + D'(V - i_L R_L) \\ &\approx D(V_g - I R_L) + D'(V - I R_L) \\ &\Rightarrow D V_g + D' V - I R_L = 0 \quad (1) \end{aligned}$$


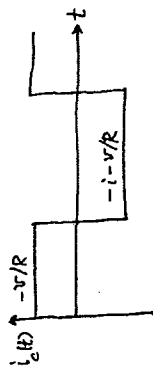
$$\begin{aligned} \langle i_L \rangle &= 0 = D\left(-\frac{V}{R}\right) + D'\left(-I - \frac{V}{R}\right) \\ &\Rightarrow -D'I - \frac{V}{R} = 0 \\ &\Rightarrow I = -\frac{V}{D'R} \quad (2) \end{aligned}$$




Now insert (2) into (1) and solve for V:

$$D V_g + D' V + \frac{V R_L}{D' R} = 0$$

$$D V_g = D' V \left(1 + \frac{R_L}{D' R}\right)$$

$$\Rightarrow V = \frac{D}{D'} \left(1 + \frac{R_L}{D' R}\right) V_g$$

3.1 part (b)

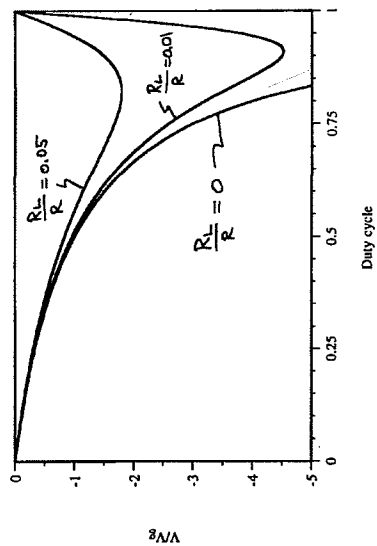

Part (c)

Average powers: $P_{in} = V_g \langle i_g \rangle = D I V_g$
 $P_{out} = V D' I$

so $\eta = \frac{P_{out}}{P_{in}} = \frac{V D' I}{D I V_g} = \frac{D'}{D} \frac{V}{V_g}$

substitute solution for V from part (a), and simplify:

$$\eta = \frac{1}{\left(1 + \frac{R_L}{D'^2 R}\right)}$$


Solution to Problem 3.2

See solution to Problem 3.1 for schematic and for derivation of the following equations:

$$0 = D'V_g + D'V - IR_L \quad (\text{from inductor volt-sec balance})$$


$$0 = -D'I - V/R \quad (\text{from capacitor charge balance})$$

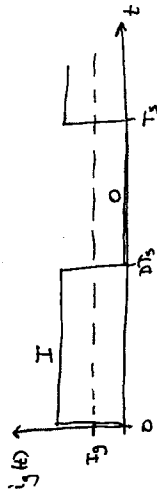To derive a complete equivalent circuit model, we also need an equation for the average input current I_g



$$I_g = \langle i_g \rangle = DI$$

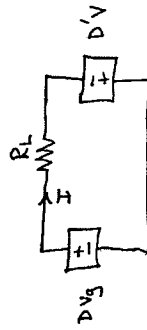
Equivalent circuit corresponding to inductor equation;




Capacitor equation;




Input current equation:

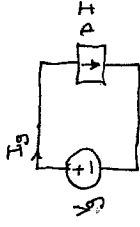

Combine circuits:

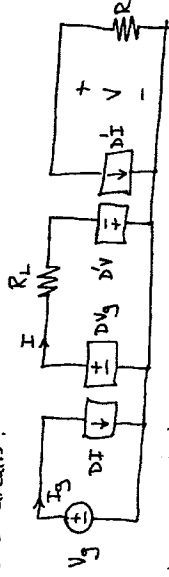


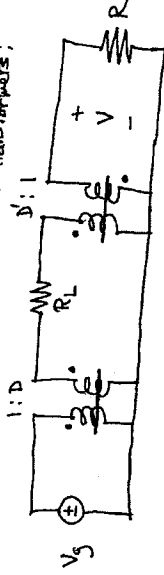Replace dependent sources with dc transformers;




Tutorial
Solution to Problem 3.6

Converter circuit, Fig. 3.33;

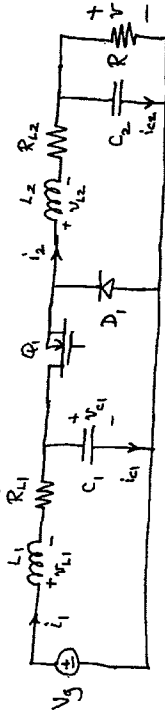

Model inductor winding resistances R_{L1} and R_{L2} , MOSFET on-resistance R_{on} , and diode forward voltage drop (constant voltage V_D plus voltage across effective resistance R_D).

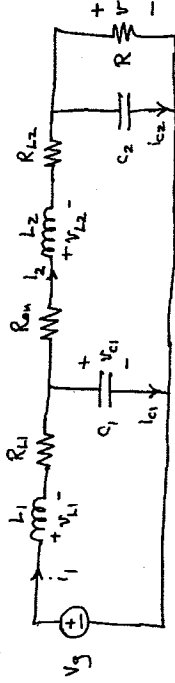Subinterval 1 $0 \leq t < DT_S$. Q_1 on, D_1 off




Inductor voltages and capacitor currents, expressed as functions of quantities that have small ripple:

$$\begin{aligned} v_{L1}(t) &= V_g - i_1(t)R_{L1} - v_{C1}(t) \\ v_{L2}(t) &= v_{C1}(t) - i_2(t)R_{on} - i_2(t)R_{L2} - v(t) \\ i_{C1}(t) &= i_1(t) - i_2(t) \\ i_{C2}(t) &= i_2(t) - v(t)/R \end{aligned}$$

Small-ripple approximation: $i_1(t) \approx I_1$, $i_2(t) \approx I_2$, $v_{C1}(t) \approx V_{C1}$, $v(t) \approx V$
we get

$$\begin{aligned} v_{L1}(t) &\approx V_g - I_1 R_{L1} - V_{C1} \\ v_{L2}(t) &\approx V_{C1} - I_2 R_{on} - I_2 R_{L2} - V \\ i_{C1}(t) &\approx I_1 - I_2 \\ i_{C2}(t) &\approx I_2 - V/R \end{aligned}$$

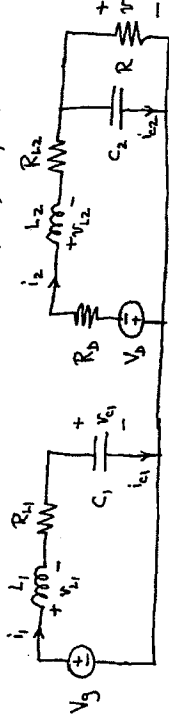Subinterval 2 $DT_S \leq t < T_S$ Q_1 off, D_1 on




$$\begin{aligned} v_{L1}(t) &= V_g - i_1(t)R_{L1} - v_{C1}(t) \\ v_{L2}(t) &= -V_D - i_2(t)R_D - i_2(t)R_{L2} - v(t) \\ i_{C1}(t) &= i_1(t) \\ i_{C2}(t) &= i_2(t) - v(t)/R \end{aligned}$$

Small ripple approximation:

$$\begin{aligned} v_{L1}(t) &\approx V_g - I_1 R_{L1} - V_{C1} \\ v_{L2}(t) &\approx -V_D - I_2 R_D - I_2 R_{L2} - V \\ i_{C1}(t) &\approx I_1 \\ i_{C2}(t) &\approx I_2 - V/R \end{aligned}$$

Switched waveforms:

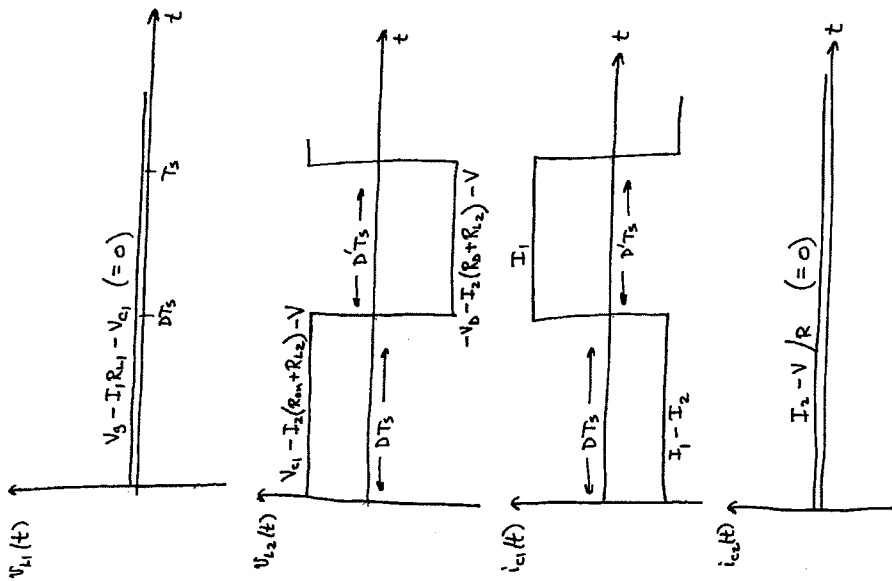

Equate average inductor voltages and capacitor currents to zero:

$$\langle v_{L1}(t) \rangle = 0 = V_g - I_1 R_{L1} - V_{C1}$$


$$\langle v_{L2}(t) \rangle = 0 = D[V_{C1} - I_2(R_{L2} + R_{L1}) - V] + D'[-V_g - I_2(R_{L2} + R_{L1}) - V]$$

$$\langle i_{C1}(t) \rangle = 0 = D[I_1 - I_2] + D'[I_1]$$


$$\langle i_{C2}(t) \rangle = 0 = I_2 - V/R$$

Derive equivalent circuit

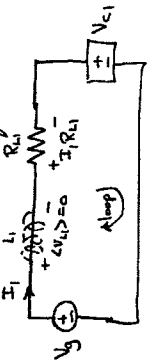Inductor L_1 : $\langle v_{L1} \rangle = 0 = V_g - I_1 R_{L1} - V_{C1}$
A loop equation containing L_1 , with current I_1




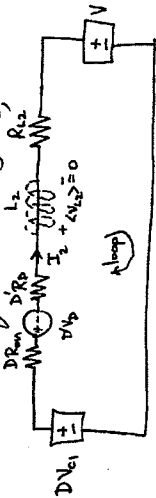Inductor L_2 : $\langle v_{L2} \rangle = 0 = DV_{C1} - DR_{L2}I_2 - DR_{L1}I_2 - R_{L2}I_2 - V - DV_g$
A loop equation containing L_2 , with current I_2




Capacitor C_1 : $\langle i_{C1} \rangle = 0 = I_1 - DI_2$

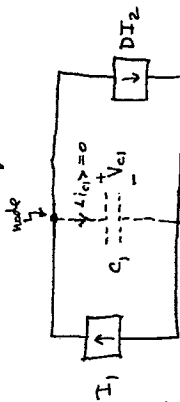A node equation containing C_1 , with voltage V_{C1}




Capacitor C_2 : $\langle i_{C2} \rangle = 0 = I_2 - V/R$

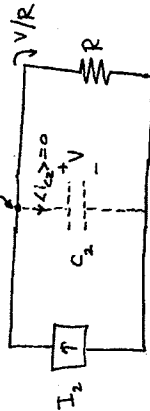A node equation including C_2 , with voltage V .



* Note that 1:1 transformers are not needed in these locations - a direct connection will suffice! In fact, in the actual converter there is no switching at these points. Inductor L_1 is directly connected to C_1 , and L_2 is always connected to C_2

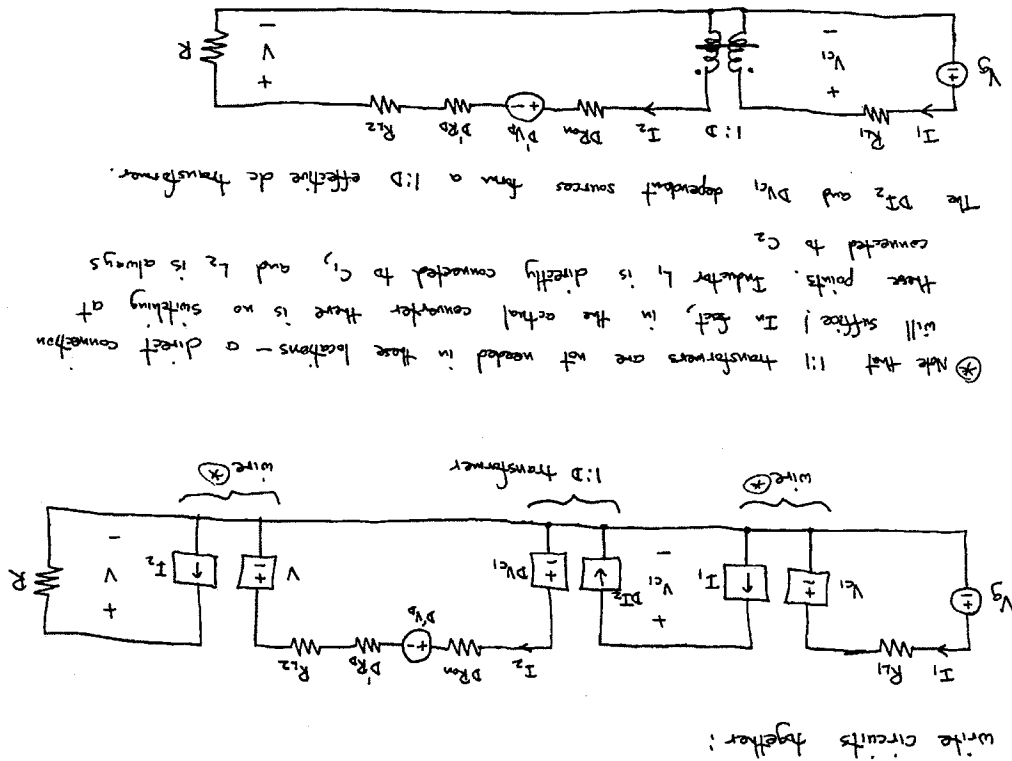
The DI_2 and DI_{C1} dependent sources form a 1:1 effective dc transformer.




write circuits together:

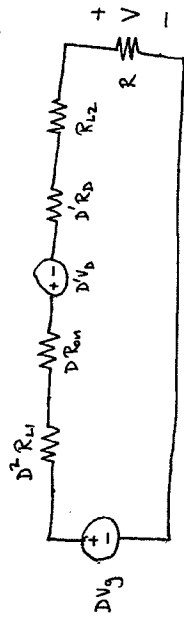b) Solve model to find V

Push V_g and R_{L1} through dc transformer;



Combine elements:

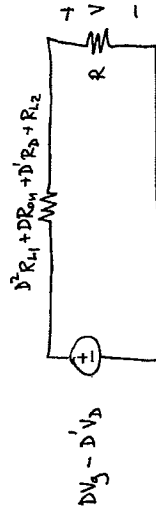

Voltage divider formula:

$$V = (DV_g - D'V_b) \frac{R}{R + D^2 R_{L1} + D'R_D + R_{L2}}$$

c) Derive an expression for efficiency γ . Manipulate into form similar to Eq. (3.35)

From the equivalent circuit on page 6,

$$P_{in} = V_g I_1$$

$$P_{out} = V I_2$$

$$\text{and } I_1 = D I_2$$

So

$$\gamma = \frac{P_{out}}{P_{in}} = \frac{V I_2}{V_g I_1} = \frac{1}{D} \frac{V}{V_g}$$

From part (b),

$$\frac{V}{V_g} = (D - D' \frac{V_b}{V_g}) \frac{R}{R + D^2 R_{L1} + D'R_D + D'R_D + R_{L2}}$$

(note that it is OK for the right side of the equation to depend on V_g).


So

$$\gamma = (1 - D' \frac{V_b}{V_g}) \frac{1}{(1 + D^2 \frac{R_{L1}}{R} + D \frac{R_{in}}{R} + D' \frac{R_D}{R} + \frac{R_{L2}}{R})}$$

This is a good design-oriented way to express the efficiency, because it exposes how each loss element reduces the efficiency. The effect of the diode voltage drop V_b is expressed in terms of V_g , while the loss resistances are compared to R . The various losses also depend on duty cycle.

End of problem 3.6

Problem 3.11 Buck converter

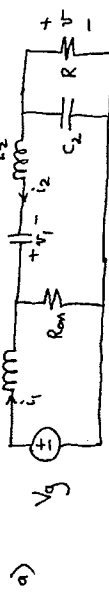


when D_1 conducts
 $0 < t < DT_s$

$$v_{L1} = V_g - (i_1 + i_2) R_{on} \approx V_g - (I_1 + I_2) R_{on}$$

$$i_{C1} = -i_2 \approx -I_2$$

$$v_{L2} = V - v_1 - (i_1 + i_2) R_{on} \approx V + V_1 - (I_1 + I_2) R_{on}$$
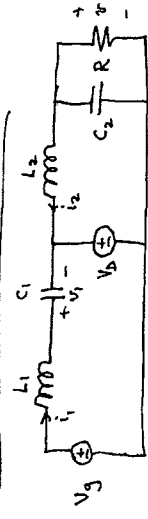
$$i_{C2} = -i_2 - \frac{V}{R} \approx -I_2 - \frac{V}{R}$$



when D_1 conducts
 $DT_s < t < T_s$

$$v_{L1} = V_g - v_1 - V_D \approx V_g - V_1 - V_D$$

$$i_{C1} = i_1 \approx I_1$$

$$v_{L2} = V - V_D \approx V - V_D$$

$$i_{C2} = -i_2 - \frac{V}{R} \approx -I_2 - \frac{V}{R}$$

Averaged equations (volt-sec and charge balance)

$$0 = V_g - D(I_1 + I_2) R_{on} - D'V_1 - D'V_D$$


$$0 = -D'I_2 + D'I_1$$

$$0 = V + DV_1 - D(I_1 + I_2) R_{on} - D'V_D$$

$$0 = -I_2 - \frac{V}{R}$$

Construct equivalent circuit

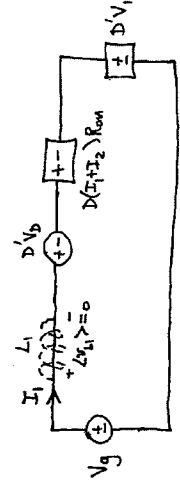
$$0 = V_g - D(I_1 + I_2) R_{on} - D'V_1 - D'V_D$$



loop equation
for inductor L_1
loop current = I_1


How to handle the $D(I_1 + I_2) R_{on}$ term? We would like to model this term using a $D R_{on}$ resistor. But it also depends on I_2 . Let's follow the hint, and leave it as a dependent source for now.

$$0 = -D'I_2 + D'I_1$$

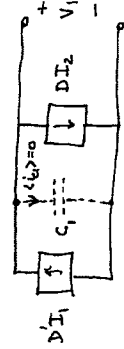


node equation for
capacitor C_1
Node voltage = V_1
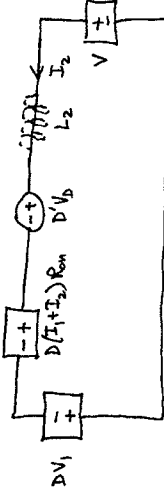
$$0 = V + DV_1 - D(I_1 + I_2) R_{on} - D'V_D$$




loop equation
for inductor L_2
loop current = I_2

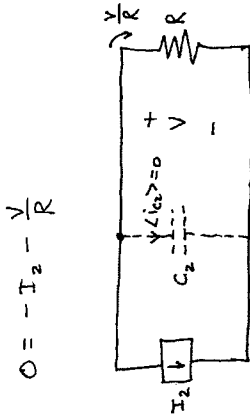
node equation for capacitor C_2
Node voltage = V




Put the circuits together

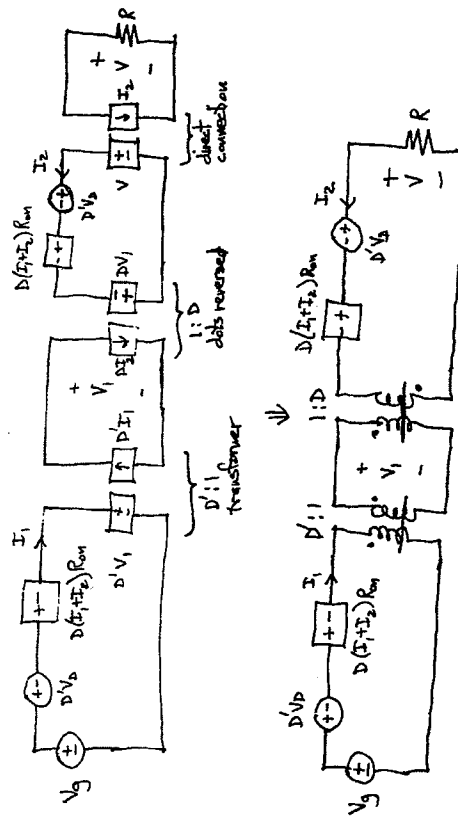

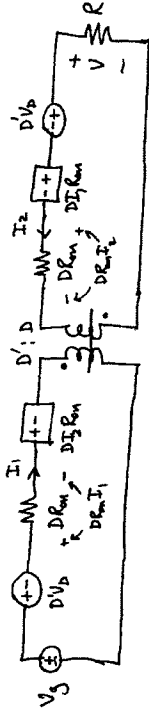
One way to handle the $D(I_1 + I_2)R_{on}$ sources:



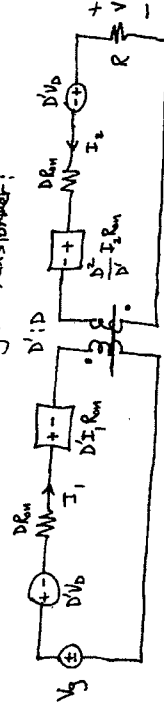
Now push dependent sources through transformer:




Sources now become resistors

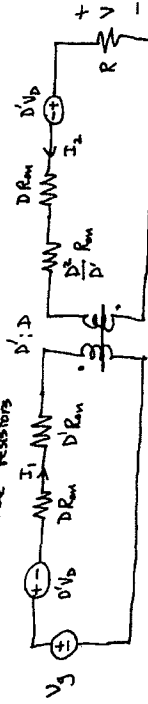


Combine series resistors:

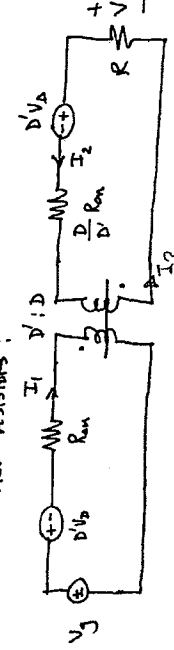

$$D' \cdot I_1 = I_2$$

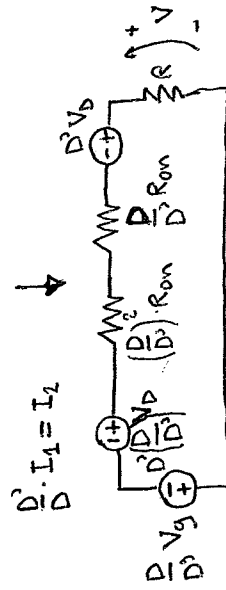

Next stage

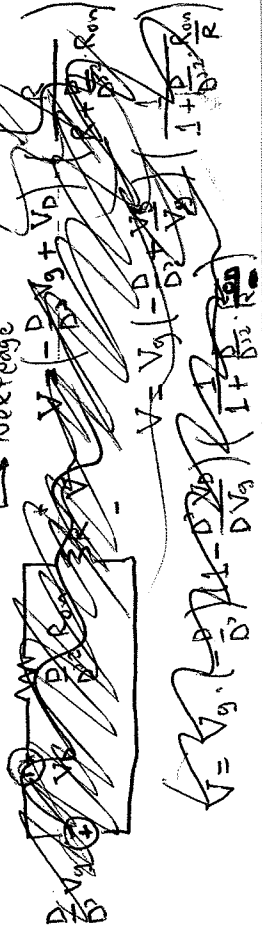

b) solve model for V and η

$$V = \left[-\frac{D}{D'} (V_g - D'V_b) + D'V_b \right] \frac{R}{R + \frac{D}{D'} R_{on} + \left(\frac{D}{D'}\right)^2 R_{on}}$$

$$\frac{V}{V_g} = -\frac{D}{D'} \frac{\left(1 - \frac{D'V_b}{D'V_g}\right)}{\left(1 + \frac{D}{(D')^2} \frac{R_{on}}{R}\right)}$$

$$\eta = \frac{\left(1 - \frac{D'V_b}{D'V_g}\right)}{\left(1 + \frac{D}{(D')^2} \frac{R_{on}}{R}\right)}$$

$$P_{in} = \frac{D}{D'} V_g I_2$$

$$P_{out} = V I_2$$

$$\frac{P_{out}}{P_{in}} = \frac{V I_2}{\frac{D}{D'} V_g I_2} = \frac{D'}{D} \frac{V}{V_g}$$

$$\eta = -\frac{D'}{D} \frac{V}{V_g}$$

c) and d) see plots on next page

(c) and (d)

