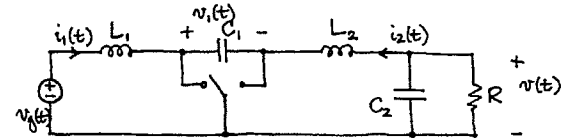


Problem 7.b

Ideal Cuk converter in CCM:



(a) Averaged nonlinear equations:

$$L_1 \frac{d\langle i_1 \rangle_{T_s}}{dt} = \langle v_g \rangle_{T_s} - d' \langle v_1 \rangle_{T_s}$$

$$C_1 \frac{d\langle v_1 \rangle_{T_s}}{dt} = d' \langle i_1 \rangle_{T_s} - d \langle i_2 \rangle_{T_s}$$

$$L_2 \frac{d\langle i_2 \rangle_{T_s}}{dt} = \langle v \rangle_{T_s} + d \langle v_1 \rangle_{T_s}$$

$$C_2 \frac{d\langle v \rangle_{T_s}}{dt} = -\langle i_2 \rangle_{T_s} - \frac{\langle v \rangle_{T_s}}{R}$$

Small signal AC equations:


$$L_1 \frac{d\hat{i}_1}{dt} = \hat{v}_g - D' \hat{v}_1 + V_1 \hat{d}$$

$$C_1 \frac{d\hat{v}_1}{dt} = D \hat{i}_1 - D \hat{i}_2 - (I_1 + I_2) \hat{d}$$

$$L_2 \frac{d\hat{i}_2}{dt} = \hat{v} + D \hat{v}_1 + V_1 \hat{d}$$


$$C_2 \frac{d\hat{v}}{dt} = -\hat{i}_2 - \frac{\hat{v}}{R}$$

(b) Small signal AC equivalent circuit

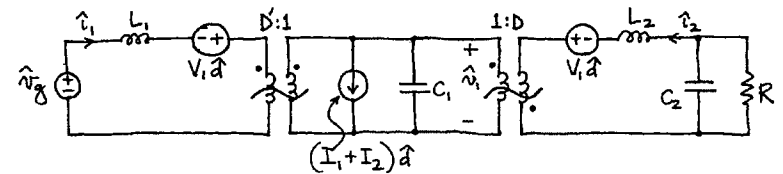

Problem 7.1


Ideal boost converter in CCM:

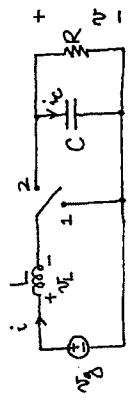

(a) Switch in position 1, $0 < t \leq dT_s$

$$L \frac{di}{dt} = v_L = v_g$$

$$C \frac{dv}{dt} = i_c = -\frac{v}{R}$$

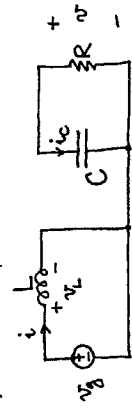

Small-ripple approximation:


$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = \langle v_g(t) \rangle_{T_s}$$

$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = -\frac{\langle v(t) \rangle_{T_s}}{R}$$

Switch in position 2, $dT_s < t \leq T_s$

$$L \frac{di}{dt} = v_L = v_g - v$$
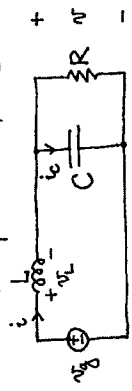
$$C \frac{dv}{dt} = i_c = i - \frac{v}{R}$$



Small ripple approximation:

$$L \frac{d\langle i(t) \rangle_{T_s}}{dt} = \langle v_g(t) \rangle_{T_s} - \langle v(t) \rangle_{T_s}$$

$$C \frac{d\langle v(t) \rangle_{T_s}}{dt} = \langle i(t) \rangle_{T_s} - \frac{\langle v(t) \rangle_{T_s}}{R}$$

Nonlinear averaged equations:

$$L \frac{d\langle i \rangle_{T_s}}{dt} = d\langle v_g \rangle_{T_s} + d'(\langle v_g \rangle_{T_s} - \langle v \rangle_{T_s})$$

$$= \langle v_g \rangle_{T_s} - d'\langle v \rangle_{T_s}$$

$$C \frac{d\langle v \rangle_{T_s}}{dt} = d\left(-\frac{\langle v \rangle_{T_s}}{R}\right) + d'\left(\langle i \rangle_{T_s} - \frac{\langle v \rangle_{T_s}}{R}\right)$$

$$= d'\langle i \rangle_{T_s} - \frac{\langle v \rangle_{T_s}}{R}$$

(b) Perturbo and linearize. Let

$$\langle v_g \rangle_{T_s} = V_g + \hat{v}_g(t)$$

$$d(t) = D + \hat{d}(t)$$

$$\langle i \rangle_{T_s} = I + \hat{i}(t)$$

$$\langle v \rangle_{T_s} = V + \hat{v}(t)$$

then

$$L \frac{d}{dt}(I + \hat{i}(t)) = V_g + \hat{v}_g(t) - (D' - \hat{d}(t))(V + \hat{v}(t))$$

Large signal DC components:

$$0 = V_g - DV$$

1st order AC terms:

$$L \frac{d\hat{i}}{dt} = \hat{v}_g(t) - D'\hat{v}(t) + V\hat{d}(t)$$

$$C \frac{d}{dt}(V + \hat{v}(t)) = (D' - \hat{d}(t))(I + \hat{i}(t)) - \frac{V + \hat{v}(t)}{R}$$

Large signal DC components


$$0 = D'I - \frac{V}{R}$$

1st order AC terms:

$$C \frac{d\hat{v}}{dt} = D'\hat{i}(t) - I\hat{v}(t) - \frac{\hat{v}(t)}{R}$$

Problem 7.14

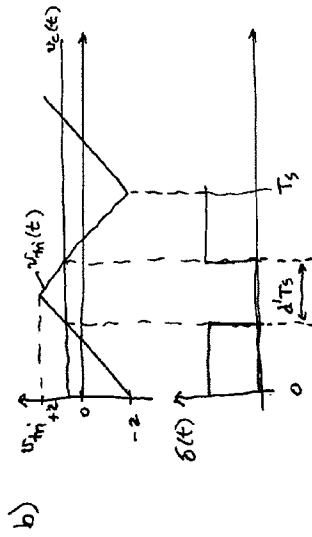
a) $T_s = 50 \mu s$ so $f_s = \frac{1}{50 \mu s} = 20 kHz$



$d' = 0$ when $v_c = +2$

$d' = 1$ when $v_c = -2$



d' varies linearly with v_c

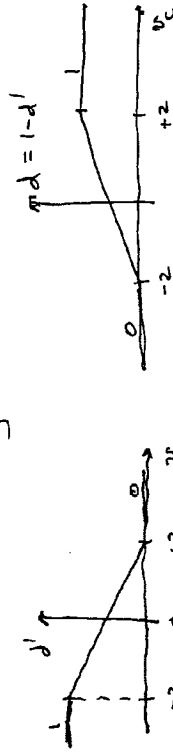

$$d = \begin{cases} 1 & \text{for } v_c \geq 2V \\ \frac{v_c + 2}{4} & \text{for } -2V \leq v_c \leq +2V \\ 0 & \text{for } v_c \leq -2V \end{cases}$$

The gain $\frac{1}{4}$ is $\frac{1}{4}$, valid for $-2 \leq v_c \leq +2$ (c)

Problem 7.8 a,b

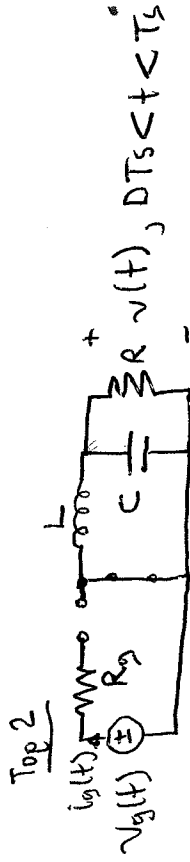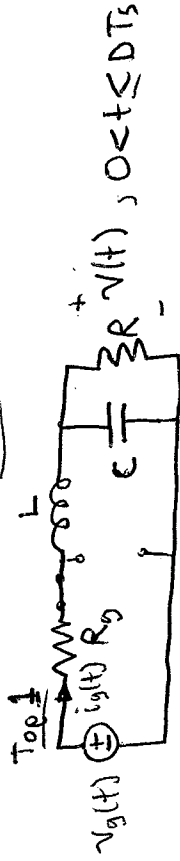

Top 1
 $\frac{d}{dt} v_L(t) = L \cdot \frac{d}{dt} i_L(t) = V_g - i_L R_g - v(t)$
 $\frac{d}{dt} i_L(t) = C \cdot \frac{d}{dt} v(t) = i_L - \frac{v}{R}$
 $i_g = i_L$

Top 2
 $\frac{d}{dt} v_L(t) = L \cdot \frac{d}{dt} i_L(t) = -v(t)$
 $\frac{d}{dt} i_L(t) = C \cdot \frac{d}{dt} v(t) = i_L - \frac{v}{R}$
 $i_g = 0$

Top 1 K
 $\begin{bmatrix} L & 0 \\ 0 & C \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} = \begin{bmatrix} -R_g & -1 \\ 1 & -1/R \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} v_g$

$[i_g] = \begin{bmatrix} 1 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} v_g$

Top 2 K
 $\begin{bmatrix} L & 0 \\ 0 & C \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} = \begin{bmatrix} 0 & -1 \\ 1 & -1/R \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} v_g$
 $[i_g] = \begin{bmatrix} 0 & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_L \\ v \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \end{bmatrix} v_g$

7.8 (cont)

Remember:
(D+D')=1

* Averaged matrices

$$A = DA_1 + D'A_2 = \begin{bmatrix} -DR_g & -1 \\ 1 & -1/R \end{bmatrix}; C = DC_1 + D'C_2 = \begin{bmatrix} D & 0 \end{bmatrix}$$

$$B = DB_1 + D'B_2 = \begin{bmatrix} D \\ 0 \end{bmatrix}; E = DE_1 + D'E_2 = \begin{bmatrix} 0 \end{bmatrix}$$

$$(A_1 - A_2) = \begin{bmatrix} -R_g & 0 \\ 0 & 0 \end{bmatrix}$$

$$(B_1 - B_2) = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$(C_1 - C_2) = \begin{bmatrix} 1 & 0 \end{bmatrix}$$

* AC small signal equations

$$K \cdot \frac{d}{dt} X(t) = A X + B \hat{u} + [(A_1 - A_2)X + (B_1 - B_2)u] \hat{d}(t)$$

$$\begin{bmatrix} L & 0 \\ 0 & C \end{bmatrix} \frac{d}{dt} \begin{bmatrix} \hat{i}_L \\ \hat{v}_C \end{bmatrix} = \begin{bmatrix} -DR_g - 1 & 1 \\ 1 & -1/R \end{bmatrix} \begin{bmatrix} \hat{i}_L \\ \hat{v}_C \end{bmatrix} + \begin{bmatrix} D \\ 0 \end{bmatrix} \begin{bmatrix} \hat{v}_g \\ \hat{d} \end{bmatrix} + \begin{bmatrix} -R_g I_L + V_g \\ 0 \end{bmatrix} \hat{d}(t)$$


$$L \hat{i}_g = [D \ 0] \begin{bmatrix} \hat{i}_L \\ \hat{v}_C \end{bmatrix} + [I] \hat{d}(t) + [0] \hat{v}_g(t)$$

b) Equivalent circuit model

$$L \frac{d\hat{i}_L}{dt} = \hat{v}_L(t) = -DR_g \hat{i}_L - \hat{v}_C + D \hat{v}_g - R_g I_L \hat{d} + V_g \hat{d}$$


$$C \frac{d\hat{v}_C}{dt} = \hat{i}_C = \hat{i}_L - \frac{\hat{v}_C}{R}$$

$$\hat{i}_g = D \hat{i}_L + I \hat{d}$$

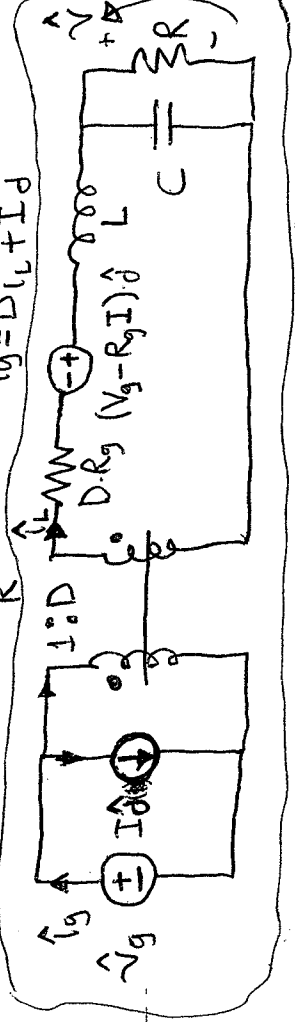


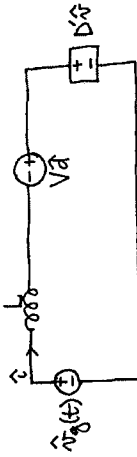Problem 7.2



$$L \frac{d\hat{i}(t)}{dt} = -D' \hat{v}(t) + V \hat{v}(t) + \hat{v}_g(t)$$


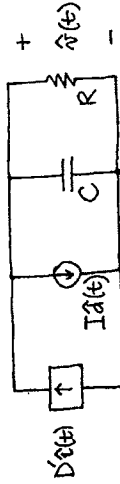
$$C \frac{d\hat{v}(t)}{dt} = D' \hat{v}(t) - I \hat{v}(t) - \frac{\hat{v}(t)}{R}$$



Combine circuits:

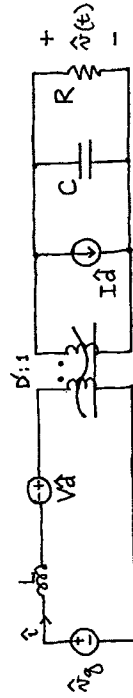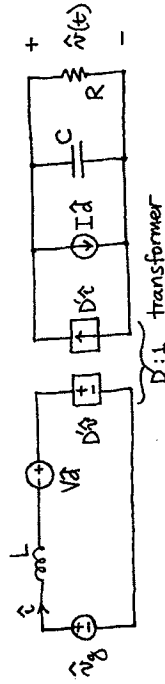

Averaged small-signal AC equivalent circuit model of the ideal CCM boost converter.