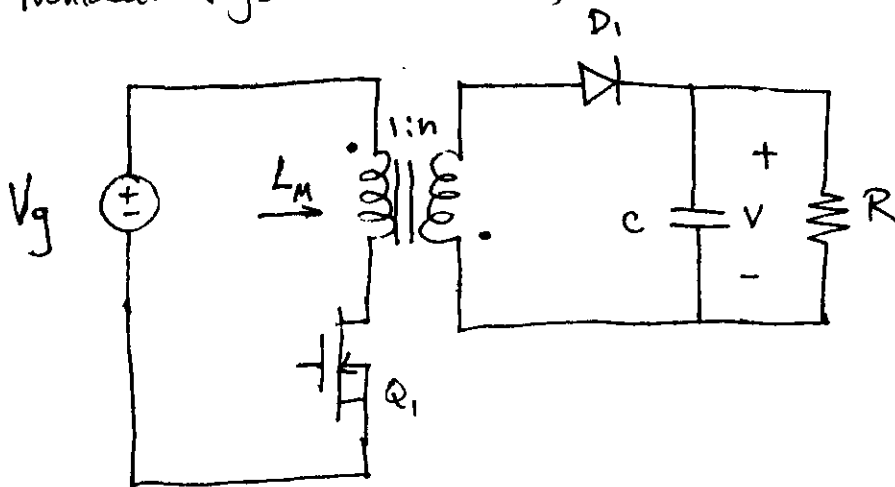


Solution to Problem 6.5

Nonideal flyback converter, CCM




Model MOSFET on-resistance R_{on}


Diode forward voltage drop V_D

Flyback transformer winding resistances
 R_p and R_s

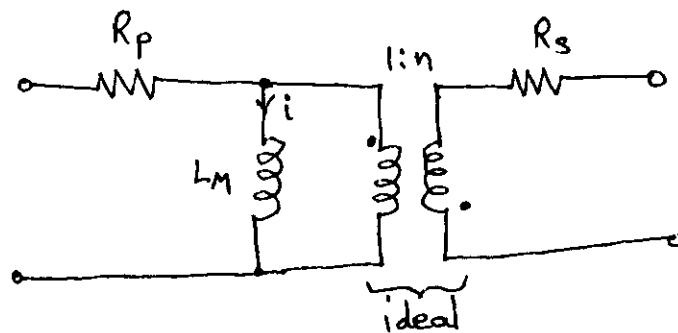Equivalent circuit model used for flyback transformer:



Switch in position 1 : Q_1 on, D_1 off

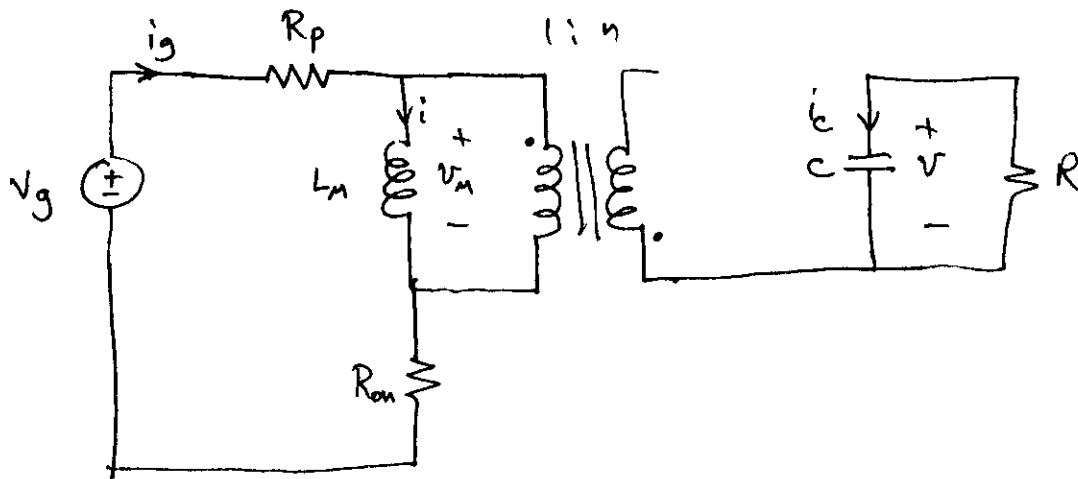


$$v_m = L_m \frac{di}{dt} = V_g - iR_p - iR_{on} \approx V_g - IR_p - IR_{on}$$

$$i_c = C \frac{dv}{dt} = -\frac{v}{R} \approx -\frac{V}{R}$$

$$i_g = i \approx I$$

Switch in position 2 : Q_1 off, D_1 on

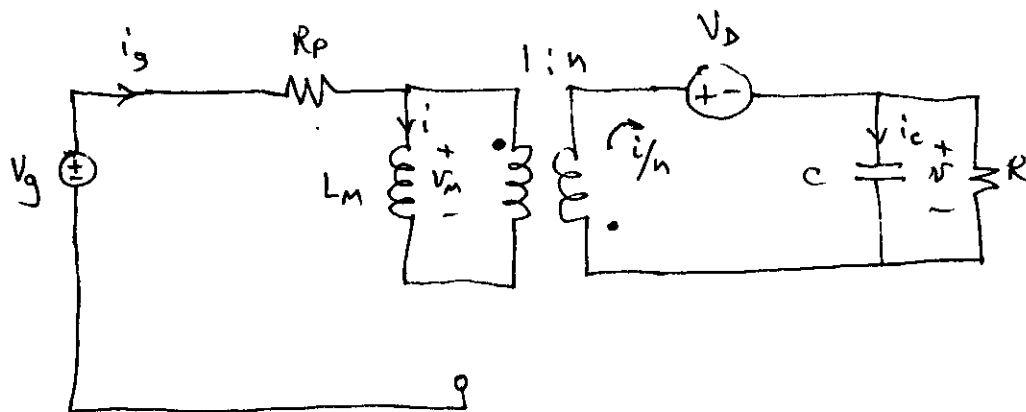

$$v_m = -\frac{v}{n} \approx -\frac{V+V_D}{n}$$

$$i_g = 0$$



$$i_c = \frac{i}{n} - \frac{v}{R} \approx \frac{I}{n} - \frac{V}{R}$$

$$\langle v_m \rangle = 0 = D(V_g - IR_p - IR_{on}) + D' \left(-\frac{V_{ds}}{n} \right)$$

$$\langle i_c \rangle = 0 = D \left(-\frac{V}{R} \right) + D' \left(\frac{I}{n} - \frac{V}{R} \right) = \frac{D'I}{n} - \frac{V}{R}$$

$$\langle i_g \rangle = I_g = DI$$

Equivalent circuit model

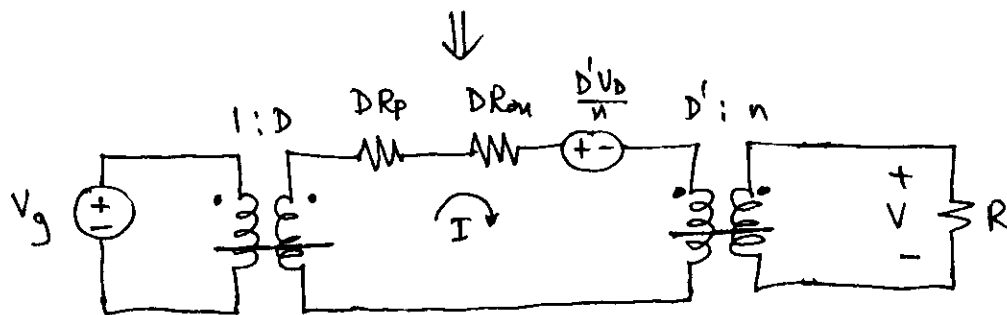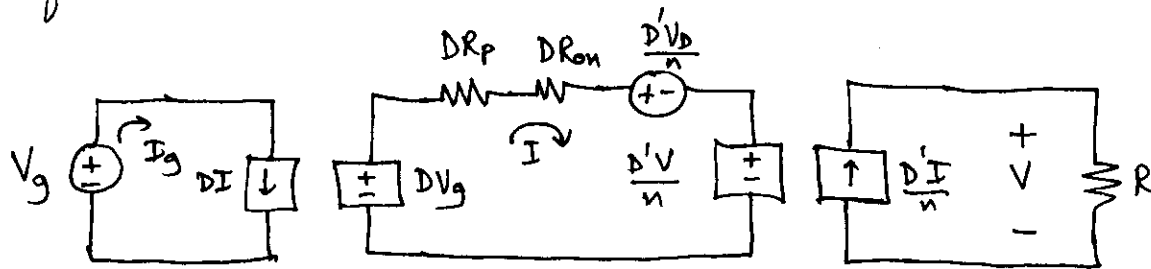

b) Find converter efficiency

$$P_{in} = (V_g)(DI)$$

$$P_{out} = (V) \left(\frac{D'I}{n} \right)$$

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V}{V_g} \frac{D'I}{nDI} = \frac{V}{V_g} \frac{D'}{nD}$$

$$\text{Also, } V = \left(DV_g - \frac{D'V_d}{n} \right) \left(\frac{n}{D'} \right) \frac{R}{R + \frac{n^2 DR_p}{D'^2} + \frac{n^2 DR_{on}}{D'^2}}$$

$$\frac{V}{V_g} = \frac{nD}{D'} \underbrace{\frac{\left(1 - \frac{D'V_d}{nDV_g} \right)}{\left(1 + \frac{n^2 D(R_p + R_{on})}{D'^2 R} \right)}}_{\eta}$$