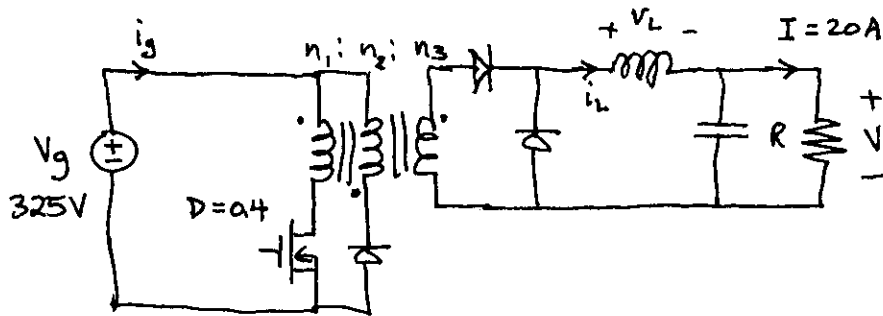


Problem 6.6

Forward converter with synchronous rectifiers

- a) with schottky diodes having $V_F = 0.5V$
MOSFET $R_{on} = 5\Omega$. Assume magnetizing current is negligible




inductor volt-sec balance: $\langle V_L \rangle = 0 = D \left[\frac{n_3}{n_1} V_g - \frac{n_3}{n_1} \langle i_L \rangle R_{on} \right] - V_F - V$
 $+ D' [-V_F - V]$

so $0 = D \frac{n_3}{n_1} V_g - D \left(\frac{n_3}{n_1} \right)^2 R_{on} I_L - V_F - V$

average input current: $\langle i_g \rangle = D \frac{n_3}{n_1} I_L$

(note that, even if transformer magnetizing current is modeled, its effect on the average i_g is zero)

Equivalent circuit model

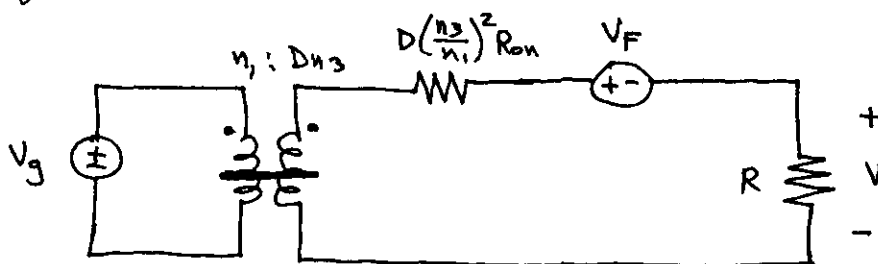

b) Solve model

$$V = \left(\frac{D n_3}{n_1} V_g - V_F \right) \frac{R}{R + D \left(\frac{n_3}{n_1} \right)^2 R_{on}}$$

Solve for required turns ratio:

$$\frac{n_3}{n_1} = \frac{D V_g - \sqrt{D^2 V_g^2 - 4 V D \frac{R_{on}}{R} (V + V_F)}}{2 V D \left(\frac{R_{on}}{R} \right)}$$

Solve for efficiency: $P_{in} = V_g \cdot \frac{D n_3}{n_1} I$

$$P_{out} = V I$$

$$\text{so } \eta = \frac{P_{out}}{P_{in}} = \frac{V I}{V_g \left(\frac{D n_3}{n_1} \right) I} = \frac{V}{V_g} \frac{n_1}{D n_3}$$


$$= \left(1 - \frac{V_F}{\left(\frac{D n_3}{n_1} \right) V_g} \right) \frac{1}{1 + D \left(\frac{n_3}{n_1} \right)^2 \frac{R_{on}}{R}}$$

calculations

<u>case</u>	<u>$\frac{n_3}{n_1}$</u>	<u>η</u>
(i) $V = 5$	0.0429	89.7%
(ii) $V = 3.3$	0.0295	86.1%
(iii) $V = 1.5$	0.0155	74.6%

c) With synchronous rectifiers

model becomes

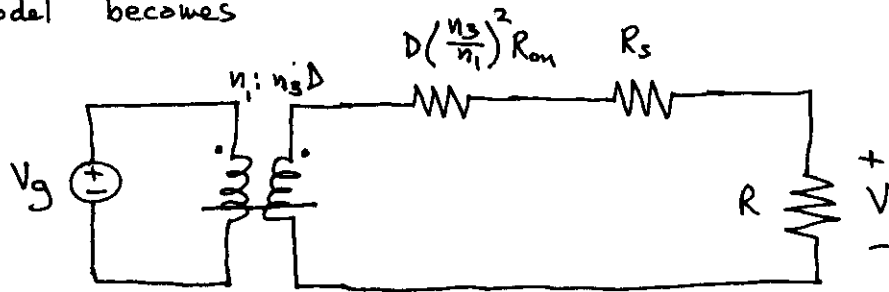

with $R_s = \text{synchronous rectifier on-resistance} = 4 \text{ m}\Omega$

solve:
$$V = D \frac{n_3}{n_1} V_g \frac{1}{\left(1 + \frac{R_s}{R} + D \left(\frac{n_3}{n_1}\right)^2 \frac{R_{on}}{R}\right)}$$

$$\eta = \frac{1}{\left(1 + \frac{R_s}{R} + D \left(\frac{n_3}{n_1}\right)^2 \frac{R_{on}}{R}\right)}$$

required turns ratio is

$$\frac{n_3}{n_1} = \frac{1 - \sqrt{1 - 4 \left(\frac{V}{V_g}\right)^2 \frac{R_{on}}{DR} \left(1 + \frac{R_s}{R}\right)}}{2 \left(\frac{V}{V_g}\right) \left(\frac{R_{on}}{R}\right)}$$

calculations

<u>case</u>	<u>n_3/n_1</u>	<u>η</u>
(i) $V = 5$	0.0396	97.2%
(ii) $V = 3.3$	0.0262	96.8%
(iii) $V = 1.5$	0.0122	94.6%