

PROBLEM 9.9

For the buck-boost converter, $D = \frac{15}{15+48} = 0.2381$

$$G_{do} = \frac{V}{DD'} = 82.7 \Rightarrow 38 \text{ dB}$$

$$\omega_o = \frac{D'}{\sqrt{LC}} = 7264 \text{ rad} \Rightarrow f_o = 1156 \text{ Hz}$$

$$Q = D'R\sqrt{\frac{C}{L}} = 8 \Rightarrow 18 \text{ dB}$$

$$\omega_z = \frac{D'^2 R}{DL} = 244 \text{ k rad} \Rightarrow f_z \approx 39 \text{ kHz}$$

$$(a) \quad H = -\frac{1}{3} \quad \text{and} \quad G_{pwm} = \frac{1}{V_m} = \frac{1}{3}$$

$\therefore$ Uncompensated loop gain is

$$T_u(s) = \frac{G_{do}}{g} \frac{\left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{Q\omega_o} + \frac{s^2}{\omega_o^2}\right)}$$


We can have a cross-over frequency between 5 kHz and 20 kHz. We need a phase margin of 52° at least and high low-frequency gain hence a PID compensator is required.

The transfer function of the compensator is

$$\begin{array}{ll} \text{Eq. 9.43} & G_c(s) = G_{cm} \frac{\left(1 + \frac{\omega_L}{s}\right) \left(1 + \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{\omega_{p1}}\right) \left(1 + \frac{s}{\omega_{p2}}\right)} \\ \text{Fig. 9.21} & \end{array}$$

We should select $f_L, f_z < f_c < f_{p1}, f_{p2}$

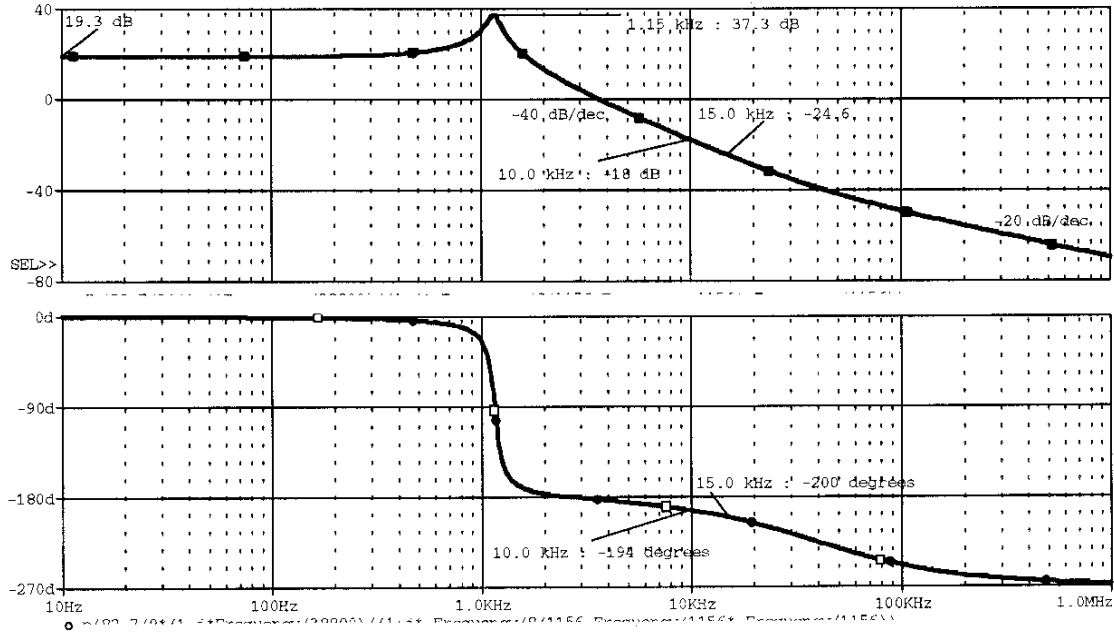(a) Uncompensated loop gain magnitude and phase




Compensator design: It is required that the crossover frequency be less than 20 kHz. If we have a crossover frequency tending to 20 kHz then the compensator poles will be placed near or beyond 200 kHz (switching frequency) and the attenuation of switching frequency ripple would not be sufficient. This is important here because the switching ripple is high for a buck-boost converter. If we have f_c near 5 kHz then we can not place the PI controller to have a high gain at 120 Hz. The location of the inverted zero of the PI stage as well as the high frequency roll-off pole affects the maximum compensator phase at f_c . The phase at f_c will be reduced by 5.7° if either a pole is placed at $10 f_c$ or an inverted zero is placed at $f_c/10$. The total phase reduction will be about 12° with both.

We select a crossover frequency to be 10 kHz. We need the compensator to have a gain of 18 dB and phase of 66° at 10 kHz. We design for a maximum phase of $66^\circ + 12^\circ = 78^\circ$. From Eq. 9.57, approximately, $f_z = 1$ kHz and $f_p = f_{p1} = 100$ kHz. Then $G_{c0} = 0.814$ from Eq. 9.58. We also choose $f_{p2} = 10 f_c = 100$ kHz and $f_L = f_c/10 = 1$ kHz. The plots for part (b) are attached.


(c) The loop gain at 120 Hz is 36 dB. More loop gain at 120 Hz can be obtained at the expense of switching frequency attenuation or phase margin. f_L could be pushed higher but the compensator will have to be redesigned to increase the maximum phase.

Crossover frequency improvement is mainly limited by the required attenuation at switching frequency.

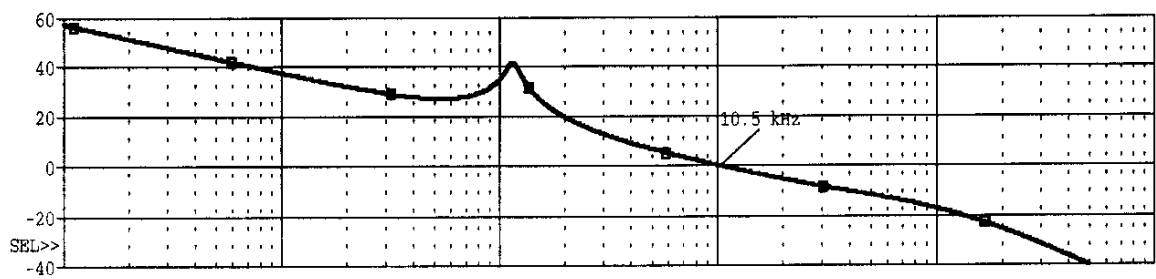(b) Bode plot of the compensated loop gain $T(s)$



□

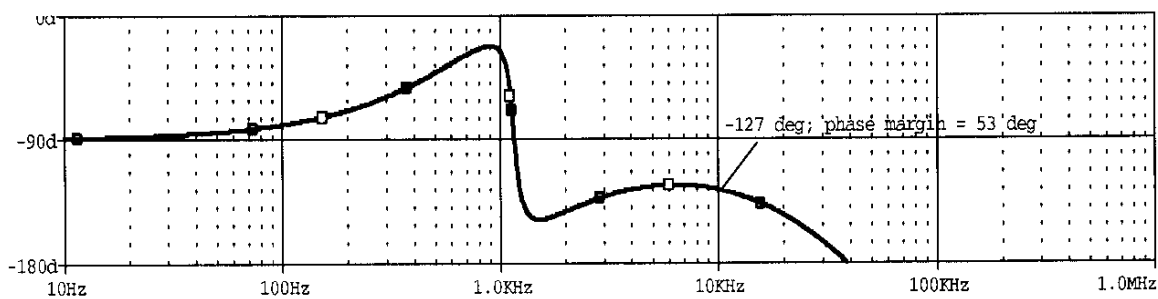

Magnitude of $1/(1+T)$ and $T/(1+T)$

