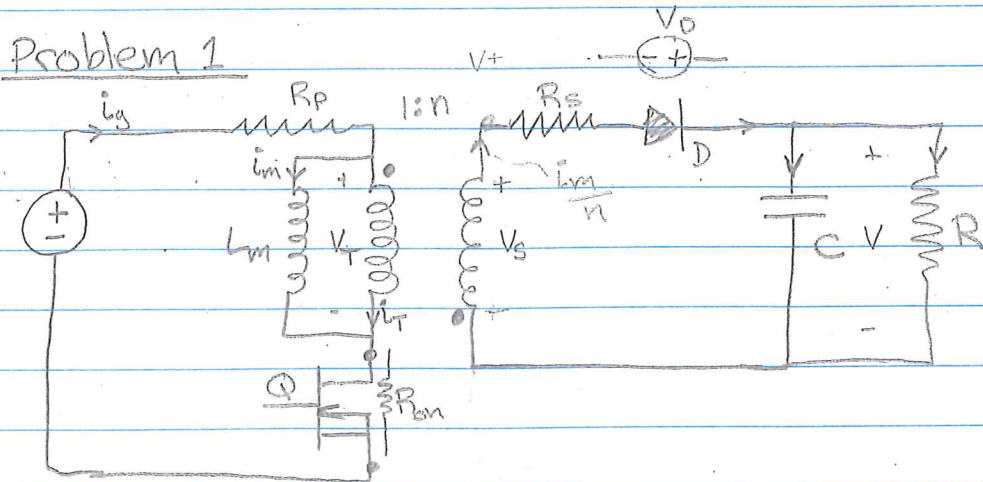


$$\frac{V_1}{V_2} = \frac{N_1}{N_2} \rightarrow V_1 = \frac{N_1}{N_2} V_2 \quad \frac{i_1}{i_2} = \frac{N_2}{N_1} \rightarrow i_2 = \frac{N_1}{N_2} i_1 = \frac{i_m}{n}$$

Problem 1



a) Derive the steady-state equivalent circuit model.

Top 1 (Q on)

$$V_T = V_g - i_g R_p - i_g R_{on}$$

$$i_c = -V/R$$

$$i_g = i_m$$

Top 2 (Q off)

$$V_s = [V + V_D + \frac{i_m}{n} R_s]$$

$$V_T = (-V_s)/n = -\frac{1}{n} [V + V_D + \frac{i_m}{n} R_s]$$

$$i_c = \frac{i_m}{n} - V/R$$

$$i_g = 0$$

• Volt-second and charge balance


$$\langle V_T \rangle = 0 = D [V_g - i_g R_p - i_g R_{on}] + \frac{D'}{n} [V + V_D + \frac{i_m}{n} R_s]$$

$$0 = D V_g - D i_m [R_p + R_{on}] - \frac{D'}{n} V - \frac{D'}{n} V_D - \frac{D' i_m}{n^2} R_s$$

$$\langle i_c \rangle = 0 = -V/R + \frac{i_m}{n} D'$$

$$\langle i_g \rangle = i_m D$$

• Draw the equiv. circuit

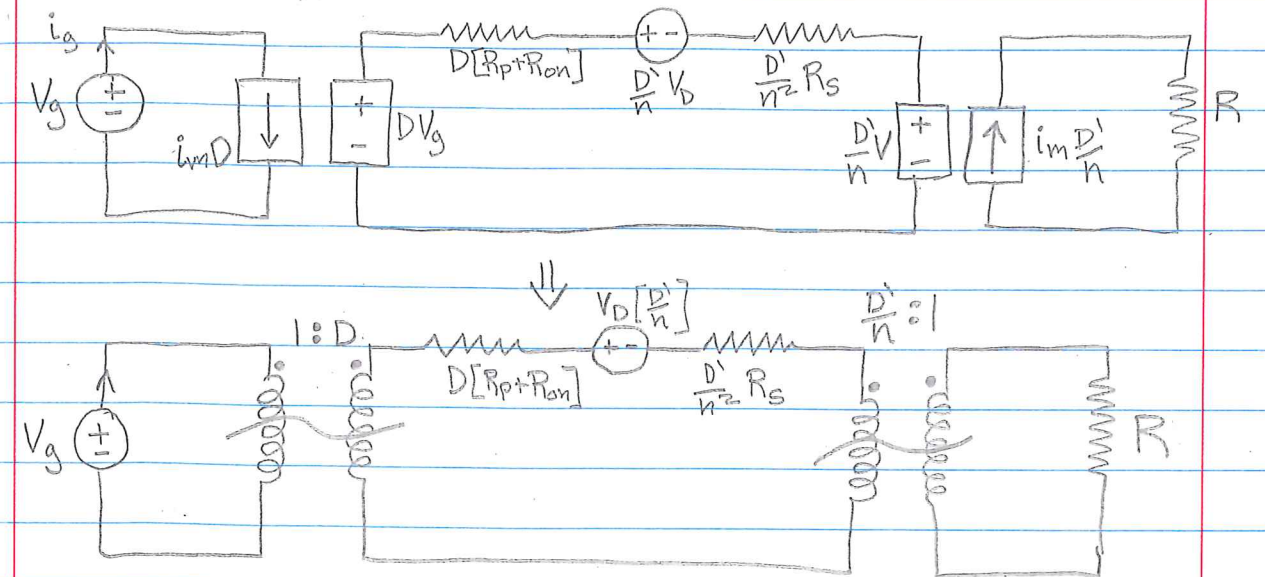


b) Derive the analytical expression for η

• Move all components to output side

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$V_2 = \frac{N_2}{N_1} V_1$$

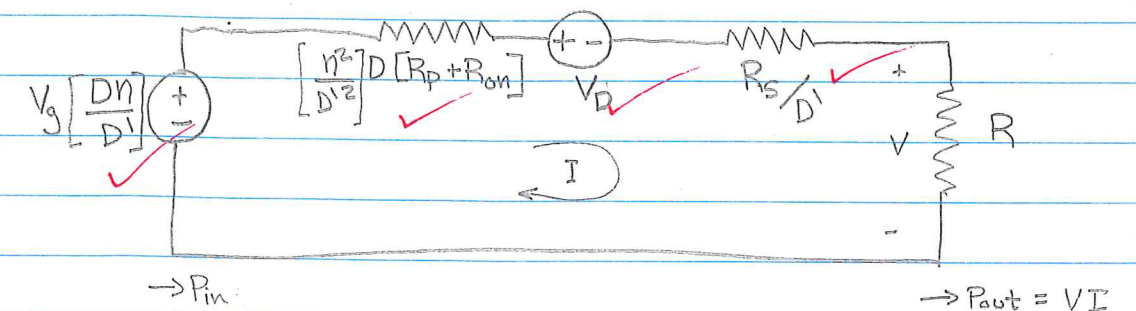

$$\eta = \frac{P_{out}}{P_{in}} = \frac{V \cdot I}{V_g \frac{Dn}{D'} n}$$

• Express $V(V_g)$;

• use voltage divider;

$$V = (V_g \frac{Dn}{D'} - V_d) \left[\frac{R}{\frac{n^2 D}{D'^2} [R_p + R_{on}] + \frac{R_s}{D'} + R} \right]$$

$$\eta = \frac{V_g \frac{Dn}{D'} - V_d}{V_g \frac{Dn}{D'}} \cdot \frac{(1 - \frac{V_d D'}{V_g Dn})}{\frac{n^2 D}{D'^2} \frac{[R_p + R_{on}]}{R} + \frac{R_s}{R D'} + 1}$$

10/10

10/10

c) Derive the max blocking voltage across the mosfet.


• MOSFET is off in Top 2

$$V_Q = V_g - V_T - 0$$

$$V_Q^{\max} = V_g + \frac{1}{n} \left[V + V_D + \frac{i_m}{n} R_s \right] \quad \checkmark \text{ 5/5}$$

• note: this does not take into account voltage ripple

d) Output voltage ripple

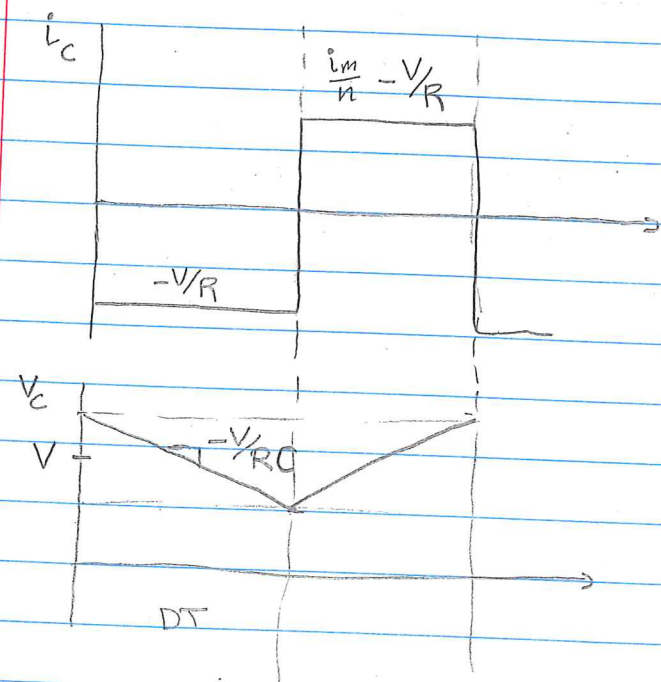


$$2\Delta V = -\frac{V}{RC} DT \rightarrow \Delta V = -\frac{DT}{2RC} V$$

• need $V(I_m)$;

• Use charge balance: $\frac{V}{R} = \frac{i_m}{n} D' \rightarrow V = \frac{i_m R}{n} D'$

• need $i_m(\Delta i_m)$;

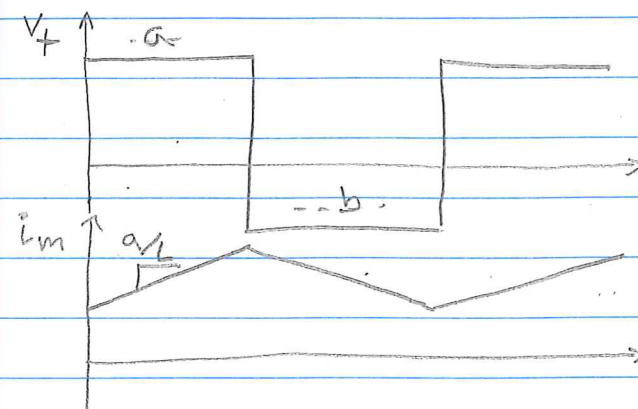

$$2\Delta i_m = \frac{[V_g - I_m R_p - I_m R_{on}] DT}{L}$$

$$\frac{2\Delta i_m L}{V_g DT} = -I_m DT [R_p + R_{on}]$$

$$\therefore \Delta V = \left[-\frac{DT}{2RC} \right] \left[\frac{R}{n} D' \right] \left[\frac{-2\Delta i_m L}{V_g DT [R_p + R_{on}]} \right]$$

$$\Delta V = \frac{D' L \Delta i_m}{C n V_g DT [R_p + R_{on}]}$$

Bonus:

Problem 2

a) Determine DC operating characteristics

i) Find D ;

Top 1

$$V_L = V_g$$

$$I_C = -V/R$$

$$I_g = I_L$$

Top 2

$$V_L = V_g - V$$

$$I_C = I_L - V/R$$

$$I_g = I_L$$

• Volt-second balance;


$$\langle V_L \rangle = 0 = V_g - VD' \rightarrow \frac{V}{V_g} = \frac{1}{D'}$$

$$\frac{1}{(1-D)} = \frac{100}{20} \Rightarrow 20 = 100 - 100D$$

$$\therefore \boxed{D = 0.8}$$

ii) Prove CCM

• For CCM $I_L > \Delta I_L$

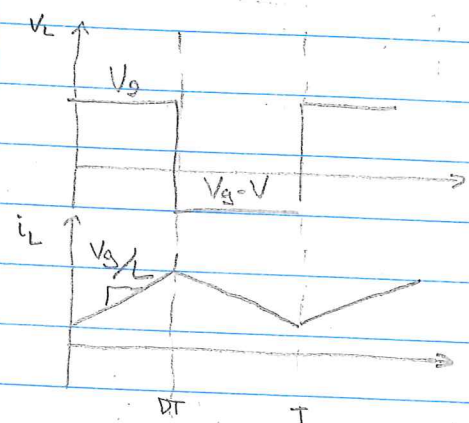

$$\langle I_C \rangle = 0 = -\frac{V}{R} + D'I_L$$

$$I_L = \frac{V}{RD'}$$

$$2\Delta I_L = \frac{V_g}{L} DT \Rightarrow \Delta I_L = \frac{V_g DT}{2L}$$

• For CCM

$$\frac{V}{RD'} > \frac{V_g DT}{2L}$$

$$100 > 40 \checkmark \therefore \text{CCM}$$

5/8

b) Find $Z_{out}(s)$, $G_{vg}(s)$, $G_{vd}(s)$

• Use AC small signal equiv circuit.

$$\langle V_L \rangle = L \frac{d\langle i_L \rangle}{dt} = d\langle V_g \rangle + d'[\langle V_g \rangle - \langle V \rangle] = \langle V_g \rangle - d'\langle V \rangle$$

$$L \frac{d\hat{i}_L}{dt} = (V_g + \hat{V}_g) - (D' - \hat{d})(V + \hat{V})$$

$$\therefore L \frac{d\hat{i}_L}{dt} = \hat{V}_g - D'\hat{V} + \hat{d}V$$



$$\langle I_C \rangle = C \frac{d\langle V \rangle}{dt} = -\frac{\langle V \rangle}{R} + d'\langle I_L \rangle$$

$$C \frac{d\hat{V}}{dt} = -\frac{1}{R}(V + \hat{V}) + (D' - \hat{d})(I_L + \hat{i}_L)$$


$$\therefore C \frac{d\hat{V}}{dt} = -\frac{\hat{V}}{R} + D'\hat{i}_L - \hat{d}I_L$$

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$V_2 = \frac{N_2 V_1}{N_1}$$

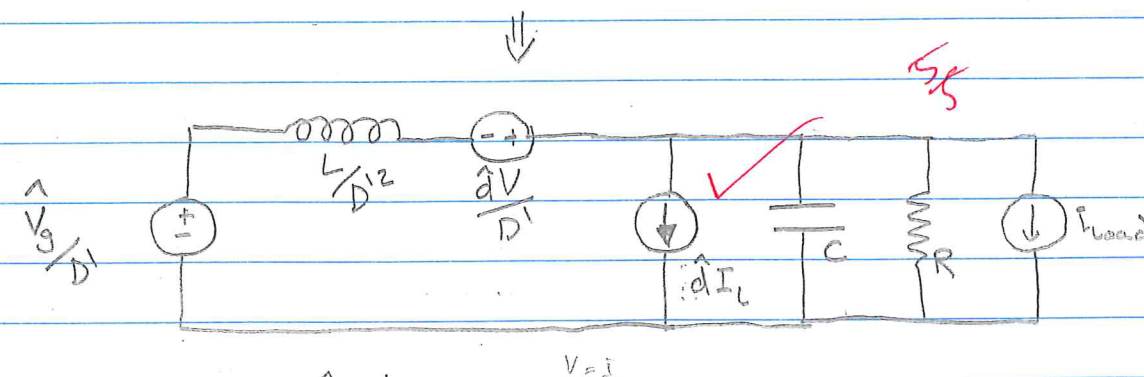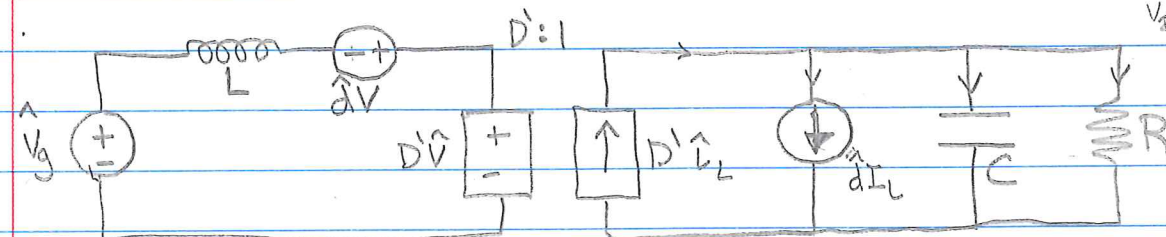

$$i) Z_{out}(s) = \frac{\hat{V}}{\hat{i}_{load}} \bigg|_{\substack{\hat{V}_g=0 \\ \hat{d}=0}}$$

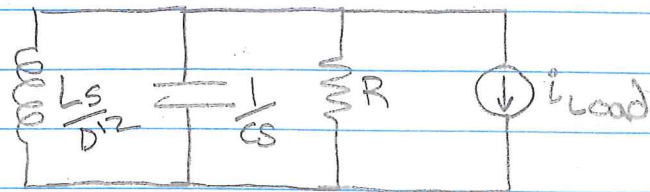

$$Z_{out}(s) = sL // \frac{1}{cs} // R$$


$$= \frac{L's \left[\frac{R}{Rcs+1} \right]}{L's + \frac{R}{Rcs+1}}$$

$$= \frac{L's R}{L'RCs^2 + L's + R}$$

$R // \frac{1}{cs} = \frac{R/cs}{R + 1/cs} = \frac{R}{Rcs + 1}$
 $L' = L/D^{1/2}$

$$\therefore Z_{out}(s) = \frac{LS/D^{1/2}}{\frac{LCS^2}{D^{1/2}} + \frac{Ls}{RD^{1/2}} + 1}$$

ii) $G_{vg}(s) = \frac{V}{V_g} \bigg|_{\hat{d}=0, i_{load}=0}$

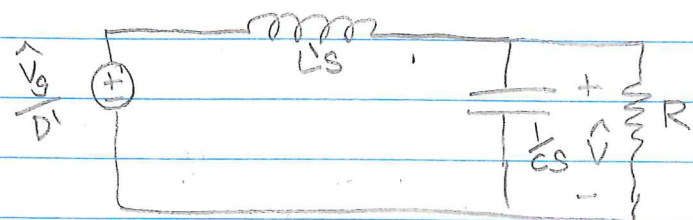

• Use voltage divider;


$$\hat{V} = \frac{\hat{V}_g}{D^1} \left[\frac{R/RCs+1}{Ls + R/RCs+1} \right]$$

$$= \frac{\hat{V}_g}{D^1} \left[\frac{R}{L'RCs^2 + L's + R} \right]$$


$$\therefore G_{vg}(s) = \frac{1}{D^1} \frac{1}{\frac{LCS^2}{D^{1/2}} + \frac{Ls}{RD^{1/2}} + 1} \checkmark$$

iii) $G_{vd}(s) = \frac{\hat{V}}{\hat{d}} \bigg|_{\hat{V}_g=0, i_{load}=0}$

• must use superposition

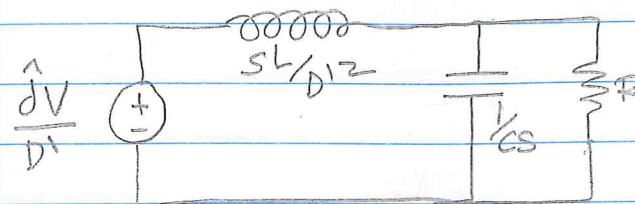
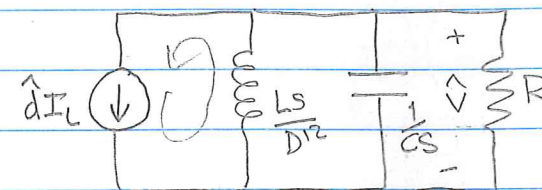
$$\frac{\hat{V}}{\hat{d}} = \frac{V}{D^1} \left[\frac{1}{\frac{LCS^2}{D^{1/2}} + \frac{Ls}{D^{1/2}R} + 1} \right]$$



$$\frac{\hat{V}}{\hat{d}} = \frac{-Ls/D^{1/2}}{\frac{LCS^2}{D^{1/2}} + \frac{Ls}{RD^{1/2}} + 1}$$

$$\therefore G_{vd} = \frac{\frac{V}{D^1} + \frac{Ls/D^{1/2}}{D^{1/2}}}{\frac{LCS^2}{D^{1/2}} + \frac{Ls}{RD^{1/2}} + 1}$$

$\frac{1}{2}$ 14/15

c) i) $VH(s) = V_{ref} \rightarrow H(s) = \frac{5}{100} = \frac{1}{20} \checkmark$

• select $R_1 = R_2 = \text{large}$

• Voltage divider on input

$$V_o = 100 \frac{R_2}{R_1 + R_2} \Rightarrow \frac{R_2}{R_1 + R_2} = \frac{1}{20} \therefore \begin{cases} R_2 = 10k \\ R_1 + R_2 = 200k \\ \therefore R_1 = 190k \end{cases} \checkmark$$


R_3 is to balance opamp?
 $R_3 = R_1 // R_2$

$\frac{2}{3}$

ii) Draw the PWM waveform

At DC steady-state desire $V_{comp} = 0$

$$D = 0.8$$

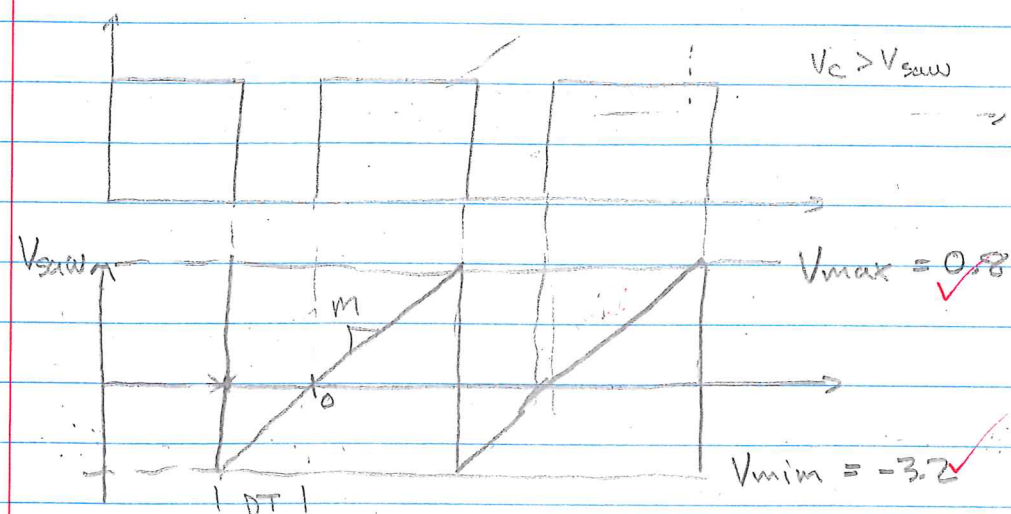

$$V_{saw}(0) = V_{min}$$


$$V_{saw}(T) = V_{max}$$

$$V_{saw}(DT) = 0 = V_{min} + MDT$$

$$\Rightarrow V_{min} = -MDT$$

$$M = \frac{(4)}{T} = 8 \times 10^5$$
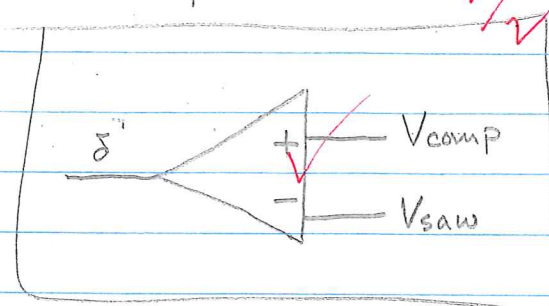
$$\therefore \begin{cases} V_{min} = -3.2 \text{ V} \\ V_{max} = 0.8 \text{ V} \end{cases}$$



Express the PWM TF;

$$V_{saw}(DT) = V_{min} + mDT = V_c \rightarrow \frac{\hat{d}}{V_c} = mT(D + \hat{d})$$

$$\frac{\hat{d}}{V_c} = \frac{1}{mT}$$

$$\therefore G_{pwm}(s) = \frac{1}{4}$$

$$iii) T_o(s) = H(s) G_{pwm}(s) G_{vd}(s)$$

$$= \left(\frac{1}{4}\right) \left(\frac{1}{20}\right) \frac{V}{D'} \left(1 - s \frac{L}{D'V}\right) \left(\frac{LCS^2}{D'^2} + \frac{L}{RD'}s + 1\right)$$

$$T_o(s) = G_{co} \frac{(1 - s/\omega_z)}{\left(\frac{s^2}{\omega_p^2} + \frac{1}{Q\omega_p} + 1\right)}$$


$$T_o(0) = G_{co} = \left(\frac{1}{4}\right) \left(\frac{1}{20}\right) \left(\frac{100}{0.2}\right) \rightarrow T_o(0) = 6.25 = 15.9 \text{ dB}$$

$$\omega_z = \frac{D'V}{L} = \frac{0.2(100)}{(1 \times 10^{-6})} \Rightarrow \omega_z = 2 \times 10^7 \text{ rad/s}$$

$$\omega_p^2 = \omega_o^2 = \left(\frac{D'^2}{LC}\right) = \frac{0.2^2}{(1 \times 10^{-6})(400 \times 10^{-6})} \Rightarrow \omega_o = 10,000 \text{ rad/s}$$

$$Q\omega_p = \frac{RD'^2}{L} \rightarrow Q = \frac{RD'}{L} \left(\frac{\sqrt{LC}}{D'}\right) = \frac{R}{\sqrt{L}} \sqrt{C} \rightarrow Q = 100 = 40 \text{ dB}$$

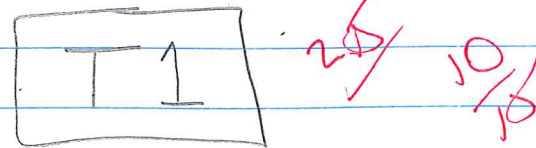iv) Select the plot that corresponds to $T_0(s)$;




d) ii) To reject disturbance we need high (∞) steady-state gain and high gain at low freq. To achieve the a PI controller can be used.

i) Desire a cross-over frequency of 1 kHz (100 krad/s). To do this the $T_0(s)$ must be shifted up by ~ 24 dB. The stability at this point is marginal $\therefore$ Phase margin needs to be increased. $\frac{4}{4}$

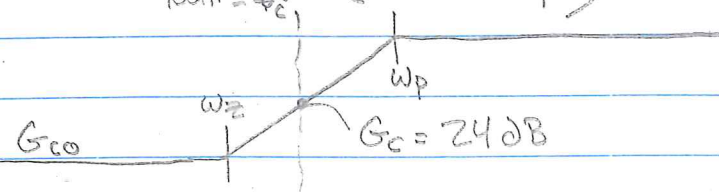ii) A PD controller must be selected b/c phase margin must be added to ensure stability at the desired crossover frequency of 1 kHz. With this controller there will still be some disturbances at low freq. To ^{further limit} remove these a PID should be used. $\frac{4}{4}$

$$iii) G_c(s) = G_{co} \frac{(1 + s/\omega_z)}{(1 + s/\omega_p)}$$




Select the following values for $\omega_c = 100 \text{ krad/s}$;

$$\omega_z = 10 \text{ krad/s}$$

$$\omega_p = 1 \text{ M rad/s}$$

$$\text{dB} = 20 \log(\text{Mag})$$

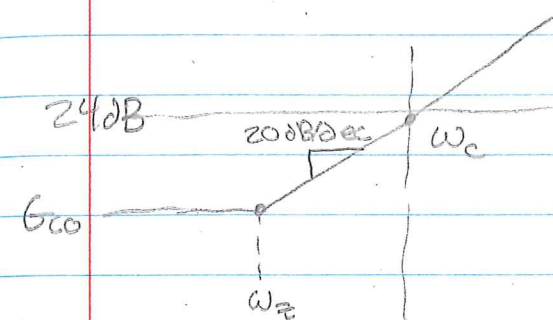

... must remember how to work w/ log plots ...

$$24 = G_{co} + 10 \left(\frac{24}{20} \right)$$

$$\therefore G_{co} = 8.15 \text{ dB}$$


$$G_{co} = 24 \text{ dB}$$

$$G_{co} = 1.58$$

good work though!

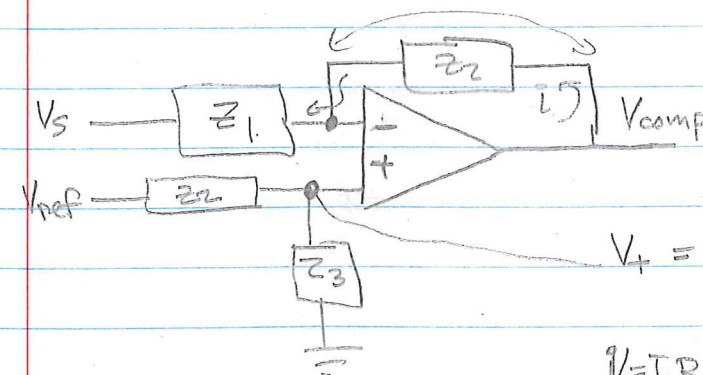iv) Calculate Resistor and Cap. Values

$$G_c = G_{co} \frac{(1 + s/\omega_z)}{(1 + s/\omega_p)}$$



$$V_+ = \frac{Z_3}{Z_2 + Z_3} = V_-$$

$$V = IR \Rightarrow I = \frac{V_+ - V_-}{Z_1}$$

$$V_{comp} = \frac{V_+ - V_{comp}}{Z_2}$$

... times up

$$\frac{1.5}{3} = \frac{12.5}{15}$$

$$\hat{i}_L(dT) = \hat{i}_L(0) + m_1 dT = \hat{i}_c$$

$$\hat{i}_c = 0 = \hat{i}_L(0) + m_1 T \hat{d} \rightarrow \hat{d} = -\frac{\hat{i}_L(0)}{m_1 T}$$

$$\hat{i}_L(t) = \hat{i}_L(0) + \mathcal{F}\left(-\frac{\hat{i}_L(0)}{m_1 T}\right)(m_1 - m_2)$$

$$\hat{i}_L(0) \cancel{u(0)} = -\hat{i}_L(0) + \frac{m_2}{m_1} \hat{i}_L(0)$$



$$\hat{i}_L(T) = \hat{i}_L(0) \left[\frac{m_2}{m_1} \right]$$


$$\hat{i}_L(T) = \hat{i}_L(0) \left[\frac{D}{D'} \right]$$

$$\hat{i}_L(nT) = \hat{i}_L(0) \left[\frac{D}{D'} \right]^n \text{ for stability } \frac{D}{D'} < 1$$

$$\frac{D}{D'} < 1 \rightarrow D < 1-D \rightarrow 2D < 1 \rightarrow \boxed{D < 0.5}$$


Problem 3

a)

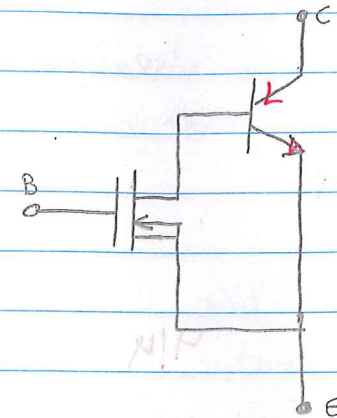

- Advantage over MOSFET:
 - Higher blocking voltage
 - Higher efficiency b/c minority carrier.
- Advantage over BJT:
 - Higher efficiency B/c no Base current ~~5.3/4~~ ^{3.4/4}

c)

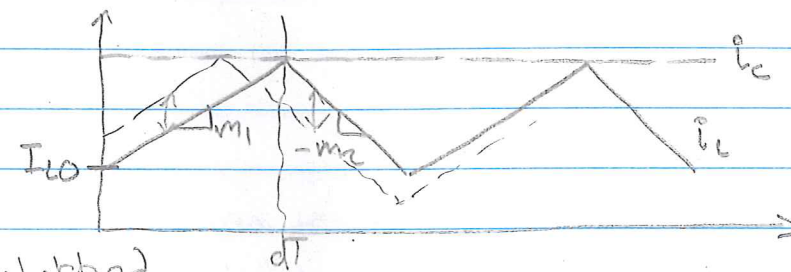

• perturbed

$$\hat{i}_L(dT) = \hat{i}_L(0) + m_1 dT = \hat{i}_c$$

$$\hat{i}_c = \hat{i}_L(dT) = \hat{i}_L(0) + m_1 T(D + \hat{d}) = I_{L0} + \hat{i}_L(0) + m_1 T D + m_1 T \hat{d}$$

$$\hat{i}_L(T) = \hat{i}_L(dT) - m_2 d'T$$

$$\hat{i}_L(T) = I_{L0} + \hat{i}_L(0) + m_1 T(D + \hat{d}) - m_2 T(D' - \hat{d})$$

$$\cancel{I_{L0}} + \hat{i}_L(T) = \cancel{I_{L0}} + \hat{i}_L(0) + m_1 T D + m_1 T \hat{d} - \underbrace{m_2 T D'}_{m_1 T D/D'} - m_2 T \hat{d}$$

$$\hat{i}_L(T) = \hat{i}_L(0) \left(\frac{m_1}{m_2} \right)$$

$$\hat{i}_L(T) = \hat{i}_L(0) + m_1 T \hat{d} - m_2 T \hat{d} = \hat{i}_L(0) + T \hat{d} (m_1 - m_2)$$

• Eliminate $\hat{d}$; $\hat{i}_L(0) =$

steady-state

$$I(0T) = I_{L0} + m_1 DT$$

$$\hat{i}_c = I_{L0} + m_1 DT$$

$$I(T) = I(0T) - m_2 D'T$$

$$I_{L0} = I_{L0} + m_1 DT - m_2 D'T$$

$$D m_1 = m_2 D'$$

$$\frac{m_1}{m_2} = \frac{D'}{D}$$


- d) • Simpler dynamics to control. $T_o(s)$ is lower order ✓
 • Can take advantage ✓ of circuitry already likely present which monitors Transistor current.
 4/14

- g) High Efficiency is desired b/c
 • Don't want to generate heat 4/14
 • Don't want to waste power. Want the load to use / dissipate the power not the converter

- f) Top 1
 $V_T = V_g$
 $I_c = I_s - V/R$
 • Assume I_m is negligible
 • Condition for stability is that the I_m must reset

Top 2
 $V_T = -V_g$

Top 3 ($I_m < 0$)
 $V_T = 0$

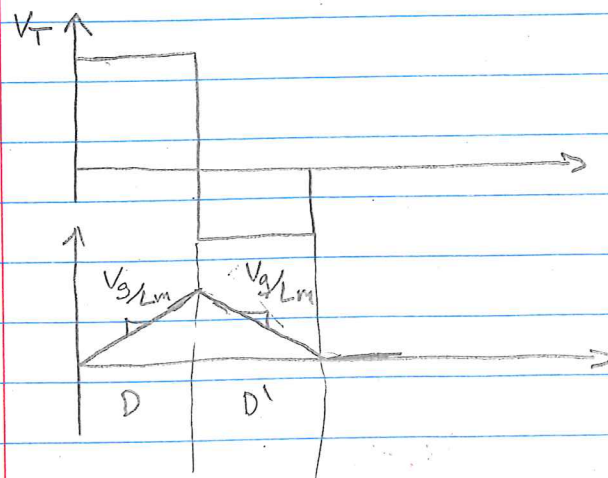


- For this setup $M_1 = -M_2$
 ∴ for I_m to properly reset

$$M_1 < M_2$$

$$\therefore \boxed{D < 0.5}$$

4/14

(8)

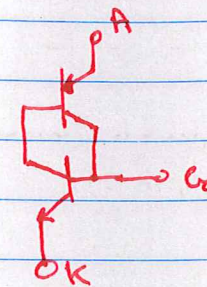

- Cannot be turned off b/c of a positive feedback loop between the two transistors.

- (e) • Required for Safety. The transformer acts as an interface that restricts Powerflow.
 • Put inside the device b/c it operates at a higher frequency, which allows us to use a much smaller transformer core → Less flux required (according to Faraday's law).

- (h) The ripple in the inductor is greater than its average current. A switch in the device prevents reverse current flow, so the circuit enters a topology where there is no current through the inductor (and thus, no voltage across it).

The tendency of a circuit to enter this state is related to the size of the inductor. If we are okay with the gain that our converter produces (i.e. less inductive) in PCM we can use a smaller inductor.

