

Boolean Algebra and Logic Gates
Chapter 2

EECE 256
Dr. Sidney Fels
Steven Oldridge

Topics

- Definitions of Boolean Algebra
- Axioms and Theorems of Boolean Algebra
 - two valued Boolean Algebra
- Boolean Functions
 - simplification
- Canonical forms
 - minterm and maxterms
- Other logic gates

9/18/10 (c) S. Fels, since 2010 2

Boolean Algebra

- Allows us to define and simplify functions of binary variables
- Important for designers to create complex circuits
 - functions of computer
 - ASIC devices
 - programmable logic
 - determine machine state transitions

9/18/10 (c) S. Fels, since 2010 3

Boolean Algebra

- Adheres to the laws of an algebra
 - closure
 - associative
 - commutative
 - identity
 - inverse
 - distributive
 - + for addition (0 is identity)
 - for multiplication (1 is identity)

9/18/10 (c) S. Fels, since 2010 4


Axioms of Boolean Algebra

- closure for + and •
- Identity:
 - $x + 0 = x$ $x \bullet 1 = x$
- commutative
 - $x + y = y + x$ $x \bullet y = y \bullet x$
- distributive
 - $x(y + z) = xy + xz$ $x + (y \bullet z) = (x + y) \bullet (x + z)$

9/18/10 (c) S. Fels, since 2010 5

Axioms of Boolean Algebra

- Complement
 - $x + x' = 1$ $x \bullet x' = 0$
- two elements for Two-Valued Boolean Algebra
 - 0 and 1; $0 \neq 1$
 - AND = •, OR = +, NOT = inverse
 - check with Truth tables and you'll see it meets all the axioms
- switching algebra (Shannon, 1928)
 - basis of all digital computers
- Precedence:
 - parentheses, NOT, AND, OR



9/18/10 (c) S. Fels, since 2010

Theorems and Properties of Boolean Algebra

Table 2.1
Postulates and Theorems of Boolean Algebra

Postulate 2 identity	(a)	$x + 0 = x$
Postulate 5 complement	(a)	$x + x' = 1$
Theorem 1 idempotent	(a)	$x + x = x$
Theorem 2 0 and 1 ops	(a)	$x + 1 = 1$
Theorem 3, involution		$(x')' = x$
Postulate 3, commutative	(a)	$x + y = y + x$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$
Theorem 6, absorption	(a)	$x + xy = x$

9/18/10 (c) S. Fels, since 2010 7

Theorems and Properties of Boolean Algebra

Table 2.1
Postulates and Theorems of Boolean Algebra

Postulate 2 identity	(a)	$x + 0 = x$
Postulate 5 complement	(a)	$x + x' = 1$
Theorem 1 idempotent	(a)	$x + x = x$
Theorem 2 0 and 1 ops	(a)	$x + 1 = 1$
Theorem 3, involution	(a)	$(x')' = x$
Postulate 3, commutative	(a)	$x + y = y + x$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$
Theorem 6, absorption	(a)	$x + xy = x$

Duality: interchange 0 for 1 and AND and OR

9/18/10 (c) S. Fels, since 2010 8

Theorems and Properties of Boolean Algebra

Table 2.1
Postulates and Theorems of Boolean Algebra

Postulate 2 identity	(a)	$x + 0 = x$	(b)	$x \cdot 1 = x$
Postulate 5 complement	(a)	$x + x' = 1$	(b)	$x \cdot x' = 0$
Theorem 1 idempotent	(a)	$x + x = x$	(b)	$x \cdot x = x$
Theorem 2 0 and 1 ops	(a)	$x + 1 = 1$	(b)	$x \cdot 0 = 0$
Theorem 3, involution		$(x')' = x$		
Postulate 3, commutative	(a)	$x + y = y + x$	(b)	$xy = yx$
Theorem 4, associative	(a)	$x + (y + z) = (x + y) + z$	(b)	$x(yz) = (xy)z$
Postulate 4, distributive	(a)	$x(y + z) = xy + xz$	(b)	$x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a)	$(x + y)' = x'y'$	(b)	$(xy)' = x' + y'$
Theorem 6, absorption	(a)	$x + xy = x$	(b)	$x(x + y) = x$

Duality: interchange 0 for 1 and AND and OR

Theorems used to simplify complex functions of binary variables

9/18/10 (c) S. Fels, since 2010 9

Useful Theorems

- Simplification Theorems:
 - $X \cdot Y + X \cdot Y' = X$
 - $X + X \cdot Y = X$
 - $(X + Y') \cdot Y = Y'$
- **DeMorgan's Law:**
 - $(X + Y)' = X' \cdot Y'$
- Theorems for Multiplying and Factoring:
 - $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$
- Proofs by algebra complicated
 - use truth tables instead

9/18/10 (c) S. Fells, since 2010 10

Some algebraic proofs

Proving Theorems via axioms of Boolean Algebra:

e.g., Prove: $X \cdot Y + X \cdot Y' = X$

e.g., Prove: $X + X \cdot Y = X$

e.g., Prove: $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$

9/18/10 (c) S. Fells, since 2010 11

Some algebraic proofs

Proving Theorems via axioms of Boolean Algebra:

e.g., Prove: $X \cdot Y + X \cdot Y' = X$

LHS = $X(Y + Y')$ distributive
 = $X(1)$ complement
 = $X =$ RHS identity

e.g., Prove: $X + X \cdot Y = X$

LHS = $X(1 + Y)$ distributive
 = $X(1)$ identity
 = $X =$ RHS

9/18/10 (c) S. Fells, since 2010 12

Some algebraic proofs

e.g., Prove: $(X + Y) \cdot (X' + Z) = X \cdot Z + X' \cdot Y$
 LHS = $(X+Y)X' + (X+Y)Z$ distributive
 = $XX' + YX' + XZ + YZ$ distributive
 = $0 + X'Y + XZ + YZ$ complement, associative, distributive
 = $X'Y(Z + Z') + XZ(Y + Y') + YZ(X + X')$ identity/complement
 = $X'YZ + X'YZ' + XYZ + XY'Z + XYZ + X'YZ$ distributive, associative
 = $XZ(Y+Y') + X'Y(Z+Z')$ idempotent, associative, distributive
 = $XZ + X'Y =$ RHS complement

Some proofs using truth tables

DeMorgan's Law
 $(X + Y)' = X' \cdot Y'$

X	Y	X'	Y'	$(X+Y)$	$(X+Y)'$	$X' \cdot Y'$
0	0	1	1	0	1	1
0	1	1	0	1	0	0
1	0	0	1	1	0	0
1	1	0	0	1	0	0

$(X \cdot Y)' = X' + Y'$

X	Y	X'	Y'	$(X \cdot Y)$	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	0	1	1
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	1	0	0

Some proofs using truth tables

DeMorgan's Law
 $(X + Y)' = X' \cdot Y'$

X	Y	X'	Y'	$(X+Y)$	$(X+Y)'$	$X' \cdot Y'$
0	0	1	1	0	1	1
0	1	1	0	1	0	0
1	0	0	1	1	0	0
1	1	0	0	1	0	0

$(X \cdot Y)' = X' + Y'$

X	Y	X'	Y'	$(X \cdot Y)$	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	0	1	1
0	1	1	0	0	1	1
1	0	0	1	0	1	1
1	1	0	0	1	0	0

DeMorgan's Theorem

Example:

$$Z = A'B'C + A'BC + AB'C + ABC'$$

$$Z' = (A+B+C') \cdot (A+B'+C') \cdot (A'.....$$

9/18/10

(c) S. Fels, since 2010

16

Boolean Functions

- Now, we have everything to make Boolean Functions
 - $F = f(x,y,z,...)$ where x, y, z etc. are binary values (0,1) with Boolean operators
 - circuits can implement the function
 - algebra used to simplify the function to make it easier to implement

9/18/10

(c) S. Fels, since 2010

17

Example

- $F_1 = x + y'z$

x	y	z	$y'z$	$x+y'z$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

9/18/10

(c) S. Fels, since 2010

18

Example

- $F_1 = x + y'z$

x	y	z	$y'z$	$x+y'z$
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	0	0	1
1	1	1	0	1

9/18/10 (c) S. Fels, since 2010 19

Simplification allows for different implementations

- $F = AB + C(D + E)$ requires 3 levels of gates

9/18/10 (c) S. Fels, since 2010 20

2-level implementation

- $F = AB + C(D + E) = AB + CD + CE$

9/18/10 (c) S. Fels, since 2010 21

Canonical Forms

- Express all Boolean functions as one of two canonical forms
 - enumerates all combinations of variables as either
 - Sum of Products, i.e., $m_1 + m_2 + m_3 \dots$ etc
 - Product of Sums, i.e., $M_1 \cdot M_2 \cdot M_3 \dots$ etc
 - each variable appears in normal form (x) or its complement (x')
 - if it is a product it is called a MINTERM
 - if it is a sum it is called a MAXTERM
 - n variables $\rightarrow 2^n$ MINTERMS or MAXTERMS

9/18/10

(c) S. Fels, since 2010

22

Canonical Forms

Table 2.3
Minterms and Maxterms for Three Binary Variables

			Minterms		Maxterms	
x	y	z	Term	Designation	Term	Designation
0	0	0	$x'y'z'$	m_0	$x + y + z$	M_0
0	0	1	$x'y'z$	m_1	$x + y + z'$	M_1
0	1	0	$x'yz'$	m_2	$x + y' + z$	M_2
0	1	1	$x'yz$	m_3	$x + y' + z'$	M_3
1	0	0	$xy'z'$	m_4	$x' + y + z$	M_4
1	0	1	$xy'z$	m_5	$x' + y + z'$	M_5
1	1	0	xyz'	m_6	$x' + y' + z$	M_6
1	1	1	xyz	m_7	$x' + y' + z'$	M_7

9/18/10

(c) S. Fels, since 2010

23

Canonical Form Example

Table 2.4
Functions of Three Variables

x	y	z	Function f_1	Function f_2
0	0	0	0	0
0	0	1	1	0
0	1	0	0	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

9/18/10

(c) S. Fels, since 2010

24

Canonical Form Example

Table 2.4
Functions of Three Variables

x	y	z	Function f_1	Function f_2
0	0	0	0	0
0	0	1	1 m1	0
0	1	0	0	0
0	1	1	0	1 m3
1	0	0	1 m4	0
1	0	1	0	1 m5
1	1	0	0	1 m6
1	1	1	1 m7	1 m7

9/18/10

(c) S. Fels, since 2010

25

Canonical Form Example: Sum of Products (Minterms)

- So we can read off of TT directly
- Sum of products is sum of Minterms

$$\sum m_i$$

$$F1 = m1 + m4 + m7$$

$$= x'y'z + xy'z' + xyz$$

$$F2 = m3 + m5 + m6 + m7$$

$$= x'yz + xy'z + xyz' + xyz$$

9/18/10

(c) S. Fels, since 2010

26

Canonical Form Example

Table 2.4
Functions of Three Variables

x	y	z	Function f_1	Function f_2
0	0	0	0 M0	0 M0
0	0	1	1	0 M1
0	1	0	0 M2	0 M2
0	1	1	0 M3	1
1	0	0	1	0 M4
1	0	1	0 M5	1
1	1	0	0 M6	1
1	1	1	1	1

9/18/10

(c) S. Fels, since 2010

27

Canonical Form Example: Product of Sums (Maxterms)

- So we can read off of TT directly
- Product of sums is product of Maxterms

$$\prod M_i$$

$$F1 = M0 \cdot M2 \cdot M3 \cdot M5 \cdot M6$$

$$= (x + y + z)(x + y' + z)(x + y' + z')(x' + y + z')(x' + y' + z)$$

$$F2 = M0 \cdot M1 \cdot M2 \cdot M4$$

$$= (x+y+z)(x+y+z')(x+y'+z)(x'+y+z)$$

9/18/10 (c) S. Fels, since 2010 28


Converting between them

- You can use complement and deMorgan's theorem
 - if $F = m1 + m3 + m5$ i.e. $\Sigma(1, 3, 5)$ then
 - $F' = m0 + m2 + m4 + m6 + m7$
 - $F = (m0 + m2 + m4 + m6 + m7)'$
 - use DeMorgan's now to get Product of Sum
 - $F = \Pi(0,2,4,6,7)$
- Remember to include all Minterms/Maxterms
 - n variables, 2^n terms


9/18/10 (c) S. Fels, since 2010 29

Standard form

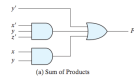- Sum of Products with one, two, three or more variables in product form
 - $F1 = y' + xy + x'yz'$



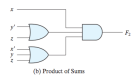- Product of Sum with one, two, three or more variables in sum form
 - $F2 = x \cdot (y'+z) \cdot (x'+y+z')$



- Notice: canonical and standard form are 2-level implementations
 - but may have many inputs for gate
 - called fan-in; limited by pins on IC and manufacturing

9/18/10 (c) S. Fels, since 2010 30

Other logical operations

- for 2 input gates, you can have 16 different logic operations 2^{2^n} where $n = 2$

Table 2.7
Truth Tables for the 16 Functions of Two Binary Variables

x	y	F_0	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}
0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	1	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

Other logical operations

Table 2.8
Boolean Expressions for the 16 Functions of Two Variables

Boolean Functions	Operator Symbol	Name	Comments
$F_0 = 0$		Null	Binary constant 0
$F_1 = xy$	$x \cdot y$	AND	x and y
$F_2 = xy'$	xy'	Inhibition	x, but not y
$F_3 = x$		Transfer	x
$F_4 = x'y$	y/x	Inhibition	y, but not x
$F_5 = y$		Transfer	y
$F_6 = xy' + x'y$	$x \oplus y$	Exclusive-OR	x or y, but not both
$F_7 = x + y$	$x + y$	OR	x or y
$F_8 = (x + y)'$	$x \downarrow y$	NOR	Not-OR
$F_9 = xy + x'y'$	$(x \oplus y)'$	Equivalence	x equals y
$F_{10} = y'$		Complement	Not y
$F_{11} = x + y'$	$x \supset y$	Implication	If y, then x
$F_{12} = x'$		Complement	Not x
$F_{13} = x' + y$	$x \supset y$	Implication	If x, then y
$F_{14} = (xy)'$	$x \uparrow y$	NAND	Not-AND
$F_{15} = 1$		Identity	Binary constant 1

Digital Logic Gates

Name	Graphic symbol	Algebraic function	Truth table															
AND		$F = xy$	<table border="1"><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$F = x + y$	<table border="1"><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	1
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
Inverter		$F = x'$	<table border="1"><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	x	F	0	1	1	0									
x	F																	
0	1																	
1	0																	
Buffer		$F = x$	<table border="1"><tr><th>x</th><th>F</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	x	F	0	0	1	1									
x	F																	
0	0																	
1	1																	
NAND		$F = (xy)'$	<table border="1"><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$F = (x + y)'$	<table border="1"><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	0
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
Exclusive-OR (XOR)		$F = xy' + x'y = x \oplus y$	<table border="1"><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	x	y	F	0	0	0	0	1	1	1	0	1	1	1	0
x	y	F																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
Exclusive-NOR (XNOR) equivalence		$F = (x \oplus y)' = xy + x'y'$	<table border="1"><tr><th>x</th><th>y</th><th>F</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	x	y	F	0	0	1	0	1	0	1	0	0	1	1	1
x	y	F																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

Extending to multiple inputs

- works fine for
 - AND, OR; no problem – commute and associate
 - NAND, NOR – commute but don't associate ☹
 - so, be careful when using them cascaded
 - instead:
 - define multi-input NAND as multi-input AND that is inverted at the end
 - » $x \text{ NAND } y \text{ NAND } z = (xyz)'$
 - define multi-input NOR as multi-input OR that is inverted at the end
 - » $x \text{ NOR } y \text{ NOR } z = (x+y+z)'$

9/20/10
(c) S. Fels, since 2010
34

Extending to multiple inputs

x

y

$(x \downarrow y) \downarrow z = (x + y)z'$

x

y

z

$x \downarrow (y \downarrow z) = x'(y + z)$

9/20/10
(c) S. Fels, since 2010
35

Extending to multiple inputs

(a) 3-input NOR gate

(b) 3-input NAND gate

A

B

C

D

E

$F = [(ABC)' \cdot (DE)']' = ABC + DE$

(c) Cascaded NAND gates

9/21/10
(c) S. Fels, since 2010
36

Summary

- two-valued Boolean algebra supports
 - switching logic
 - simplification postulates and theorems
 - digital logic gates
- Truth tables can be used to define function
- Canonical and standard forms make it easy to create functions that can be implemented
- finite number of 2 input gates
 - easy to implement larger complex functions
- 2 input gates can be extended to multiple inputs

9/21/10

(c) S. Fels, since 2010

37



9/21/10

(c) S. Fels, since 2010

38
