

# Memory and Programmable Logic

Chapter 7  
Steve Oldridge  
Dr. Sidney Fels

---

---

---

---

---

---

---

---

## Topics

- Random Access Memory (RAM)
- Memory Decoding
- Error Detection & Correction
- Read-Only Memory (ROM)
- Programmable Logic Array
- Programmable Array Logic
- Sequential Programmable Devices

---

---

---

---

---

---

---

---

## Memory

- RAM
  - Write and Read from the system
- ROM
  - Read from the system
  - Written during configuration
- Programmable Logic Device
  - ROM
  - PLA
  - FPGA



(a) Conventional symbol



(b) Array logic symbol

---

---

---


---

---

---

---

---

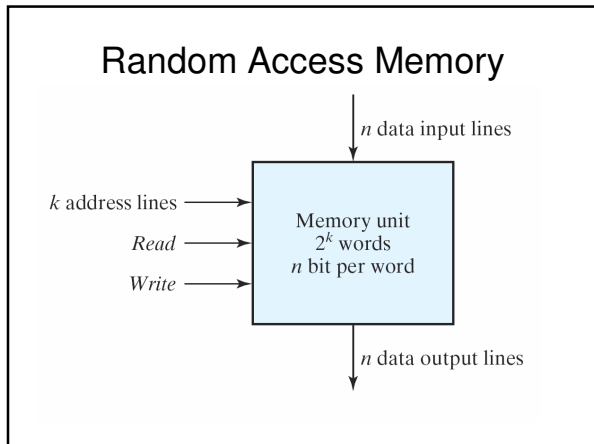


---

---

---

---

---

---

---

---

### Memory Content

Memory address		Memory content
Binary	Decimal	
000000000	0	1011010101011101
000000001	1	1010101110001001
000000010	2	0000110101000110
	⋮	⋮
111111101	1021	1001110100010100
111111110	1022	0000110100011110
111111111	1023	110111000100101

---

---

---

---

---

---

---

---

- ### Read & Write Ops
- Read
    - Set the binary address lines
    - Activate the Read signal
  - Write
    - Set the binary address lines
    - Set the input
    - Activate Write

---

---

---

---

---

---

---

---

## Memory Control

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word

---

---

---

---

---

---

---

---

## HDL Memory

---

---

---

---


---

---

---

---

## Timing Waveforms

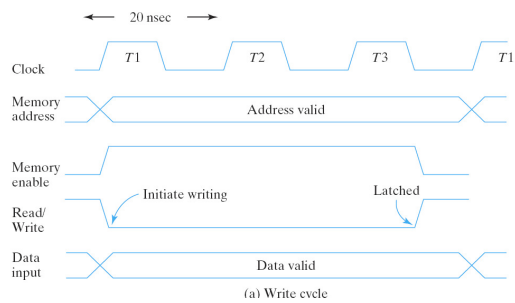


---

---

---

---


---

---

---

---

## Timing Waveforms (Read)

 


---

---

---

---

---

---

---

---

## Types of Memories

- Sequential Access Memory
- Static RAM
  - Latches store the values
- Dynamic RAM
  - Electric charge stored on capacitors
  - Capacitors must be periodically refreshed
- ROM
  - Nonvolatile memory

---

---

---

---


---

---

---

---

## Binary Memory Cells

 


---

---

---


---

---

---

---

---

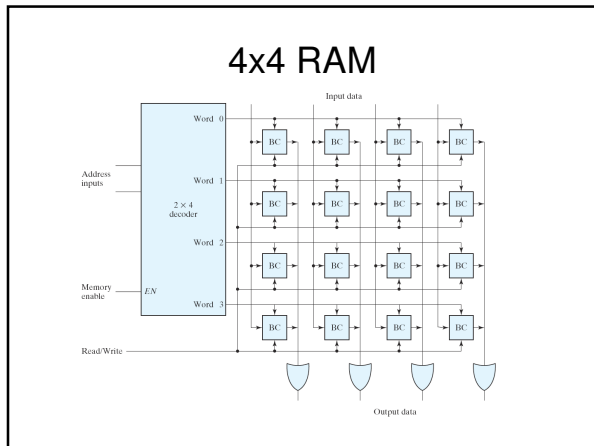


---

---

---


---

---

---

---

---

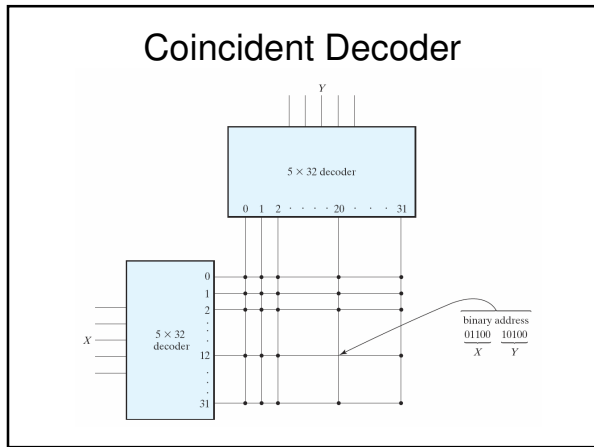


---

---

---


---

---

---

---

---

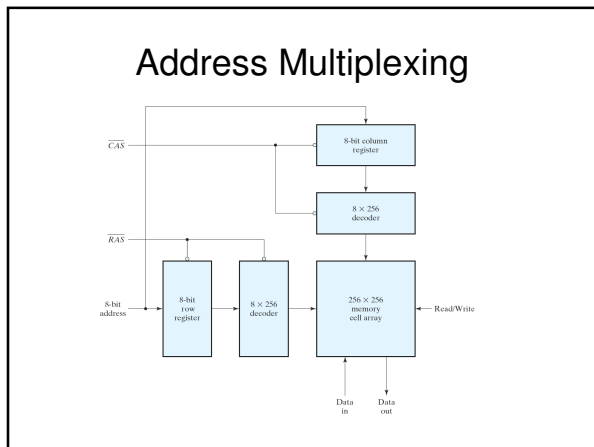


---

---

---

---

---

---

---

---

## Error Detection and Correction

- Hamming Code
  - K 'parity' bits are added to an N bit word
  - Bits have a particular calculable value
- Positioned in Powers of 2
  - 1, 2, 4, 8

---

---

---

---

---

---

---

---

## Hamming Code Example

- 11000100
- $P_1 P_2 1 P_4 100 P_8 0100$
- $P_1 = \text{XOR}(3,5,7,9,11)$
- $P_2 = \text{XOR}(3,6,7,10,11)$
- $P_3 = \text{XOR}(5,6,7,12)$
- $P_4 = \text{XOR}(9,10,11,12)$

---

---

---

---

---

---

---

---

## Hamming Code Check

- 001110010100
- $C_1 = \text{XOR}(1,3,5,7,9,11)$
- $C_2 = \text{XOR}(2,3,6,7,10,11)$
- $C_3 = \text{XOR}(4,5,6,7,12)$
- $C_4 = \text{XOR}(8,9,10,11,12)$

---

---

---

---

---

---

---

---

## Hamming Code continued

- How do we determine Parity and Check equations for other size numbers?
- Determine the numbers from  $[0, 2^k-1]$ 
  - Least significant bit is 1 for (1,3,5,7 etc.)
  - Bit 1 is a 1 for (2,3,6,7 etc.)

---

---

---

---

---

---

---

---

## Single Error Correction, Double Error Detection

- 001110010100P<sub>13</sub>
- P<sub>13</sub>= XOR of all 12 bits
  - Tells us if there was only one error or not
- If C=0, P=0 No Error
- If C!=0, P=1 Only 1 error, Correct it
- If C!=0, P=0 More than one Error
- If C=0, P=1 Error occurred in P<sub>13</sub>

---

---

---

---

---

---

---

---

## Size of Parity

*Range of Data Bits for k Check Bits*

Number of Check Bits, $k$	Range of Data Bits, $n$
3	2–4
4	5–11
5	12–26
6	27–57
7	58–120

---

---

---

---

---


---

---

---
 
## Read Only Memory

- Permanent Storage
- Allows for configuration of devices to be stored on device without requiring load




---

---

---

---


---

---

---

---

## 32x8 ROM

 


---

---

---

---

---

---

---

---

## ROM Truth Table

Inputs					Outputs							
$I_4$	$I_3$	$I_2$	$I_1$	$I_0$	$A_7$	$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
			⋮						⋮			
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	1	0	0	0	1	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

---

---

---

---


---

---

---

---



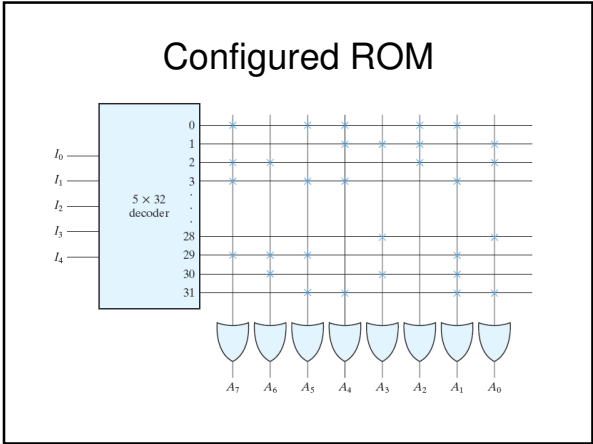


---

---

---


---

---

---

---

---

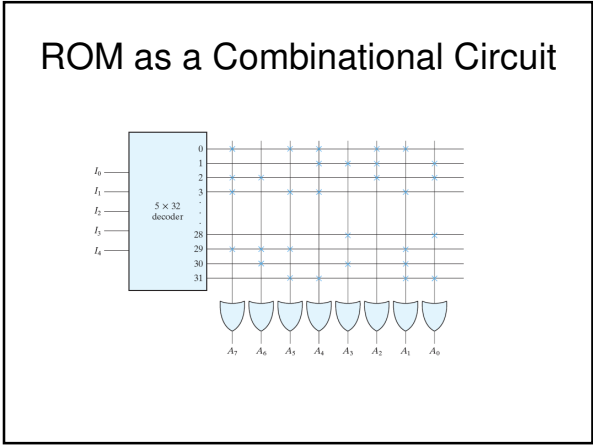


---

---

---

---

---

---

---

---

### ROM 'Circuit' Example

Inputs			Outputs							Decimal
$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$	$B_1$	$B_0$		
0	0	0	0	0	0	0	0	0	0	
0	0	1	0	0	0	0	0	1	1	
0	1	0	0	0	0	1	0	0	4	
0	1	1	0	0	1	0	0	1	9	
1	0	0	0	1	0	0	0	0	16	
1	0	1	0	1	1	0	0	1	25	
1	1	0	1	0	0	1	0	0	36	
1	1	1	1	1	0	0	0	1	49	

---

---

---

---


---

---

---

---

## ROM 'Circuit' Example

 

$A_2$	$A_1$	$A_0$	$B_5$	$B_4$	$B_3$	$B_2$
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	1
0	1	1	0	0	1	0
1	0	0	0	1	0	0
1	0	1	0	1	1	0
1	1	0	1	0	0	1
1	1	1	1	1	0	0

(b) ROM truth table

---

---

---

---

---

---

---

---

---

---

---

---

## 4 Types of ROMs

- Mask Programming
  - Done during the fab process
- Programmable ROM (PROM)
  - All fuses are intact (set to 1) and are 'Blown'
- Erasable PROM (EPROM)
  - Ultraviolet light used to reprogram
- Electronically Erasable PROM (EEPROM)
  - Programmed connections can be erased via signal

---

---

---

---

---

---

---

---




---

---

---

---

## Combinational PLDs

   


---

---

---

---

---

---

---

---


---

---

---

---

## Programmable Logic Arrays

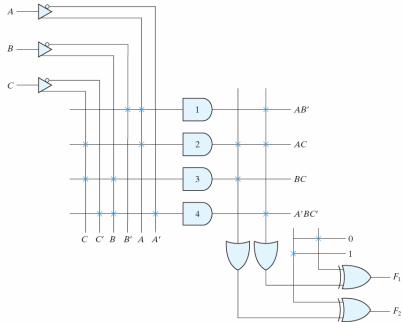


---

---

---

---

---

---

---

---

## Programming PLAs

Product Term		Inputs			Outputs	
		A	B	C	F <sub>1</sub>	F <sub>2</sub>
AB'	1	1	0	—	1	—
AC	2	1	—	1	1	1
BC	3	—	1	1	—	1
A'BC'	4	0	1	0	1	—

---

---

---

---

---

---

---

---

## PLA Example

- $F_1(ABC) = \text{Sum}(0,1,2,4)$
- $F_2(ABC) = \text{Sum}(0,5,6,7)$

---

---

---

---

---

---

---

---

PLA programming table

Product term	Inputs <i>A B C</i>	Outputs (C) (T)	
		$F_1$	$F_2$
$AB$	1		
$AC$	2		
$BC$	3		
$A'B'C'$	4		

---

---

---


---

---

---

---

---

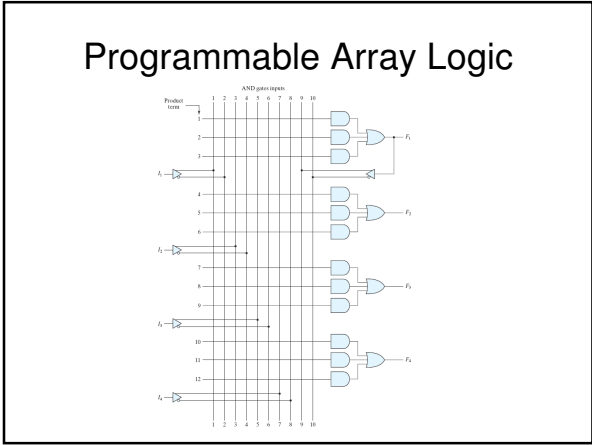


---

---

---

---

---

---

---

---

### Example

- $X = A + BCD$
- $Y = A'B + CD + B'D'$
- $Z = ABC' + A'B'CD' + AC'D' + A'B'C'D$
  
- $W = ABC' + A'B'CD'$
- $Z = W + AC'D' + A'B'C'D$

---

---

---

---

---

---

---

---

## PAL Programming Table

Product Term	AND Inputs				w	Outputs
	A	B	C	D		
1	1	1	0	—	—	$w = ABC' + A'B'CD'$
2	0	0	1	0	—	
3	—	—	—	—	—	$x = A + BCD$
4	1	—	—	—	—	
5	—	1	1	1	—	
6	—	—	—	—	—	$y = A'B + CD + B'D'$
7	0	1	—	—	—	
8	—	—	1	1	—	
9	—	0	—	0	—	$z = w + AC'D' + A'B'C'D$
10	—	—	—	—	1	
11	1	—	0	0	—	
12	0	0	0	1	—	

---

---

---

---

---

---

---

---


---

---

---

---

## Configured PAL

 


---

---

---

---

---

---

---

---

---

---

---

---

## Sequential Programmable Devices

- Sequential Programmable Logic Device (SPLD)
- Complex Programmable Logic Device (CPLD)
- Field Programmable Gate Array (FPGA)

---

---

---

---

---

---

---

---


---

---

---

---

## SPLDs

 

---

---

---

---


---

---

---

---

## SPLD Macrocell

 

---

---

---

---


---

---

---

---

## CPLD

 

---

---

---


---

---

---

---

---

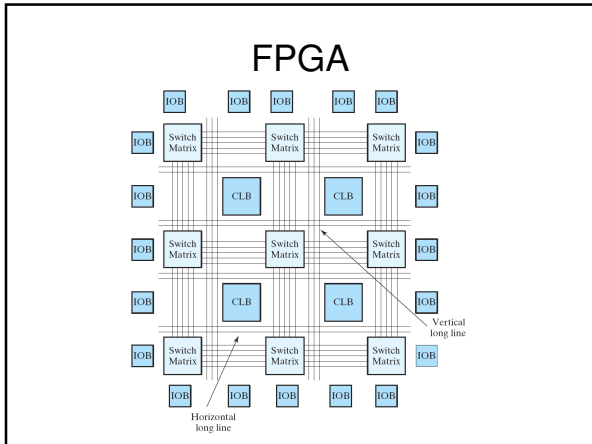


---

---

---

---

---

---

---

---

- ### FPGA CAD
- Synthesis
    - How can we best fit our design onto the device?
  - Placement
    - Which blocks should go next to each other?
  - Routing
    - How can we connect the wires that need connecting?

---

---

---


---

---

---

---

---

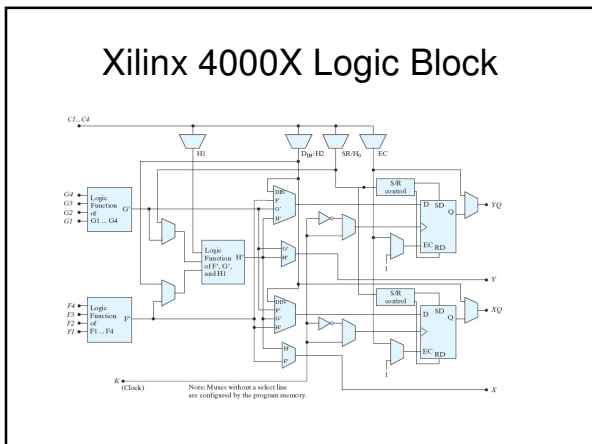


---

---

---

---


---

---

---

---

## Switch Block Interconnect

 


---



---



---



---



---




---



---

## PIPs at the Switch

 


---



---



---



---



---




---



---

## I/O Blocks

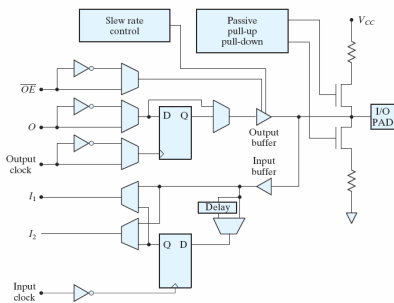


---



---



---



---



---




---



---



## LUT as Memory

 


---

---

---

---

---

---

---

---

## Spartan XL Device Family

Attributes of the Xilinx Spartan XL Device Family

Spartan XL	XC505/XL	XC510/XL	XC520/XL	XC530/XL	XC540/XL
System Gates <sup>1</sup>	2K-5K	3K-10K	7K-20K	10K-30K	13K-40K
Logic Cells <sup>2</sup>	238	466	950	1,368	1,862
Max Logic Gates	3,000	5,000	10,000	13,000	20,000
Flip-Flops	360	616	1,120	1,536	2,016
Max RAM Bits	3,200	6,272	12,800	18,432	25,088
Max Avail I/O	77	112	160	192	224

<sup>1</sup> 20-30% of CLBs as RAM.

<sup>2</sup> 1 Logic cell = four-input lookup table + flip-flop.

---

---

---

---

---

---

---

---

## Spartan II Family

Spartan II Device Attributes

Spartan II FPGAs	XC2515	XC2530	XC2550	XC25100	XC25150	XC25200
System Gates <sup>1</sup>	6K-15K	13K-30K	23K-50K	37K-100K	52K-150K	71K-200K
Logic Cells <sup>2</sup>	432	972	1,728	2,700	3,888	5,292
Block RAM Bits	16,384	24,576	32,768	40,960	49,152	57,344
Max Avail I/O	86	132	176	196	260	284

<sup>1</sup> 20-30% of CLBs as RAM.

<sup>2</sup> 1 Logic cell = four-input lookup table + flip-flop.

---

---

---

---

---

---

---

---

## Family Comparisons

Part	Spartan	Spartan XL	Spartan II
Architecture	XC4000 Based	XC4000 Based	Virtex Based
Max # System Gates	5K-40K	5K-40K	15K-200K
Memory	Distributed RAM	Distributed RAM	Block + Distributed
I/O Performance	80 MHz	100 MHz	200 MHz
I/O Standards	4	4	16
Core Voltage	5 V	3.3 V	2.5 V
DLLs	No	No	Yes

---

---

---

---

---

---

---

---


---

---

---

---

## Spartan II Architecture

 


---

---

---

---

---

---

---

---


---

---

---

---

## Spartan II CLBs

 


---

---

---

---

---

---

---

---


---

---

---

---

# Virtex Family

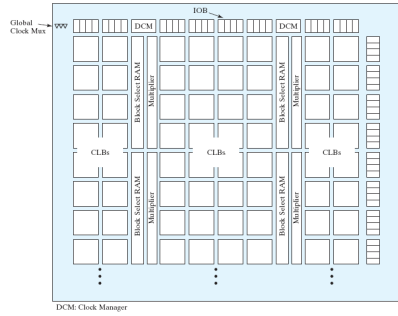

---

---

---


---

---

---

---

---

 

---

---

---

---

---

---

---

---