

HBTs: high-frequency attributes


LECTURE 17

- Recapitulation of equivalent circuits
- Two components of Emitter-Base capacitance
- Figures of merit
- f_T : definition and derivation
- Design for high f_T
- f_{max} : definition and derivation
- Design for high f_{max}

DC Equivalent circuit

$$J_e = -qn_0B \left[e^{qV_{BE}/kT} - e^{qV_{BC}/kT} \right] \left[\frac{W_B}{D_e} + \frac{1}{v_R} \right]^{-1}$$
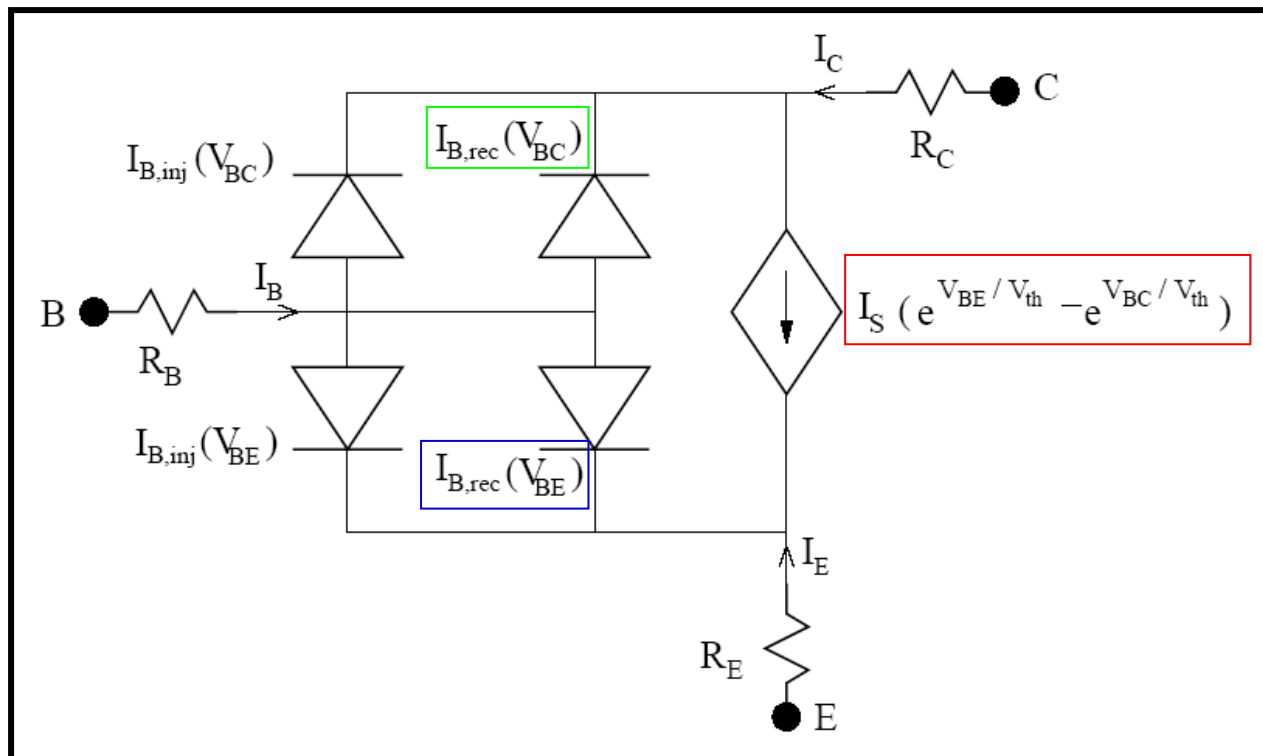
$$I_{B,rec} = Aqn_0B \left[(e^{V_{BE}/V_{th}} - 1) + (e^{V_{BC}/V_{th}} - 1) \right] \left\{ \frac{1}{\frac{2\tau_e}{W_B} + \frac{1}{2v_R}} \right\}$$




AC small-signal equivalent circuit

small-signal base current


$$i_3 = \frac{\partial I_3}{\partial V_{31}} v_{31} + \frac{\partial I_3}{\partial V_{21}} v_{21}$$

$$= g_{33} v_{31} + g_{32} v_{21}$$

2-generator circuit

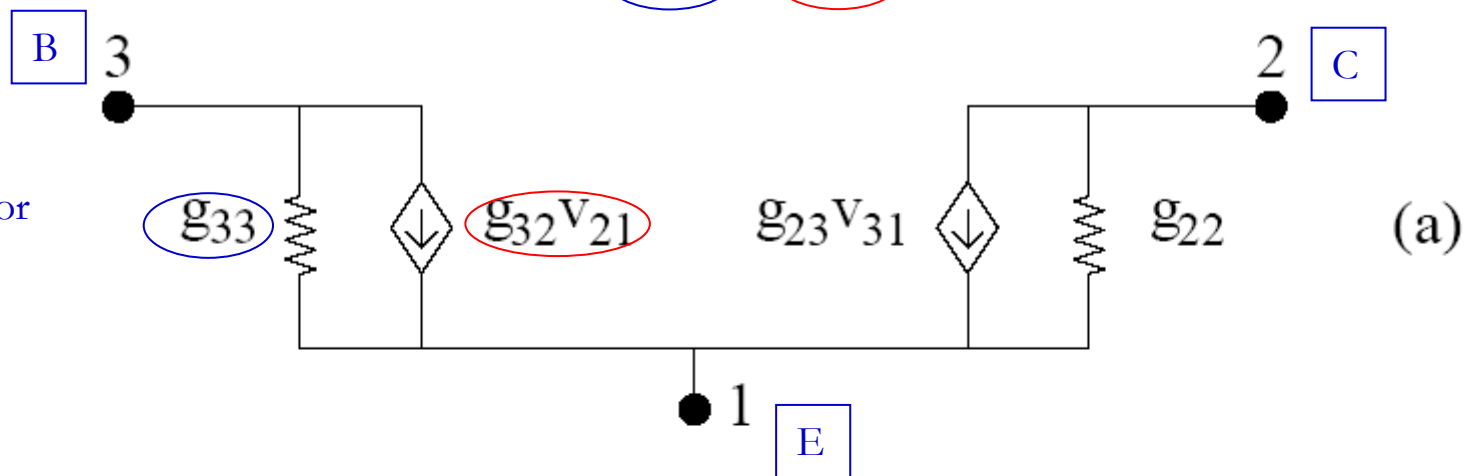


1-generator circuit

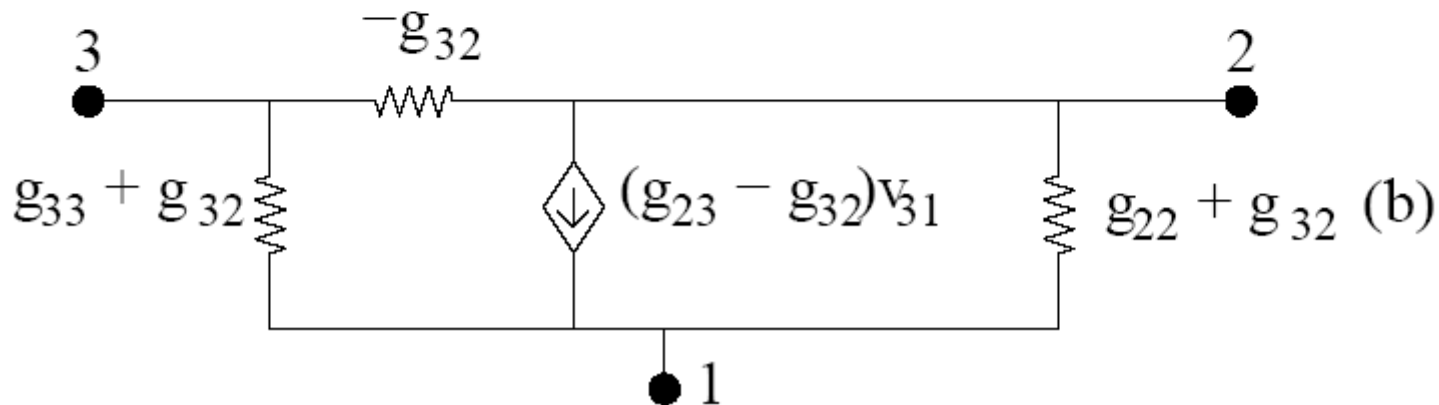


Hybrid- π equivalent circuit

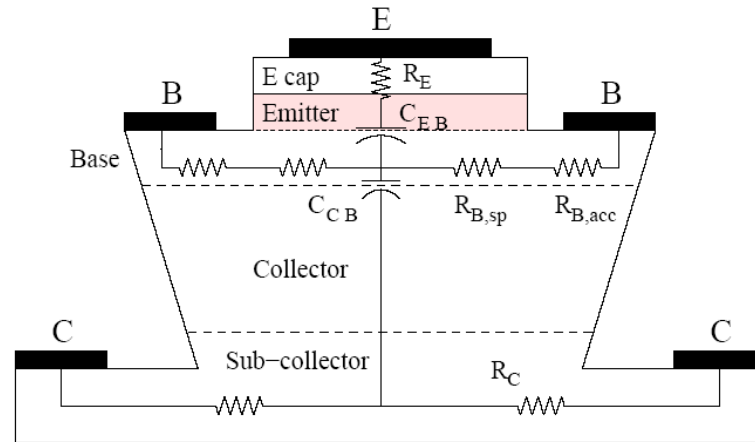
HBT with parasitic R's
and C's identified



Omit small-value
components

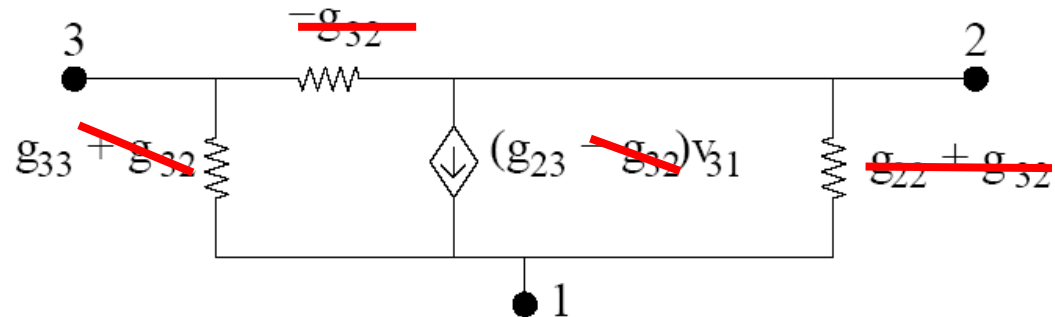


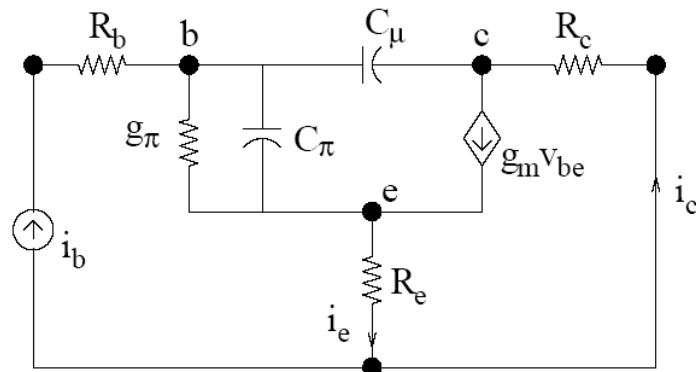Hybrid- π equivalent circuit
under AC short-circuit at the
output.




$$\begin{aligned} g_\pi &\equiv g_{33} \\ g_m &\equiv g_{23} \\ C_\pi &\equiv C_{EB} \\ C_\mu &\equiv C_{CB} \end{aligned}$$

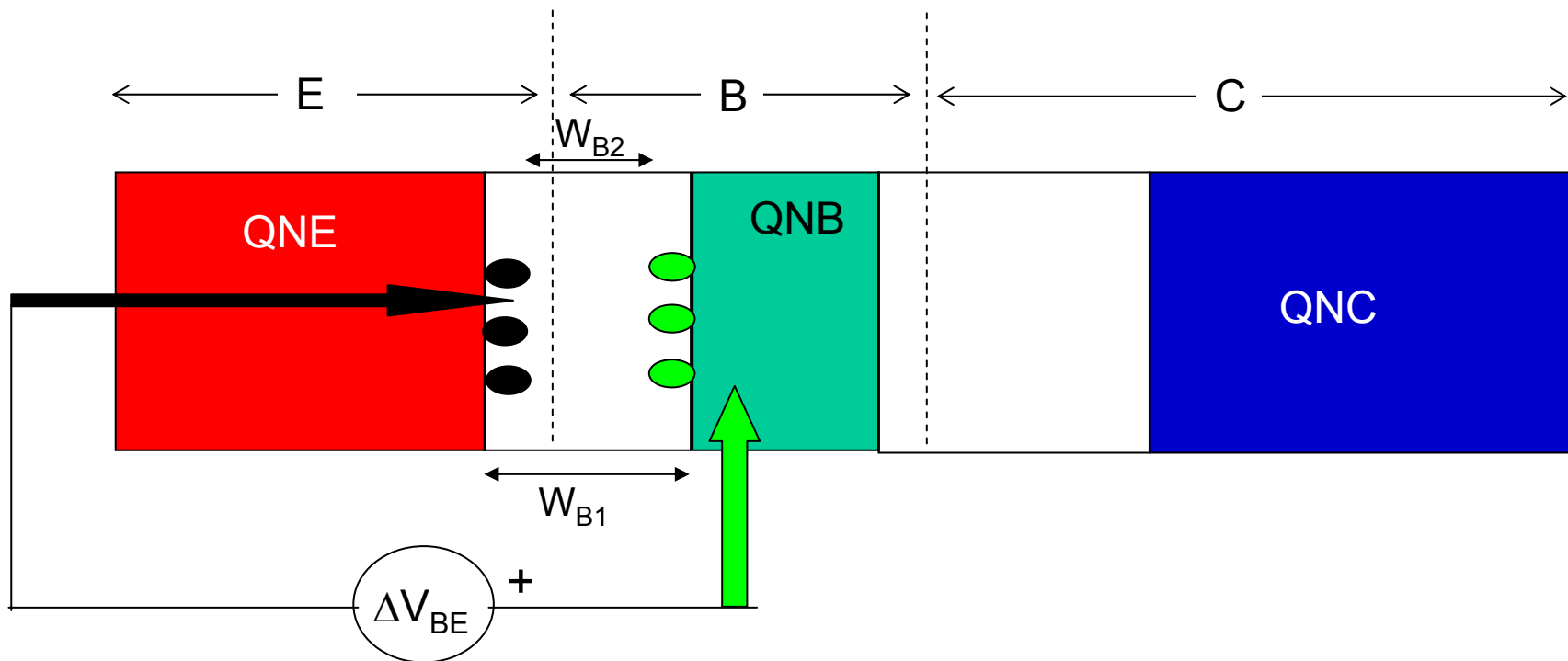
Emitter-base junction-storage capacitance



$$C_{EB,j} =$$

 

$$C_{EB,j} \equiv$$

 


- $\Delta Q_{E,j}$ is the change in charge entering the device through the emitter and creating the new width of the depletion layer (narrowing it in this example),
- in response to a change in V_{BE} (with E & C at AC ground).
- It can be regarded as a parallel-plate cap.

What is the voltage dependence of this cap?

Sec.
12.3.2

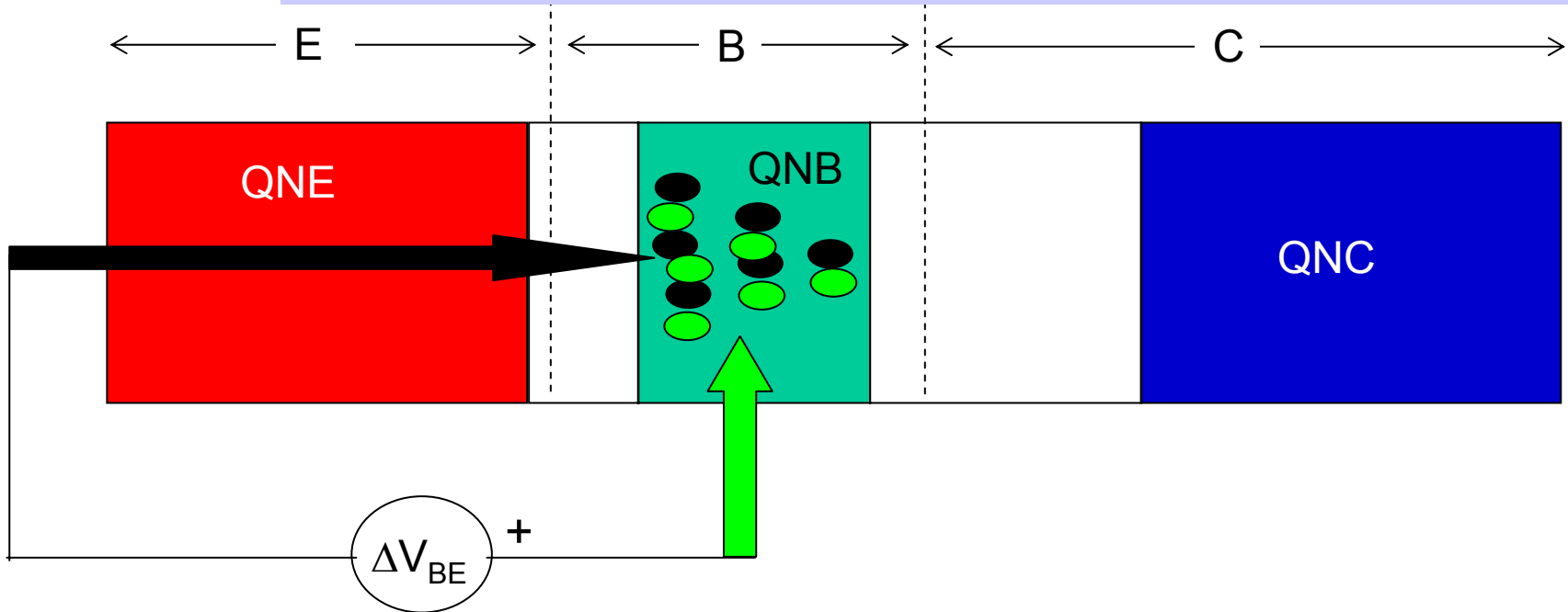Emitter-base base-storage capacitance: concept




$$C_{EB,b} = -$$



- $\Delta Q_{E,b}$ is the change in charge entering the device through the emitter and resting in the base (the black electrons),
- in response to a change in V_{BE} (with E & C at AC ground).
- It's not a parallel-plate cap, and we only count one carrier.

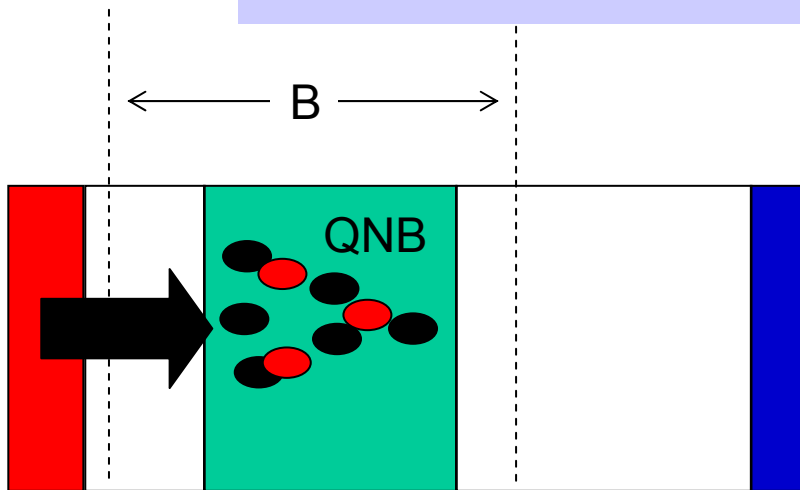Emitter-base base-storage capacitance: evaluation



$$Q_{E,b}(V_{BE}) = -q \frac{1}{2} W_B A \left[n_{0p} \exp\left(\frac{V_{BE}}{V_{th}}\right) - n(W_B) \right] - q W_B A n(W_B)$$

$$\text{Take } \frac{\Delta Q_{E,b}}{\Delta V_{BE}} \rightarrow \frac{dQ_{E,b}}{dV_{BE}}$$

$$\text{Hence } C_{EB,b}$$



$$\underline{n(0, V_{BE1}) = n_{0p} \exp(V_{BE1} / V_{th})}$$

$$\underline{n(0, V_{BE2}) = n_{0p} \exp(V_{BE2} / V_{th})}$$

What is the voltage dependence of $C_{EB,b}$?

HF figures of merit

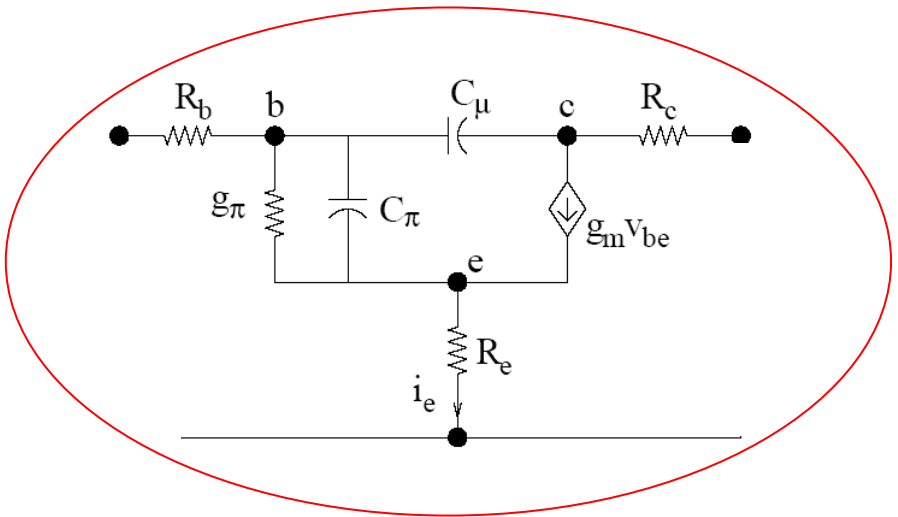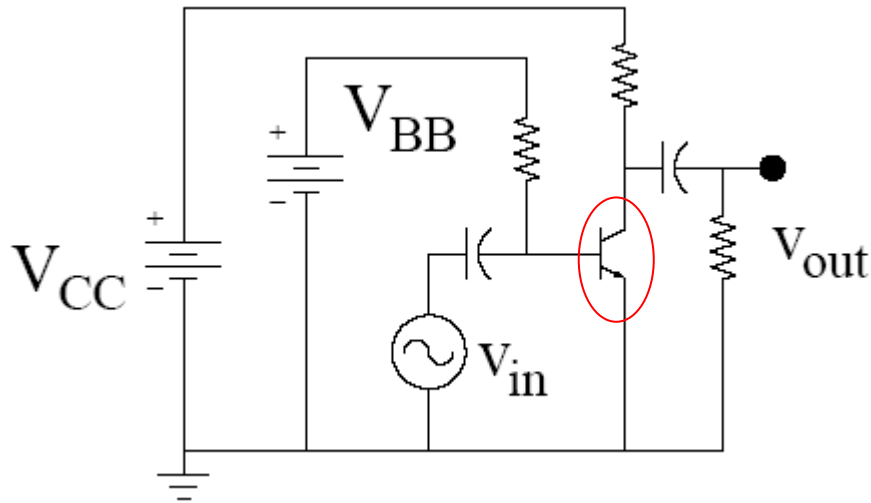Represent transistor by its small-signal equivalent circuit



Consider frequency dependence of some current gain




Consider frequency dependence of some power gain



What are the associated figures of merit?

Sec. 14.4

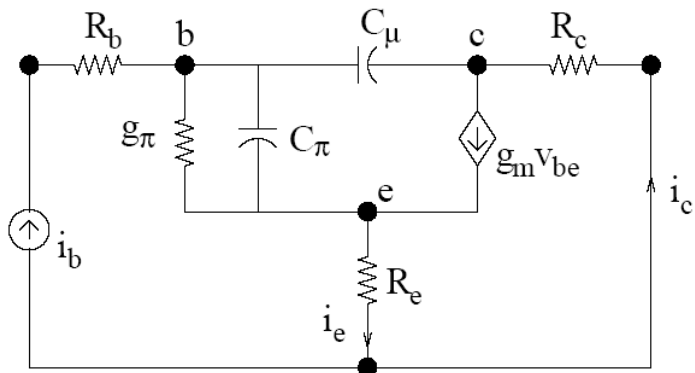
 f_T from hybrid- π equivalent circuit

- f_T is measured under AC short-circuit conditions.

- We seek a solution for $|i_c/i_b|^2$ that has a single-pole roll-off with frequency.

- Why?

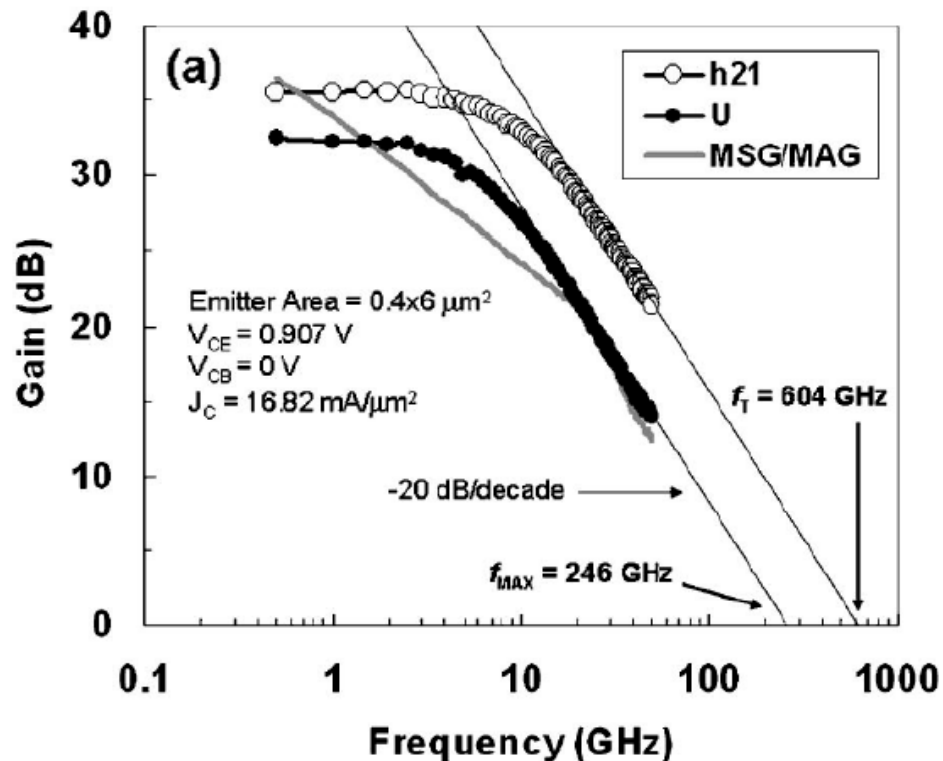- Because we wish to extrapolate at -20 dB/decade to unity gain.



Extrapolated f_T

- Assumption:

$$i_b R_e \ll i_c (R_e + R_c)$$

- Conditions:

$$\omega^2 \ll \frac{g_m^2}{C_\mu^2}$$

$$\omega^2 \ll \frac{1}{C_\mu^2 R_{ec}^2}$$


$$\omega^2 \gg \frac{g_\pi^2}{(C_\pi + C_\mu(1 + R_{ec}g_m))^2}$$

- Current gain:

$$\left| \frac{i_c}{i_b} \right|^2 = \frac{g_m^2}{\omega^2 (C_\pi + C_\mu(1 + g_m R_{ec}))^2}$$


- Extrapolated f_T :

$$2\pi f_T =$$

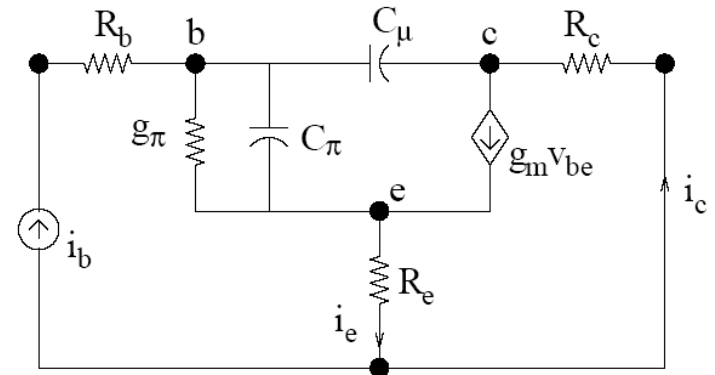

Improving f_T
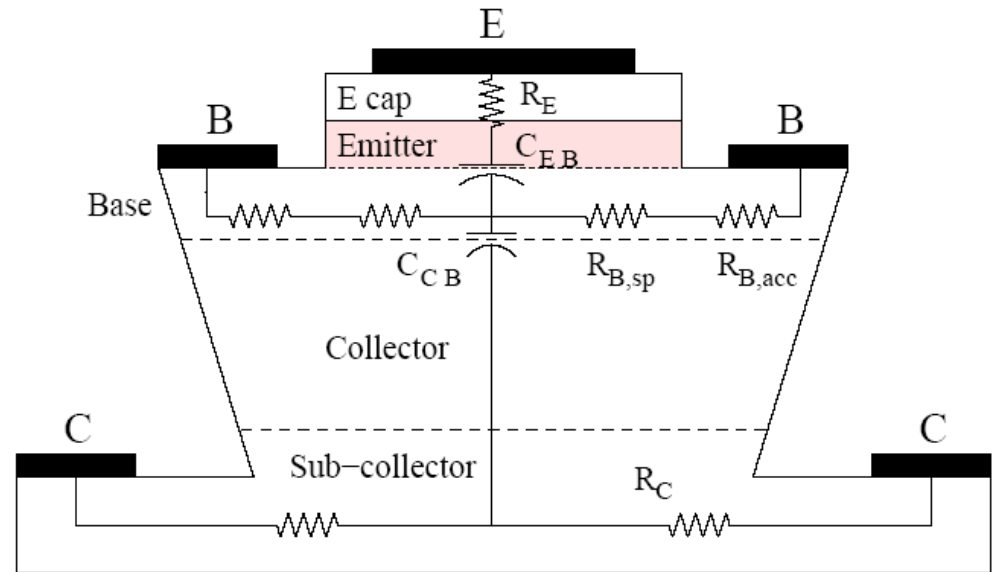
$$2\pi f_T = \frac{g_m}{C_\pi + C_\mu(1 + g_m R_{ec})}$$



- III-V for high g_m
- Highly doped sub-collector and supra-emitter to reduce R_{ec}
- Dual contacts to reduce R_c and R_B
- Lateral shrinking to reduce C's

What is required to get $f_T > 200$ GHz ?



Sec. 14.6

Circuit for derivation of f_{max}

Justify these omissions

Add source and load


Model with Thévenin equivalent circuit

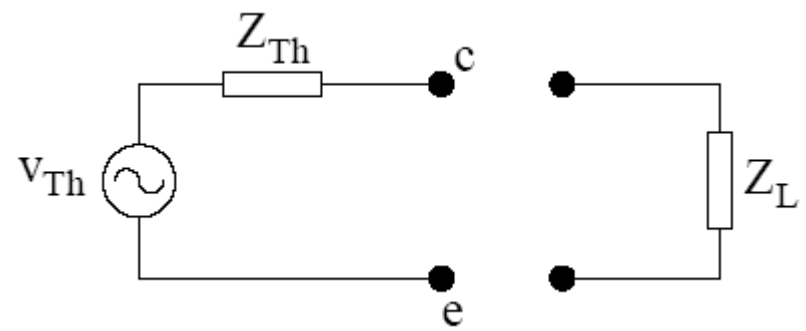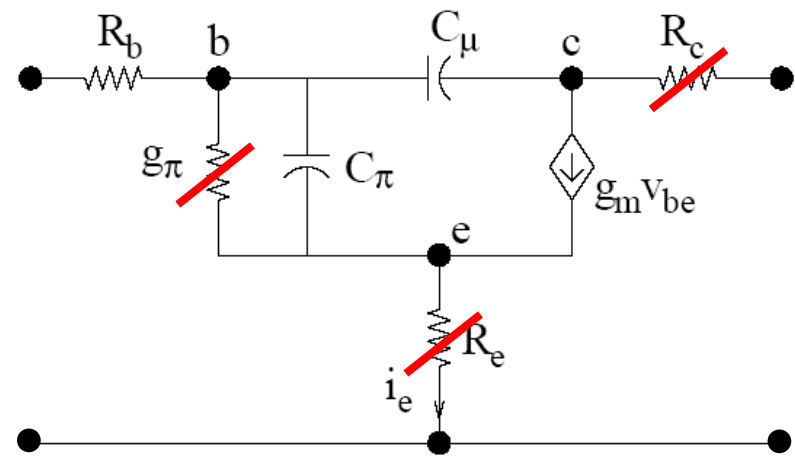

$$v_{Th} = v_{in} \frac{j\omega C_{\mu} - g_m}{j\omega C_{\mu}(1 + g_m R_b) - \omega^2 C_{\mu} C_{\pi} R_b}$$

$$Z_{Th} = \frac{R_b^{-1} + j\omega C_T}{j\omega C_{\mu}(g_m + R_b^{-1}) - \omega^2 C_{\mu} C_{\pi}}$$

Developing an expression for f_{\max}

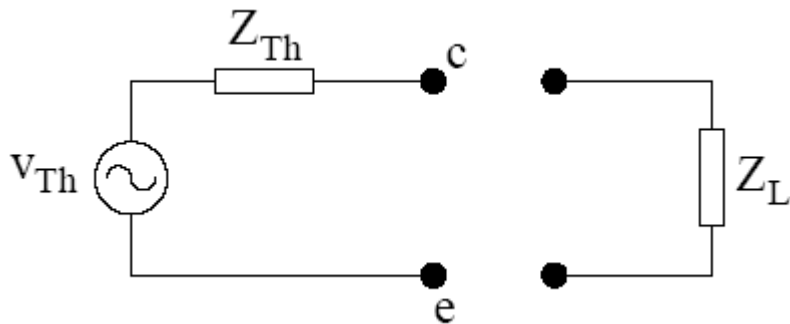

Further conditions:

$$\omega^2 \ll \frac{g_m^2}{C_\mu^2}$$

$$\omega^2 \gg \frac{g_\pi^2}{C_\pi^2}$$

$$\omega^2 \ll \frac{g_m^2}{C_\pi^2}$$

$$\omega^2 \ll \frac{(g_m + R_b^{-1})^2}{C_\pi^2}$$

Conjugately match at the output

$$\Re(Z_{Th}) \approx \frac{C_T}{C_\mu g_m} \quad P_{out,max} = \frac{|v_{Th}|^2}{4\Re(Z_L)} \approx \frac{|v_{in}|^2}{4R_b^2} \frac{g_m}{\omega^2 C_\mu C_T}$$

Conjugately match at the input


$$P_{in,max} = \frac{|v_S|^2}{4\Re(Z_{in})} = \frac{|v_{in}|^2}{R_b}$$

Sec. 14.6


Improving f_{\max}

$$\text{MAG} = \frac{P_{\text{out,max}}}{P_{\text{in,max}}} = \frac{g_m}{4\omega^2 C_\mu C_T R_b}$$


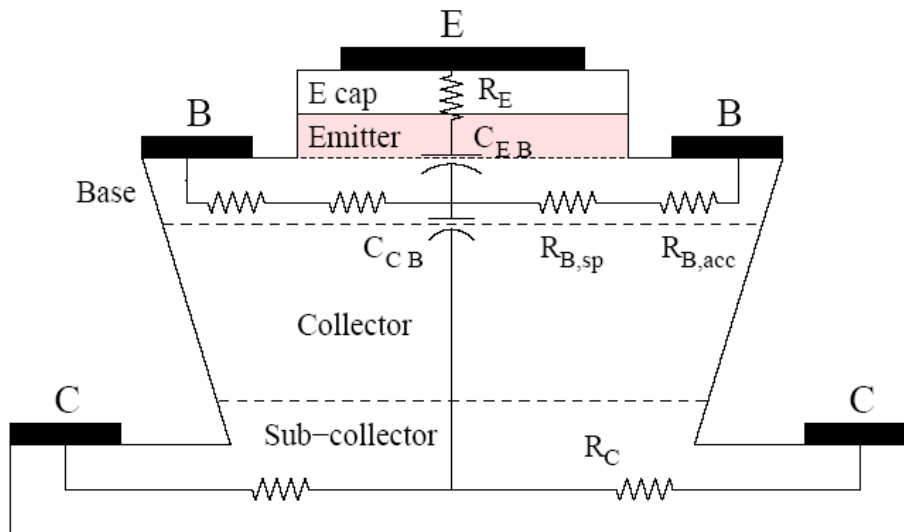
$$f_{\max} = \sqrt{\frac{f_{T,i}}{8\pi C_\mu R_b}}$$



- Pay even more attention to R_b and C_μ

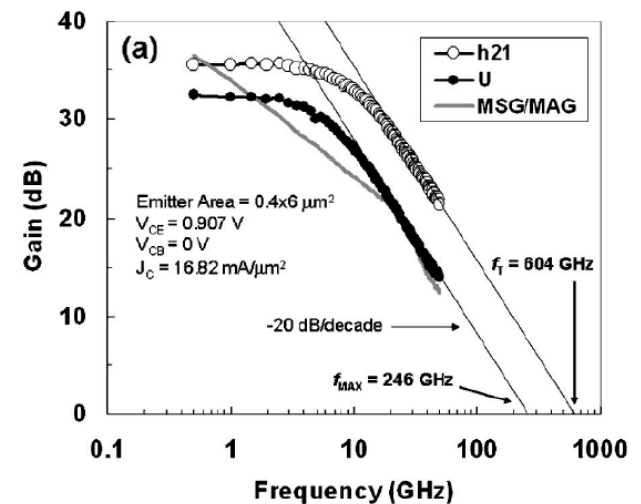

Base-spreading resistance

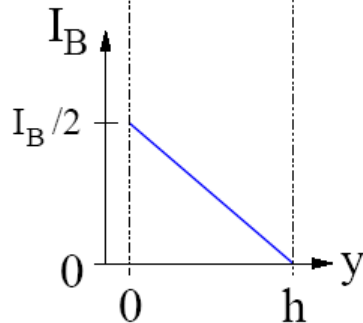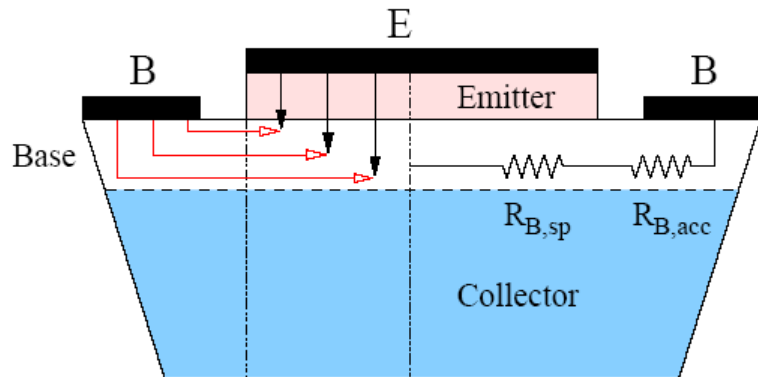

$$P_{\text{left}}(y) = I_B(y)^2 R$$

$$P_{\text{left}} = \int_0^h \frac{I_B^2}{4} \left(1 - \frac{y}{h}\right)^2 \frac{\rho dy}{A}$$

What is rho?

$$P = \frac{I_B^2}{12} R_{B,QNB} \equiv I_B^2 R_{B,sp}$$

What is $R_{B,QNB}$?

Do you now see why HBTs have helped enable portable wireless products?

What is required to get $f_{\text{max}} > 300$ GHz ?