

---

## Lecture 7

### Noise Margin in Digital Circuits

Res Saleh  
Dept. of ECE  
University of British Columbia  
res@ece.ubc.ca

---


## Overview

- **Reading**
  - HJS Chapter 4; Sections 4.1, 4.2, 4.3
- **Background**
  - Digital IC designs must operate properly in noisy environments. We would like to have some notion of how robust a circuit is to external noise sources. There are a variety of measures of noise for logic circuits such as single stage noise margin (SSNM) and the classical noise margins are based on the unity gain points of the VTC. These metrics eventually lead us to desirable properties that logic gates must have in order to work properly. We will look at how to calculate this for inverters in the next lecture.


## Noise Margins and Sensitivity

- Robustness of a circuit (i.e., its ability to operate properly in the presence of noise) depends on two factors:
  1. Noise margins (voltage metric)
    - how much noise can we apply before the gate fails
    - many different ways to measure this
  2. Noise sensitivity
    - how much noise can actually couple into the gate
    - depends on gate type and its connection to noise source
- First component sets requirements on the gate to handle noise
- Second component captures the response of the circuit to a given noise input (will be discussed in later chapters of HJS)
- Start by examining the first issue using basic inverter circuit...

## Ideal Inverter Characteristics

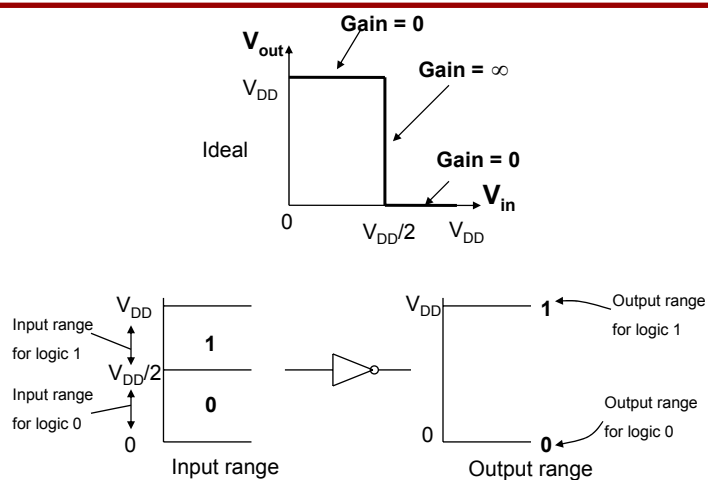


## Actual Inverter Characteristics

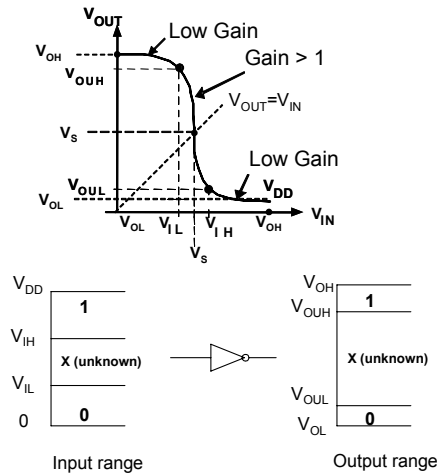
 
## Noise Attenuation


- What does this type of VTC imply about a noisy signal as it passes through a logic gate?
- Noise is reduced:



- Next, consider metrics for noise tolerance and the implications on the characteristics of the gate

 
## Single Stage Noise Margins

- Simplest type of noise margin is the single-stage noise margin
- Defined as maximum noise,  $v_n$ , in a single stage that still allows subsequent stages to recover to the right value (regenerative property)




- In the above circuit  $V_{i2} = V_{o1} - v_n = V_{OH} - v_n$
- For noise added to a high level input, the correct levels will be maintained if  $V_{OH} - v_n > V_{TH}$  (point where  $V_{in} = V_o$ )
- For noise added to a low level input, correct levels will be maintained if  $V_{OL} + v_n < V_{TH}$

## Single Stage Noise Margins

 
 
## Multistage Noise Margins

- Noise actually occurs between every gate and not at a single stage, as we have assumed so far





- In the above circuit, we need to determine how much noise we can tolerate before the circuit stops working as expected
- We note that  $V_{out} = f(V_{in})$
- With noise  $V_{out}' = f(V_{in}) + V_{noise} \times \text{Gain} + \text{Higher-order terms}$
- If the Gain  $< 1$ , then noise is attenuated; otherwise it is amplified
- IDEA: Develop a metric based on keeping the Gain  $< 1$

## Classical Noise Margins

$$NM_H = V_{OH} - V_{IH}$$

$$NM_L = V_{IL} - V_{OL}$$

  


## Requirements for a Valid Logic Gate

- Must have a high gain region between two low gain regions
- Gain must be below 1 for low gain regions
- Gain must be greater than 1 for high gain region
- Output must swing from valid low to valid high
  - Low output should be below  $V_{IL}$
  - High output should be above  $V_{IH}$
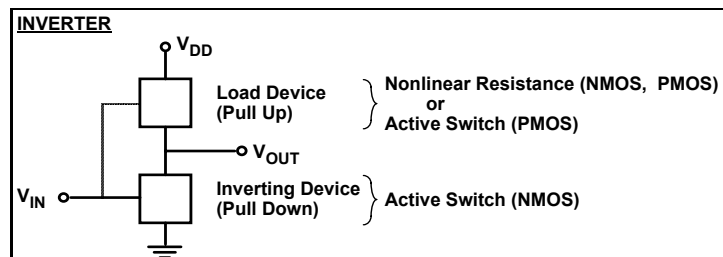
## Next lecture: MOS Inverters

- Basic structure of MOS inverter is shown below: NMOS pulldown device with a variety of possible pullup devices



- We will derive the noise margin parameters for different types of inverters